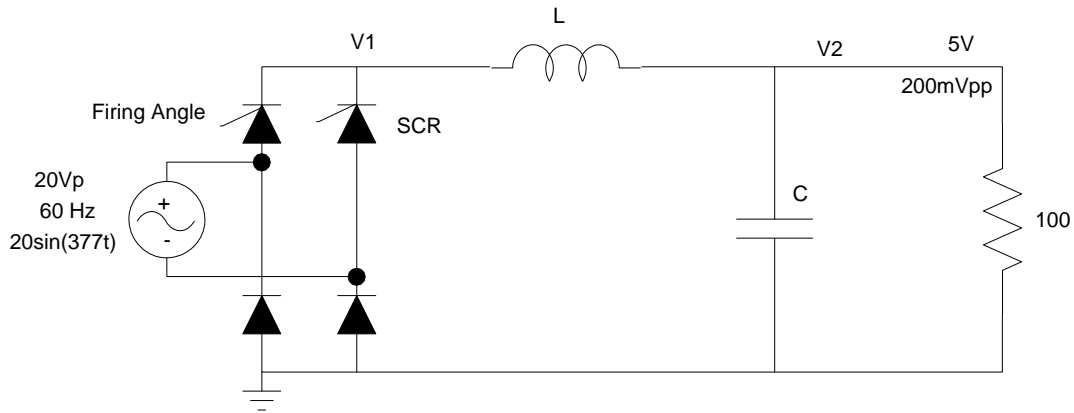


ECE 320 - Homework #6

DC to AC Converter, SCR. Due Monday, October 3rd

SCR



- 1) Determine the firing angle so that the mean of V_1 is $5V$
- 2) Find L so that the ripple at V_2 is $2V_{pp}$ assuming $C = 0$.
- 3) Find C so that the ripple at V_2 is reduced to $200mV_{pp}$
- 4) Simulate this circuit with a firing angle of zero degrees (making the SCR just a diode).
 - What is the DC voltage at V_2 ? Why isn't it $5V$ any more?
 - What is the AC voltage at V_2 (V_{2pp})?

AC to DC

- 5) Find the Fourier transform for the signal at V_1 with the firing angle you computed in problem 1.
- 6) If you ignore the DC term, what percentage of the energy is in the 1st harmonic?