

# ECE 320 - Homework #8

Schmitt Triggers, MOSFET's, MOSFET Switch. Due Monday, October 17th

## Schmitt Trigger:

1) Assume you have a light sensor whose resistance is



$$R = \left( \frac{100,000}{Lux} \right) \Omega$$

Design a circuit which is capable of driving a 1k Ohm load where

- The output goes to +10V when the light level drops below 20 Lux and
- The output goes to 0V when the light level goes above 25 Lux.

**MOSFET:** The VI characteristics for a MOSFET are shown below.

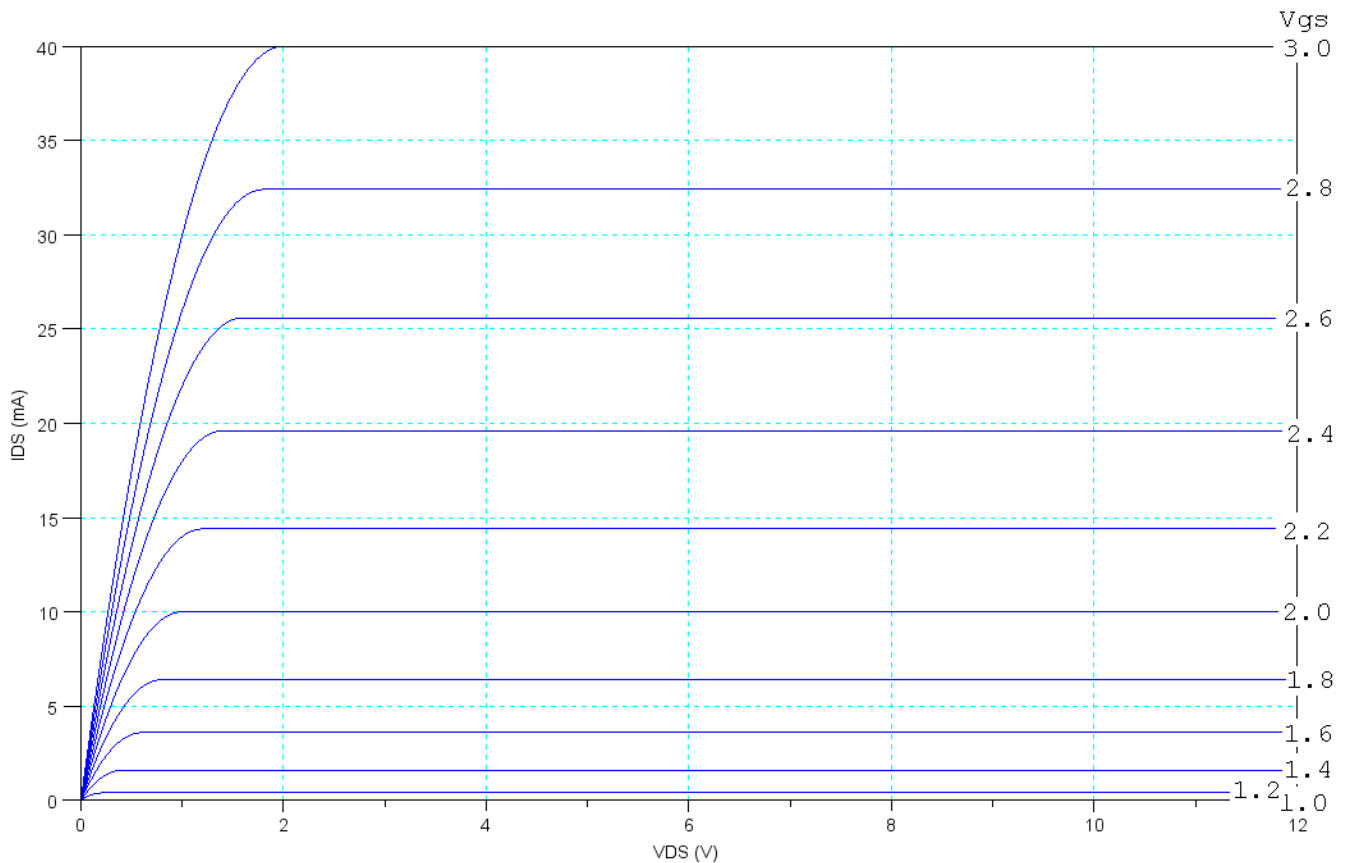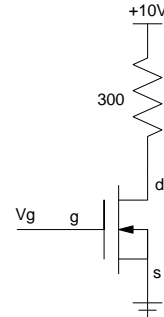- 2) Label the off / saturated / and ohmic regions.
- 3) Determine the turn-on voltage and transconductance gain, gm
- 4) Draw the load-line for the circuit shown to the right.
- 5) Determine the Q-point for
  - $V_g = 0V$
  - $V_g = 2V$
  - $V_g = 3V$



6) Design a circuit to turn on and off a 12V DC motor which draws 3A. Assume the MOSFET characteristics are:

- $V_{DS\ max} = 100V$
- $I_{D\ max} = 11A$  (continuous)
- $R_{DS\ max} = 173\ m\Omega$  @  $I_D = 5A$ ,  $V_{GS} = 10V$
- $V_T = 2V$  @  $1mA$

## Term Project (part 1)

Lab: 7-10) Design, build, and test one part of your term project

7) Requirements: Specify

- Inputs
- Outputs
- How they relate

8) Analysis: Give calculations for resistors, capacitors, etc. for a circuit which meets these requirements.

9) Testing: Simulate your circuit in PartSim (or similar software) to check if your calculations were correct.

10) Validation: Build your circuit and collect data to verify your design meets your requirements.