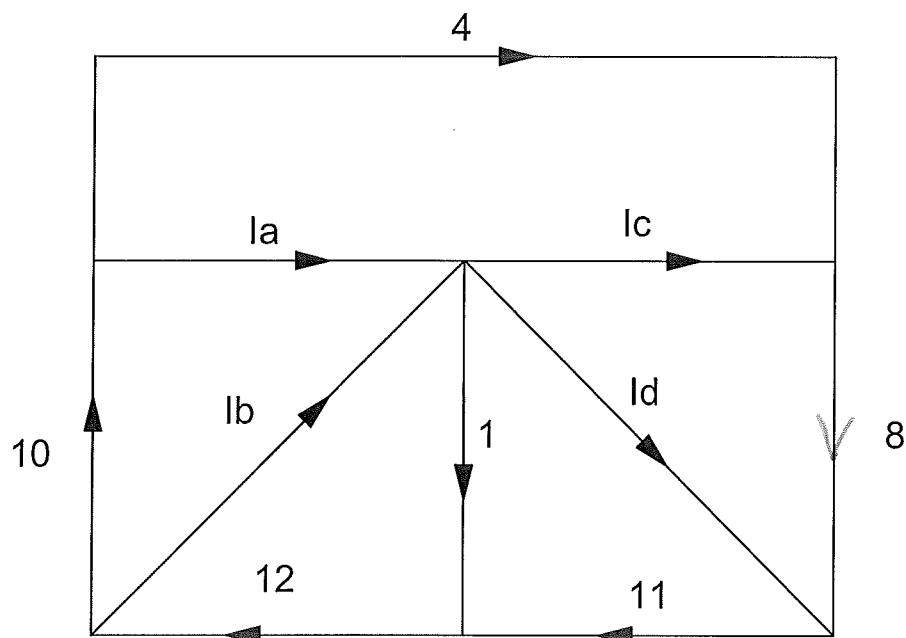


ECE 320: Quiz #1: Name Key

EE 206 Review


- 1) Conservation of Current: Determine the currents I_a , I_b , I_c , and I_d

I_a	I_b	I_c	I_d
6	2	4	3




2) Conservation of Voltage: Determine the voltages V1, V2, V3, and V4

V1	V2	V3	V4
60	20	80	75

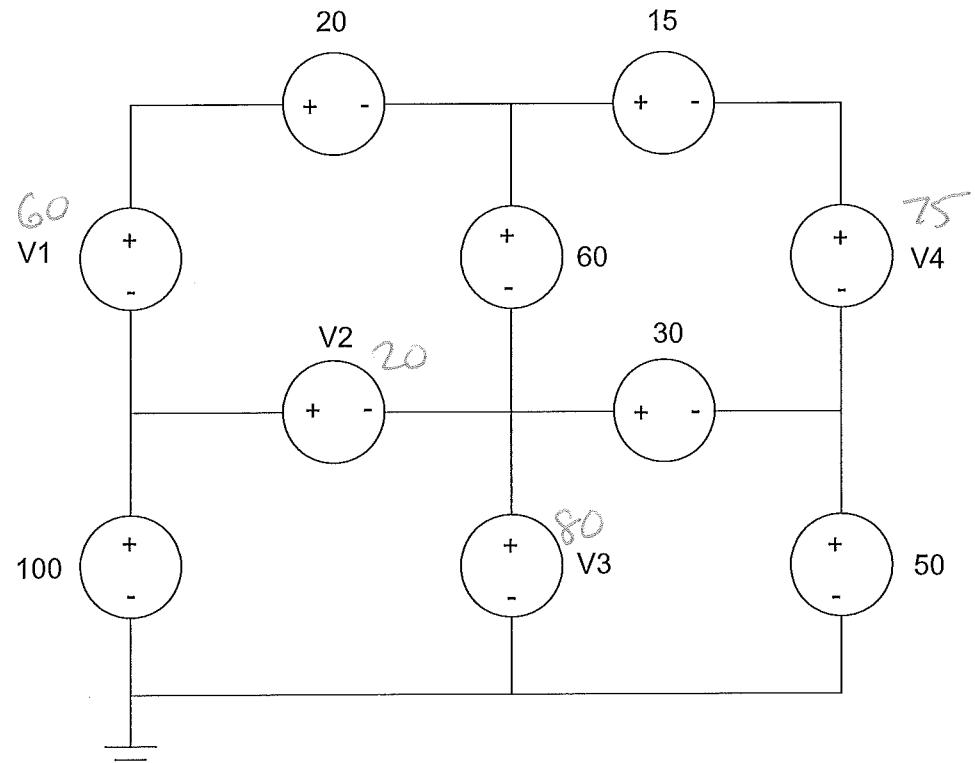

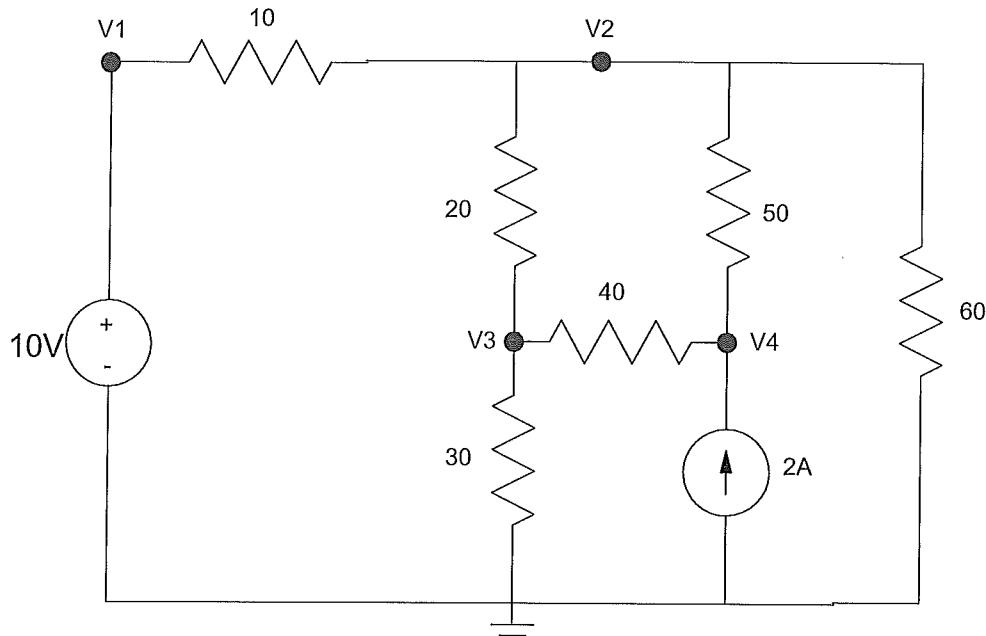3) Write the voltage node equations for V1..V4 (sum of currents = zero).




$$V_1 = 10$$

$$\frac{V_2 - 10}{10} + \frac{V_2 - V_3}{20} + \frac{V_2 - V_4}{50} + \frac{V_2}{60} = 0$$

$$\frac{V_3 - V_2}{20} + \frac{V_3 - V_4}{40} + \frac{V_3}{30} = 0$$

$$\frac{V_4 - V_2}{50} + \frac{V_4 - V_3}{40} - 2 = 0$$

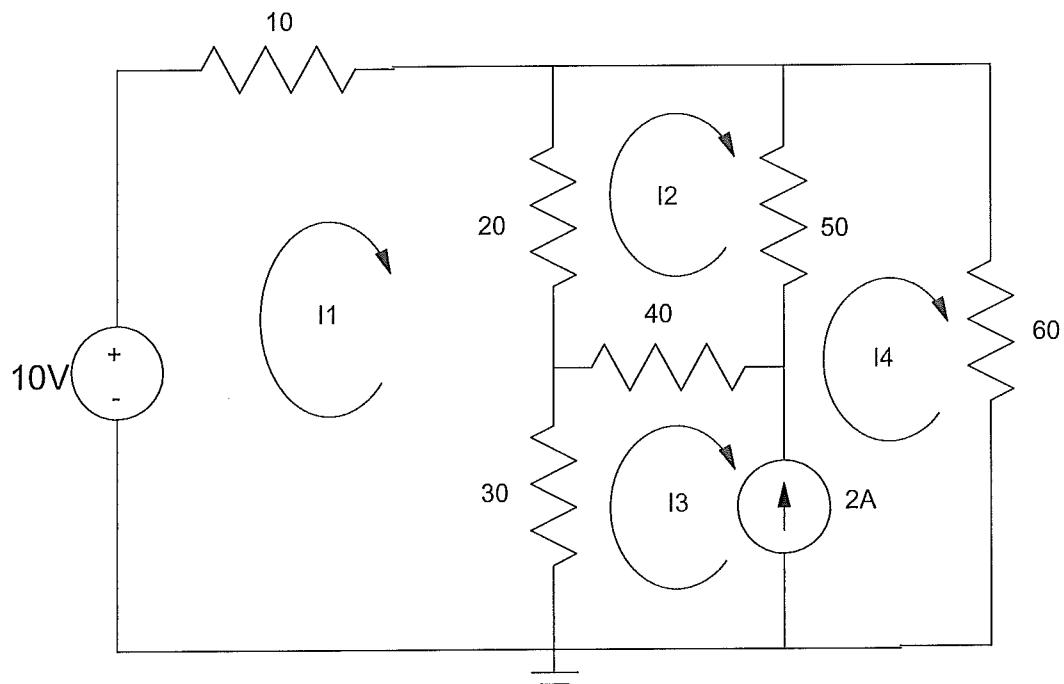4) KCL: Write the current loop equations for I₁..I₄ (sum of voltages equals zero)



$$-10 + 10I_1 + 20(I_1 - I_2) + 30(I_1 - I_3) = 0$$

$$20(I_2 - I_1) + 50(I_2 - I_4) + 40(I_2 - I_3) = 0$$



$$I_4 - I_3 = 2$$

$$-10 + 10I_1 + 60I_4 = 0$$

(various paths)

5) Thevenin Equivalents: Find the Thevenin equivalent for the following circuit:

V _{th}	R _{th}
5V	55Ω

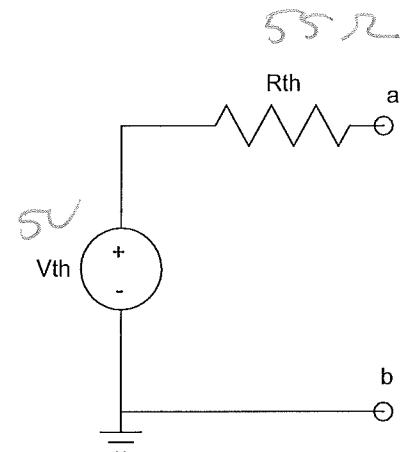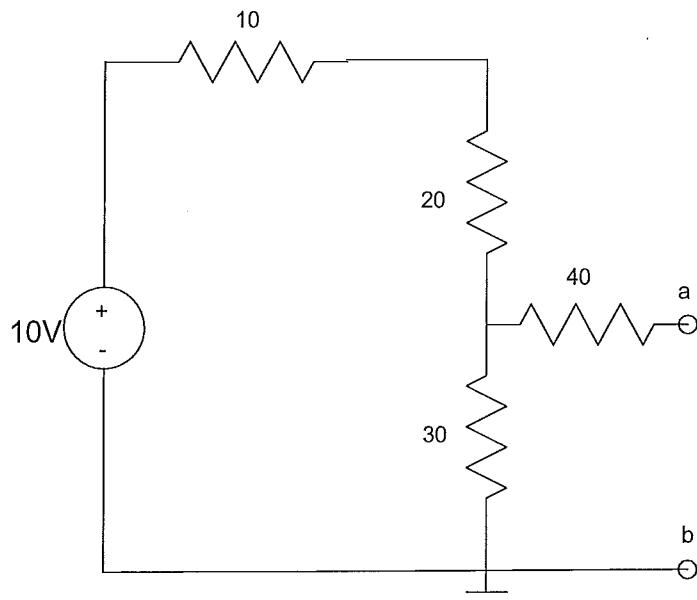

$$V_{th} = \left(\frac{30}{30+30} \right) 10 = 5$$

$$R_{th} = 40 + 30 \parallel 30 = 55$$

Bonus! In Fargo, what is the maximum number of dwellings you can build on a lot zoned for a single dwelling?

12!