


ECE 320: Quiz #6 Name Key

DTL, TTL Logic, Op-Amps - October 13, 2016

- 1) Assume ideal transistors with $V_f = 0.7V$ and $\beta = 100$. Determine the voltages and currents


I1	V2	I3	V4
$290\mu A$	$2.1V$	$290\mu A$	$0.2V$

Saturated

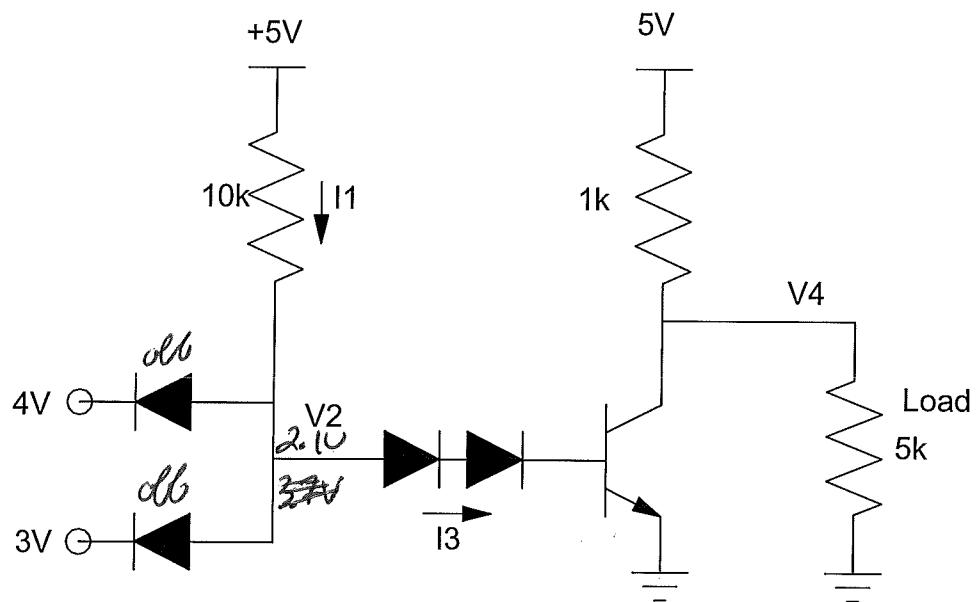


2) Assume ideal transistors with $V_f = 0.7V$ and $\beta = 100$. Determine the voltages and currents

I1	I2	V3	V4
0	$190\mu A$	$3.3V$	$0.2V$

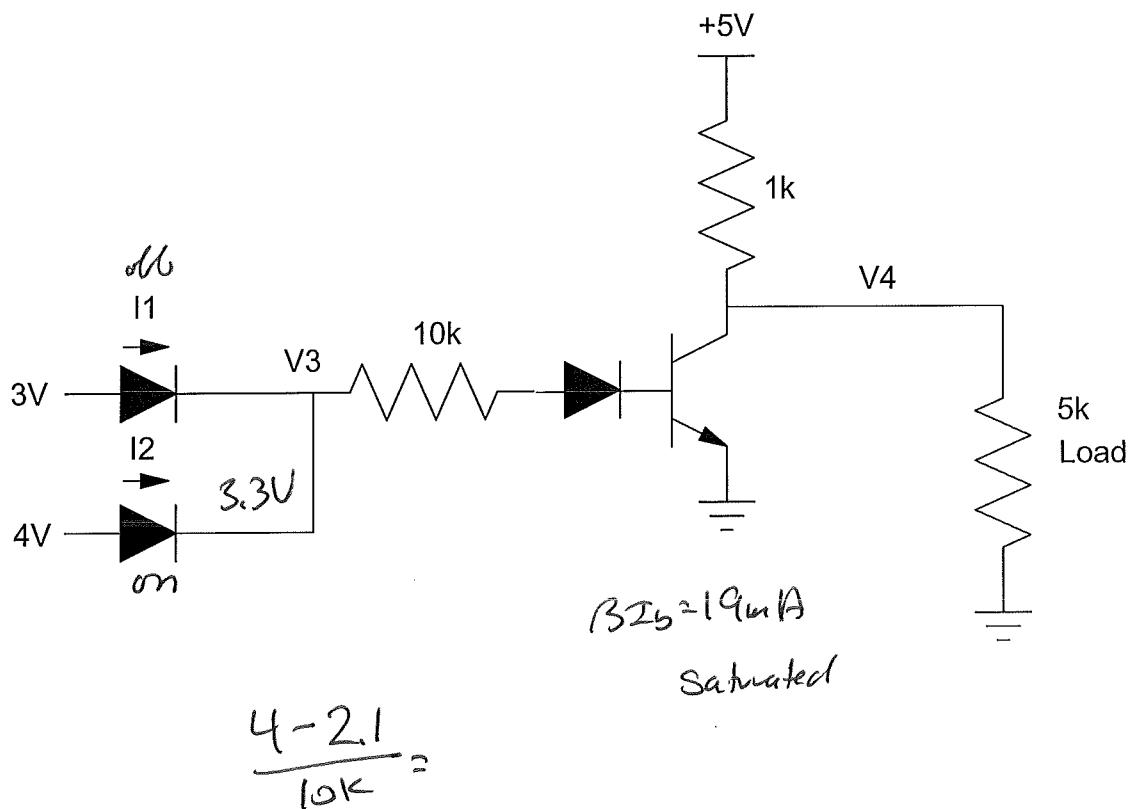


- 3) Determine the voltages and currents for the following H-bridge. Assume all transistors are ideal silicon transistors with $V_f = 0.7V$ and $\beta = 100$

V1	Ib	Ic	V4
1.4V	396μA	4.76mA	0.2V

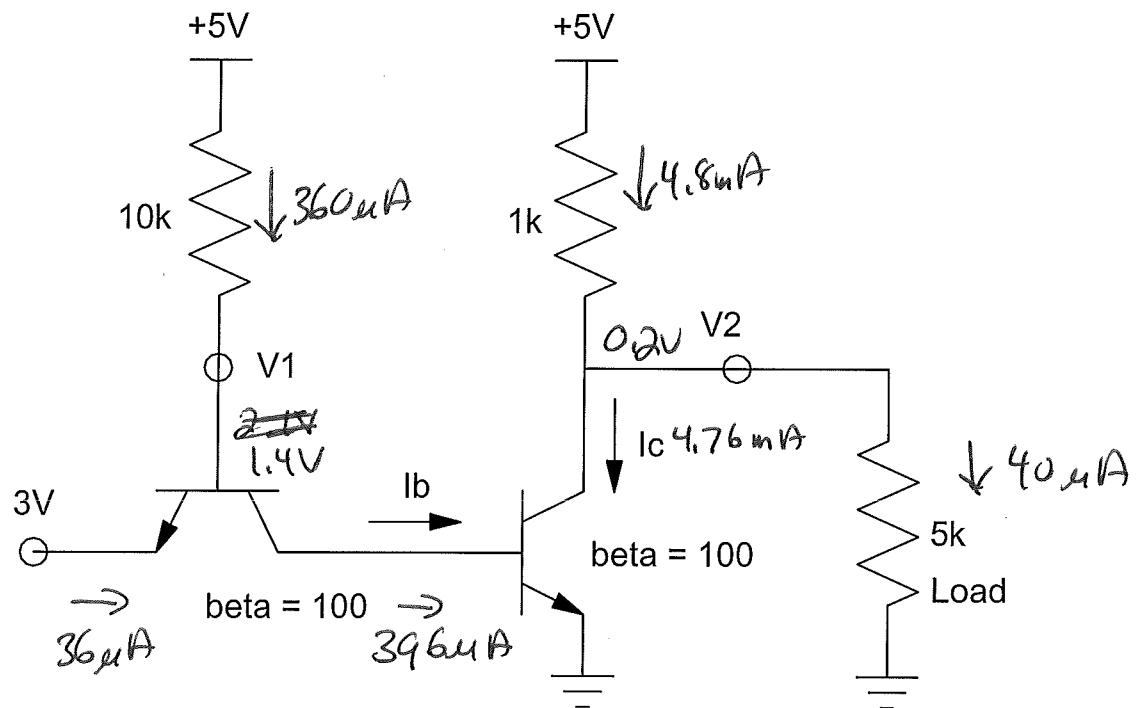

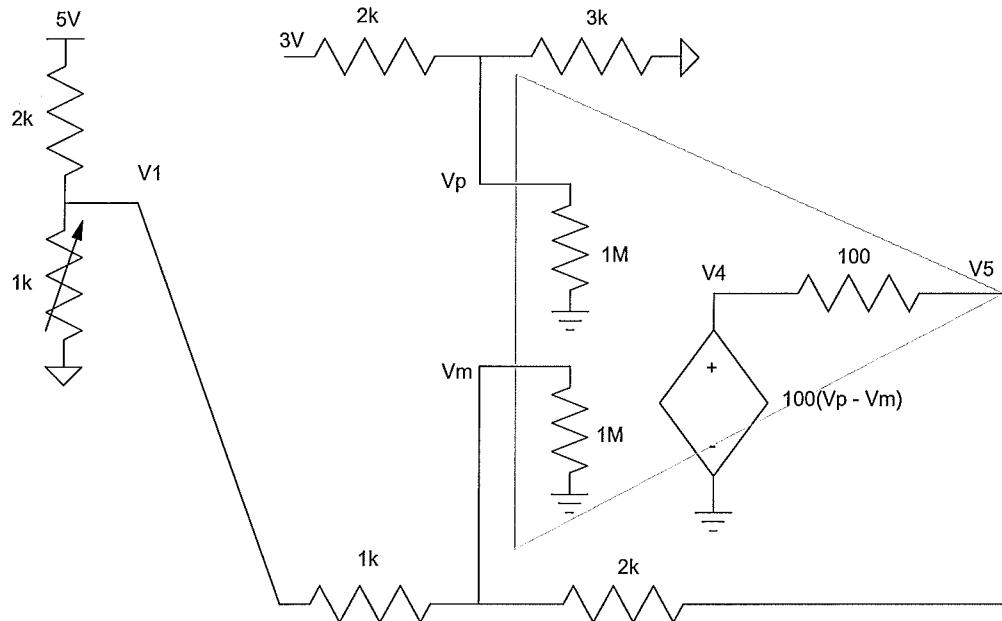4) Write the voltage node equations for the following circuit (non-ideal op-amp)



$$\frac{V_1 - 5}{2k} + \frac{V_1}{1k} + \frac{V_1 - V_m}{1k} = 0$$


$$\frac{V_m - V_1}{1k} + \frac{V_m}{1M} + \frac{V_m - V_5}{2k} = 0$$

$$\frac{V_5 - V_4}{100} + \frac{V_5 - V_m}{2k} = 0$$

$$V_4 = 100(V_p - V_m)$$

$$\frac{V_p - 3}{2k} + \frac{V_p}{3k} = 0$$

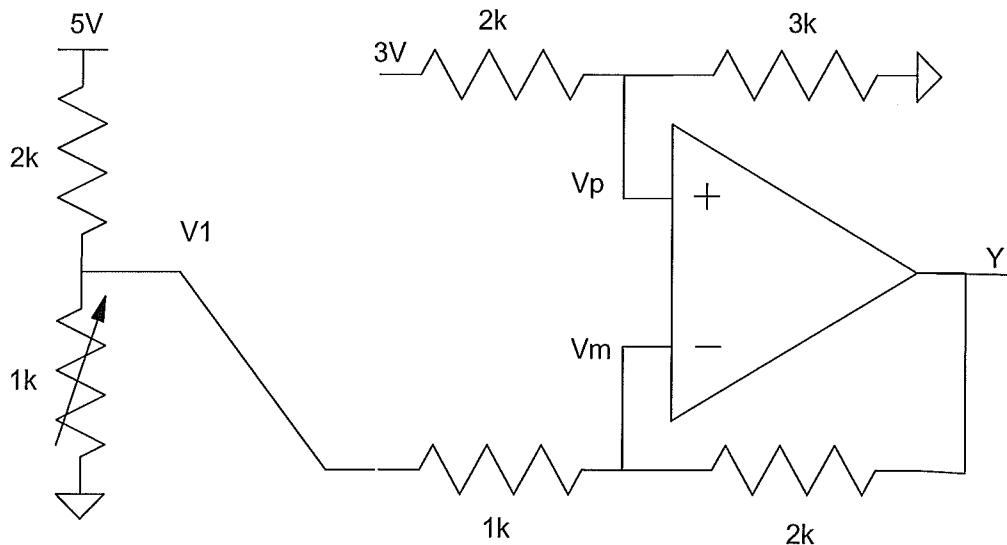5) Assume an ideal op-amp. Write 4 equations to solve for the 4 unknown voltages.



$$V_p = V_m$$

$$\frac{V_p - 3}{2k} + \frac{V_p}{3k} = 0$$

$$\frac{V_m - Y}{2k} + \frac{V_m - V_1}{1k} = 0$$

$$\frac{V_1 - 5}{2k} + \frac{V_1}{1k} + \frac{V_1 - V_m}{1k} = 0$$

Bonus! According to the North Dakota Department of Health, how many oil spills occurred in North Dakota over the last 12 months?

915 contained
270 not contained
1185 total