

# ECE 320 - Homework #8

Schmitt Triggers, MOSFET's, MOSFET Switch. Due Monday, October 17th

## Schmitt Trigger:

1) Assume you have a light sensor whose resistance is

$$R = \left( \frac{100,000}{Lux} \right) \Omega$$

Design a circuit which is capable of driving a 1k Ohm load where

- The output goes to +10V when the light level drops below 20 Lux and
- The output goes to 0V when the light level goes above 25 Lux.

Assume you are using a voltage divider with a 5k resistor:

At 20 Lux:

$$R = 5000$$

$$V_a = \left( \frac{5000}{5000+5000} \right) 10V = 5V$$

At 25 Lux:



$$R = 4000$$

$$V_a = \left( \frac{4000}{4000+5000} \right) 10V = 4.444V$$

The gain is

$$gain = \left( \frac{10V-0V}{5V-4.444V} \right) = 18.0$$

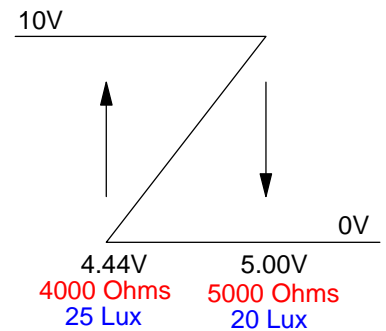
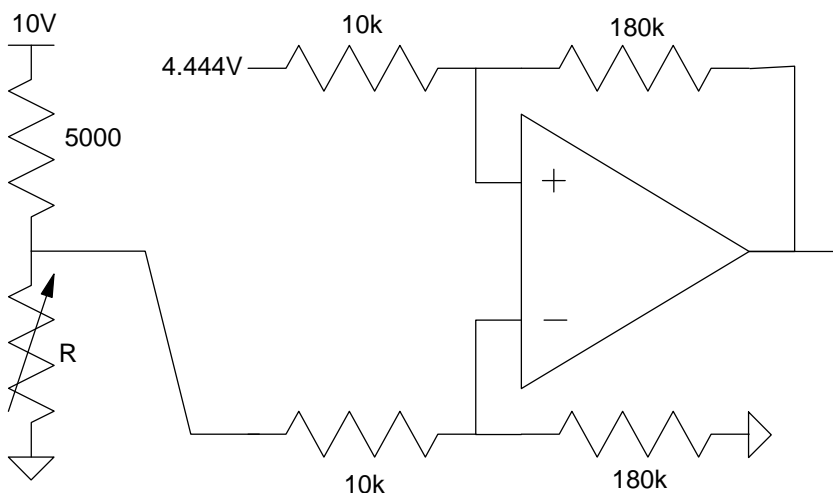
When the output is 0V, you're on the verge of switching at 4.444V. The offset is 4.444V.



**MOSFET:** The VI characteristics for a MOSFET are shown below.

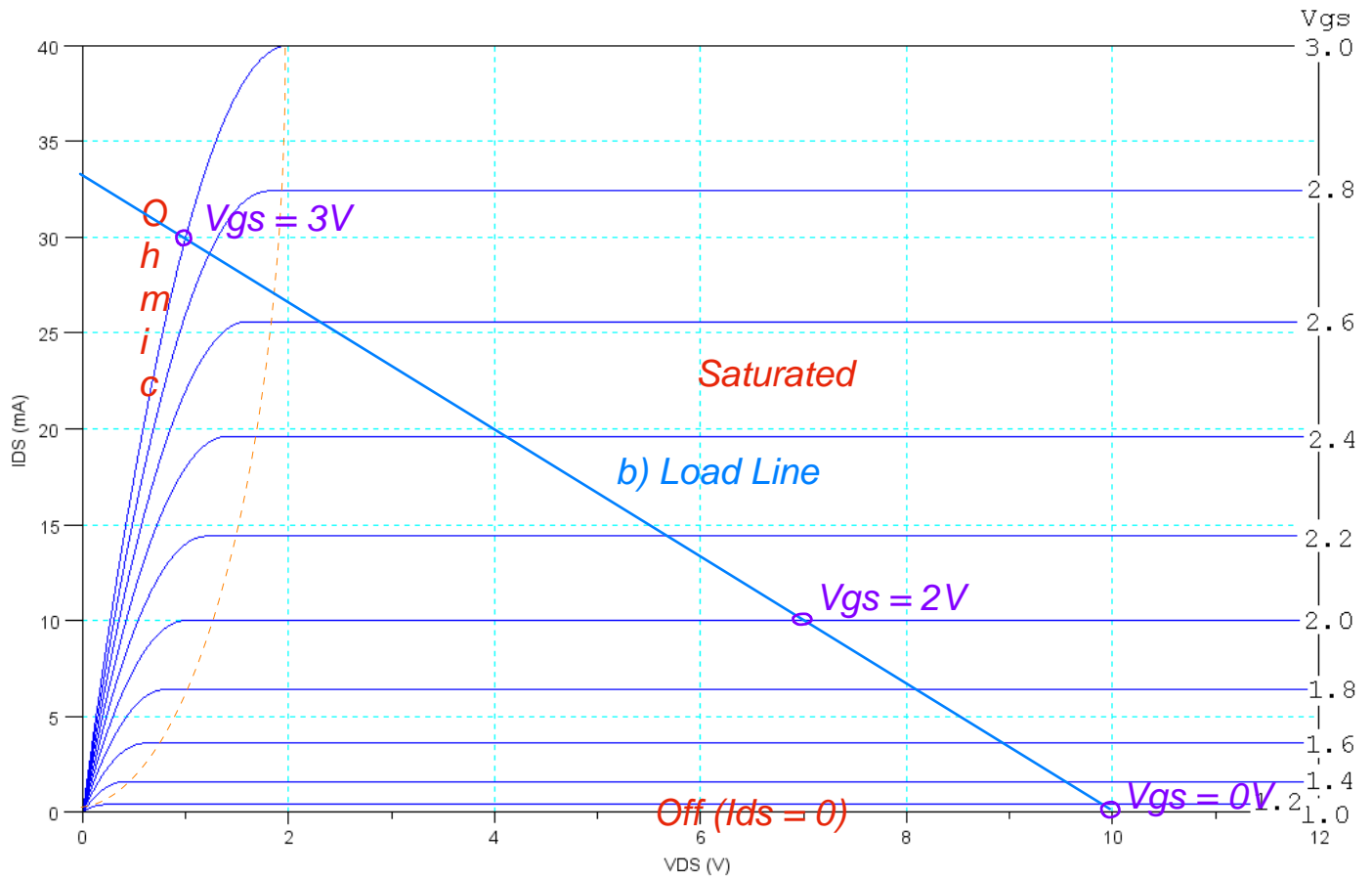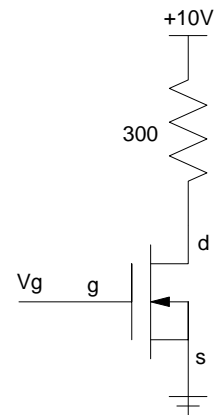- 2) Label the off / saturated / and ohmic regions.
- 3) Determine the turn-on voltage and transconductance gain,  $g_m$
- 4) Draw the load-line for the circuit shown to the right.
- 5) Determine the Q-point for

- $V_g = 0V$        $V_{ds} = 10V$        $I_{ds} = 0mA$       off
- $V_g = 2V$        $V_{ds} = 7V$        $I_{ds} = 10mA$       saturated
- $V_g = 3V$        $V_{ds} = 1V$        $I_{ds} = 30mA$       Ohmic



6) Design a circuit to turn on and off a 12V DC motor which draws 3A. Assume the MOSFET characteristics are:


- $V_{DS \text{ max}} = 100V$
- $I_{D \text{ max}} = 11A$  (continuous)
- $R_{DS} = 173 \text{ m}\Omega @ I_D = 5A, V_{GS} = 10V$
- $V_T = 2V @ 1mA$

MOSFET's are actually really easy to use as a switch:

- The motor acts like a 4 Ohm resistor (12V @ 3A)
- The MOSFET acts like a 0.173 Ohm resistor when  $V_{GS} = 10V$ .
- The net current when on ( $V_{GS} = 10V$ ) is approximately:

$$I_{ds} \approx \left( \frac{10V}{4\Omega + 0.173\Omega} \right) = 2.39A$$

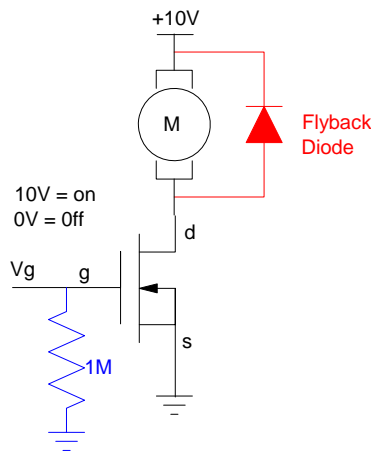- The current when  $V_{GS} = 0V$  is 0 (the MOSFET is off)



More Exact Solution: The resistance changes when you change  $I_{ds}$  - so it's not exactly 0.173 Ohms in this case. To get a more accurate answer, first, find  $K_n$ . In the ohmic region

$$R_{DS} = 0.173 \text{ when } V_{GS} = 10V \text{ and } I_{ds} = 5A \text{ (meaning } V_{ds} = R_{ds} * I_{ds} = 0.865V \text{)}$$

$$I_{ds} = k_n \left( V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$

$$5A = k_n \left( 10V - 2V - \frac{0.865V}{2} \right) 0.865V$$

$$k_n = 0.7638 \frac{A}{V^2}$$

For the above circuit with a 4 Ohm resistor

$$I_{ds} = 0.7638 \left( 10V - 2 - \frac{V_{ds}}{2} \right) V_{ds}$$

$$V_{ds} = 10 - 4I_{ds}$$

Solving 2 equations for 2 unknowns numerically:

$$I_{ds} = 2.3993A \quad (\text{vs. } 2.39A \text{ computed above})$$

$$V_{ds} = 0.4028V$$

$$R_{ds} = \left( \frac{V_{ds}}{I_{ds}} \right) = 0.168\Omega \text{ (vs. } 0.173 \text{ Ohms assumed above)}$$

More Fun: What if you change the input voltage at  $V_g$  to 0V / 5V?

Repeating the previous calculations

$$k_n = 0.7638$$

$$I_{ds} = 0.7638 \left( 5V - 2 - \frac{V_{ds}}{2} \right) V_{ds}$$

$$V_{ds} = 10 - 4I_{ds}$$

Solving numerically:

$$I_{ds} = 2.200A \quad (\text{vs. } 2.39A)$$

$$V_{ds} = 1.200V$$

$$R_{ds} = V_{ds} / I_{ds} = 0.5455 \text{ Ohms}$$

## Term Project (part 1)

Lab: 7-10) Design, build, and test one part of your term project

7) Requirements: Specify

- Inputs
- Outputs
- How they relate

8) Analysis: Give calculations for resistors, capacitors, etc. for a circuit which meets these requirements.

9) Testing: Simulate your circuit in PartSim (or similar software) to check if your calculations were correct.

10) Validation: Build your circuit and collect data to verify your design meets your requirements.