

# ECE 320: Quiz #7: Name \_\_\_\_\_

Comparitors, Schmitt Triggers, DTL Logic. October 18, 2017



- 1) A light sensor has the following light / resistance relationship.

$$R = \frac{100,000}{Lux} \Omega$$

Design a comparator so that the output is

- $Y = 0V$  when the light level is  $> 20$  Lux
- $Y = 10V$  when the light level is  $< 20$  Lux

$$20 \text{ Lux} = 5000 \Omega$$

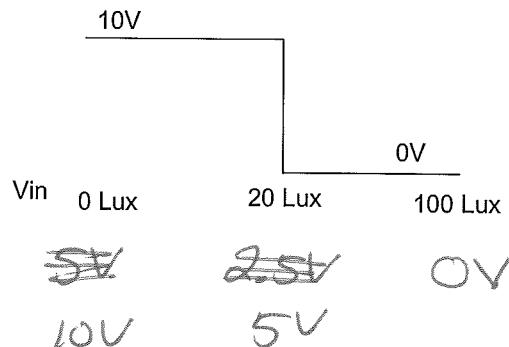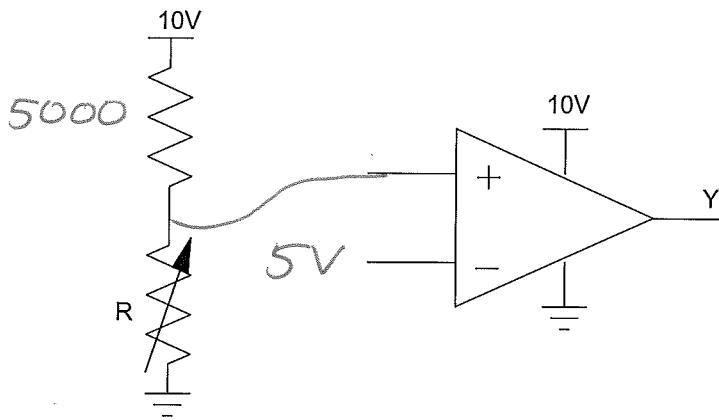


1) A light sensor has the following light / resistance relationship.

$$R = \frac{100,000}{Lux} \Omega$$


Design a Schmitt Trigger so that the output is

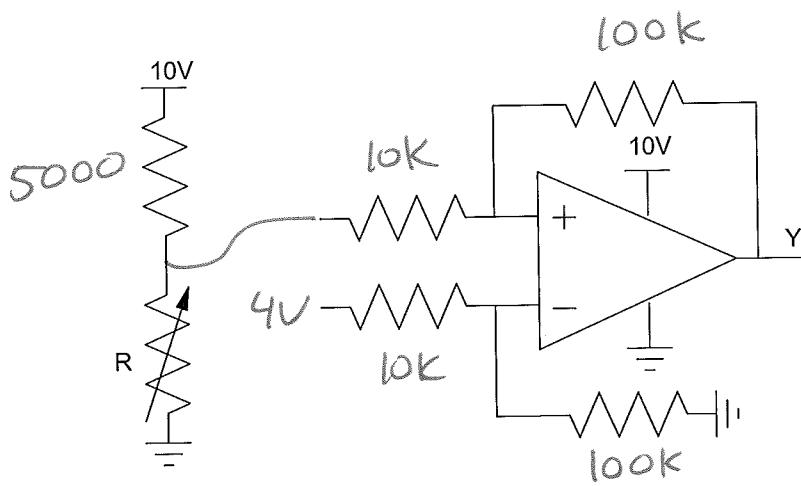- $Y = 0V$  when the light level is  $> \frac{30}{20}$  Lux
- $Y = 10V$  when the light level is  $< \frac{30}{20}$  Lux



when  $V_o = 0$

switches at 4V

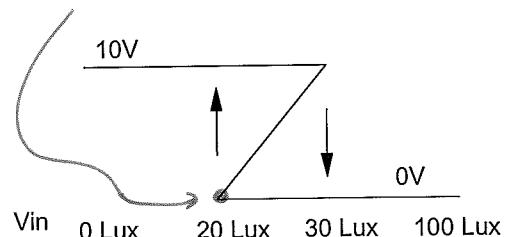


$$\text{at } 4V \quad 5000 \Omega \quad 333 \Omega$$

$$\text{gain} = \frac{10V - 0V}{5V - 4V} = 10$$

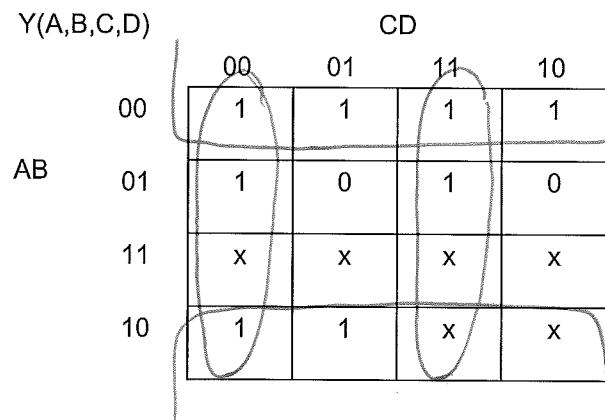3) Given the following Karnaugh map, determine  $Y = f(A,B,C,D)$ .

$$Y = \overline{B} + CD + \overline{C}\overline{D}$$




$$y = \overline{C}\overline{D} + CD + \overline{B}$$

4) For the followint DTL AND gate, determine the voltages V1 .. V4. Assume ideal silicon diodes and transistor with

- $V_f = 0.7V$
- $\beta = 100$
- $V_{ce(sat)} = 0.2V$

V1	V2	V3	V4
.7	5	1.4	0.2

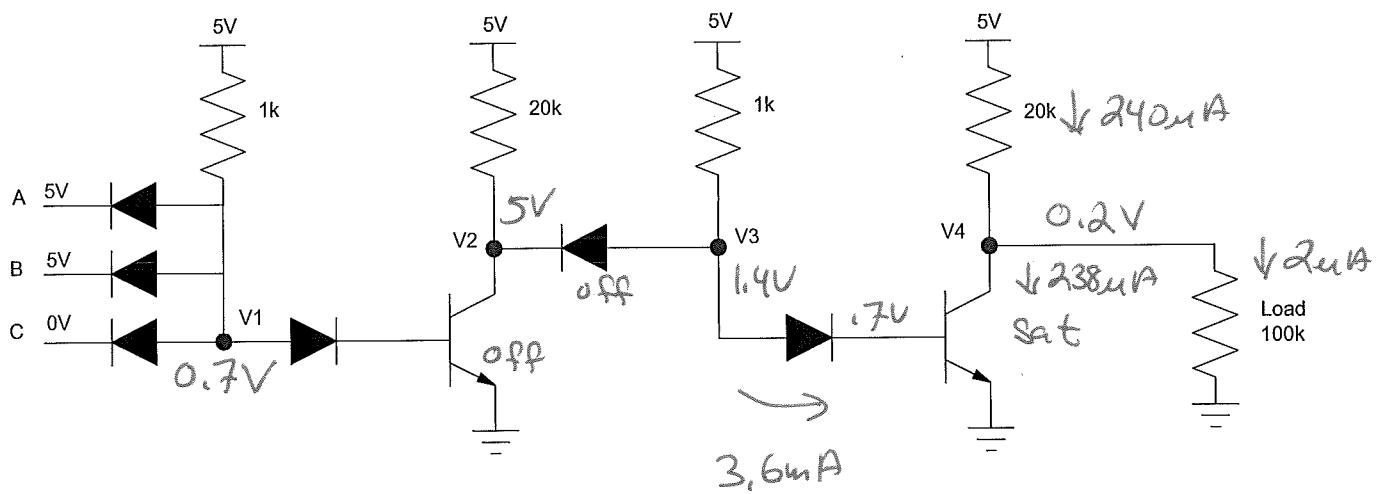

~~$\beta I_b > I_c$~~


$360\mu A > 238\mu A$

Saturated

5) For the following DTL OR gate, determine the voltages and currents. Assume ideal silicon diodes and transistor with

- $V_f = 0.7V$
- $\beta = 100$
- $V_{ce(sat)} = 0.2V$

I1	I2	V3	V4
0	195μA	5.3V	0.2V

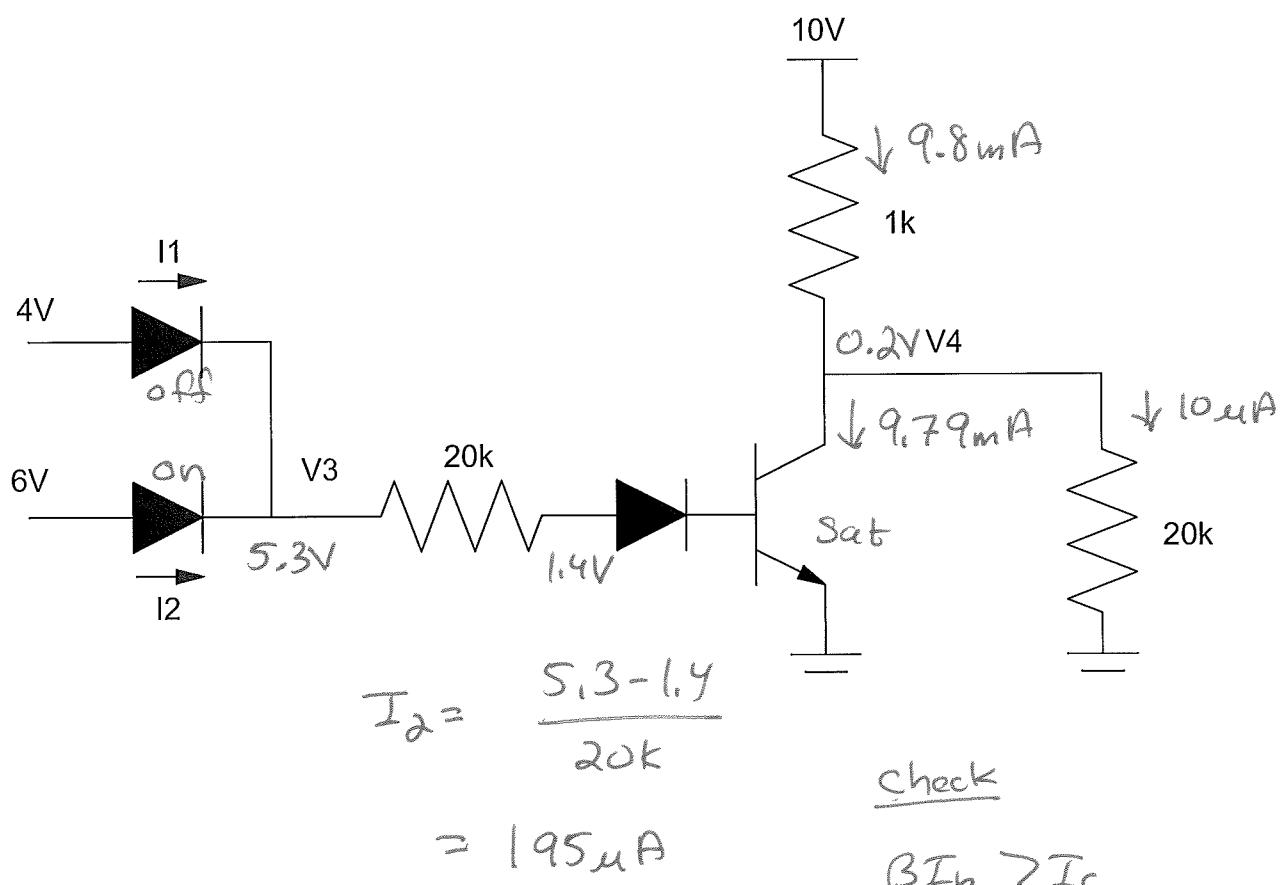

yes - saturated

Bonus! The United States uses 1 trillion kWh of electricity in 2015. According to the National Renewable Energy Lab, what percentage of that energy could North Dakota produce with wind energy?

25%