ECE 320 - Homework #6

H-Bridge, DC to DC Converters. Due Monday, October 2nd, 2017

H-Bridge

1) Assume $\beta = 100$ (worst case) for each transistor. Determine the currents and voltages for the following H-bridge



First, compute the base currents

 $\left(\frac{5-0.7V}{2k}\right) = 2.15mA$ $\left(\frac{5-0.7}{10k}\right) = 0.43mA$ $\beta I_b = 215mA$ $\beta I_b = 43mA$ This leg allows 215mA to flow
This leg allows 43mA to flow

The 25 Ohm load limits the current to

$$I_{\max} = \left(\frac{5V - 0.2V - 0.2V}{25\Omega}\right) = 184mA$$

The smallest current wins:

The current through the load is 43mA

The lower left transistor is saturated:

 $\beta I_b > I_c$

215mA > 43mA

meaning

Vce = 0.2V

The upper right transistor is active

$$\beta I_b = I_c$$

2) Redesign the above circuit to meet the following requirements:

Input:

- Four binary signals, ABCD, each 0V/5V, capable of driving up to 25mA

Output:

• 25 Ohm load

Relationship:

- Inputs ABCD can cause the load to see
 - +200mA +/- 30mA
 - -200mA +/- 30mA
 - 0mA

Solution:

Assume the transistors are saturated or off. The voltage drops should be 0.2V, giving

$$I_{load} = \left(\frac{5V - 0.2V - 0.2V}{25\Omega}\right) = 184mA$$

To saturate the transistors, you need at least 1.84mA flowing in the base. Let Ib = 3mA to be safe.

$$R_b = \left(\frac{5V - 0.7V}{3mA}\right) = 1433\Omega$$



3) Check your design in PartSim (or similar program) for the three modes of operation in the requirements Forward: +184mA (computed), +187mA (simulated)



Reverse: -184mA (comptued), -187mA (simulated)



Off: All transistors turned off

- 0mA computed
- 0.024pA simulated



Lab)

4) Build your redesigned circuit in lab and verify its operation. For the load, use

- A DC motor, or
- An 8 Ohm speaker (with 16 Ohms added to it)



Analysis:

- 5) For the above DC to DC converter, determine
- V1: DC Value

$$V_{1dc} = 0.4 \cdot 12V + 0.6 \cdot (-0.7V) = 4.38V$$

V1: AC Value

$$V_{1pp} = 12.7 V_{pp}$$

V2: DC. Same as V1

$$V_{2dc} = 4.38V$$

V2: AC

$$V_{2pp} = \left(\frac{-j53||100}{-j53||100+j628}\right) V_{1pp}$$
$$V_{2pp} = (0.0798) \cdot 12.7 V_{pp}$$
$$V_{2pp} = 1.0131 V_{pp}$$

Design:

6) Redesign the above DC to DC converter to meet the following requirements:

- Input: +12VDC, capable of 3A
- Output: 100 Ohm resistor
- Relationship: The voltage at V2 under load is +5V with 100mVpp ripple.

Duty Cycle: 44.88%

 $12V \cdot X - 0.7V \cdot (1 - X) = 5V$ $X = \frac{5.7}{12.7} = 0.488$

For the ripple to go from 12.7Vpp to 0.1Vpp,

$$\begin{pmatrix} \frac{1}{\omega C} \\ \omega L \end{pmatrix} = \frac{0.1 V_{pp}}{12.7 V_{p_l}}$$
$$\omega^2 LC = 127$$

Let L = 100 mH

C = 32 u F

7) Check your design in PartSim:



Use a PNP transistr and a pulse generator to create the pulse input. Note that the transistor is on when the base voltage is 0V, so the on-time is 55.12% (transistor is on 44.88%)

C = 0.0001 mF: This shows the ripple due to the inductor alone (mostly).

- The DC voltage is 5.00V as desired
- The ripple is 3.03Vpp





PartSim crashes



