


# ECE 320 - Quiz #2 - Name \_\_\_\_\_

LEDs, ideal diodes. September 12, 2018

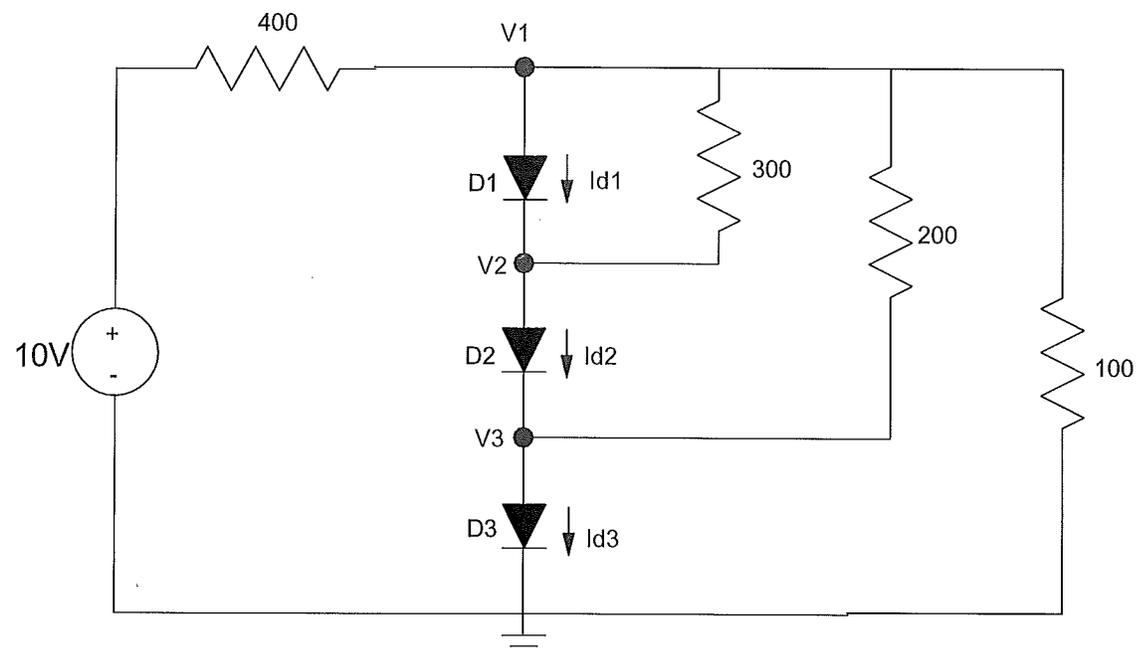1) Assume the characteristics for a diode are

$$V_d = 0.052 \cdot \ln\left(\frac{I_d}{10^{-8}} + 1\right) \quad I_d = 10^{-8} \left(\exp\left(\frac{V_d}{0.052}\right) - 1\right)$$


Write N equations to solve for the unknown voltages for the following circuit.



$I_{d1} = 10^{-8} \left( \exp\left(\frac{V_1 - V_2}{.052}\right) - 1 \right)$
$I_{d2} = 10^{-8} \left( \exp\left(\frac{V_2 - V_3}{.052}\right) - 1 \right)$
$I_{d3} = 10^{-8} \left( \exp\left(\frac{V_3}{.052}\right) - 1 \right)$
$\frac{V_1 - 10}{400} + I_{d1} + \frac{V_1 - V_2}{300} + \frac{V_1 - V_3}{200} + \frac{V_1}{100} = 0$
$-I_{d1} + I_{d2} + \frac{V_2 - V_1}{300} = 0$
$-I_{d2} + I_{d3} + \frac{V_3 - V_1}{200} = 0$


2) The VI characteristics for the diode are shown on the following graph. Draw the load-line for the following circuit and determine the voltage and current through the diode.

Load Line	Vd	Id
show on graph	3.2V	58mA

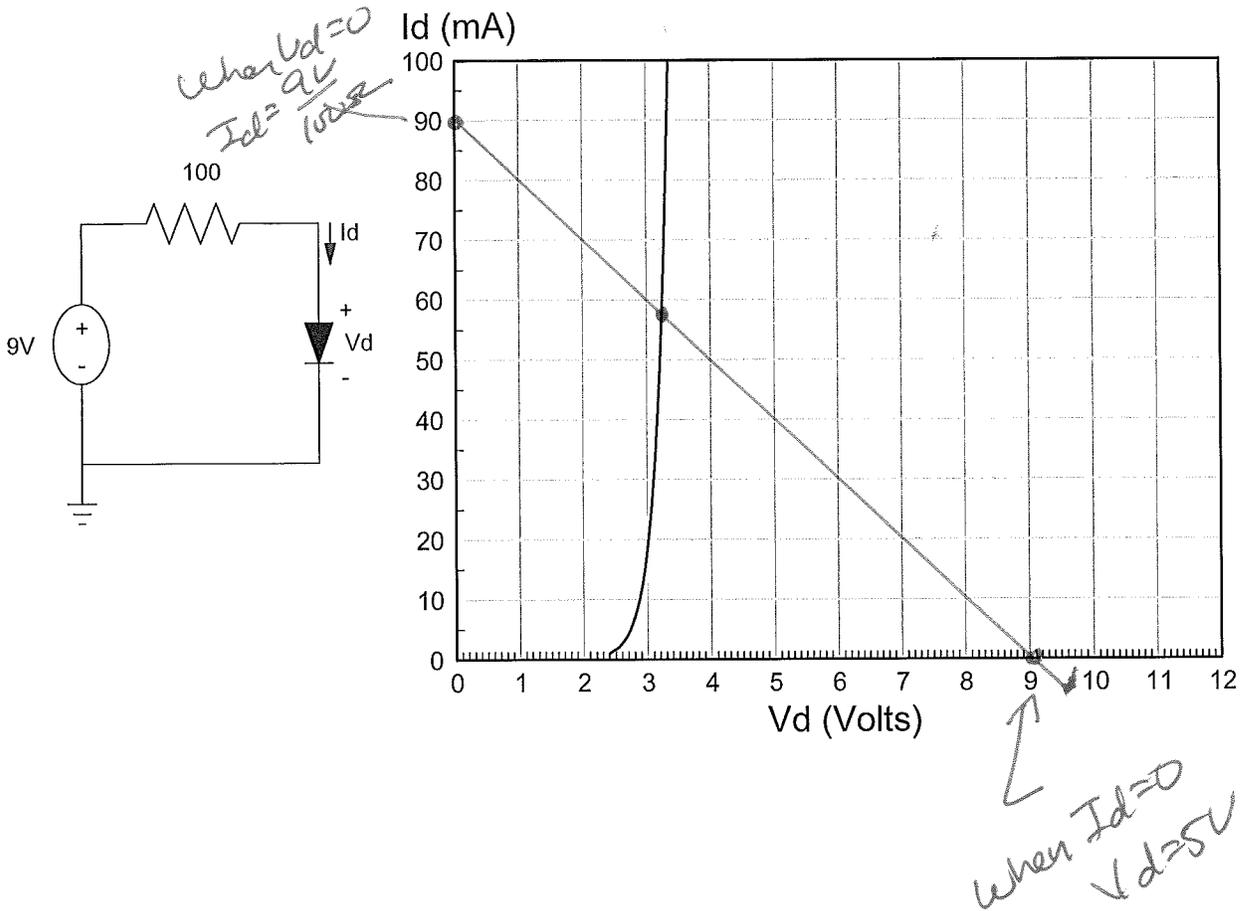


3) Assume ideal silicon diodes ( $V_f = 0.7V$ ). Determine the voltages and currents for the following circuit

V1	V2	V3	Id1	Id2	Id3
2.1	1.4	0.7	48.67 $\mu$ A	51 $\mu$ A	58 $\mu$ A

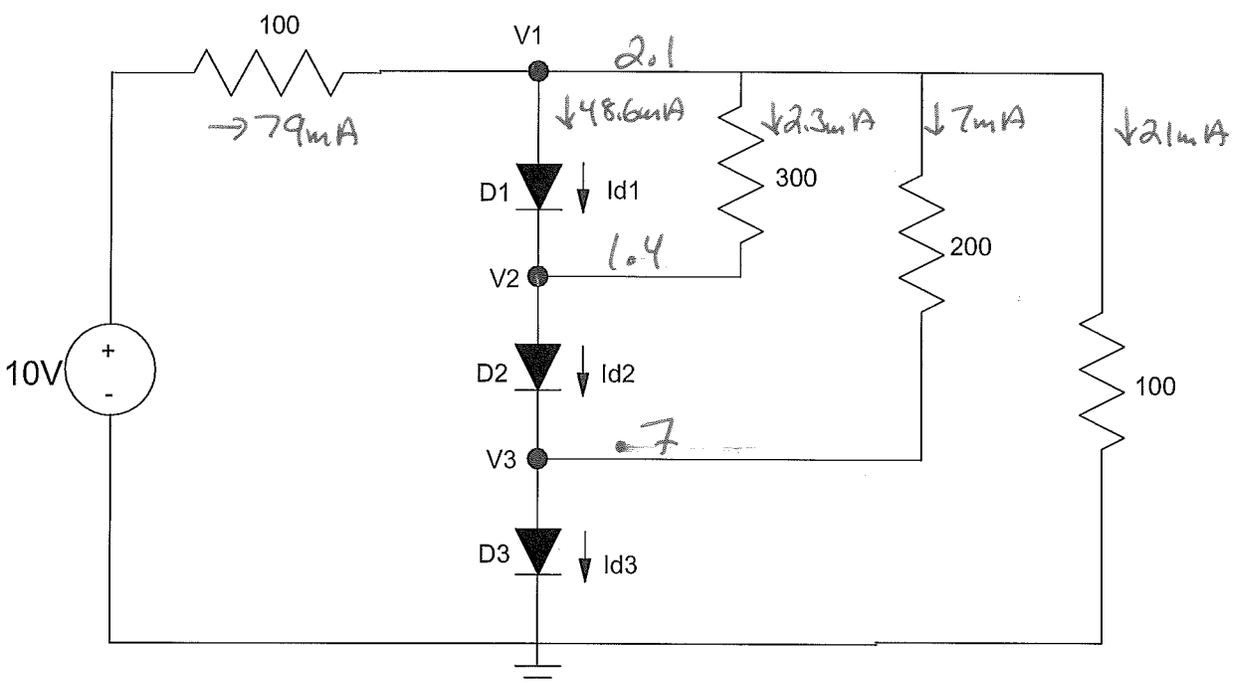

4) Assume ideal silicon diodes ( $V_f = 0.7V$ ). Determine the voltages and currents for the following circuit.

V1	V2	V3	Id1	Id2	Id3
1.592V	1.4V	0.7V	0	640 $\mu A$	52 $\mu A$

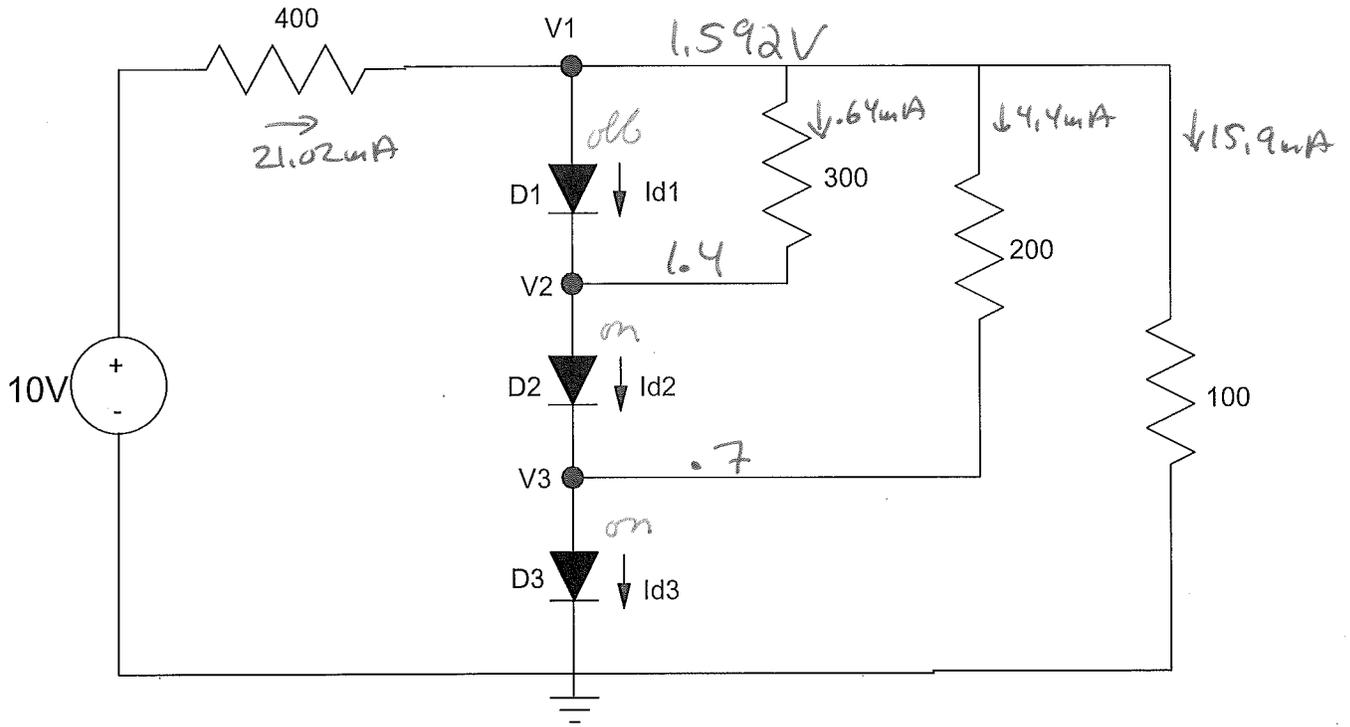

$$\frac{V_1 - 10}{400} + \frac{V_1 - 1.4}{300} + \frac{V_1 - 0.7}{200} + \frac{V_1}{100} = 0$$

$$V_1 = 1.592V$$

$$\frac{V_1 - 10}{400} + \frac{V_1 - 1.4}{300} + \frac{V_1 - 0.7}{200} + \frac{V_1}{100} = 0$$

$$V_1 = 1.592V$$

5) The specifications for a RGB LED are:

Color	Vf @ 20mA	mcd @ 20mA
red	2.0V	10,000
green	3.2V	10,000
blue	3.2V	10,000

Determine the resistors so that the LED outputs aqua blue light:




- Red = 4000 mcd  $8\text{mA}$
- Green = 3000 mcd  $6\text{mA}$
- Blue = 10,000 mcd  $20\text{mA}$

R(red)	R(green)	R(blue)
1000	1133	340

$$\frac{10 - 2}{8\text{mA}} = 1000$$

$$\frac{10 - 3.2}{6\text{mA}} = 1133$$

$$\frac{10 - 3.2}{20\text{mA}} = 340$$

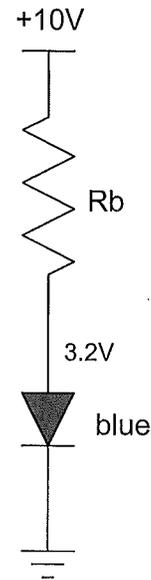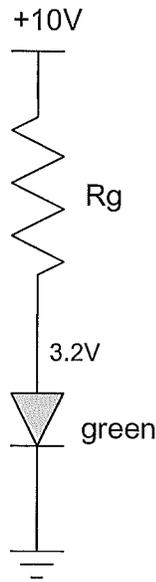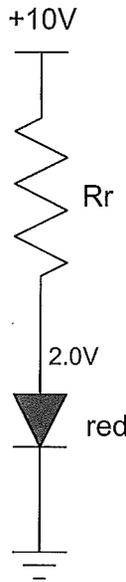

Bonus! Insurance is shared risk. For some things, insurance works well. For others, it does not.

Does insurance work with health care? Explain why or why not.

yes : 22

|||||  
|||||  
||

no : 15

|||||  
|||

no & ans : 11

|||||  
|