


ECE 320 - Quiz #3 - Name _____

AC to DC Converters, Max/Min, Clippers. September 20, 2018

- 1) Determine the DC and AC voltages for V1 and V2. Assume ideal silicon diodes ($V_f = 0.7V$)

V1		V2	
DC (max of V1)	AC (V1pp)	DC (mean)	AC (V2pp)
9.3V	.6458V _{pp}	7.48V	.0893V _{pp}

$$DC = 8.97V$$

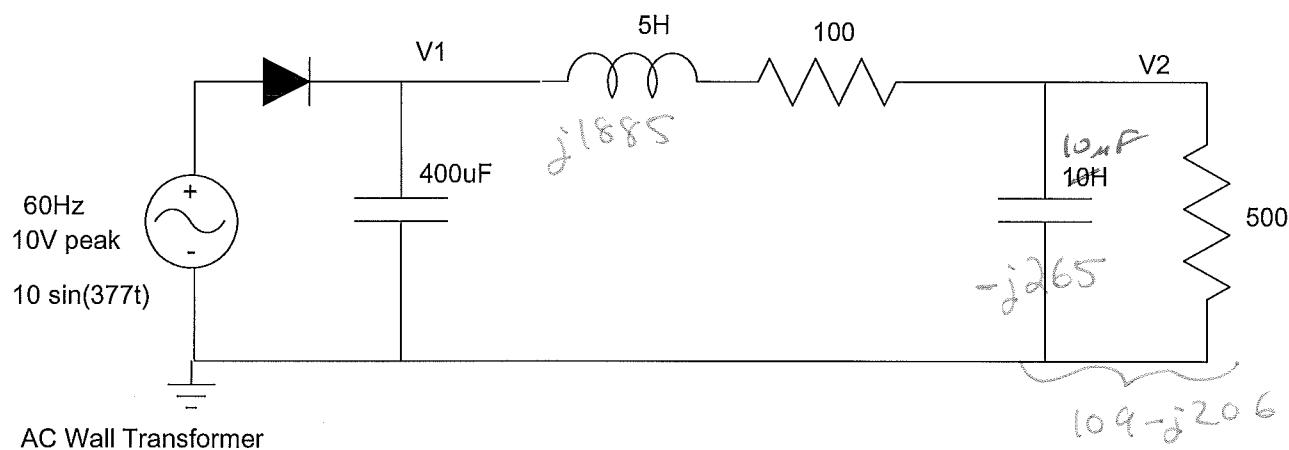

$$I = 9.3V / 600\Omega = 15.5mA$$

(a little high - should use $V_1(DC)$)

$$V_2(DC) = \left(\frac{500}{500+100} \right) 8.97$$

$$V_2(DC) = 7.48V$$

$$I = C \frac{dN}{dt}$$

$$15.5mA = 400\mu F \cdot \frac{dN}{dt}$$

$$dN = .6458V$$

$$V_2(AC) = \frac{(109-j206)}{(109-j206)+(100+j1885)}$$

$$= 0.6458$$

$$V_1(DC) = 9.3V - \frac{1}{2}(.6458V)$$

$$V_2(AC) = .0893V_{pp}$$

$$V_1(DC) = 8.97V$$


$$V_2(AC) = \left(\frac{(109-j206)}{(109-j206)+(100+j1885)} \right) \cdot 0.6458V_{pp}$$

2) Find R, L, and C so that the following AC to DC converter has

- 20mA flowing to the load
- 2Vpp ripple at V1
- 500mVpp ripple at V2

Assume ideal silicon diodes ($V_f = 0.7V$)

C1	L	C2	R
$167\mu F$	$3.34H$	0	315Ω

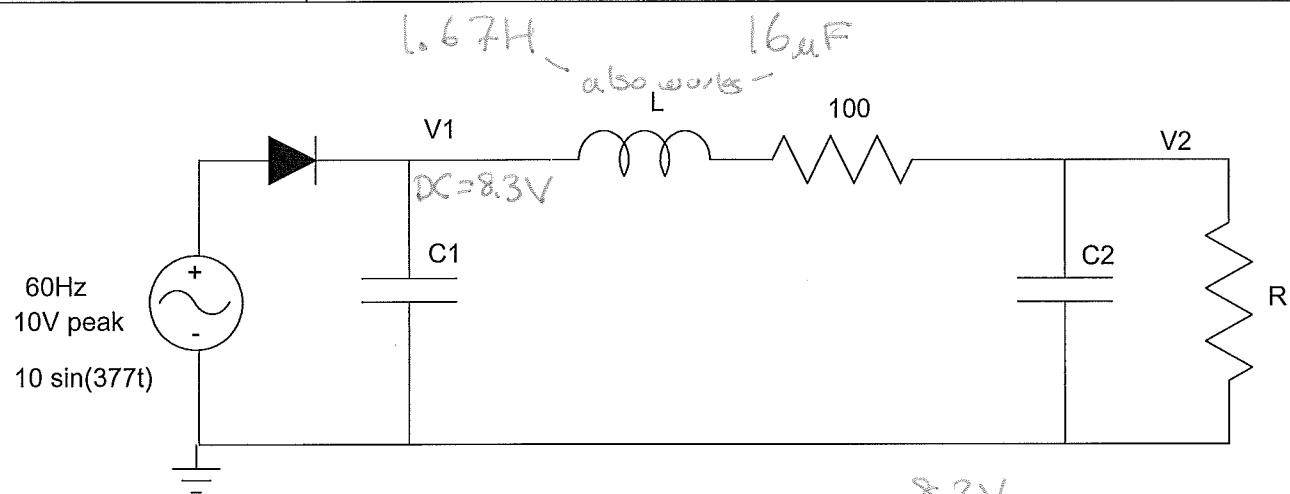

$$R_{\text{total}} = \frac{8.3V}{20\text{mA}} = 415\Omega$$

$$I = G \frac{dy}{dt}$$

$$R = 415 - 100 = 315\Omega$$

$$20\text{mA} = G_i \cdot \frac{2V}{460\Omega}$$

$$\text{Let } \omega L = 4R$$

$$\omega L = 1260$$

$$L = 3.34H$$


$$V_1(\text{peak}) = 9.3V$$

$$V_1(\text{DC}) = 9.3 - \frac{1}{2} \cdot 2V_{\text{pp}}$$

$$V_1(\text{DC}) = 8.3V$$



3) Determine the currents for the following max/min circuit. Assume ideal silicon diodes ($V_f = 0.7V$)

I1	I2	I3	I4	I5	I6
0	6.9mA	.4mA	0	0	9.3mA

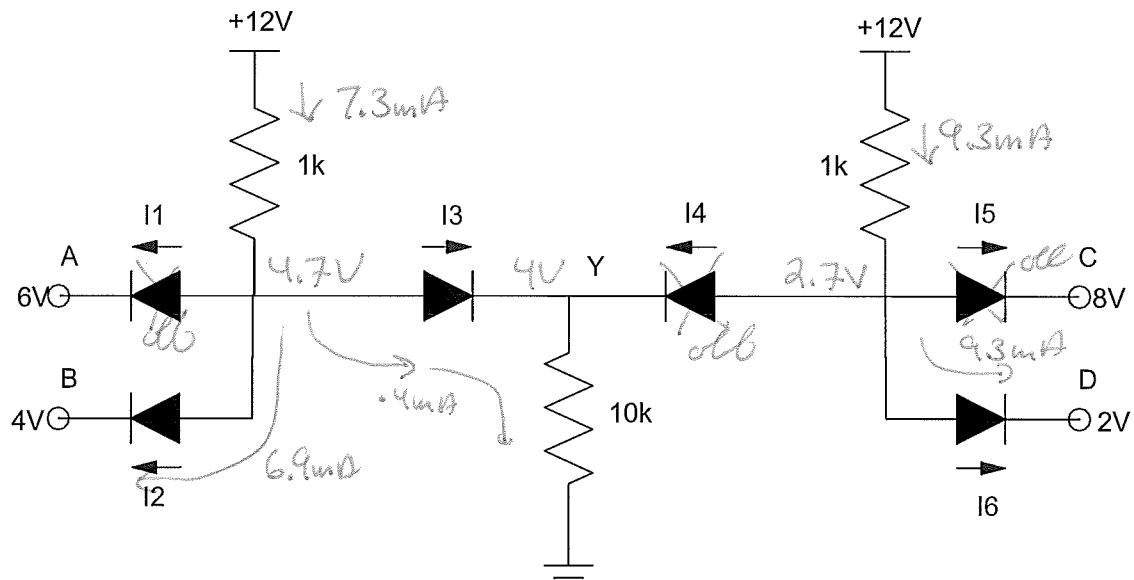


- 4) Design a clipper circuit to approximate the following function (tolerance 0.25 Volts)

R0	R1	Vz1	R2	Vz2
667	1137	5V	189	8.3V

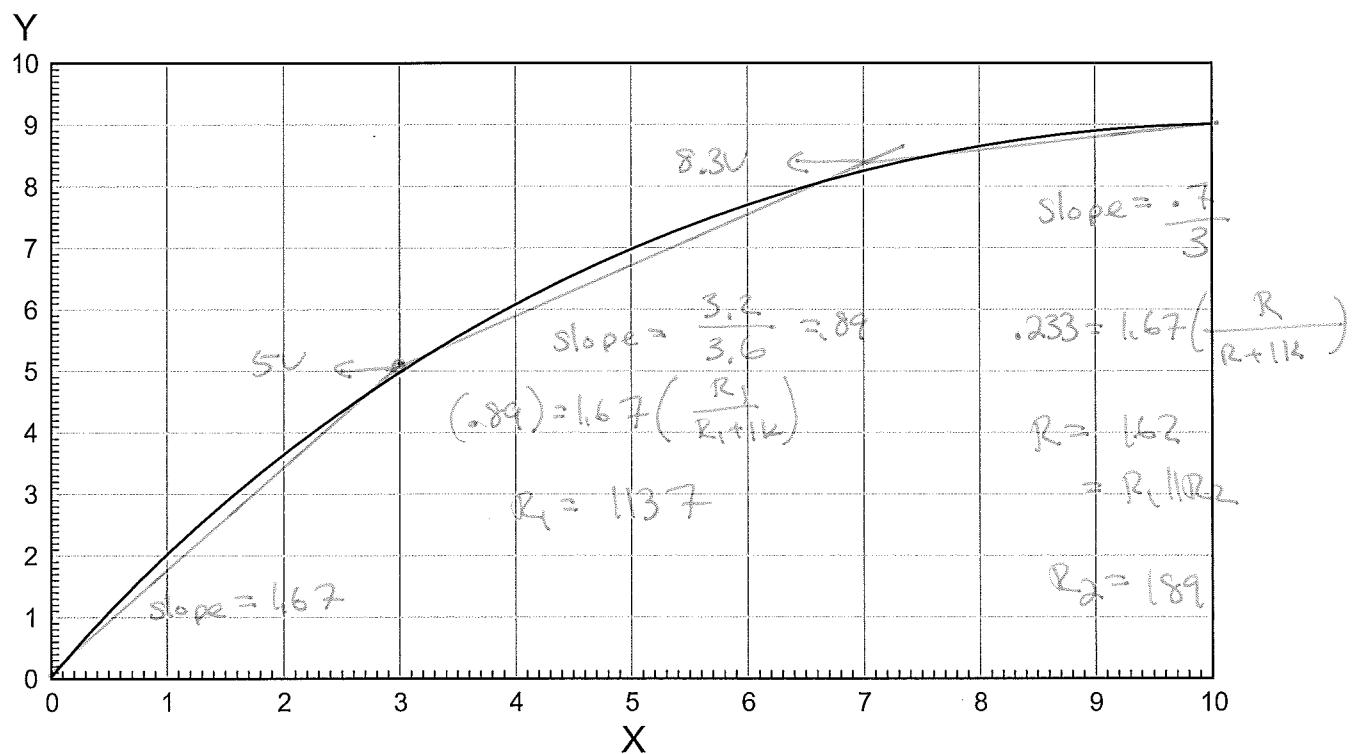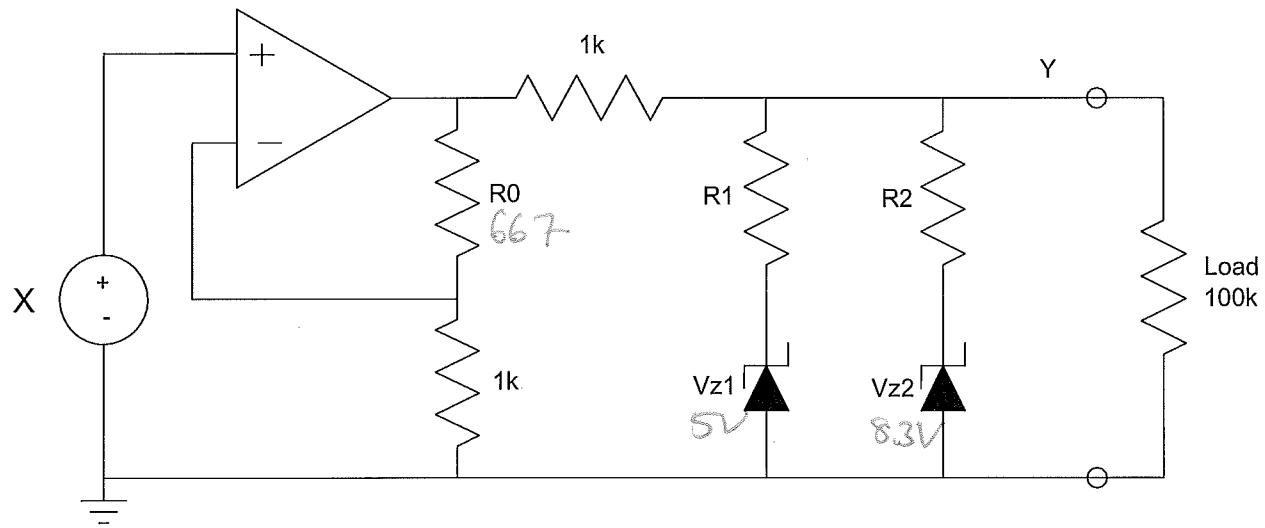

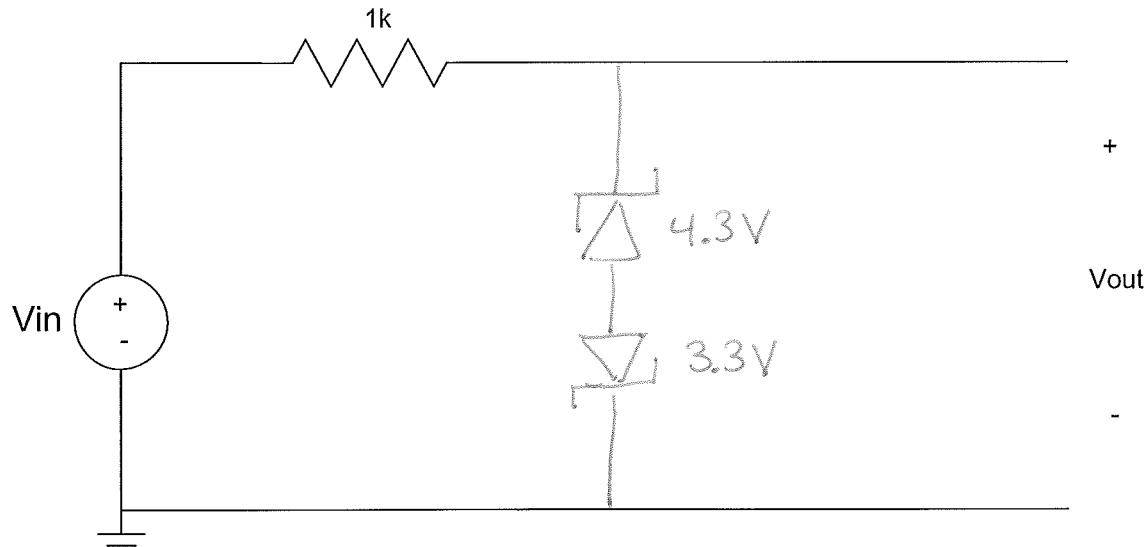5) Design a clipper circuit to limit the output voltage to

$$V_{out} = \begin{cases} +5V & V_{in} > 5V \\ V_{in} & -4V < V_{in} < 5V \\ -4V & V_{in} < -4V \end{cases}$$



Bonus! Where do health care dollars go? The following people are the CEO's of five insurance companies. Within 10%, what was their average annual salary in 2017 (within 10%)?

- John R. Strangfeld, Prudential Insurance \$19.1 million
- Mark T. Bertolini, Aetna \$18.7 million
- Brian A. Kane, Humana \$5.7 million
- David M. Cordani, Cigna \$17.5 million
- Daniel P. Amos, AFLAC \$16.3 million

avg = \$15.5 million /year

your health care dollars
at work...