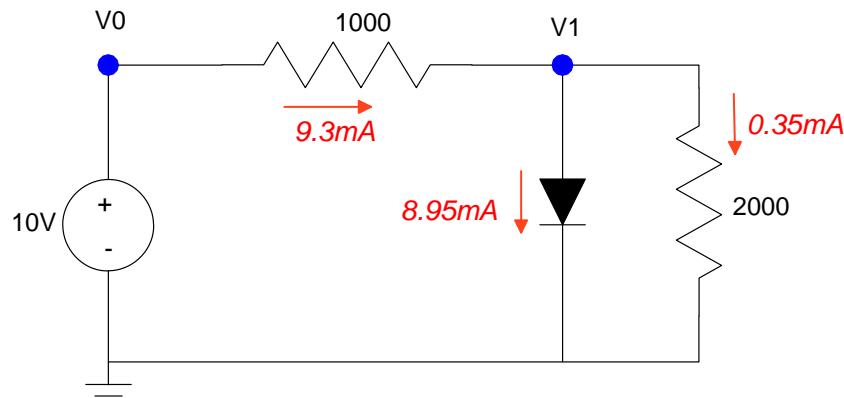


ECE 320 - Solution to Homework #3

Ideal Diodes, Light Emitting Diodes. Due Monday, September 10th, 2018

Ideal Diodes

- 1) Assume ideal silicon diodes. Determine the voltages and currents for this circuit.



Problem 1

Assume the diode is on

$$V_1 = 0.7V$$

The currents must add to zero


$$I_{in} = I_{out}$$

$$\left(\frac{10V - 0.7V}{1k} \right) = I_d + \left(\frac{0.7V}{2k} \right)$$

$$I_d = 8.95mA$$

Check: If the diode is on, the current must be positive.

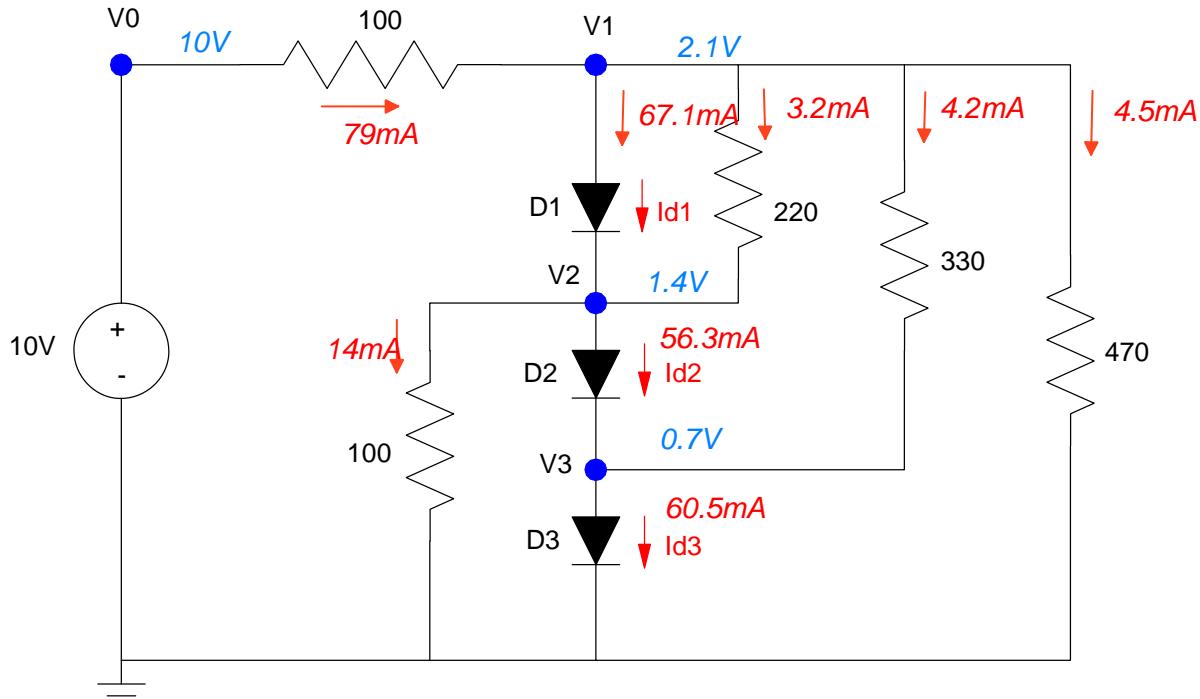2) Assume ideal silicon diodes. Determine the voltages and currents for the following circuit when $V_{in} = 10V$ as shown.



Assume all diodes are on.

- $V_3 = 0.7V, V_2 = 1.4V, V_1 = 2.1V$

Current In = Current out

$$\left(\frac{10V - 2.1V}{100}\right) = I_{d1} + \left(\frac{2.1V - 1.4V}{220}\right) + \left(\frac{2.1V - 0.7V}{330}\right) + \left(\frac{0.7V}{470}\right)$$

$$I_{d1} = 67.1mA$$

$$I_{d1} + \left(\frac{2.1V - 1.4V}{220}\right) = \left(\frac{1.4V}{100}\right) + I_{d2}$$


$$I_{ds} = 56.3mA$$

$$I_{d2} + \left(\frac{2.1V - 0.7V}{330}\right) = I_{d3}$$

$$I_{d3} = 60.5mA$$

Check: For the diodes to be on, $I_{d1} > 0, I_{d2} > 0, I_{d3} > 0$

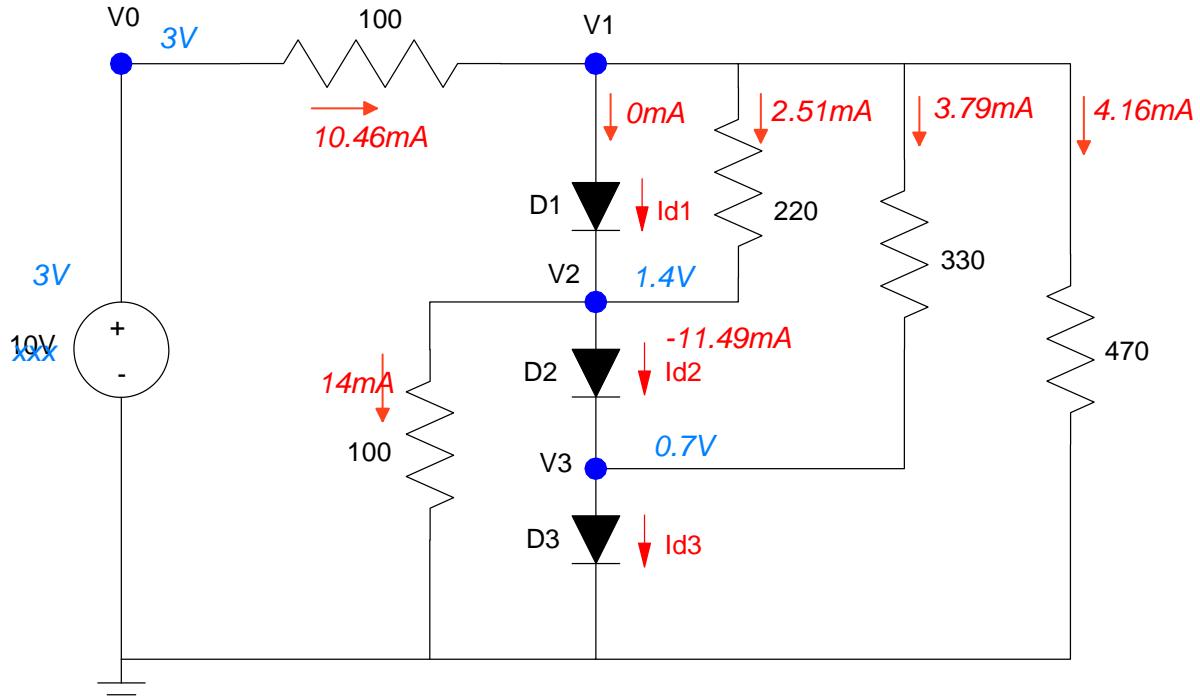- 3) Assume ideal silicon diodes. Determine the voltages and currents when Vin = 3V



Assume all diodes are on. This doesn't work since it results in

$$\left(\frac{3V-2.1V}{100}\right) = I_{d1} + \left(\frac{2.1V-1.4V}{220}\right) + \left(\frac{2.1V-0.7V}{330}\right) + \left(\frac{2.1V}{470}\right)$$

$$9mA = I_{d1} + 3.2mA + 4.2mA + 4.5mA$$

$$I_{d1} = -2.9mA$$

You can't have negative current through a diode

Assume diode 1 is off, the other two are on. Solve for V1 using voltage nodes

$$\left(\frac{V_1-3}{100}\right) + 0 + \left(\frac{V_1-1.4}{220}\right) + \left(\frac{V_1-0.7}{330}\right) + \left(\frac{V_1}{470}\right) = 0$$

$$V_1 = 1.9532V$$


For the currents to balance:

$$\left(\frac{3V-1.95V}{100}\right) = 0mA + \left(\frac{1.95V-1.4V}{220}\right) + \left(\frac{1.95V-0.7V}{330}\right) + \left(\frac{1.95V}{470}\right)$$

$$10.46mA = 0mA + 2.51mA + 3.79mA + 4.16mA$$

The current through Id2 is negative however. This isn't correct.

Assume diode 2 is off:

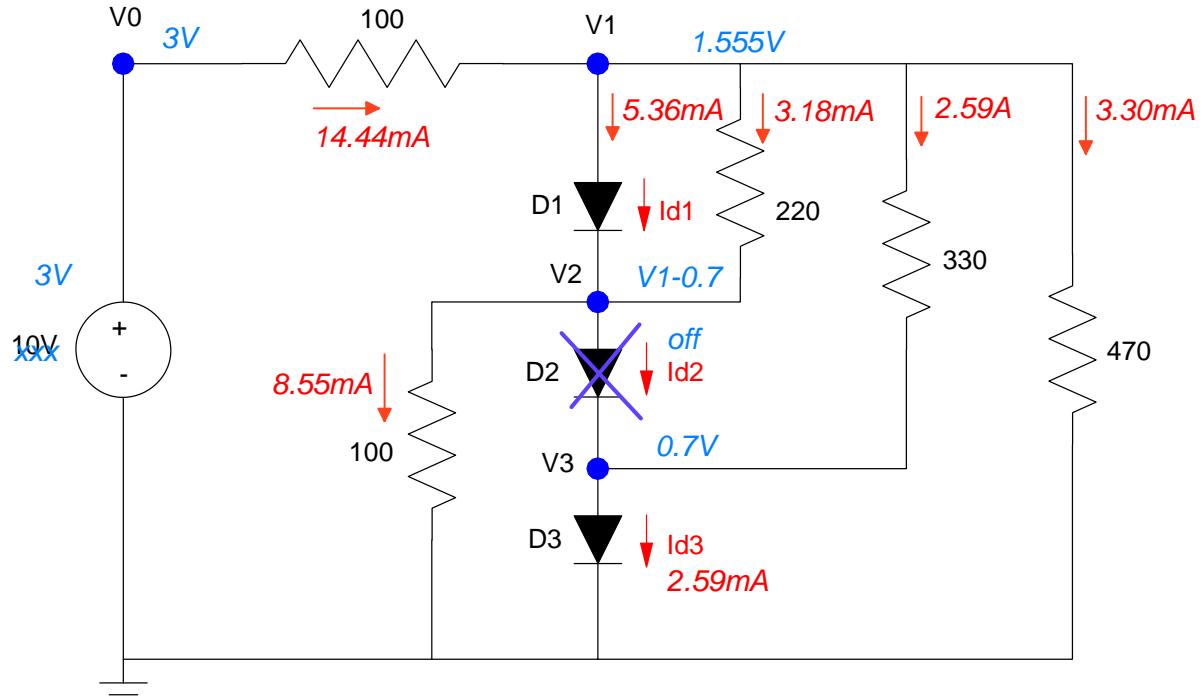

$$\left(\frac{V_1 - 3}{100}\right) + 0 + \left(\frac{V_1 - 0.7}{100}\right) + \left(\frac{V_1 - 0.7}{330}\right) + \left(\frac{V_1}{470}\right) = 0$$

$$V_1 = 1.555V$$

I_{d1} is then

$$\left(\frac{3 - V_1}{100}\right) = I_{d1} + \left(\frac{V_1 - (V_1 - 0.7)}{220}\right) + \left(\frac{V_1 - 0.7}{330}\right) + \left(\frac{V_1}{470}\right)$$

$$14.44mA = I_{d1} + 3.18mA + 2.59mA + 3.30mA$$

$$I_{d1} = 5.36mA$$

$$I_{d2} = 0 \text{ (off)}$$

$$I_{d3} = 2.59mA$$

The Piranah RGB LEDs in lab have the following characteristics:

Color	Vf @ 20mA	mcd @ 20mA
red	2.0V	10,000
green	3.2V	10,000
blue	3.2V	10,000

4) Design a circuit to drive these LEDs with a 10V source to produce purple:

- Red = 5390 mcd (53.9%)
- Green = 1797 mcd (17.97%)
- Blue = 8164 mcd (81.64%)

Red:

$$I_r = \left(\frac{5390 \text{ mcd}}{10,000 \text{ mcd}} \right) 20 \text{ mA} = 10.78 \text{ mA}$$

$$R_r = \left(\frac{10\text{V} - 2.0\text{V}}{10.78\text{mA}} \right) = 742\Omega$$

Green:


$$I_g = \left(\frac{1797 \text{ mcd}}{10,000 \text{ mcd}} \right) 20 \text{ mA} = 3.59 \text{ mA}$$

$$R_g = \left(\frac{10\text{V} - 3.2\text{V}}{3.59\text{mA}} \right) = 1894\Omega$$

Blue:

$$I_b = \left(\frac{8164 \text{ mcd}}{10,000 \text{ mcd}} \right) 20 \text{ mA} = 16.33 \text{ mA}$$
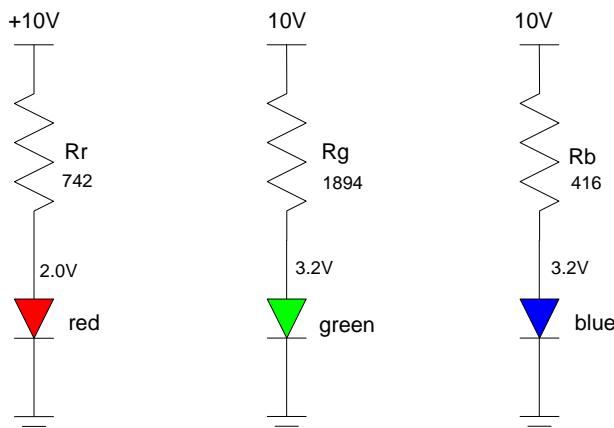
$$R_b = \left(\frac{10\text{V} - 3.2\text{V}}{16.33\text{mA}} \right) = 416\Omega$$



5) Design a circuit to drive these LEDs with a 10V source producing pink:

- Red = 10,000 mcd (100%)
- Green = 7773 mcd (77.73%)
- Blue = 9375 mcd (93.75%)

Red:

$$I_r = \left(\frac{10,000 \text{ mcd}}{10,000 \text{ mcd}} \right) 20 \text{ mA} = 20 \text{ mA}$$

$$R_r = \left(\frac{10V - 2.0V}{20 \text{ mA}} \right) = 400 \Omega$$

Green:


$$I_g = \left(\frac{7773 \text{ mcd}}{10,000 \text{ mcd}} \right) 20 \text{ mA} = 15.55 \text{ mA}$$

$$R_g = \left(\frac{10V - 3.2V}{15.55 \text{ mA}} \right) = 437 \Omega$$

Blue:

$$I_b = \left(\frac{9375 \text{ mcd}}{10,000 \text{ mcd}} \right) 20 \text{ mA} = 18.75 \text{ mA}$$
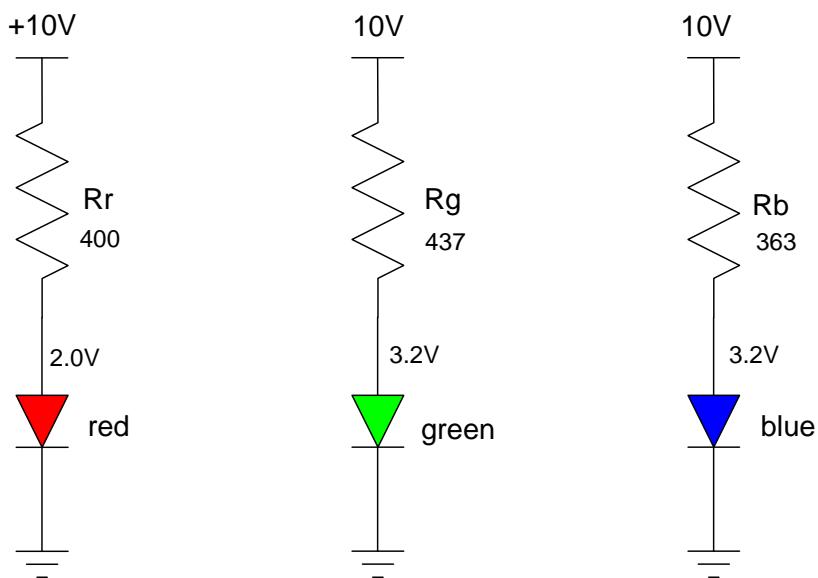
$$R_b = \left(\frac{10V - 3.2V}{18.75 \text{ mA}} \right) = 363 \Omega$$



Pink Light

note: If you want to use two different colors, please do so. You can see the intensity of each color (RGB) on the web site:

<https://www.rapidtables.com/web/color/color-wheel.html>

Lab:

- 6) Build these RGB LED circuits and measure the voltages (and compute the currents)