

# ECE 320 - Final - Name \_\_\_\_\_

Part 1: Semiconductors and Diodes. Fall 2019

## 1) Semiconductors and pn junctions


What are holes and electrons?

Why can current flow p to n for a diode but not n to p?

## 2) Load Lines

Draw the load line for the following circuit. From the load line, determine the operation point ( $I_d$ ,  $V_d$ )


Load Line	$V_d$	$I_d$
show on graph		

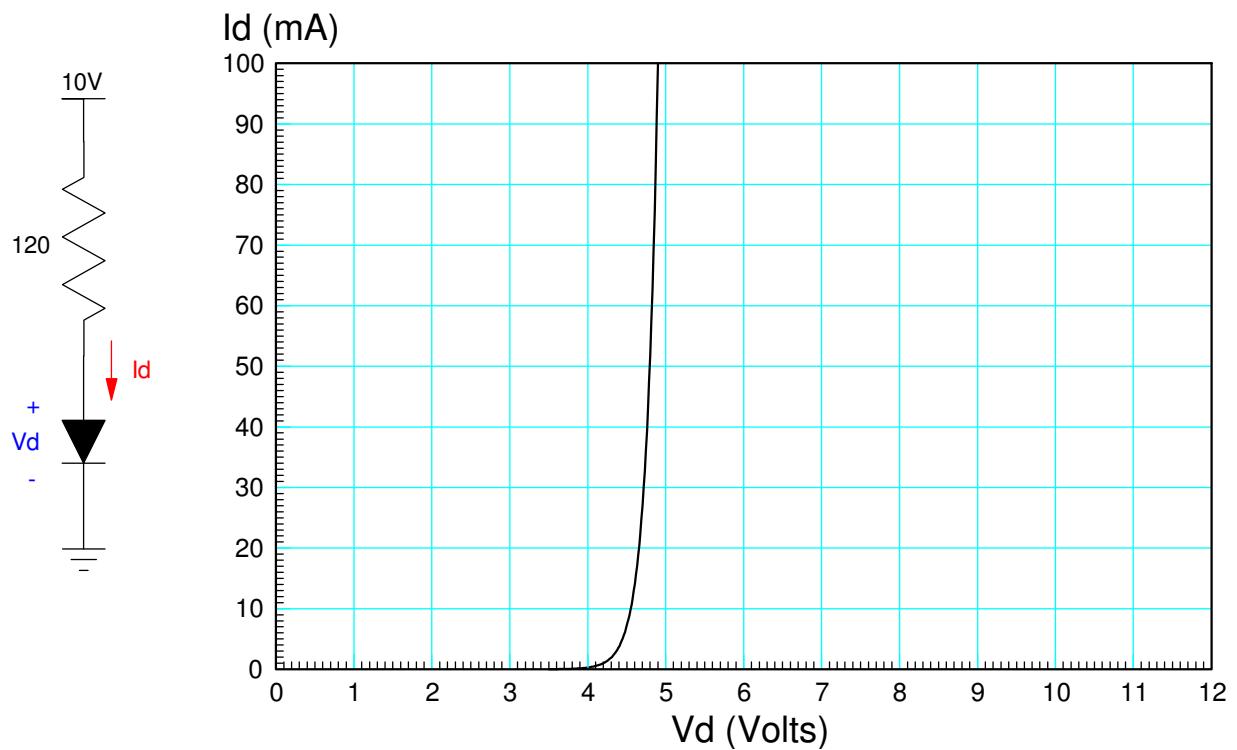

### 3) Ideal Diode

Assume ideal silicon diodes ( $V_f = 0.7V$ ). Determine the voltages and currents for the following circuit


V1	V2	V3	Id1	Id2	Id3

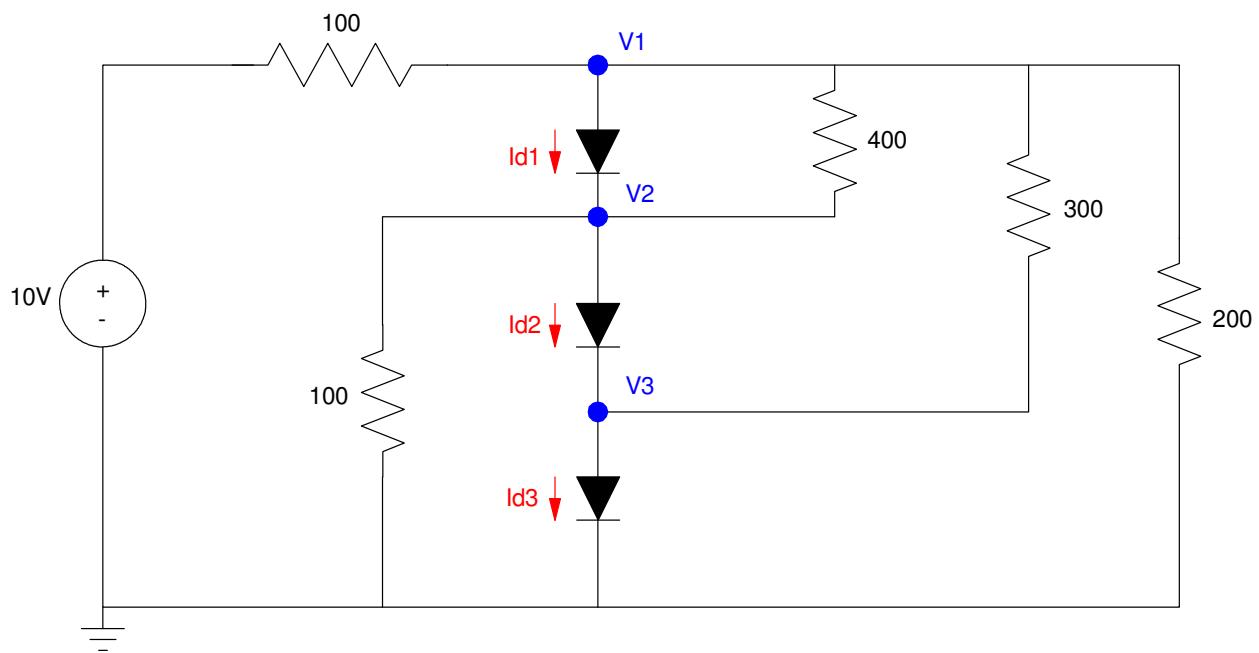

#### 4) AC to DC Converter

Determine the voltages at V1 and V2 (both DC and AC). Assume ideal silicon diodes ( $V_f = 0.7V$ )


V1		V2	
DC ( avg(V1) )	AC ( V1pp )	DC ( avg(V2) )	AC ( V2pp )

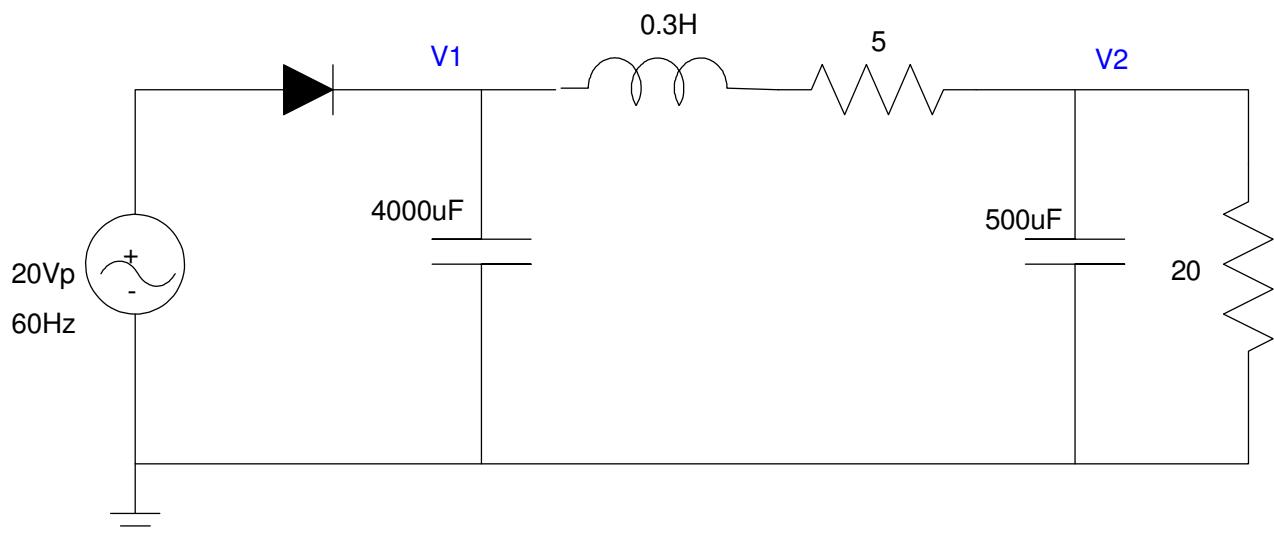

## 5) Max / Min Circuit

Determine the voltages and currents for the following max / min circuit. Assume ideal silicon diodes ( $V_f = 0.7V$ )


I1	I2	I3	I4	I5	I6

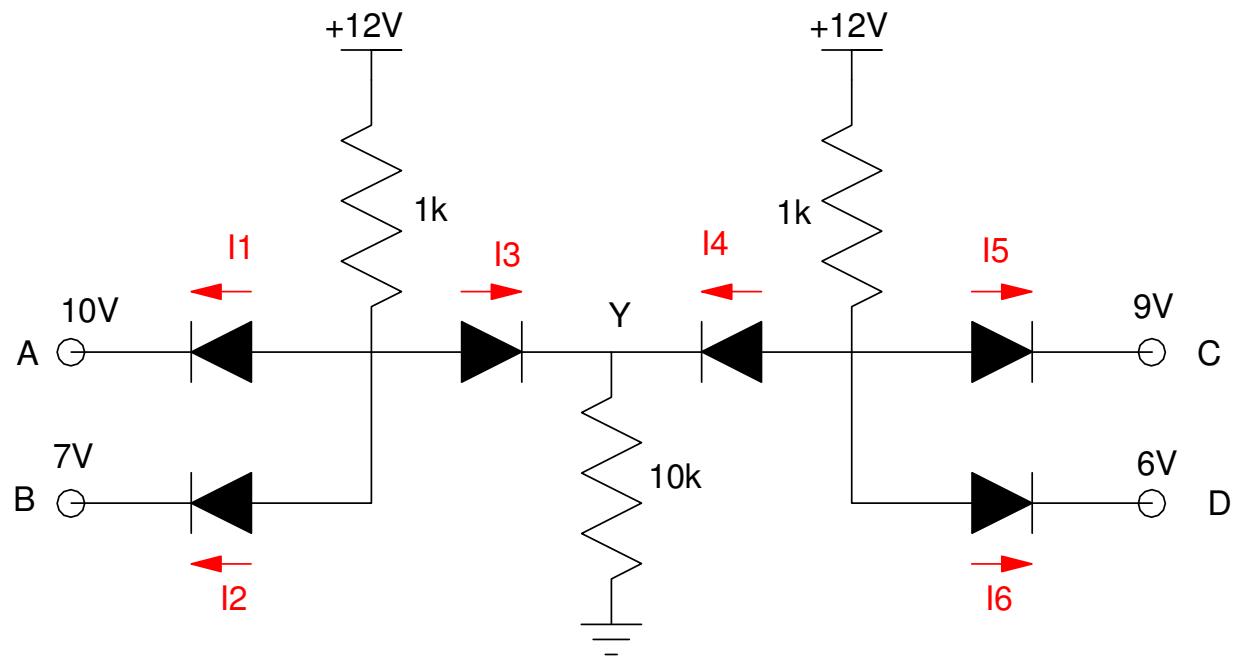

## 6) Buck Converter

Determine the voltages at V1 and V2. Assume ideal silicon diodes ( $V_f = 0.7V$ )

V1		V2	
DC ( avg(V1) )	AC ( V1pp )	DC ( avg(V2) )	AC ( V2pp )

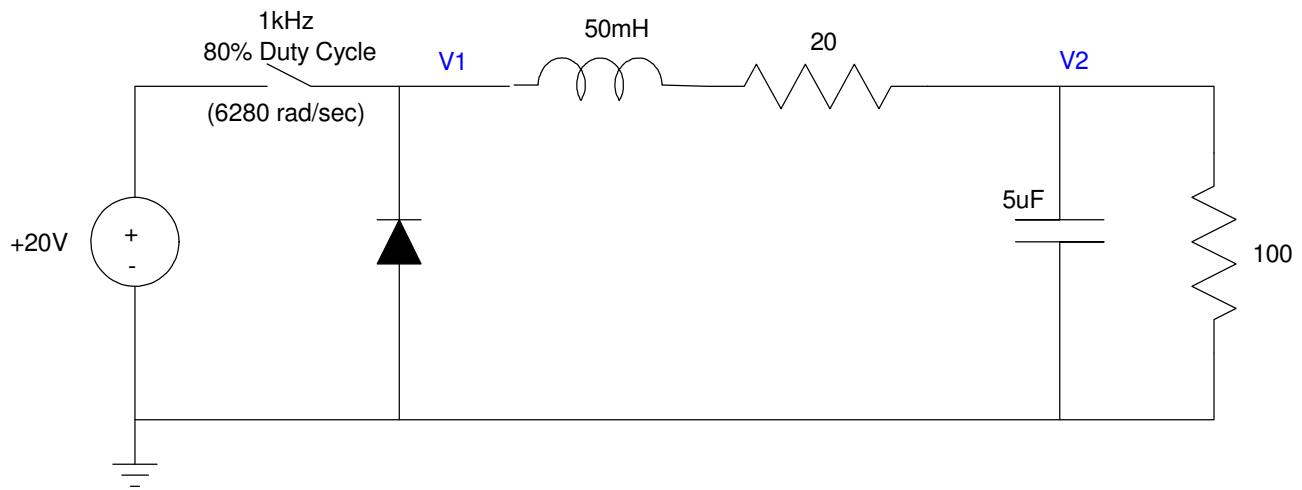

Green New Deal Bonus! Which of the following countries offer tuition-free college? (circle all that apply)

Austria - Denmark - France - Germany -Hungary - Sweeden - Spain - United States


# ECE 320 - Final - Name \_\_\_\_\_

Part 2: Transistors and Op-Amps. Fall 2019

## 1) Transistors and Load Lines

Determine the following for the following transistor circuit


Beta	Load Line	Operating Point for		
		a) $V_{in} = 0V$	b) $V_{in} = 5V$	c) $V_{in} = 10V$
	show on graph	show on graph	show on graph	show on graph

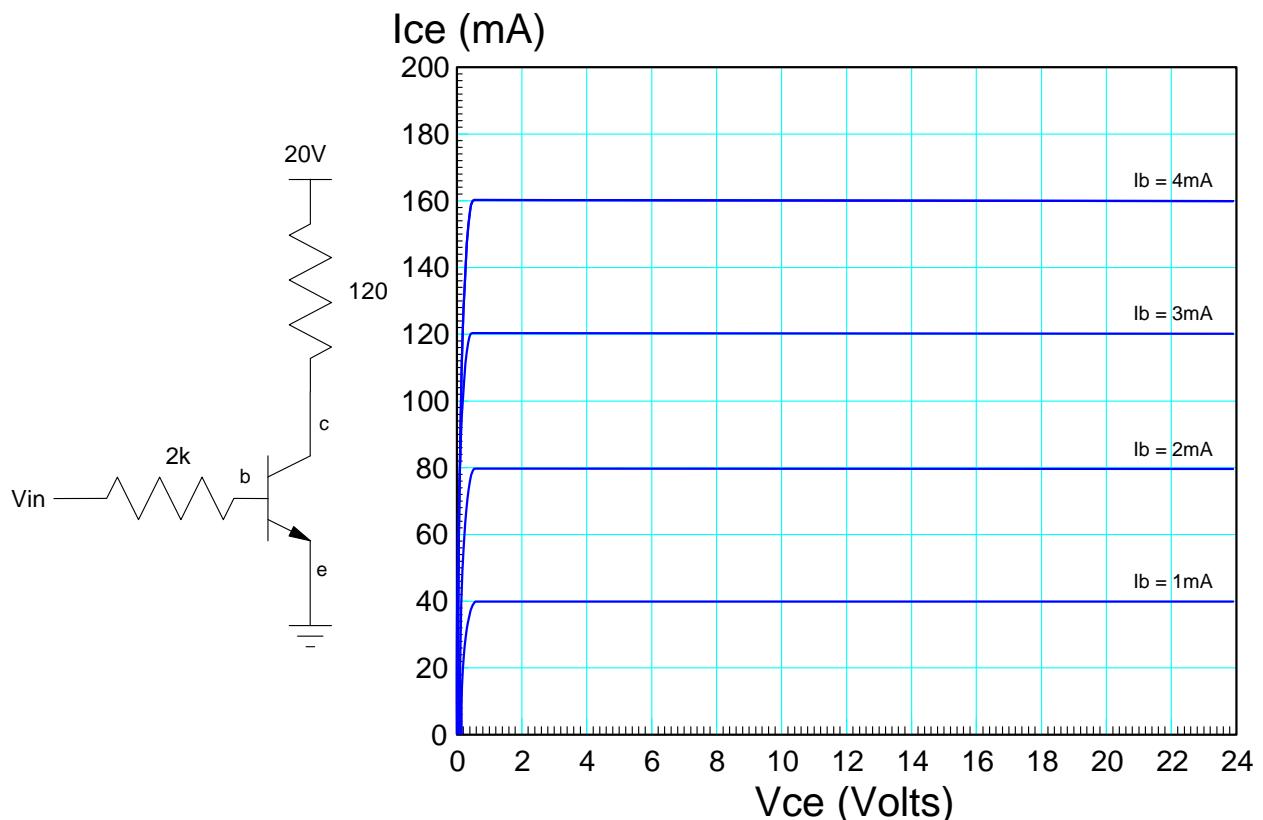

2) Transistor Switch. Determine  $R_c$  and  $R_b$  so that you can turn on and off a white LED at 2A. Assume

- $V_f = 3.0V @ 4A$  for the LED
- The transistor has a gain of 500 ( $\beta = 500$ )
- $V_{be} = 0.7V$ ,  $V_{ce(sat)} = 0.2V$
- $V_{in}$  is capable of driving currents up to 10mA


Min value of $R_b$	Max value of $R_b$	$R_c$

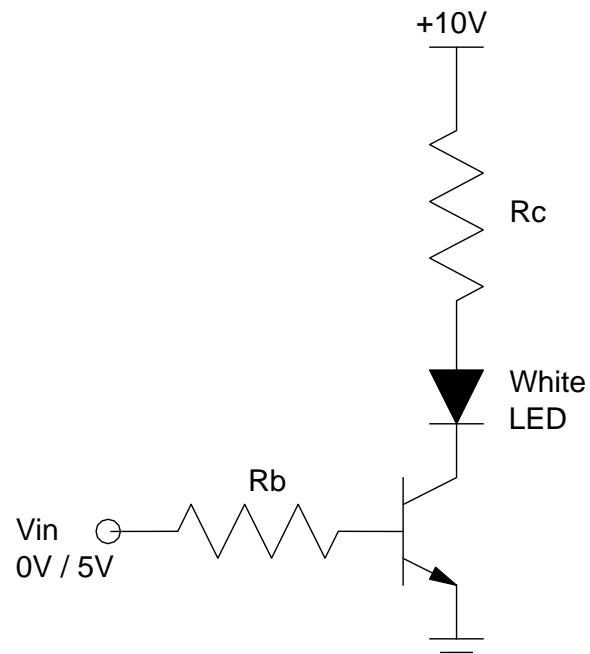

3) H-Bridge. Determine the voltages and currents for the following H-bridge. Assume all transistor have

- $|V_{be}| = 0.7V$
- $|V_{ce(sat)}| = 0.2V$
- $\beta = 500$

I1	I2	I3	V1	V2

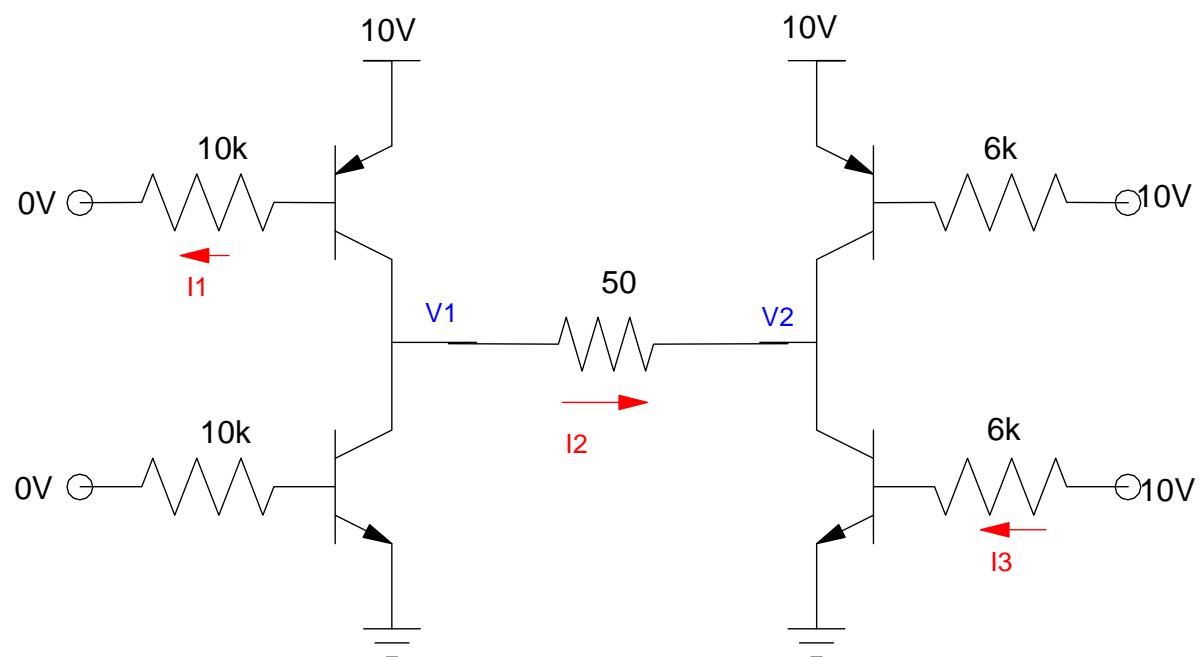

4) The data sheets for a Zetex 1051a NPN transistor are given below. From the data sheets, determine the following

max(Ic)	beta	Vbe	Vce(sat)


PARAMETER	SYMBOL	MIN.	TYP.	MAX.	UNIT	CONDITIONS.
Collector-Base Breakdown Voltage	$V_{(BR)CBO}$	150	190		V	$I_C=100\mu A$
Collector-Emitter Breakdown Voltage	$V_{CES}$	150	190		V	$I_C=100\mu A$
Collector-Emitter Breakdown Voltage	$V_{CEO}$	40	60		V	$I_C=10mA$
Collector-Emitter Breakdown Voltage	$V_{CEV}$	150	190		V	$I_C=100\mu A, V_{EB}=1V$
Emitter-Base Breakdown Voltage	$V_{(BR)EBO}$	5	8.8		V	$I_E=100\mu A$
Collector Cut-Off Current	$I_{CBO}$		0.3	10	nA	$V_{CB}=120V$
Emitter Cut-Off Current	$I_{EBO}$		0.3	10	nA	$V_{EB}=4V$
Collector Emitter Cut-Off Current	$I_{CES}$		0.3	10	nA	$V_{CES}=120V$
Collector-Emitter Saturation Voltage	$V_{CE(sat)}$		17 75 165	25 110 210	mV mV mV	$I_C=0.2A, I_B=10mA^*$ $I_C=1A, I_B=10mA^*$ $I_C=4A, I_B=100mA^*$
Base-Emitter Saturation Voltage	$V_{BE(sat)}$		920	1000	mV	$I_C=4A, I_B=100mA^*$
Base-Emitter Turn-On Voltage	$V_{BE(on)}$		825	950	mV	$I_C=4A, V_{CE}=2V^*$
Static Forward Current Transfer Ratio	$h_{FE}$	290 300 190 45	440 450 310 70	1200		$I_C=10mA, V_{CE}=2V^*$ $I_C=1A, V_{CE}=2V^*$ $I_C=4A, V_{CE}=2V^*$ $I_C=10A, V_{CE}=2V^*$
Transition Frequency	$f_T$		155		MHz	$I_C=50mA, V_{CE}=10V$ $f=100MHz$
Output Capacitance	$C_{obo}$		27	40	pF	$V_{CB}=10V, f=1MHz$
Switching Times	$t_{on}$		100		ns	$I_C=4A, I_B=40mA, V_{CC}=10V$
	$t_{off}$		300		ns	$I_C=4A, I_B=\pm 40mA, V_{CC}=10V$

5) Schmitt Trigger & Transistor Switch. Design a Schmitt trigger so that

- The motor turns on (500mA @ 20V) when  $R > 9k$
- The motor turns off  $R < 8k$
- No change for  $8k < R < 9k$

Assume

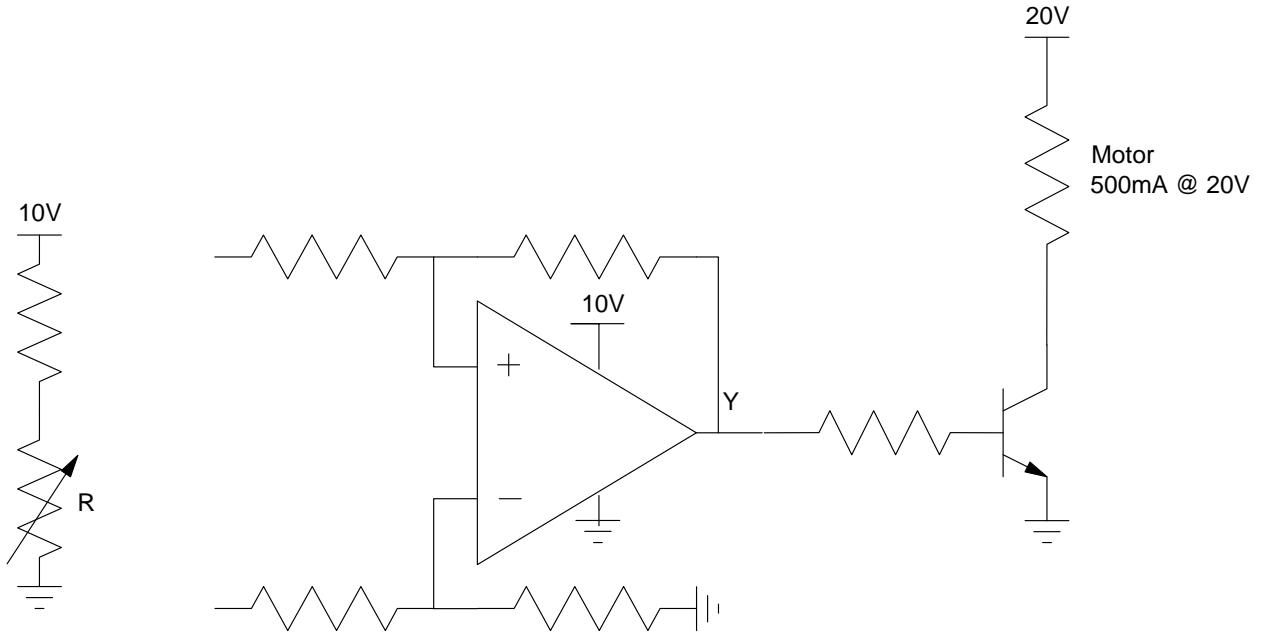- The op-amp is capable of sourcing / sinking up to 20mA
- The transistor has a gain of 1000,  $V_{be} = 1.4V$ ,  $V_{ce} = 0.9V$  (i.e. a TIP112 transistor)



6) TTL Logic: Determine the voltages and currents for the following DTL gate. Assume 3904 transistors

- $V_{be} = 0.7V$
- $V_{ce(sat)} = 0.2V$
- $\beta = 100$

$V_1$	$V_2$	$V_3$	$I_4$	$I_5$

