

# ECE 320 - Homework #4


AC to DC Converters, Max/Min Circuits, Clipper Circuits. Due Monday, Feb 4th, 2019

## AC to DC Converters

- 1) Determine the voltage at V1 and V2 (both DC and AC).
- 2) Simulate this circuit using PartSim (or similar program) to verify your answers for problem 1
- 3) **Lab:** Build this circuit in lab and compare your measured values to calculated and simulated values.

Note

- The 20Vp source is a 12VAC wall transformer in room 211 capable of 500mA. 12V is the rated RMS voltage. It's peak voltage is actually about 20V.
- The 10H / 277 Ohm resistor are the 10H inductors in room 211. The inductor's DC resistance is 277 Ohms: you don't have to add another 277 ohms to this circuit.

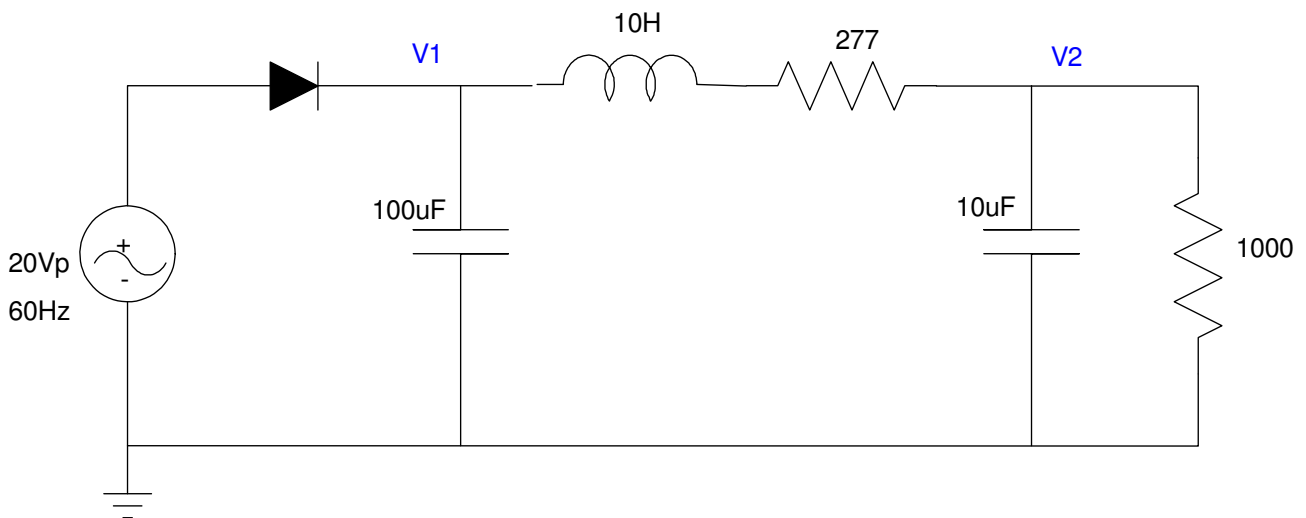

Problem 1-3

- 4) Calculate the value of the two capacitors so that
  - $V1 = 1V_{pp}$
  - $V2 = 0.2V_{pp}$

## Max/Min:

- 5) Determine the voltages and currents for the following max/min circuit. What function does this circuit implement?  $Y = f(A, B, C, D)$
- 6) Check your results in PartSim (or similar program)


## Clipper Circuits:

- 7) Design a circuit to approximate the following function subject to the following requirements:
  - Input: 0 .. 10V, capable of 100mA
  - Output: 100k resistor
  - Relationship: Graph below, +/- 200mV
- 8) Check your design in PartSim


9) Design a circuit which meets the following requirements:

- Input: -10 .. +10V, capable of 100mA
- Output: 1k resistor
- Relationship:

$$V_{out} = \begin{cases} +5V & V_{in} > +5V \\ V_{in} & -5V < V_{in} < +5V \\ -5V & V_{in} < -5V \end{cases}$$

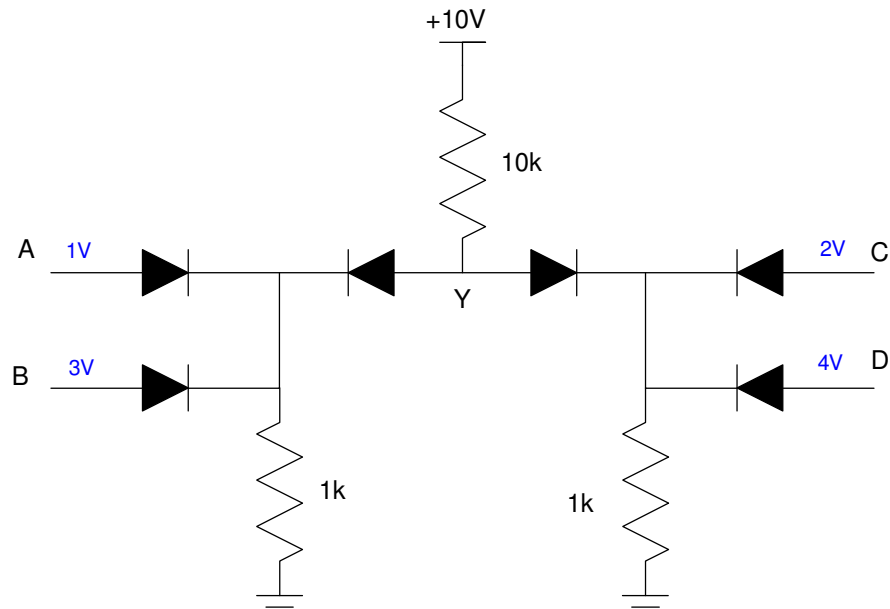

Problem 5-6

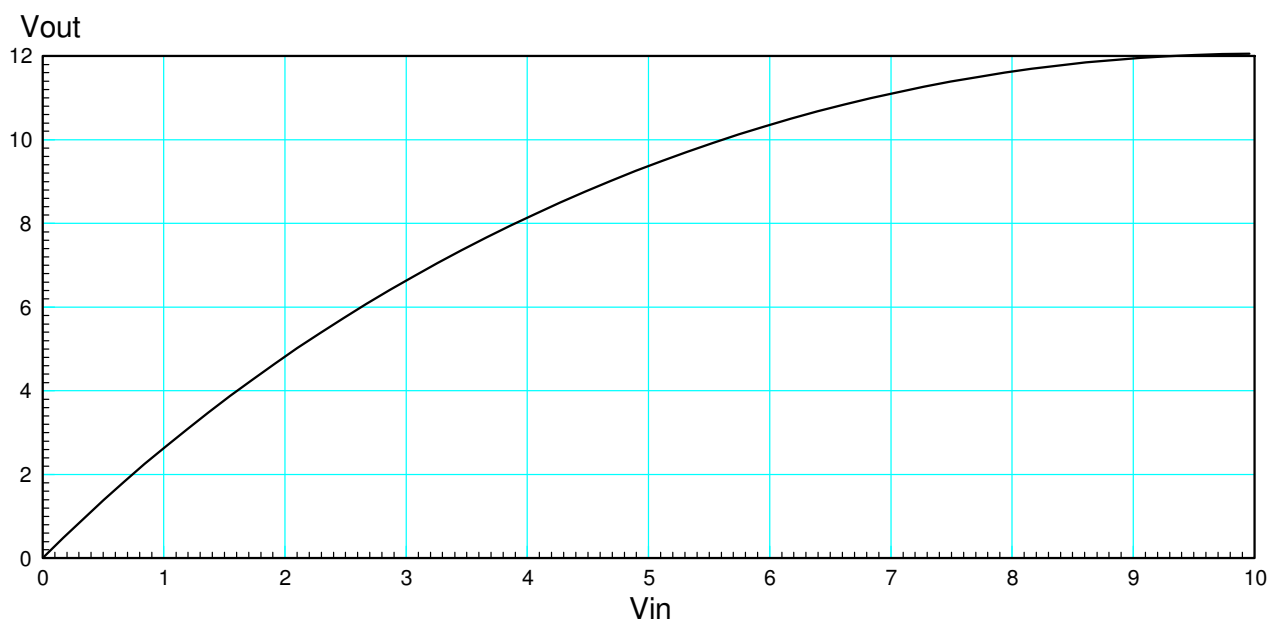

Problem 7 - 8