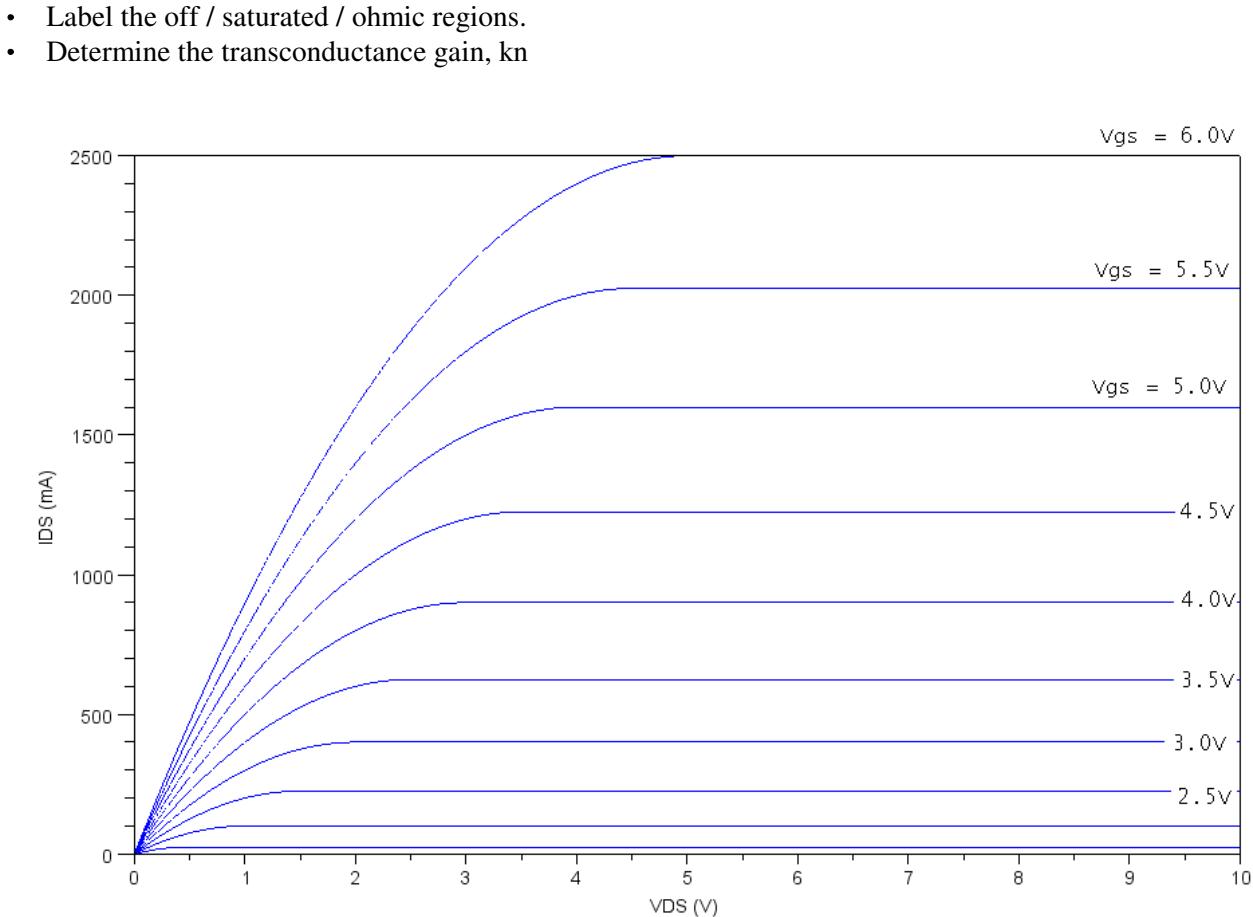


# ECE 320 - Homework #9

MOSFETs, MOSFET Switches, CMOS logic. Due Monday, October 28th


## MOSFETs

- 1) The VI characteristics for an n-channel MOSFET is shown below. Assume  $V_t = 1.0V$



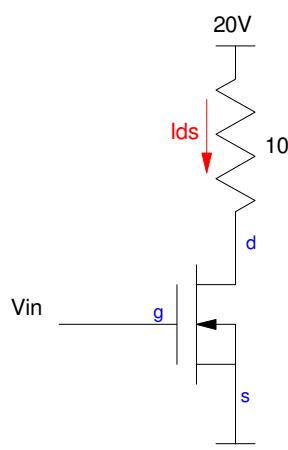- 2) Draw the load line for the following circuit. Determine the Q-point ( $V_{ds}$ ,  $I_{ds}$ ) when

- $V_{in} = V_g = 0V$
- $V_{in} = V_g = 5V$
- $V_{in} = V_g = 10V$



## MOSFET Switch

The characteristics for a MOSFET are


- Part: AOTF296L
- Current - Continuous Drain ( $I_d$ ) @  $25^\circ\text{C}$  10A (Ta), 41A (Tc)
- $R_{ds\text{ On}}$  (Max) @  $I_d$ ,  $V_{gs}$  10mOhm @ 20A, 10V
- $V_{gs(\text{th})}$  (Max) @  $I_d$  3.4V @ 250 $\mu\text{A}$

3) Determine the transconductance gain,  $k_n$

4) Determine the voltages for the following circuit for

- $V_{in} = V_g = 0\text{V}$
- $V_{in} = V_g = 5\text{V}$
- $V_{in} = V_g = 10\text{V}$

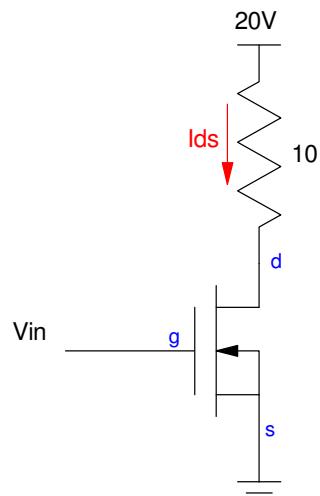5) Design a circuit using this MOSFET to turn on and off a DC servo motor. Assume the DC motor draws 200mA @ 10V.



## CMOS Logic

6) Design a CMOS gate to implement the function

$$Y = AB + A'BC$$