


# ECE 320 - Homework #9

MOSFETs, MOSFET Switches, CMOS logic. Due Monday, October 28th

## MOSFETs

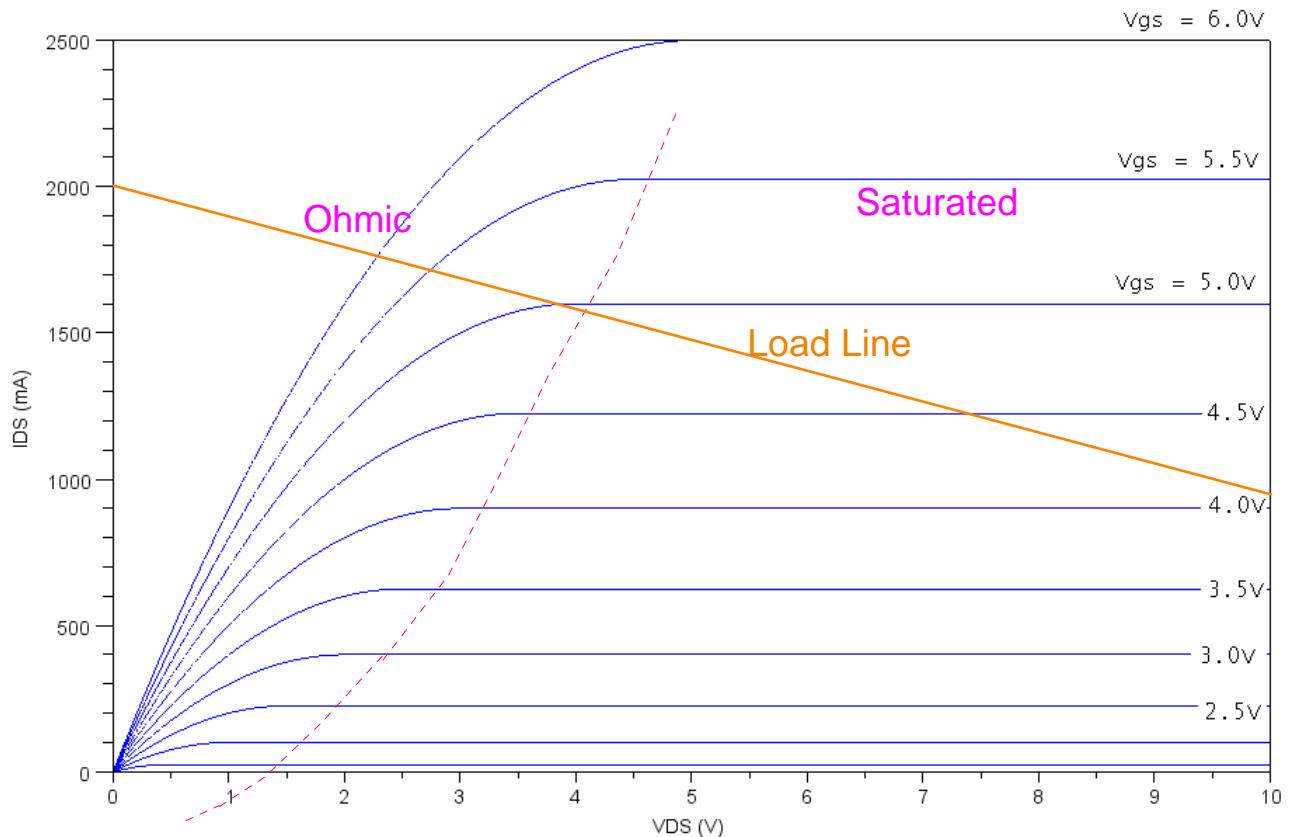
1) The VI characteristics for an n-channel MOSFET is shown below. Assume  $V_t = 1.0V$

- Label the off / saturated / ohmic regions.
- Determine the transconductance gain,  $k_n$



$$2.5A = \frac{k_n}{2}(6 - 1)^2$$

$$k_n = 0.2 \frac{A}{V^2}$$

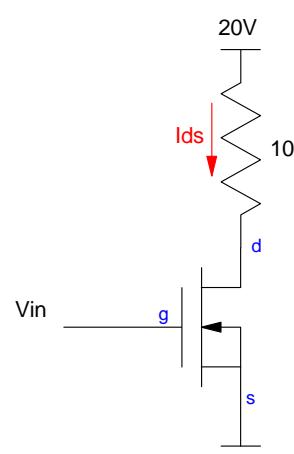

2) Draw the load line for the following circuit. Determine the Q-point ( $V_{ds}$ ,  $I_{ds}$ ) when

$$V_{in} = V_g = 0V$$

Off region

$$I_{ds} = 0V$$

$$V_{de} = 20V$$

$$V_{in} = V_g = 5V$$


Saturated Region

$$I_{ds} = \frac{k_n}{2} (V_{gs} - V_{th})^2$$

$$I_{ds} = \left(\frac{0.2}{2}\right)(5 - 1)^2$$

$$I_{ds} = 1.6A$$

$$V_{ds} = 20 - 10I_{ds} = 4.0V$$

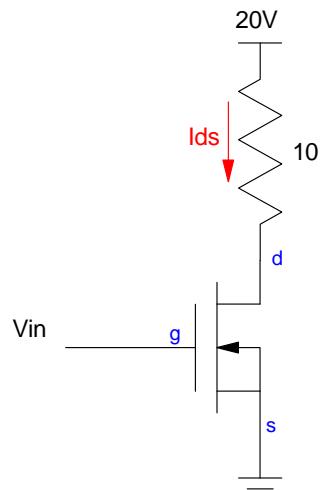

$$V_{in} = V_g = 10V$$

Ohmic Region

$$I_{ds} = k_n \left( V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds} \quad \text{1st equation}$$

$$10I_{ds} + V_{ds} = 20$$

2nd equation - load line

Solution

$$I_{ds} = 1.8888 A$$

$$V_{ds} = 1.118 V$$

## MOSFET Switch

The characteristics for a MOSFET are

- Part: AOTF296L
- Current - Continuous Drain ( $I_d$ ) @  $25^\circ\text{C}$  10A (Ta), 41A (Tc)
- **R<sub>ds</sub> On (Max) @  $I_d$ , V<sub>gs</sub> 10mOhm @ 20A, 10V**
- V<sub>gs(th)</sub> (Max) @  $I_d$  3.4V @ 250μA

3) Determine the transconductance gain,  $k_n$

In the Ohmic region

$$V_{ds} = 0.01\Omega \cdot 20A = 0.2V$$

$$I_{ds} = k_n \left( V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$

$$20A = k_n \left( 10V - 3.4V - \frac{0.2V}{2} \right) 0.2V$$

$$k_n = 15.38 \frac{A}{V^2}$$

4) Determine the voltages for the following circuit for

$$V_{in} = V_g = 0V$$

Off region

$$I_{ds} = 0$$

$$V_{ds} = 20V$$

$$V_{in} = V_g = 5V$$

assume ohmic region

$$I_{ds} = \frac{k_n}{2} (V_{gs} - V_{th})^2$$

$$I_{ds} = \frac{15.38}{2} (5 - 3.4)^2$$

$$I_{ds} = 19.68A$$

not possible. So, assume ohmic region

$$I_{ds} = k_n \left( V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$

$$I_{ds} = 15.38 \left( 5 - 3.4 - \frac{V_{ds}}{2} \right) V_{ds}$$

$$10I_{ds} + V_{ds} = 20$$

solving

$$I_{ds} = 1.992V$$

$$V_{ds} = 0.083V$$

$$R_{ds} = V_{ds} / I_{ds} = 0.042 \text{ Ohms}$$

$$V_{in} = V_g = 10V$$

assume Ohmic region

$$I_{ds} = 15.38 \left( 10 - 3.4 - \frac{V_{ds}}{2} \right) V_{ds}$$

$$10I_{ds} + V_{ds} = 20$$

Solving

$$I_{ds} = 1.998 A$$

$$V_{ds} = 0.020 V$$

$$R_{ds} = V_{ds} / I_{ds} = 0.010 \text{ Ohms}$$

5) Design a circuit using this MOSFET to turn on and off a DC servo motor. Assume the DC motor draws 200mA @ 10V.

Use the previous MOSFET.

- Apply  $V_{in} = 0V$  to turn off
- Apply  $V_{in} = 10V$  (or 5V) to turn on

MOSFET switches are really easy to use

## CMOS Logic

6) Design a CMOS gate to implement the function

$$Y = AB + A'BC$$

Use DeMorgan's Theorem

$$Y = AB + \bar{A}BC$$

$$\bar{Y} = (\bar{A} + \bar{B})(A + \bar{B} + \bar{C})$$

On the low side, implement  $\bar{Y}$

On the high side, implement  $Y$

