ECE 320 - Homework #3

LEDs, AC to DC Converters. Due Monday, September 14th

Please make the subject "ECE 320 HW#3" if submitting homework electronically to Jacob_Glower@yahoo.com (or on blackboard)

LEDs

The specifications for a Piranah RGB LED are

Color	Vf @ 20mA	mcd @ 20mA
red	2.0V	10,000
green	3.2V	10,000
blue	3.2V	10,000

1) Design a circuit to drive these LEDs with a 5V source to produce lavender:

- Red = 9020 mcd (230/255)
- Green = $6353 \mod (162/255)$
- Blue = $8706 \mod (222/255)$

2) Design a circuit to drive these LEDs with a 5V source producing teal blue:

- Red = $1412 \mod (36/255)$
- Green = $5176 \mod (132/255)$
- Blue = $5373 \mod (137/255)$

Other colors can be obtained from

https://www.rapidtables.com/web/color/color-wheel.html

AC to DC Converters

- 3) Determine the votlages at V1 and V2 (DC and AC)
- 4) Build the circuit in CircuitLab (or similar program) and verify your calculations for problem #3
- 5) Determine C1 and C2 so that AC voltages are: V1 = 2Vpp and V2 = 300mVpp.
- 6) Build this circuit in CircuitLab (or similar program) and verify your calculations for problem #5

