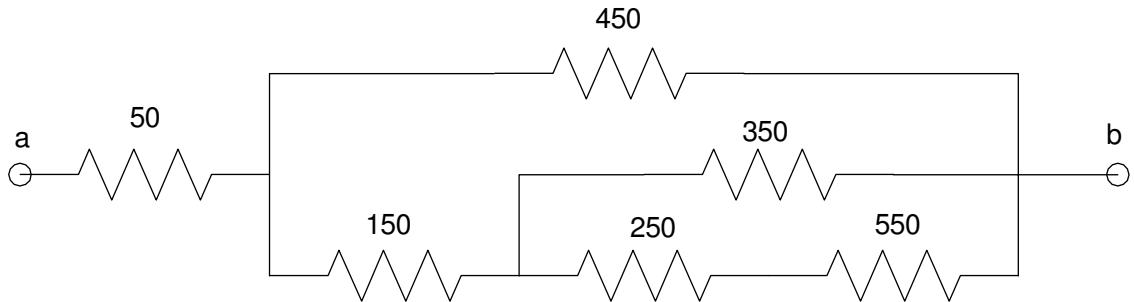


ECE 320 - Quiz #1a - Name _____

EE 206 Review. September 3, 2020


- Determine the resistance R_{ab}

$$R_{ab} = 259.92 \text{ Ohms}$$




2) Determine the resistance R_{ab} (it will be a complex number)

$$R_{ab} = 212.54 + j69.45$$

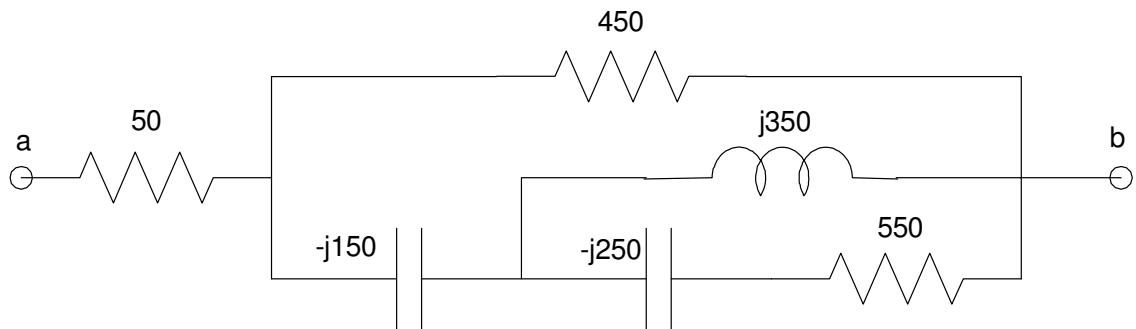

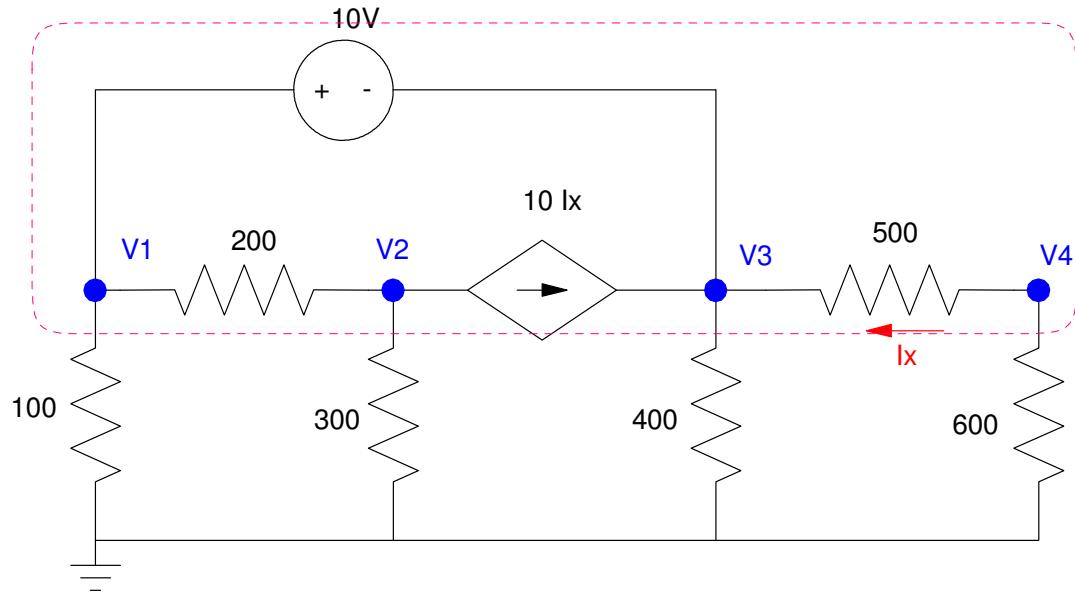3) Voltage Nodes: Give N voltage node equations to solve for the N unknown voltages.



4 nodes plus a dependent source means we need 5 equations to solve for 5 unknowns

$$V_1 - V_3 = 10$$


$$I_x = \left(\frac{V_4 - V_3}{500} \right)$$

$$\left(\frac{V_2 - V_1}{200} \right) + \left(\frac{V_2}{300} \right) + 10I_x = 0$$

$$\left(\frac{V_4 - V_3}{500} \right) + \left(\frac{V_4}{600} \right) = 0$$

$$\left(\frac{V_1}{100} \right) + \left(\frac{V_2}{300} \right) + \left(\frac{V_3}{400} \right) + \left(\frac{V_4}{600} \right) = 0$$

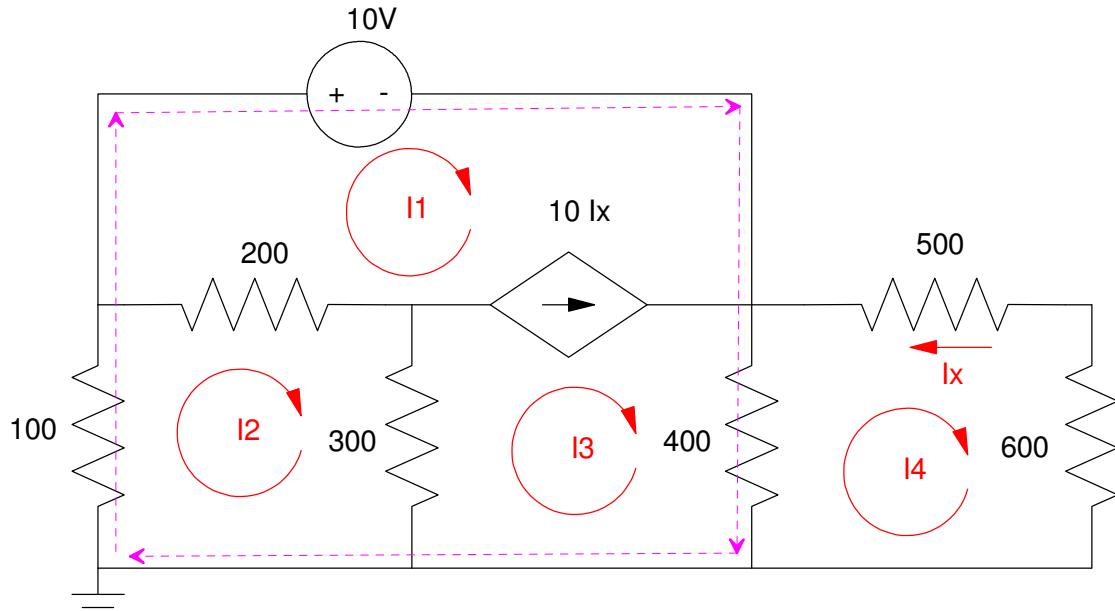4) Current Loops: Give N current loop equations to solve for the N unknown currents



4 loops plus I_x means we need 5 equations to solve for 5 unknowns

$$I_x = -I_4$$

$$10I_x = I_3 - I_1$$


$$100I_x + 200(I_2 - I_1) + 300(I_2 - I_3) = 0$$

$$400(I_4 - I_3) + 500I_4 + 600I_4 = 0$$

$$100I_2 + 10 + 400(I_3 - I_4) = 0$$

5) Signals X and Y are displayed on an oscilloscope. Give the phasor representation for these two voltages

Frequency (Hz)	X		Y	
	Amplitude	Phase	Amplitude	Phase
66.7Hz	8.5V	-72 deg	6.5V	-144 deg

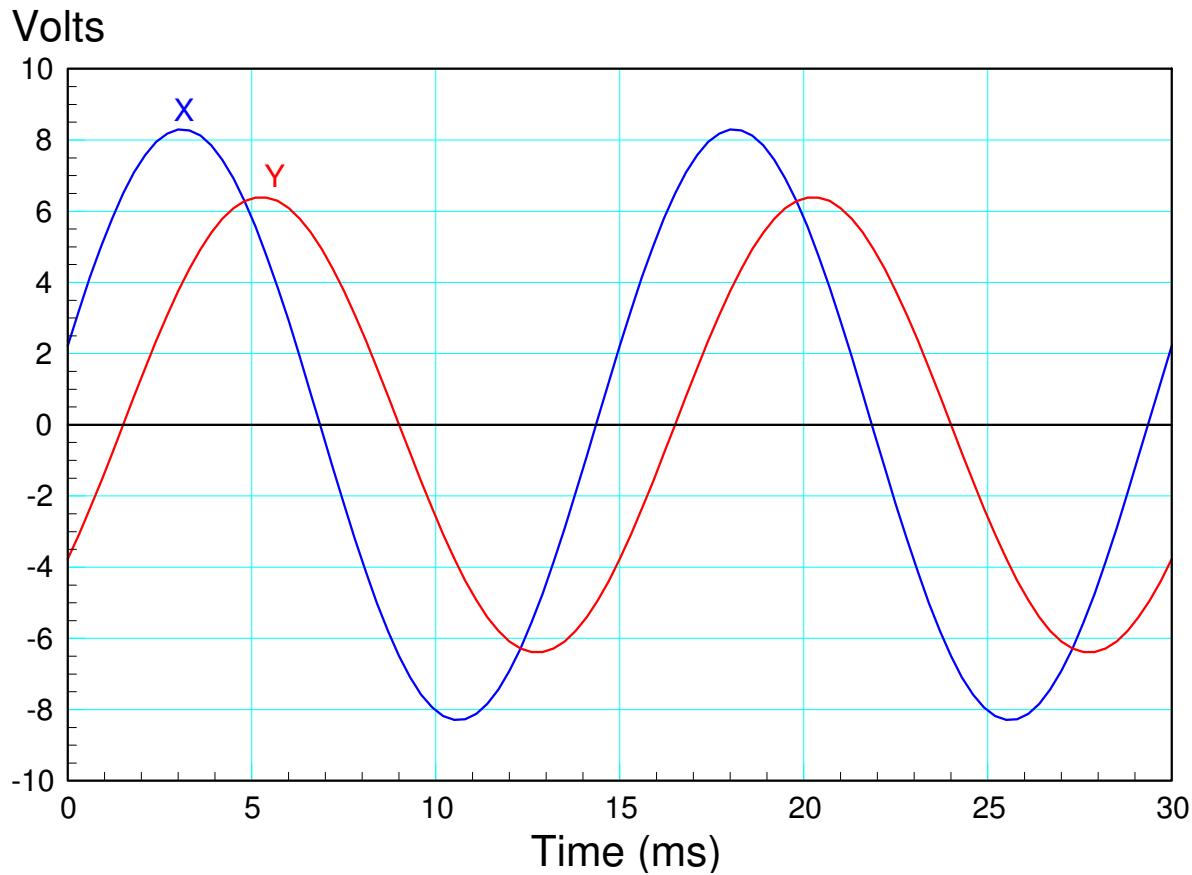

$$\text{period} = 15\text{ms}, \text{frequency} = 1/15\text{ms} = 66.7\text{Hz}$$

The amplitude is the maximum voltage.

The phase shift is the delay relative to the period


$$\phi_x = -\left(\frac{3\text{ms delay}}{15\text{ms period}}\right) 360^\circ = -72^\circ$$

$$\phi_y = -\left(\frac{6\text{ms delay}}{15\text{ms period}}\right) 360^\circ = -144^\circ$$

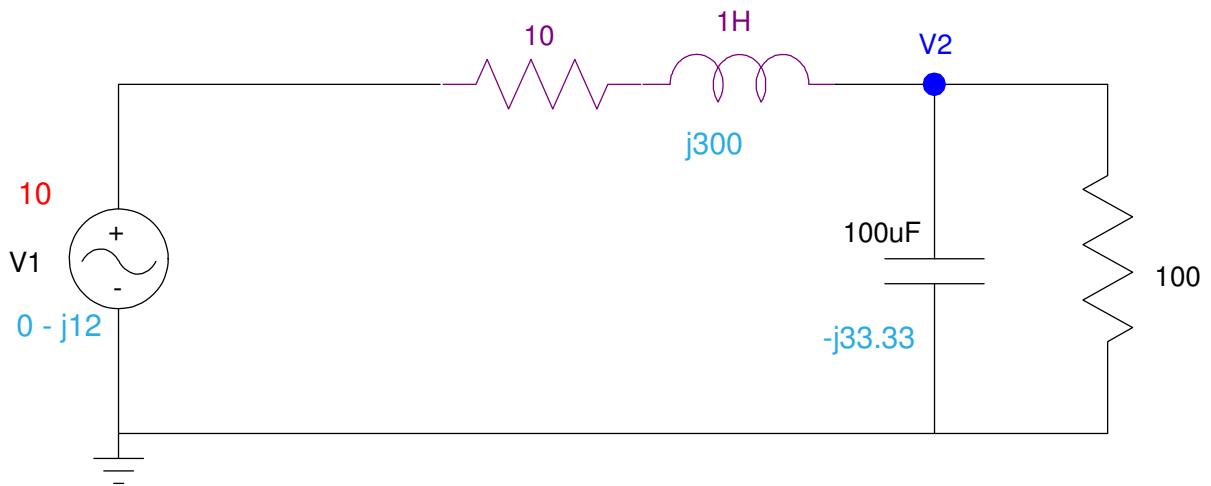6) Determine $V_2(t)$ assuming

$$V_1(t) = 10 + 12 \sin(300t)$$

$$\boxed{V_2(t) = 9.091 - 0.540 \cos(300t) - 1.293 \sin(300t)}$$



DC:

$$V_2 = \left(\frac{100}{100+10} \right) 10 = 9.091V$$

AC:

$$100 \parallel -j33.33 = 10 - j30$$

$$V_2 = \left(\frac{(10-j30)}{(10-j30)+(10+j300)} \right) (0 - j12)$$

$$V_2 = -0.540 + j1.293$$

$$v_2(t) = -0.540 \cos(300t) - 1.293 \sin(300t)$$

