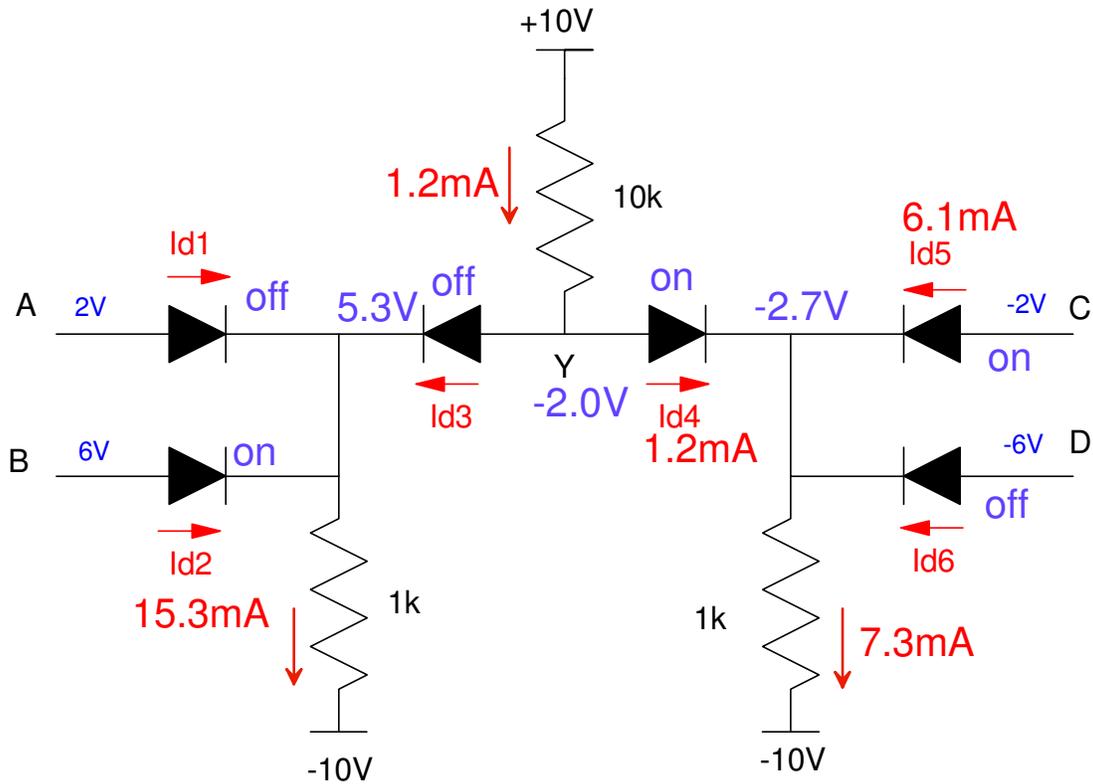


ECE 320 - Quiz #4 - Name _____

Max/Min, Clipper, Transistors - September 24, 2020

1) Max/Min: Determine the voltages and currents for the following min/max circuit

Id1	Id2	Id3	Id4	Id5	Id6
0	15.3mA	0	1.2mA	6.1mA	0





2) Clipper: Determine R and Vz to approximate the following function

$$y = 20 \sin\left(\frac{x}{7}\right) \quad 0 < x < 10$$

R0	Vz1	R1	Vz2	R2
1.67k	8.0V	5846	16.0V	854

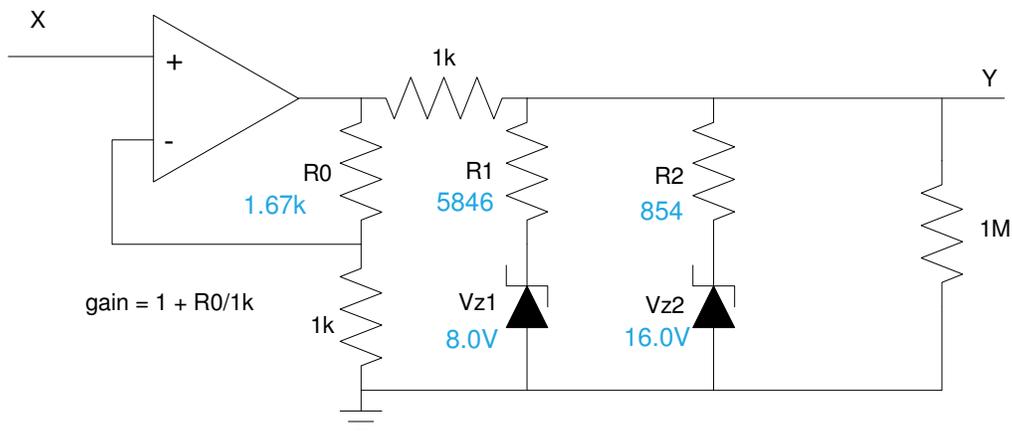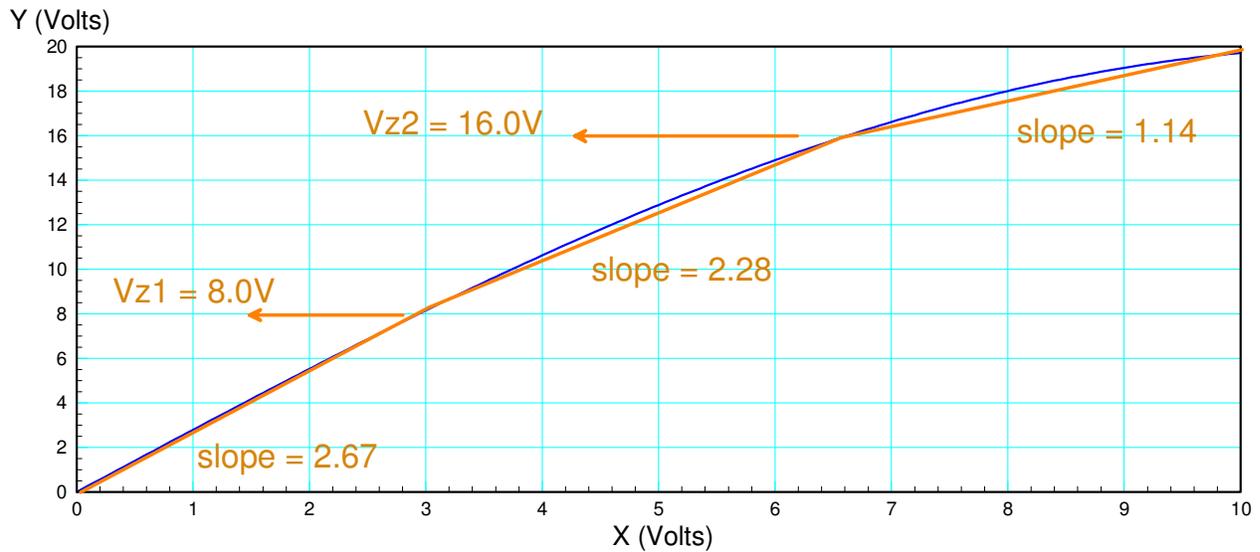answers vary depending upon how you draw your lines




Answers will vary depending upon how you draw the orange lines. As drawn

- $V_{z1} = 8.0V$
- $V_{z2} = 16.0V$
- $1 + \frac{R_0}{1k} = 2.67 \quad \Rightarrow \quad R_0 = 1.67k$
- $\left(\frac{R_1}{R_1 + 1k}\right) = \frac{2.28}{2.67} \quad \Rightarrow \quad R_1 = 5846$
- $\left(\frac{R_{12}}{R_{12} + 1k}\right) = \left(\frac{1.14}{2.67}\right) \quad \Rightarrow \quad R_{12} = R_1 || R_2 = 745\Omega$

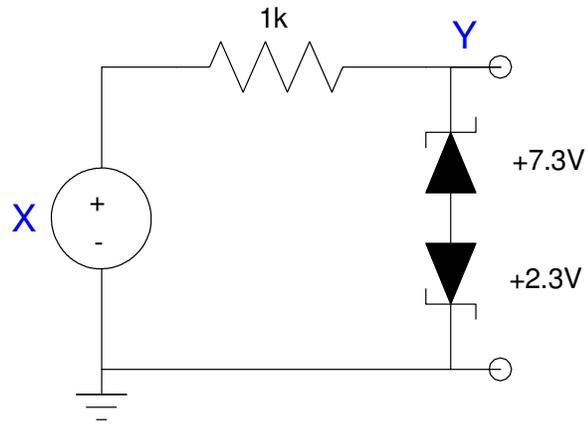3) Clipper: Design a circuit to clip the voltage at +8V and -3V

$$y = \begin{cases} +8V & x > 8 \\ x & -3 < x < 8 \\ -3V & x < -3 \end{cases}$$





4) The VI characteristics for an NPN transistor are shown below

- Draw the load line for the following circuit
- Show on the load line the operating point (V_{ce} , I_c) when $V_{in} = \{0V, 2.5V, 5V\}$

Assume

- $V_{be} = 0.7V$
- $V_{ce} = 0.2V$ when saturated

Load Line	$V_{in} = 0V$	$V_{in} = 2.5V$	$V_{in} = 5V$
show on graph	show (V_{ce} , I_c) on graph	show (V_{ce} , I_c) on graph	show (V_{ce} , I_c) on graph

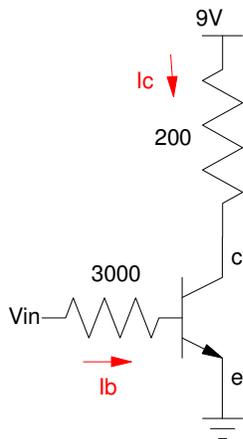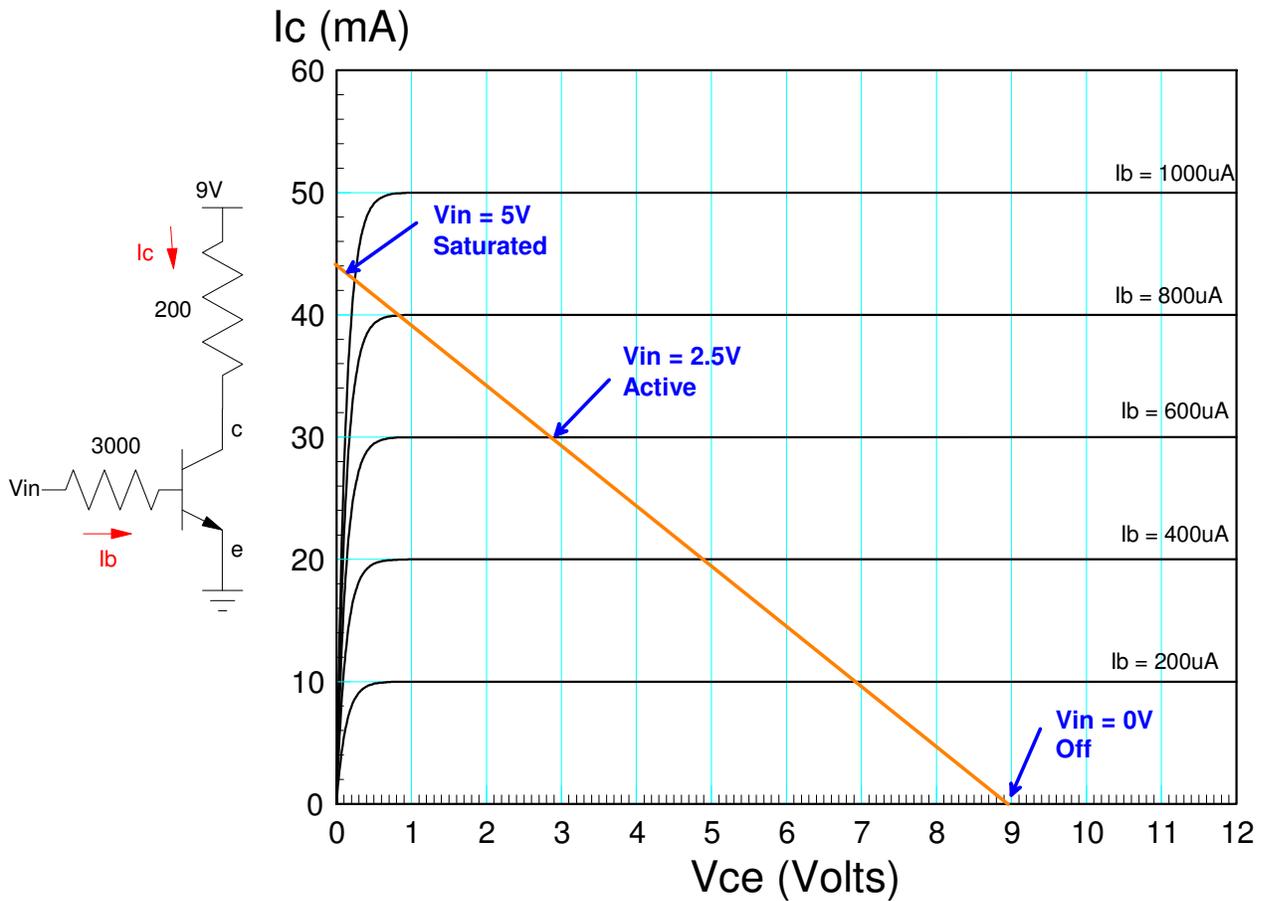

$V_{in} = 2.5V$


$$I_b = \left(\frac{2.5V - 0.7V}{3000} \right) = 600 \mu A$$

$V_{in} = 5.0V$

$$I_b = \left(\frac{5V - 0.7V}{3000} \right) = 1.433 mA$$

5) The voltages for the following circuit are measured (shown below). From these measurements, determine the following:

I_b (mA)	I_c (mA)	Current Gain (beta)	Operating Region off / active / saturated
2.150mA	61.08mA	28.41	Active $V_{ce} > 0.2V$

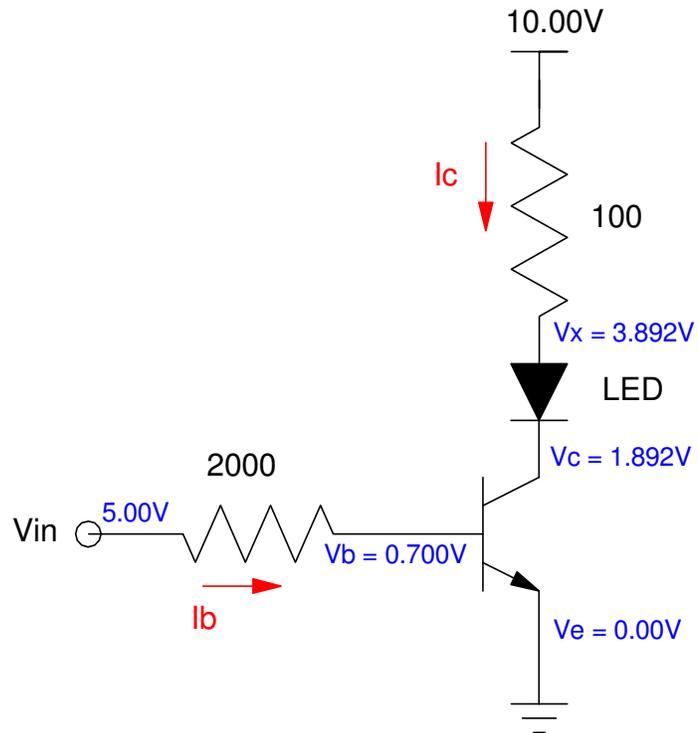

6) Assume an ideal 3904 transistor

- $V_{ce(sat)} = 0.2V$
- $V_{be} = 0.7V$
- $\beta = 100$

Determine the voltages $\{V_b, V_c\}$ and the currents $\{I_b, I_c\}$

V_b	V_c	I_b	I_c
0.70V diode V_{be}	2.2372V active mode	768.6μA	77.63mA

$$I_c = I_b + 100I_b$$

$$\left(\frac{V_c - 0.7}{2000}\right) = I_b$$


$$\left(\frac{10 - V_c}{100}\right) = I_c = 101I_b$$

$$\left(\frac{10 - V_c}{100}\right) = 101\left(\frac{V_c - 0.7}{2000}\right)$$

$$V_c = 2.2372V$$

$$I_c = 77.63mA$$

$$I_b = 768.6\mu A$$

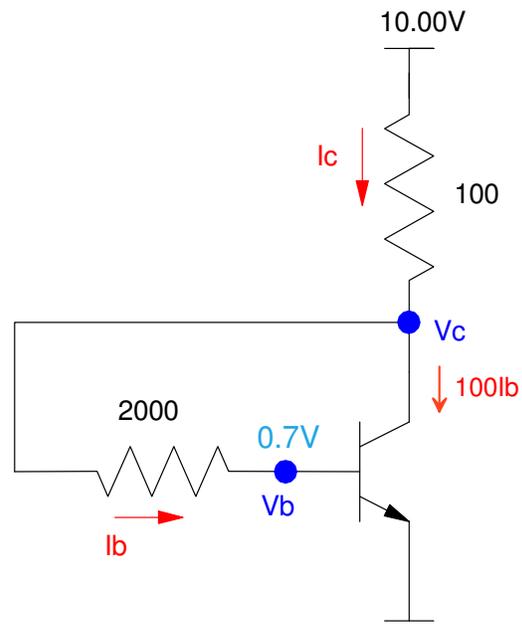

Bonus! A diode is a pn junction. A transistor is an npn junction. Why can't you make a transistor by putting two 2N1004 diodes back-to-back?

ans: The base has to be very thin so that the electrons that flow emitter to base pass right through the base and wind up at the collector. If you use two diodes, the base is too thick.

- np + pn = npn

