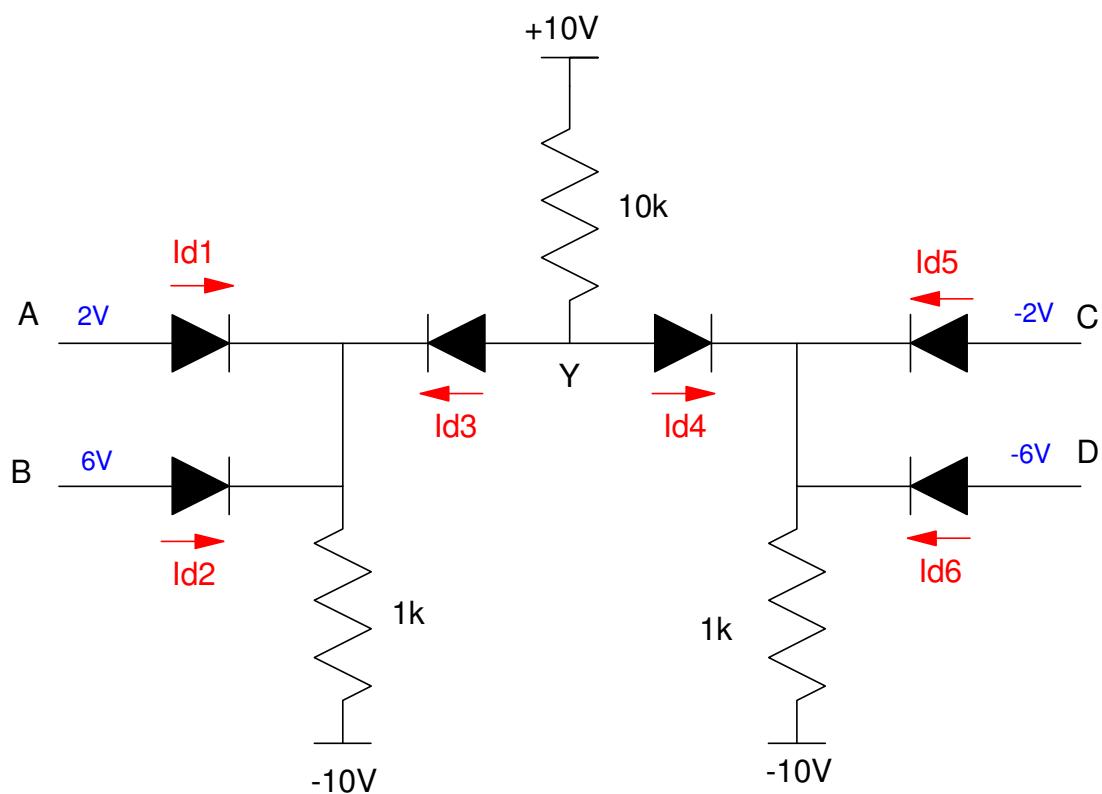


ECE 320 - Quiz #4 - Name _____

Max/Min, Clipper, Transistors - September 24, 2020

1) Max/Min: Determine the voltages and currents for the following min/max circuit

Id1	Id2	Id3	Id4	Id5	Id6





2) Clipper: Determine R and Vz to approximate the following function

$$y = 20 \sin\left(\frac{x}{7}\right) \quad 0 < x < 10$$

R0	Vz1	R1	Vz2	R2

Y (Volts)

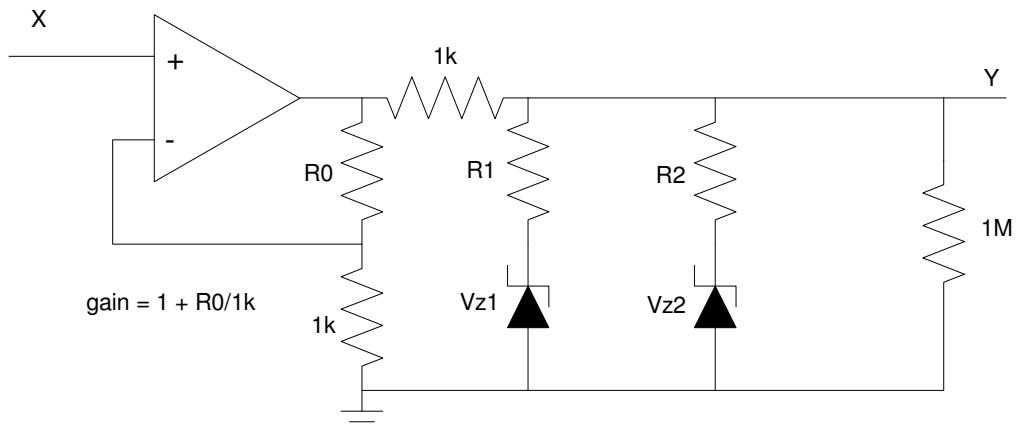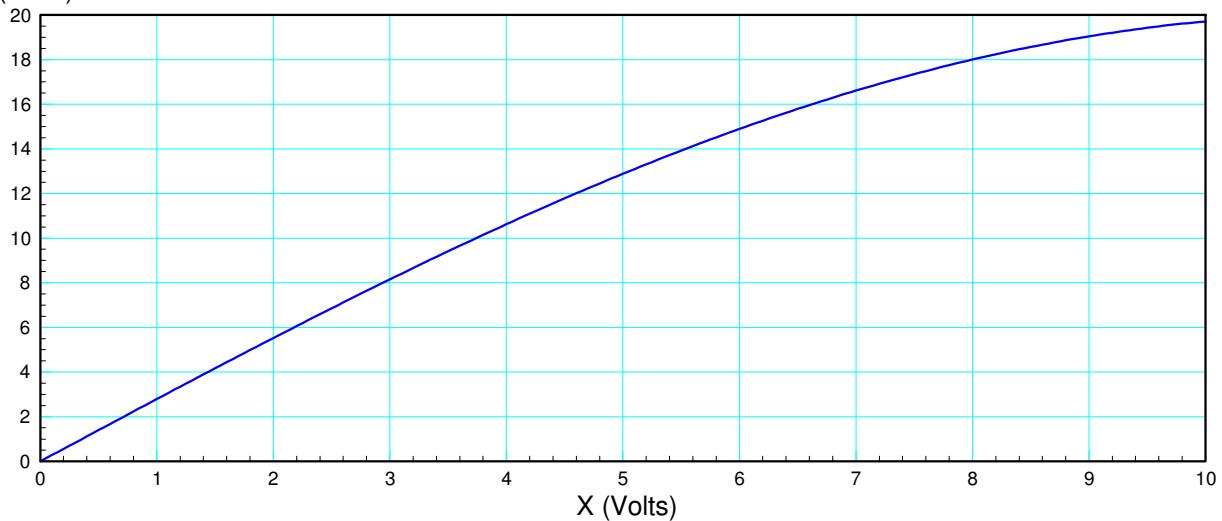

3) Clipper: Design a circuit to clip the voltage at +8V and -3V

$$y = \begin{cases} +8V & x > 8 \\ x & -3 < x < 8 \\ -3V & x < -3 \end{cases}$$


4) The VI characteristics for an NPN transistor are shown below

- Draw the load line for the following circuit
- Show on the load line the operating point (V_{ce} , I_c) when $V_{in} = \{0V, 2.5V, 5V\}$

Assume


- $V_{be} = 0.7V$
- $V_{ce} = 0.2V$ when saturated

Load Line	$V_{in} = 0V$	$V_{in} = 2.5V$	$V_{in} = 5V$
show on graph	show (V_{ce} , I_c) on graph	show (V_{ce} , I_c) on graph	show (V_{ce} , I_c) on graph

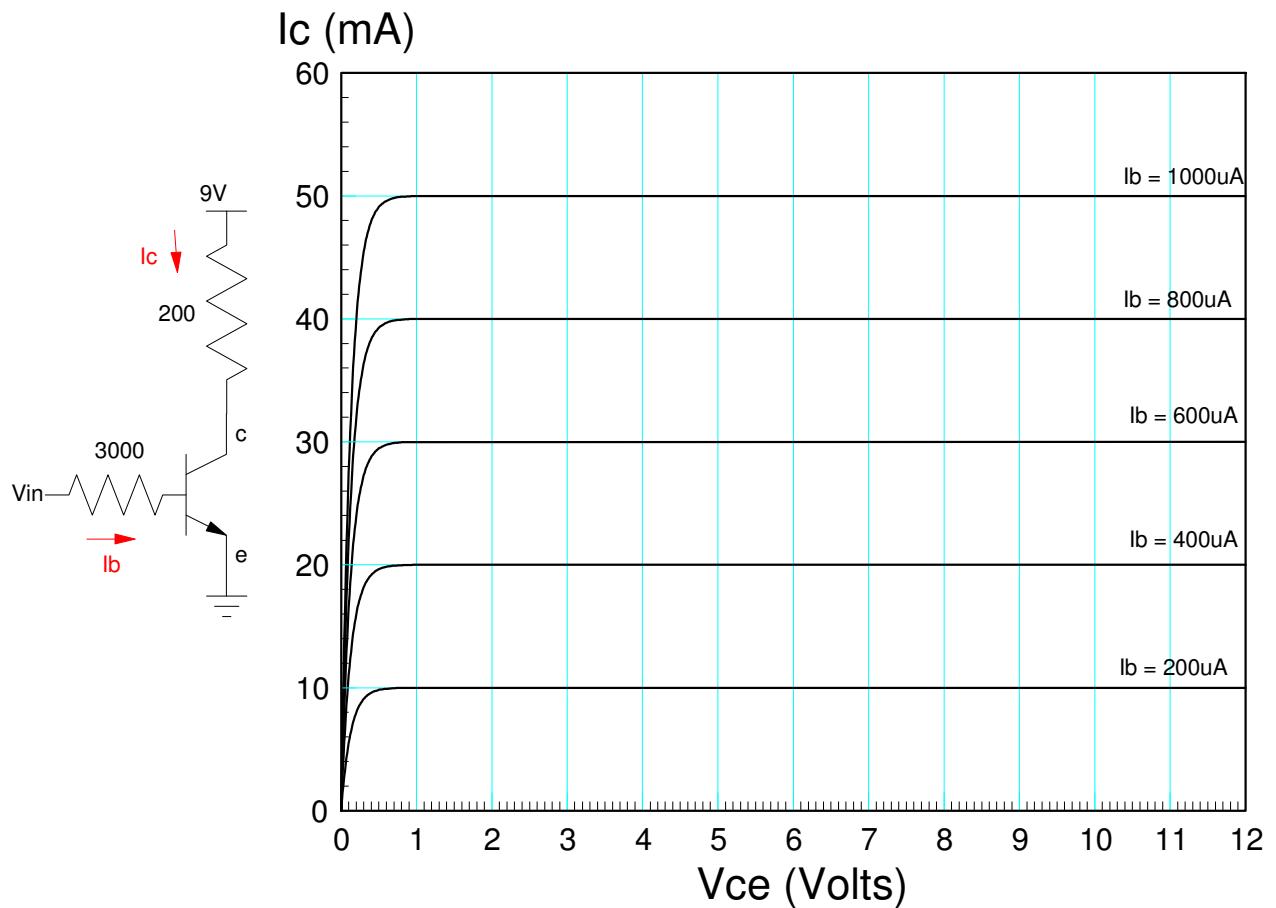

5) The voltages for the following circuit are measured (shown below). From these measurements, determine the following:

I _b (mA)	I _c (mA)	Current Gain (beta)	Operating Region off / active / saturated

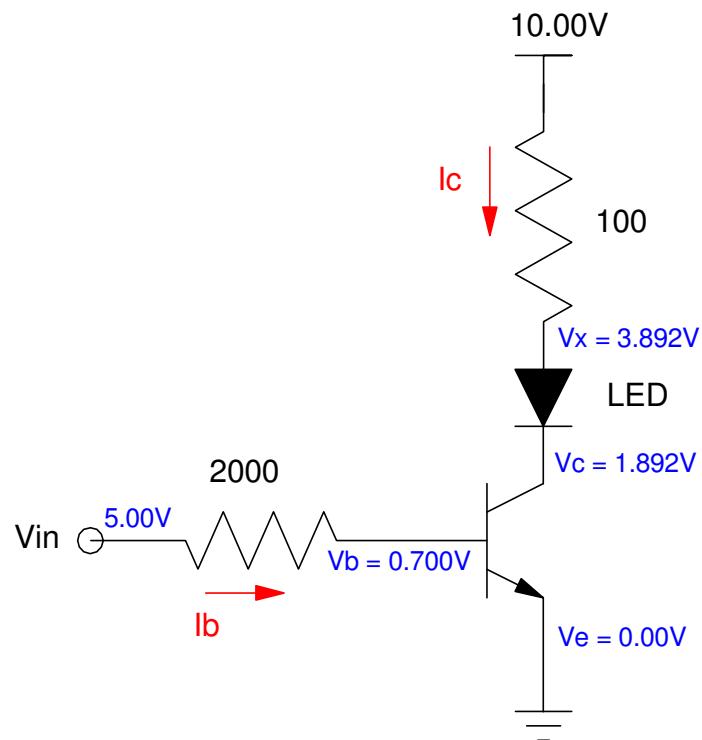


6) Assume an ideal 3904 transistor

- $V_{ce(sat)} = 0.2V$
- $V_{be} = 0.7V$
- $\beta = 100$

Determine the voltages $\{V_b, V_c\}$ and the currents $\{I_b, I_c\}$

V_b	V_c	I_b	I_c

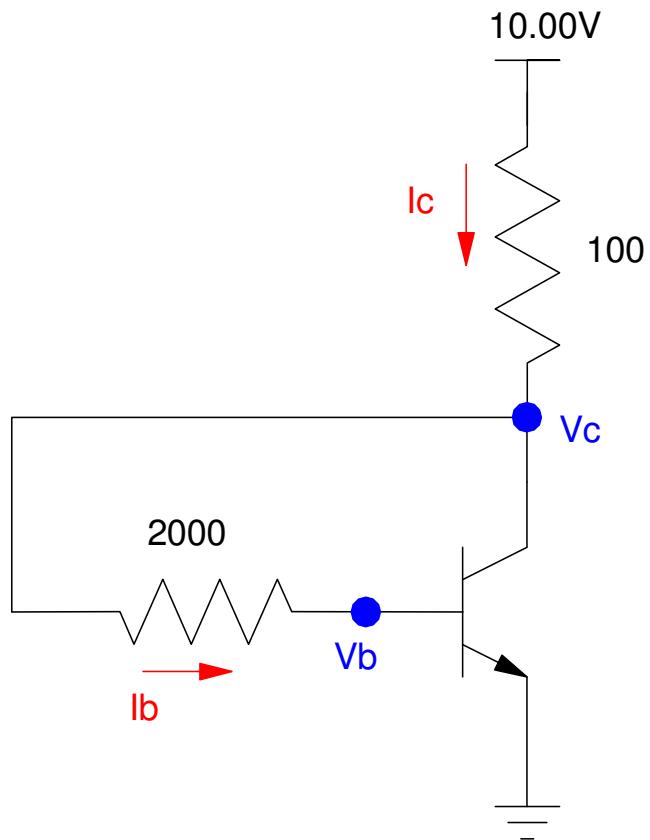

Bonus! A diode is a pn junction. A transistor is an npn junction. Why can't you make a transistor by putting two 2N1004 diodes back-to-back?

- $np + pn = npn$

