

ECE 320 - Quiz #6 - Name _____


H Bridges, DC to DC Converters, Fourier Transforms - October 8, 2020

H-Bridge Analysis:

1) Determine the voltages and currents for the following H-bridge. Assume ideal 3904 & 3906 transistors:

- $|V_{be}| = 0.7V$
- $|V_{ce}| = 0.2V$ when saturated
- Current gain = $\beta = 100$

I1	I2	I3	V4	V5

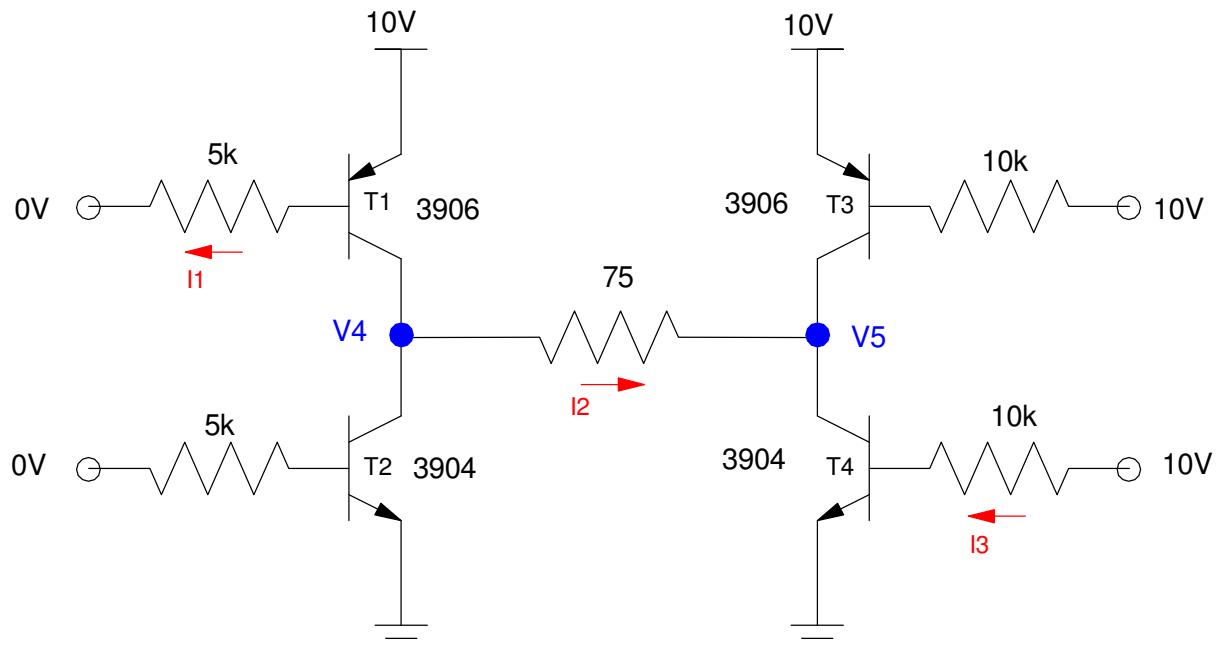


H-Bridge Analysis:

2) Determine the voltages and currents for the following H-bridge. Assume ideal 3904 & 3906 transistors:

- $|V_{be}| = 0.7V$
- $|V_{ce}| = 0.2V$ when saturated
- Current gain = beta = 100


I1	I2	I3	V4	V5

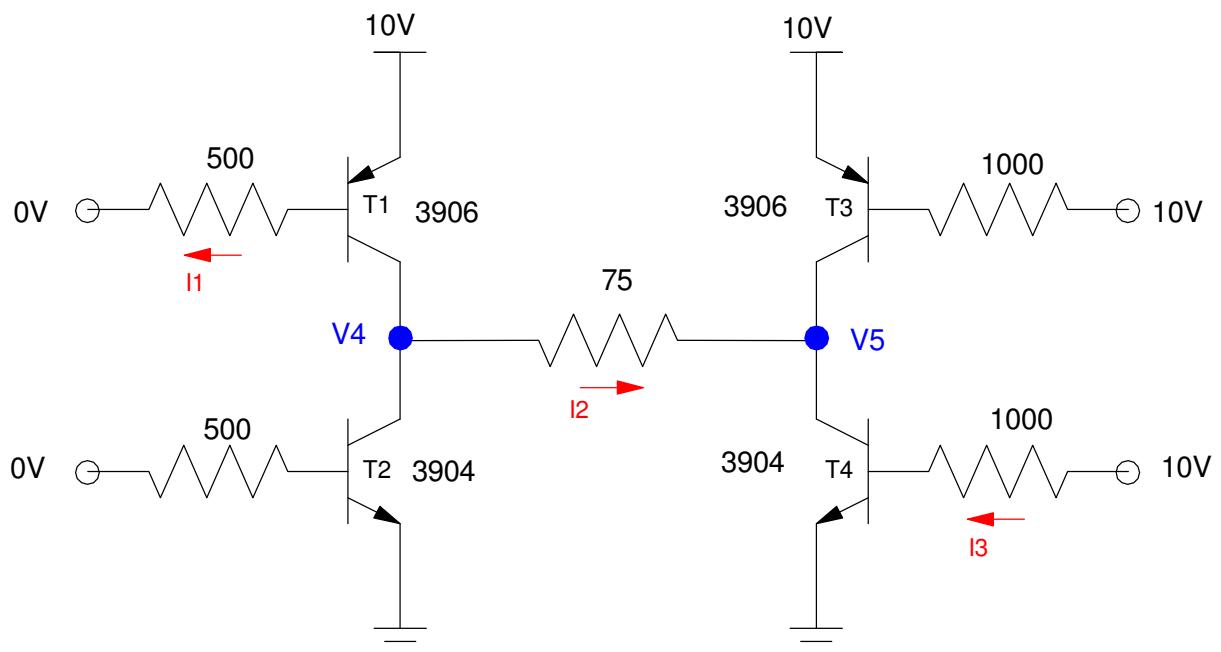

DC to DC Converter: Analysis

- 3) Determine the voltages at V1 and V2 (both DC and AC)

V1		V2	
V1(DC)	V1(AC)	V2(DC)	V2(AC)

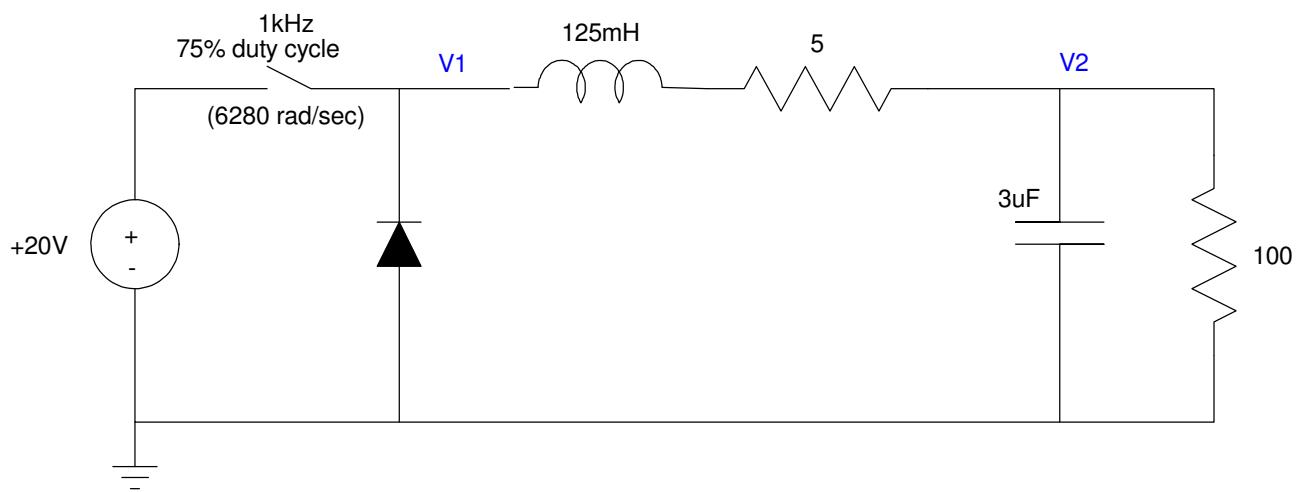


DC to DC Converter: Design

4) Determine the duty cycle, R, and C2 so that

- V2(DC) is 7.50V
- V2(AC) = 250mVpp, and
- I2 = 100mA

X% (duty cycle)	C	R

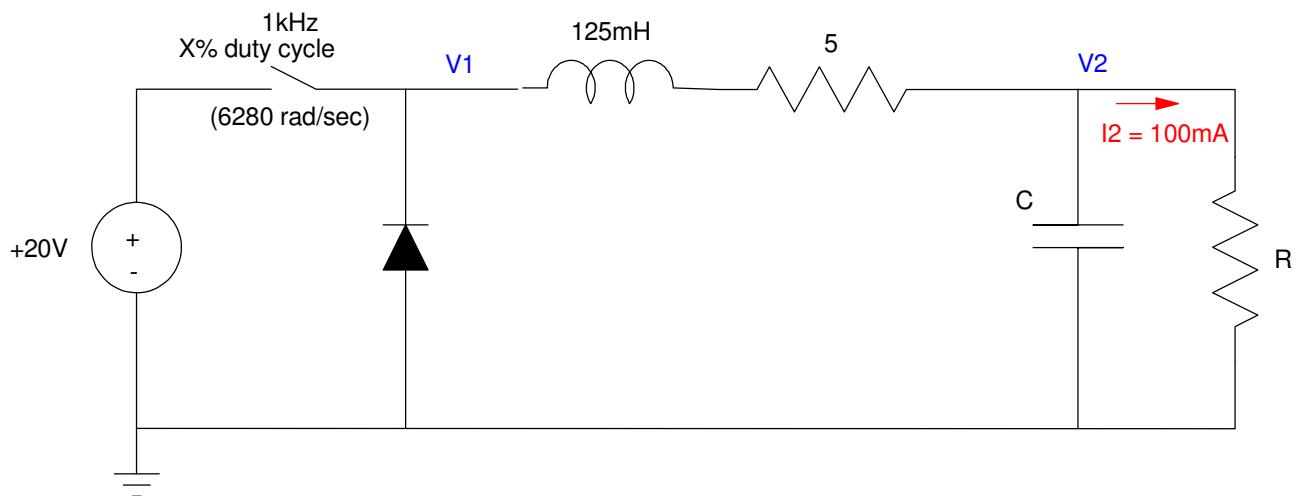

Fourier Transform

5) Determine the period (T) of the following waveform

$$x(t) = x(t + T)$$


and it's Fourier transform

$$x(t) = 5 + 6 \sin(3t) + 7 \cos(4t)$$

Fourier Transform

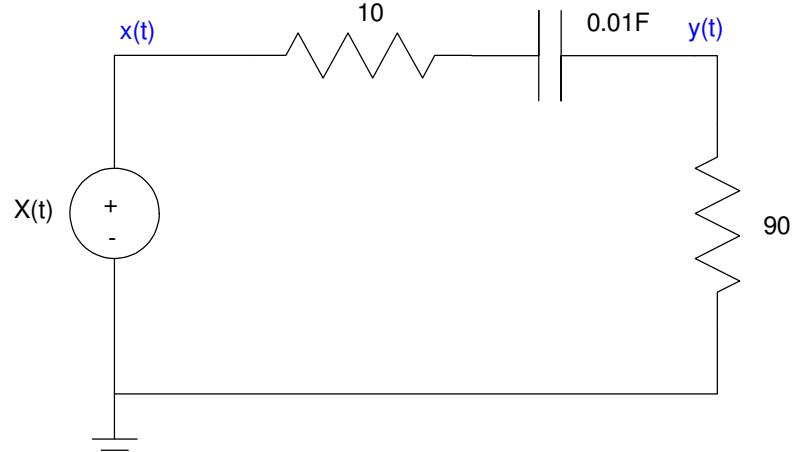6) Determine $y(t)$ given that

$$x(t) = 10 + 11 \sin(3t) + 12 \cos(6t)$$



Bonus! What is the impedance R_{ab} for the following circuit as the number of stages goes to infinity?

