

ECE 320 - Quiz #7 - Name _____


DC to AC, SCR, Boolean Logic. October 15, 2020

DC to DC Converter

1) A DC to AC converter converts 20VDC into a 20Vp, 400Hz AC sine wave. A 1:4 step-up transformer then converts this into an 80Vp, 400Hz sine wave (V0).

Determine the resulting voltage at V1 and V2 for this DC to DC converter.

V1		V2	
V1(DC)	V1(AC)	V2(DC)	V2(AC)
78.12V	2.36Vpp	74.40V	0.5285Vpp

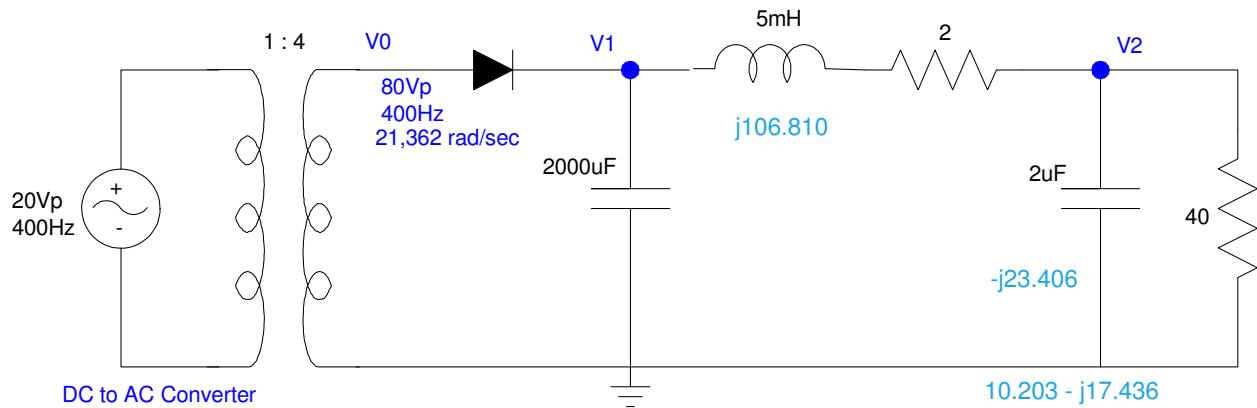

The peak of V1 is 79.3V

$$I \approx \left(\frac{79.3V}{42\Omega} \right) = 1.888A$$

$$I = C \frac{dV}{dt}$$

$$1.888A = 2000\mu F \frac{dV}{1/400s}$$

$$dV_1 = 2.36V_{pp} = V1(AC)$$

$$V_1(DC) = 79.3V - \frac{1}{2} \cdot 2.36V_{pp} = 78.12V$$


$$V_2(DC) = \left(\frac{40}{40+2} \right) 78.12V = 74.40V$$

$$V_2(AC) = \left(\frac{(10.203-j17.436)}{(10.203-j17.436)+(2+j106.810)} \right) (2.36V_{pp})$$

$$V_2(AC) = 0.5285V_{pp}$$

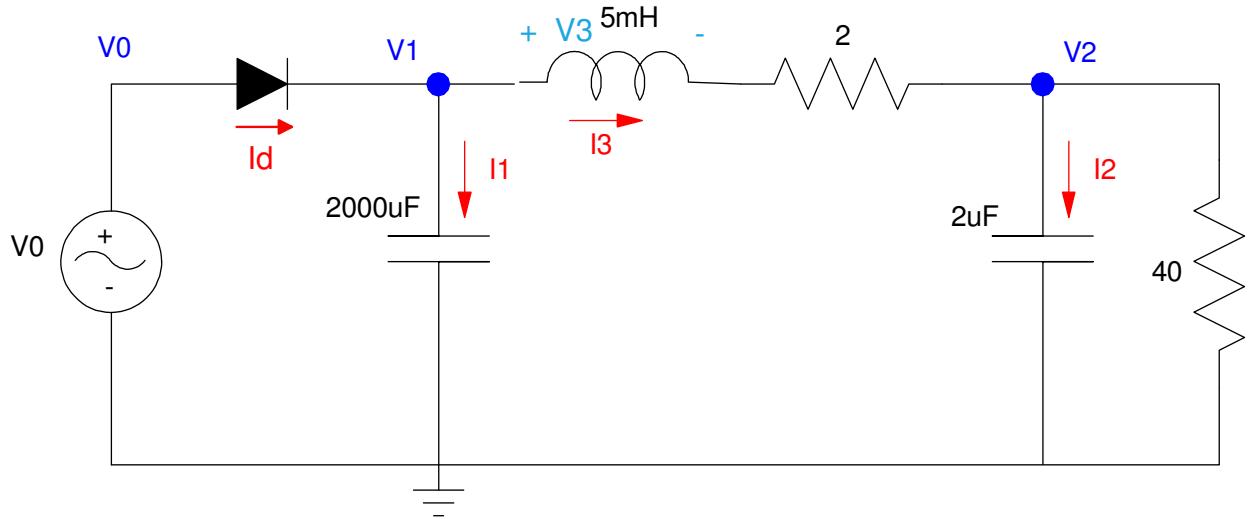2) Determine the differential equations which describe the following circuit. The differential equations should be in terms of $\{V_1, V_2, I_3\}$. Assume the VI relationship of the diode is

$$V_d = 0.052 \ln(10^8 I_d + 1) \quad I_d = 10^{-8} \left(\exp\left(\frac{V_d}{0.052}\right) - 1 \right)$$



$$I_1 = 2000\mu F \cdot \frac{dV_1}{dt} = I_d - I_3$$

$$I_2 = 2\mu F \cdot \frac{dV_2}{dt} = I_3 - \frac{V_2}{40}$$

$$V_3 = 5mH \cdot \frac{dI_3}{dt} = V_1 - V_2 - 2I_3$$

Simplifying

$$\frac{dV_1}{dt} = 500 \cdot 10^{-8} \left(\exp\left(\frac{V_0 - V_1}{0.052}\right) - 1 \right) - 500I_3$$

$$\frac{dV_2}{dt} = 500000I_3 - 12500V_2$$


$$\frac{dI_3}{dt} = 200V_1 - 200V_2 - 4I_3$$

These three coupled differential equations describe this circuit

SCR (5 diode version)

3) SCR: Analysis. Determine the voltages at V1 and V2 (both DC). Assume a firing angle of 30 degrees.

V1		V2	
V1(DC)	V1(AC)	V2(DC)	V2(AC)
27.395V	47.3Vpp	23.4814V	0.826Vpp

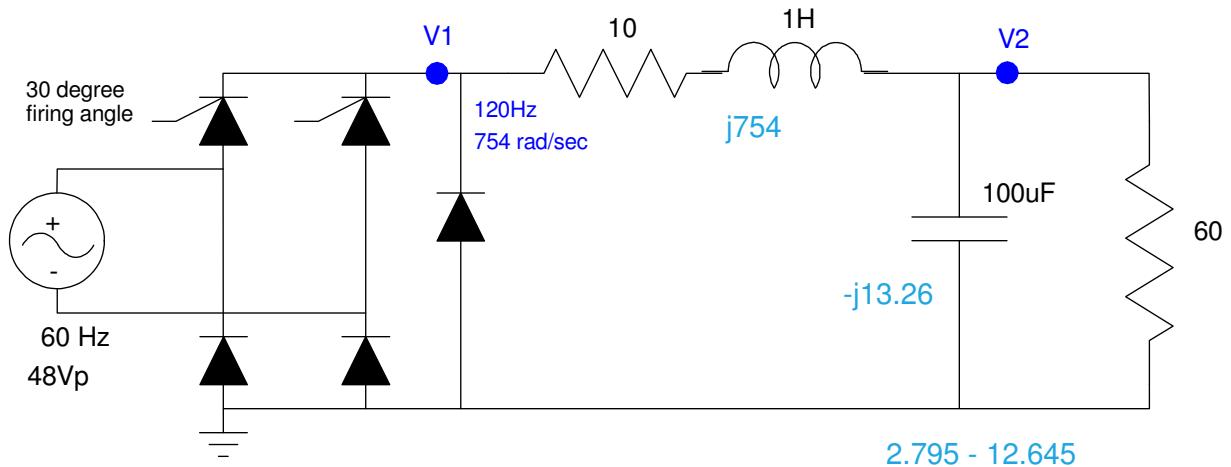

$$V_{avg} = \left(\frac{V_p + 0.7}{\pi} \right) (1 + \cos \theta) - 0.7$$

$$V_{avg} = \left(\frac{47.3}{\pi} \right) (1 + \cos (30^\circ)) - 0.7$$

$$V_1(DC) = V_{avg} = 27.395V$$

$$V_1(AC) = 48V - 1.4V + 0.7V = 47.3V_{pp}$$

$$V_2(DC) = \left(\frac{60}{60+10} \right) 27.395V = 23.4814V$$


$$V_2(AC) = \left(\frac{(2.795-j12.64)}{(2.795-j12.64)+(10+j754)} \right) (47.3V_{pp})$$

$$V_2(AC) = 0.826V_{pp}$$

4) SCR Design. Determine the firing angle, R, and C so that

- $V_2(DC) = 10.0V$
- $I(R) = 200mA$
- $V_2(AC) = 200mVpp$

$V_1(DC)$	Firing Angle	C	R
12.00V	99.003 deg	421uF	50 Ohms

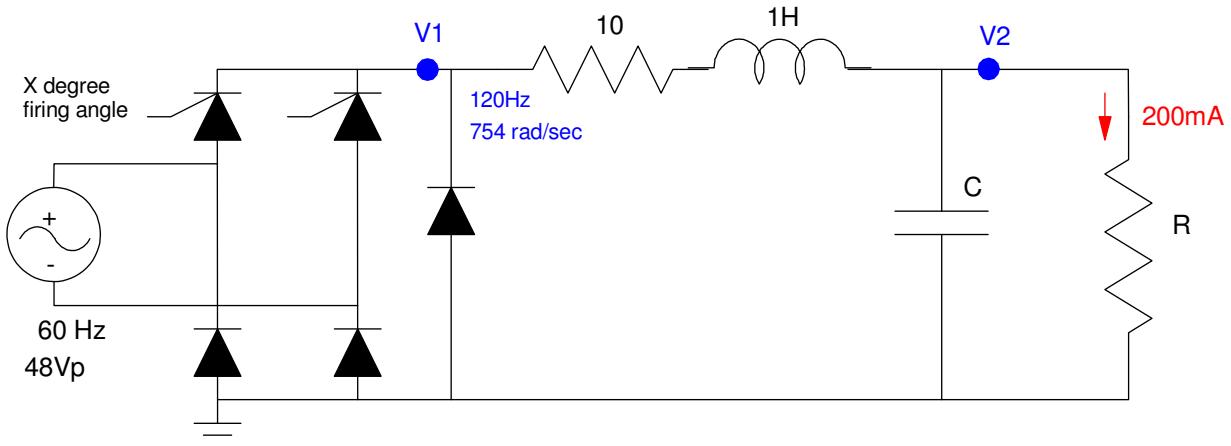

$$R = \left(\frac{10.00V}{200mA} \right) = 50\Omega$$

$$V_1(DC) = \left(\frac{50+10}{50} \right) V_2(DC) = 12.00V$$

$$V_1(DC) = \left(\frac{V_p+0.7}{\pi} \right) (1 + \cos \theta) - 0.7$$

$$12.00V = \left(\frac{(48V-1.4V)+0.7V}{\pi} \right) (1 + \cos(\theta)) - 0.7$$

$$\theta = 99.003^0$$

If $C = 0$

$$V_1(AC) = 48 \sin(99.003^0) - 1.4V + 0.7V$$

$$V_1(AC) = 48.109V_{pp}$$

$$V_2(AC) = \left(\frac{50}{50+(10+j754)} \right) 48.109V_{pp}$$

$$V_2(AC) = 3.180V_{pp}$$

To reduce the ripple to 200mVpp


$$Z_c = \left| \frac{1}{j\omega C} \right| = \left(\frac{200mV_{pp}}{3.180V_{pp}} \right) 50\Omega = 3.144\Omega$$

$$C = 421uF$$


5) Design a circuit using NAND gates to implement the following logic (i.e. circle the ones)

$$X = ABCD$$

$$Y = (X < 13)$$

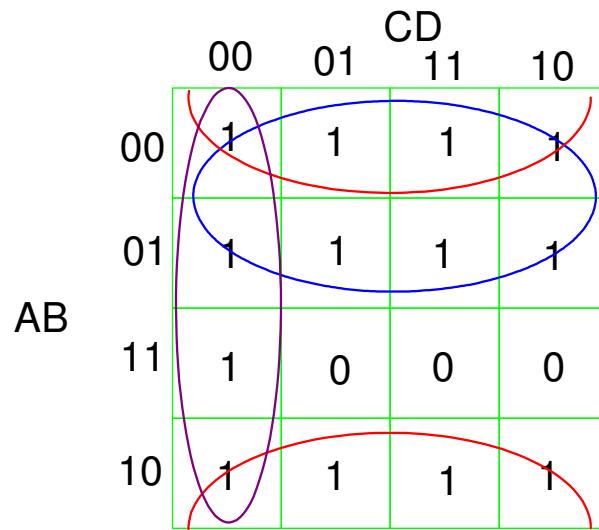

$$Y = C'D' + A' + B'$$

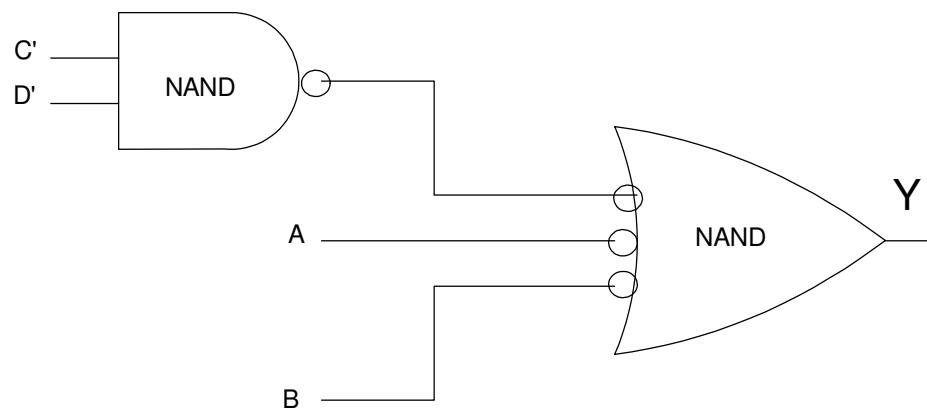

6) Design a circuit using NOR gates to implement the following logic (i.e. circle the zeros)

$$X = ABCD$$

$$Y = (X < 13)$$

		CD	
		00	01
AB		11	10
00		1	1
01		1	1
11		1	0
10		1	1

$$Y' = ABD + ABC$$

$$Y = (A' + B' + D')(A' + B' + C')$$

