


ECE 320 - Homework #1

EE 206 Review, Phasors. Due Monday, August 31st

Please make the subject "ECE 320 HW#1" if submitting homework electronically to Jacob_Glower@yahoo.com (or on blackboard)

Resistors in series and parallel

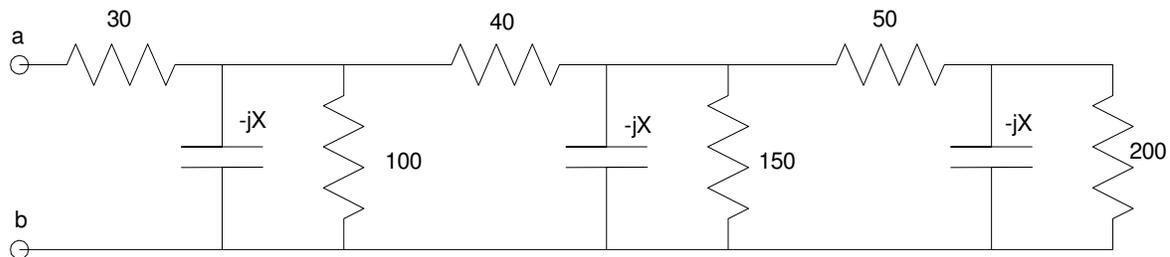1) Assume $X = \text{infinity}$ (DC analysis). Determine the resistance R_{ab}



$$200 + 50 = 250$$

$$250 \parallel 150 = 93.75$$

$$93.75 + 40 = 133.75$$

$$133.75 \parallel 100 = 57.219$$

$$57.219 + 30 = 87.219$$

answer: $R_{ab} = 87.219$ Ohms

2) Assume $-jX = -j100$. Determine the resistance R_{ab} (it will be a complex number)

$$200 \parallel -j100 = 40 - j80$$

$$(40 - j80) + 50 = 90 - j80$$

$$(90 - j80) \parallel 150 \parallel -j100 = 31.668 - j38.172$$

$$(31.668 - j38.172) + 40 = 71.668 - j38.172$$

$$(71.668 - j38.172) \parallel 100 \parallel -j100 = 30.473 - j23.055$$


$$(30.473 - j23.055) + 30 = 60.473 - j23.055$$

answer: $R_{ab} = 60.473 - j23.055$

Voltage Nodes & Current Loops

3) (Voltage Nodes): For the following circuit

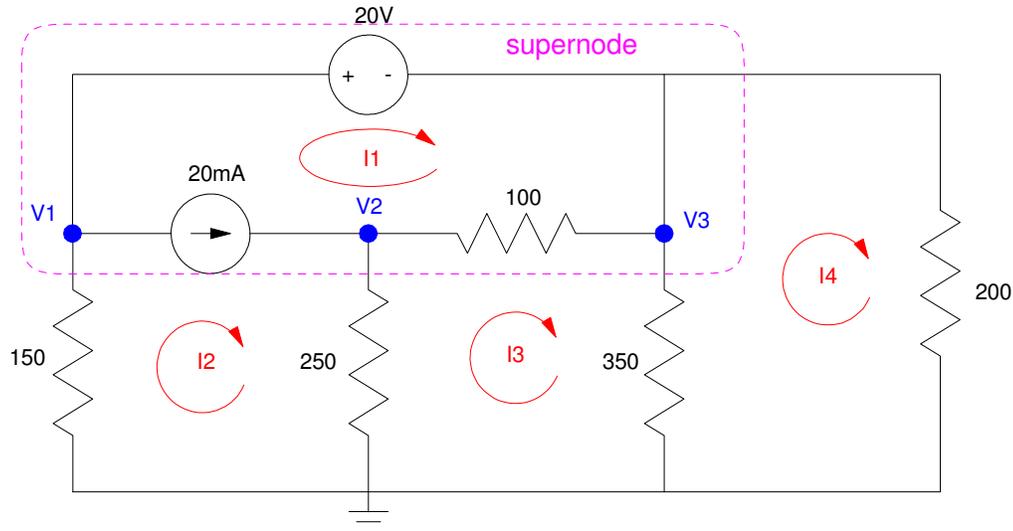- a) Write the voltage node equations
- b) Solve using Matlab (or similar program)
- c) Check your answers in CircuitLab (or similar circuit simulator)



a)

$$V_1 - V_3 = 20$$

$$-0.02 + \left(\frac{V_2}{250}\right) + \left(\frac{V_2 - V_3}{100}\right) = 0$$

$$\left(\frac{V_1}{150}\right) + \left(\frac{V_2}{250}\right) + \left(\frac{V_3}{350}\right) + \left(\frac{V_3}{200}\right) = 0$$

b) Group terms

$$V_1 - V_3 = 20$$

$$\left(\frac{1}{250} + \frac{1}{100}\right)V_2 - \left(\frac{1}{100}\right)V_3 = 0.02$$

$$\left(\frac{1}{150}\right)V_1 + \left(\frac{1}{250}\right)V_2 + \left(\frac{1}{350} + \frac{1}{200}\right)V_3 = 0$$

and place in matrix form

$$\begin{bmatrix} 1 & 0 & -1 \\ 0 & \left(\frac{1}{250} + \frac{1}{100}\right) & \left(\frac{-1}{100}\right) \\ \left(\frac{1}{150}\right) & \left(\frac{1}{250}\right) & \left(\frac{1}{350} + \frac{1}{200}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 0.02 \\ 0 \end{bmatrix}$$

Solve using Matlab

```
>> A = [1,0,-1 ; 0,1/250+1/100,-1/100 ; 1/150,1/250,1/350+1/200]
```

A =

```
1.0000      0      -1.0000
      0      0.0140     -0.0100
0.0067      0.0040      0.0079
```

```
>> B = [20;0.02;0]
```

B =

```
20.0000
 0.0200
      0
```


```
>> V = inv(A)*B
```

V =

```
12.0000
-4.2857
-8.0000
```


c) Check your answers in CircuitLab (or similar circuit simulator)

- Same answers

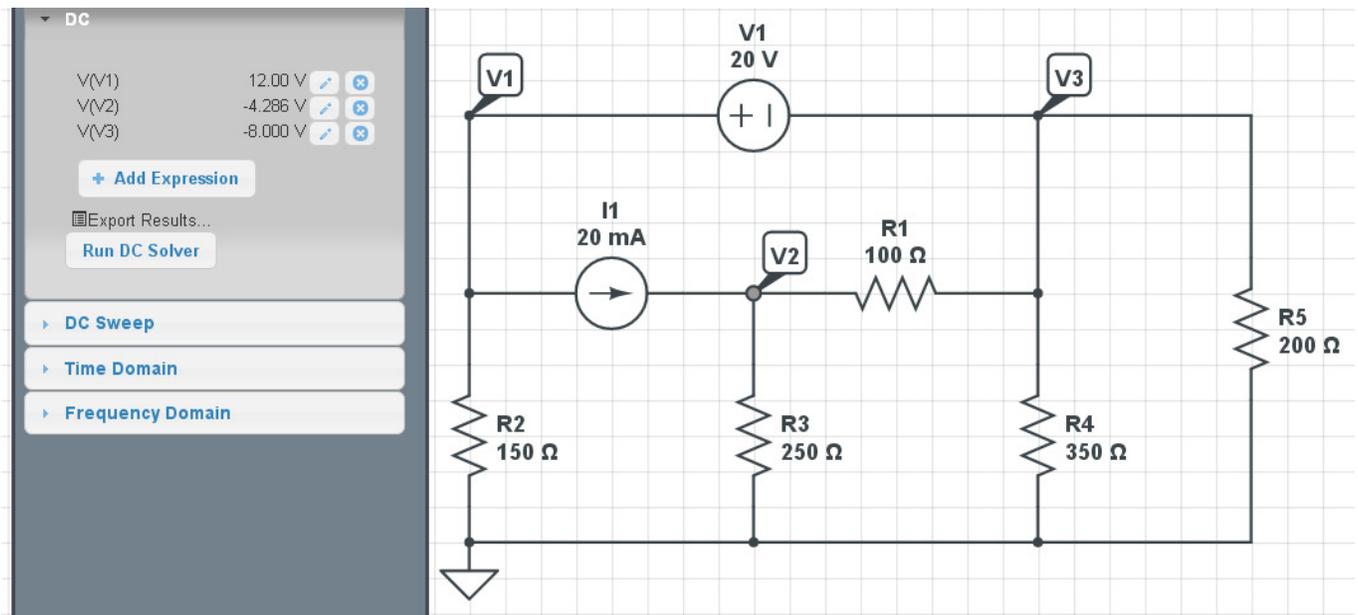

4) (Current Loops) For the following circuit

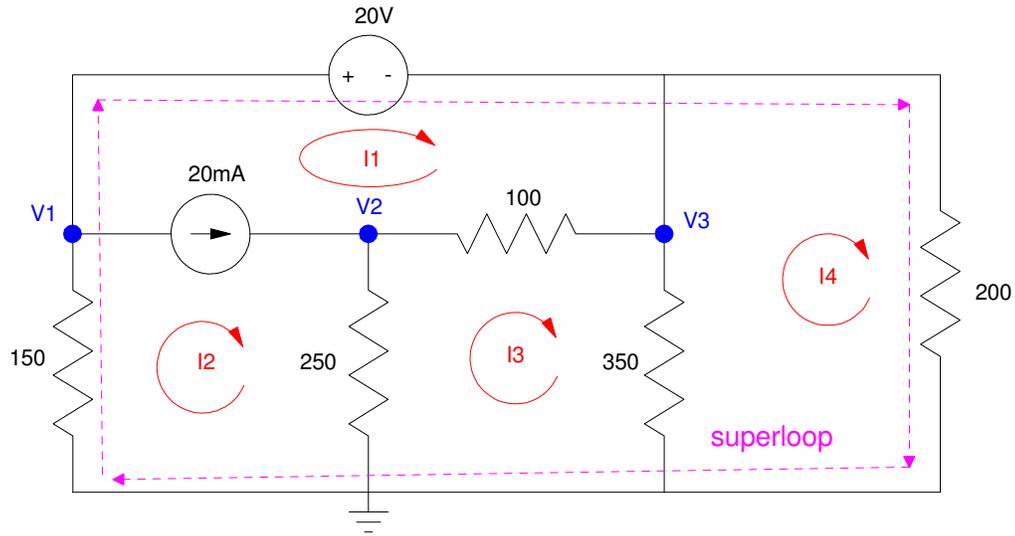- a) Write the current loop equations
- b) Solve using Matlab (or similar program)
- c) Check your answers in CircuitLab (or similar circuit simulator)



a) Write the current loop equations

$$I_2 - I_1 = 0.02$$

$$250(I_3 - I_2) + 100(I_3 - I_1) + 350(I_3 - I_4) = 0$$

$$350(I_4 - I_3) + 200I_4 = 0$$

$$150I_2 + 20 + 200I_4 = 0$$

b) Solve using Matlab (or similar program)

Group terms

$$I_2 - I_1 = 0.02$$

$$-100I_1 - 250I_2 + 700I_3 - 350I_4 = 0$$

$$-350I_3 + 550I_4 = 0$$

$$150I_2 + 200I_4 = -20$$

Place in matrix form

$$\begin{bmatrix} -1 & 1 & 0 & 0 \\ -100 & -250 & 700 & -350 \\ 0 & 0 & -350 & 550 \\ 0 & 150 & 0 & 200 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 0.02 \\ 0 \\ 0 \\ -20 \end{bmatrix}$$

Solve with Matlab

```
>> A = [-1,1,0,0 ; -100,-250,700,-350 ; 0,0,-350,550 ; 0,150,0,200]
```

```
    -1     1     0     0  
-100  -250   700  -350  
     0     0  -350   550  
     0    150     0   200
```

```
>> B = [0.02;0;0;-20]
```


```
    0.0200  
     0  
     0  
-20.0000
```

```
>> I = inv(A)*B
```


```
   -0.1000  
   -0.0800  
   -0.0629  
   -0.0400
```

```
>>
```

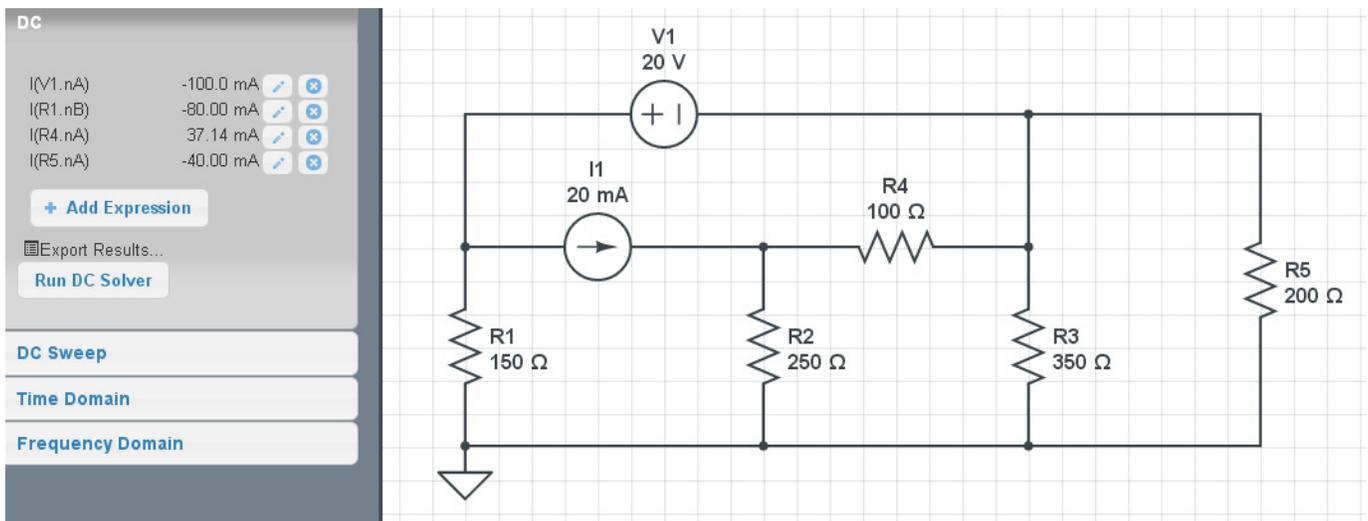c) Check your answers in CircuitLab (or similar circuit simulator)



5) Find the Thevenin equivalent for the following circuit

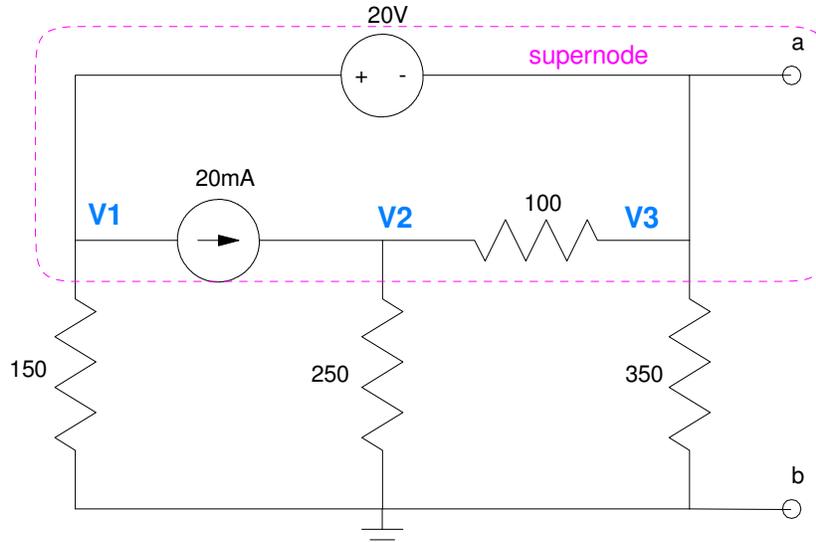

Problem 5

Rth: Set the sources to zero and solve for Rab

$$R_{ab} = 150 \parallel 350 \parallel 350 = 80.769 \text{ Ohms}$$

Vth: Compute the open-circuit voltage. Use voltage nodes (same circuit as before with $I_4 = 0$)

$$V_1 - V_3 = 20$$

$$-0.02 + \left(\frac{V_2}{250}\right) + \left(\frac{V_2 - V_3}{100}\right) = 0$$

$$\left(\frac{V_1}{150}\right) + \left(\frac{V_2}{250}\right) + \left(\frac{V_3}{350}\right) = 0$$

Group terms and place in matrix form

$$\begin{bmatrix} 1 & 0 & -1 \\ 0 & \left(\frac{1}{250} + \frac{1}{100}\right) & \left(\frac{-1}{100}\right) \\ \left(\frac{1}{150}\right) & \left(\frac{1}{250}\right) & \left(\frac{1}{350}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 0.02 \\ 0 \end{bmatrix}$$

$$\gg A = [1, 0, -1 ; 0, 1/250+1/100, -1/100 ; 1/150, 1/250, 1/350]$$

A =

$$\begin{bmatrix} 1.0000 & 0 & -1.0000 \\ 0 & 0.0140 & -0.0100 \\ 0.0067 & 0.0040 & 0.0029 \end{bmatrix}$$

```
>> B = [20;0.02;0]
```

```
B =
```

```
20.0000  
0.0200  
0
```

```
>> V = inv(A)*B
```

```
V =
```

```
8.7692  
-6.5934  
-11.2308
```

$V_3 = V_{th} = -11.23V$

Solution:


$V_{th} = -11.23V$

$R_{th} = 80.769 \text{ Ohms}$

6) Assume V_{in} contains a DC and 500 rad/sec (79.57Hz) signal:

$$V_{in} = 10 + 3 \sin(500t)$$

- a) Determine the impedances of the inductor, capacitor, and resistor at DC and 500 rad/sec
- b) Determine the voltage, V_2 , using phasor analysis
- c) Check your answer using PartSim (or similar program)

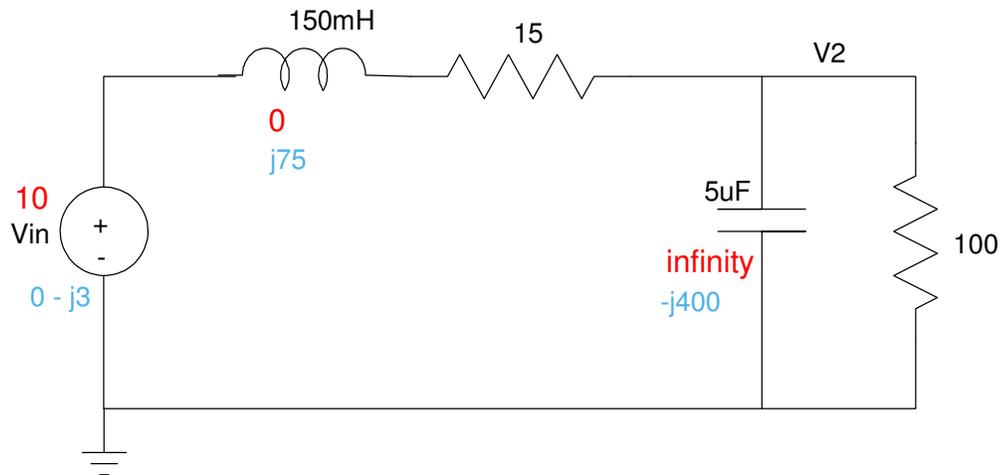

Problem 6

DC (red)

$$V_2 = \left(\frac{100}{100+15} \right) 10 = 8.696V$$

AC (blue)

$$100 \parallel -j400 = 94.118 - j23.529$$

$$V_2 = \left(\frac{94.118 - j23.529}{(94.118 - j23.529) + (15 + j75)} \right) (0 - j3)$$

$$V_2 = -1.528 - j1.867$$

$$v_2(t) = -1.528 \cos(500t) + 1.867 \sin(500t)$$

Total answer is DC + AC

$$v_2(t) = 8.696 - 1.528 \cos(500t) + 1.867 \sin(500t)$$

In CircuitLab

- Run a time-domain simulation
- V1 = 10V (DC) 3V (AC) at 79.58Hz ($2\pi f = 500$)
- A period is 13ms. Run the simulation for a couple periods (50ms)
- Make the time step 1000x smaller for 1000 points on the plot

