

ECE 320 - Homework #6


H-Bridge, DC to DC Converters, Fourier Transforms. Due Monday, October 5th

H-Bridges:


1) Determine the voltages and currents for the following 1/2 H-bridge for

- $V_1 = 0V, V_2 = 0V$
- $V_1 = 5V, V_2 = 5V$
- $V_1 = 5V, V_2 = 0V$


Assume 3904/3906 transistors

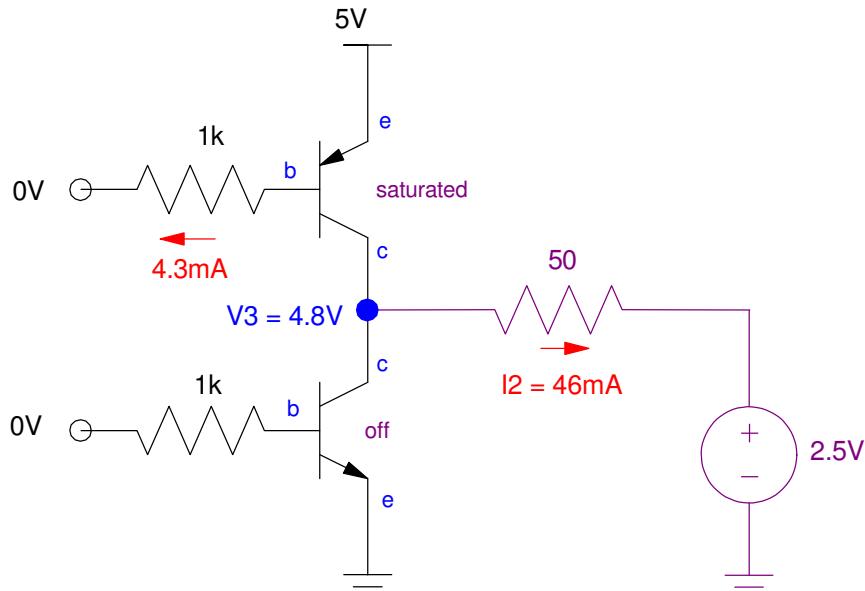

$0V : 0V$ results in $V_2 = 4.8V$


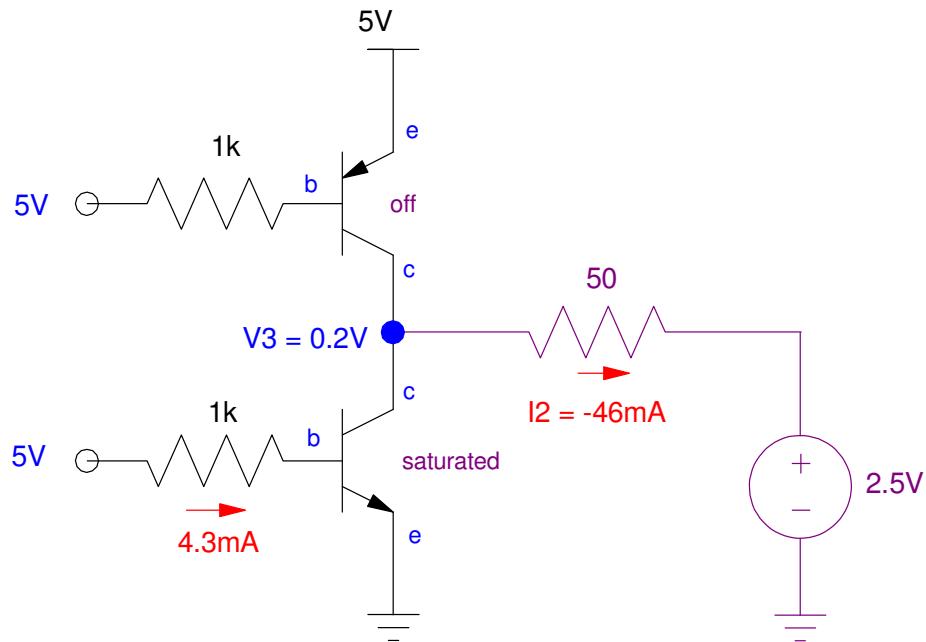


$5V : 5V$ results in $0.2V$

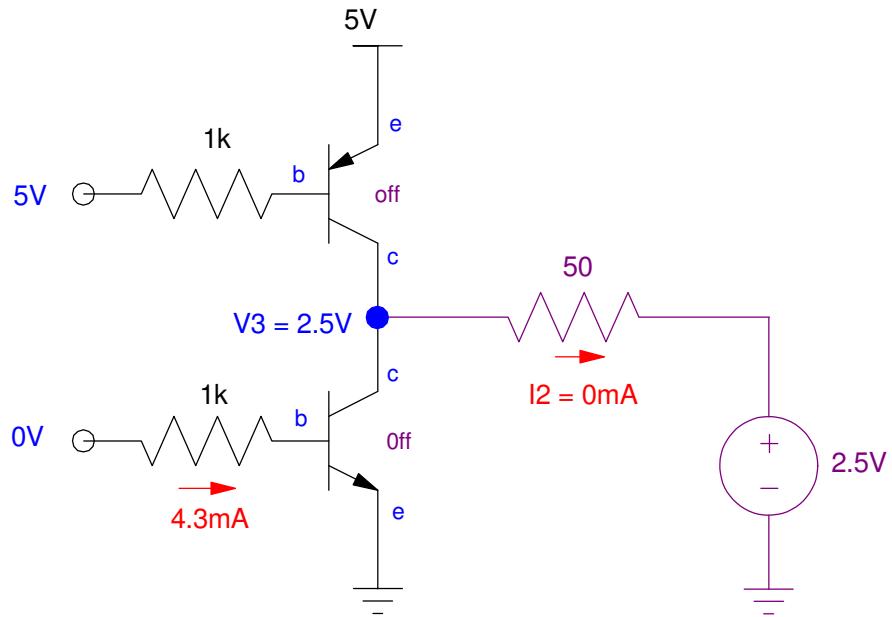

Voltages for 5V : 0V input

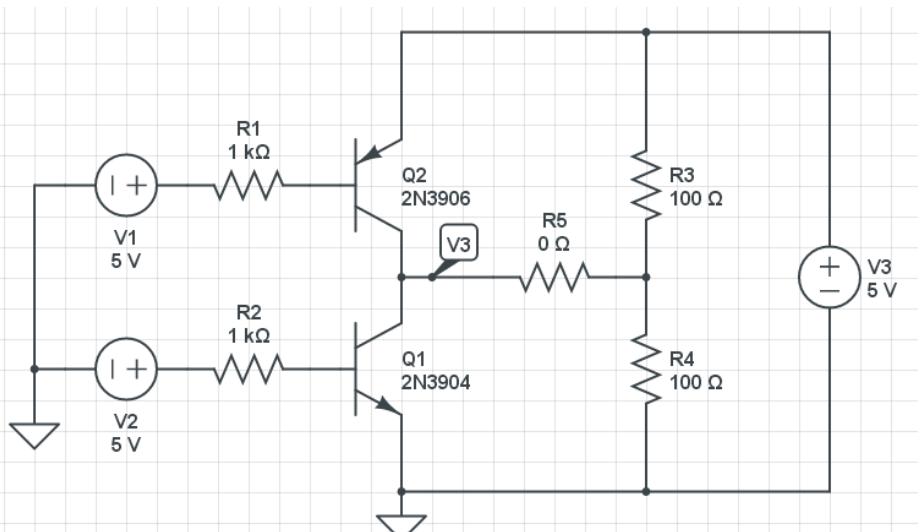
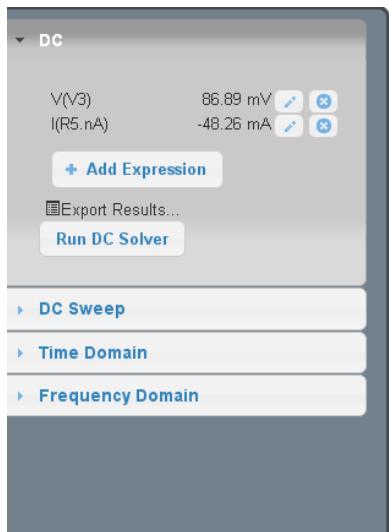
2) Check your results (voltages and currents) in CircuitLab



		Calculated	Simulated	Measured
V1 = 5V V2 = 5V	V3	0.20V	86.89mV	
	I3	-46.0mA	-48.26mA	
V1 = 0V V2 = 0V	V3	4.80V	4.884V	
	I3	+46.0mA	+46.87mA	
V1 = 5V V2 = 0V	V3	2.50V	2.500V	
	I3	0.0mA	0.0mA	


3) Lab: Build this circuit and measure the voltages and currents. (note: it's OK to compute the currents from the measured voltages).

		Calculated	Simulated	Measured
V1 = 5V V2 = 5V	V3	0.20V	86.89mV	0.09V
	I2	-46.0mA	-48.26mA	-48mA
V1 = 0V V2 = 0V	V3	4.80V	4.884V	4.96V
	I2	+46.0mA	+46.87mA	+49mA
V1 = 5V V2 = 0V	V3	2.50V	2.500V	2.46V
	I2	0.0mA	0.0mA	-1mA

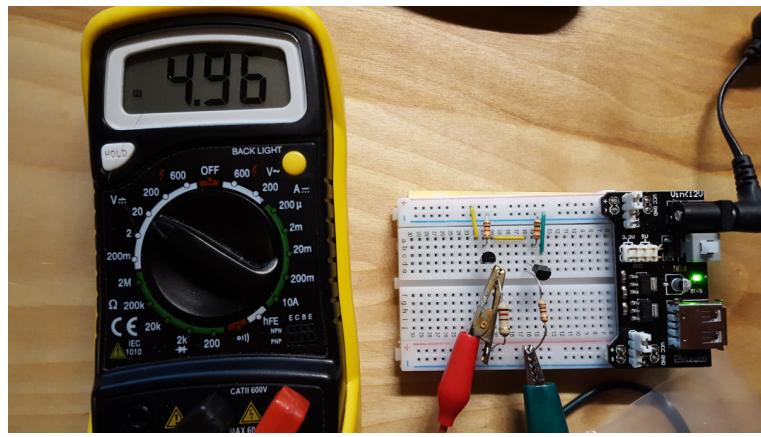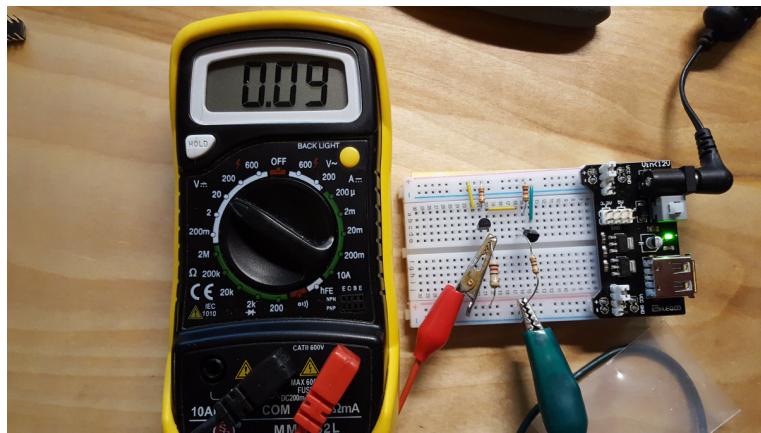

DC to DC Converters

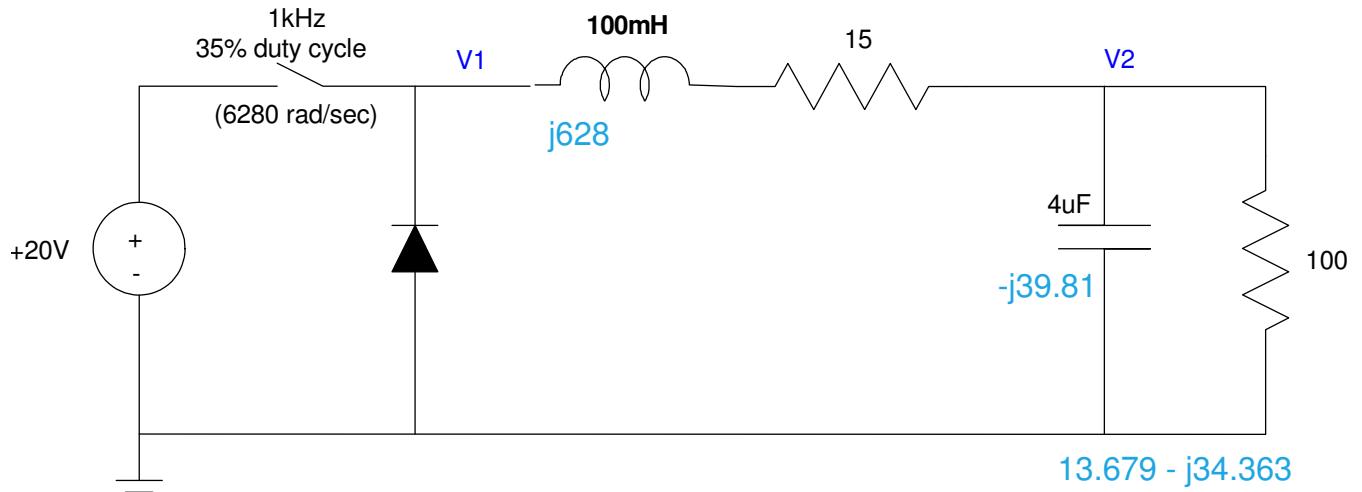4) Determine the voltages (both DC and AC) for V1 and V2.



DC

$$V_1(DC) = 0.35 \cdot (+20V) + 0.65 \cdot (-0.70V)$$

$$V_1(DC) = 6.545V$$

$$V_2(DC) = \left(\frac{100}{100+15} \right) 6.545V$$

$$V_2(DC) = 5.6913V$$

AC

$$V_1(AC) = 20.7V_{pp}$$

$$V_2(AC) = \left(\frac{(13.679-j34.363)}{(13.679-j34.363)+(15+j628)} \right) \cdot 20.7V_{pp}$$

$$V_2(AC) = 1.2882V_{pp}$$

5) Change the duty cycle and C so that

- The DC voltage at V2 = 5.00V
- The ripple at V2 is 100mVpp

If V2 = 5.00V, then V1 is

$$V_1(DC) = \left(\frac{100+15}{100} \right) V_2(DC)$$

$$V_1(DC) = 5.750V$$

The duty cycle is then

$$\alpha \cdot 20V + (1 - \alpha)(-0.7V) = 5.750V$$

$$\alpha = \left(\frac{5.750V + 0.7V}{20V - 0.7V} \right)$$

$$\alpha = 0.3116 = 31.16\%$$

If C = 0, the ripple at C2 is

$$V_2(AC) = \left(\frac{100}{(100)+(15+j628)} \right) 20.7V_{pp}$$

$$V_2(AC) = 3.2423V_{pp}$$


To make the ripple 100mVpp, C2 must have an impedance of

$$Z_{c2} = \left(\frac{0.1V_{pp}}{3.2423V_{pp}} \right) \cdot 100\Omega$$

$$Z_{c2} = 3.084\Omega$$


$$\left| \frac{1}{j\omega C_2} \right| = 3.084\Omega$$

$$C_2 = 51.62\mu F$$

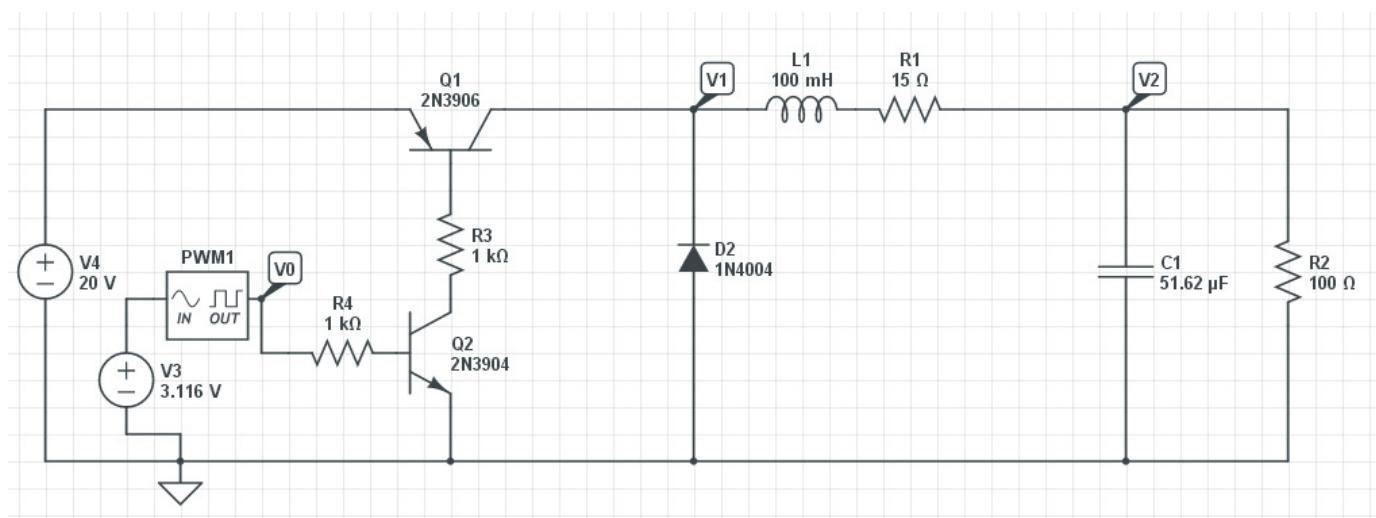

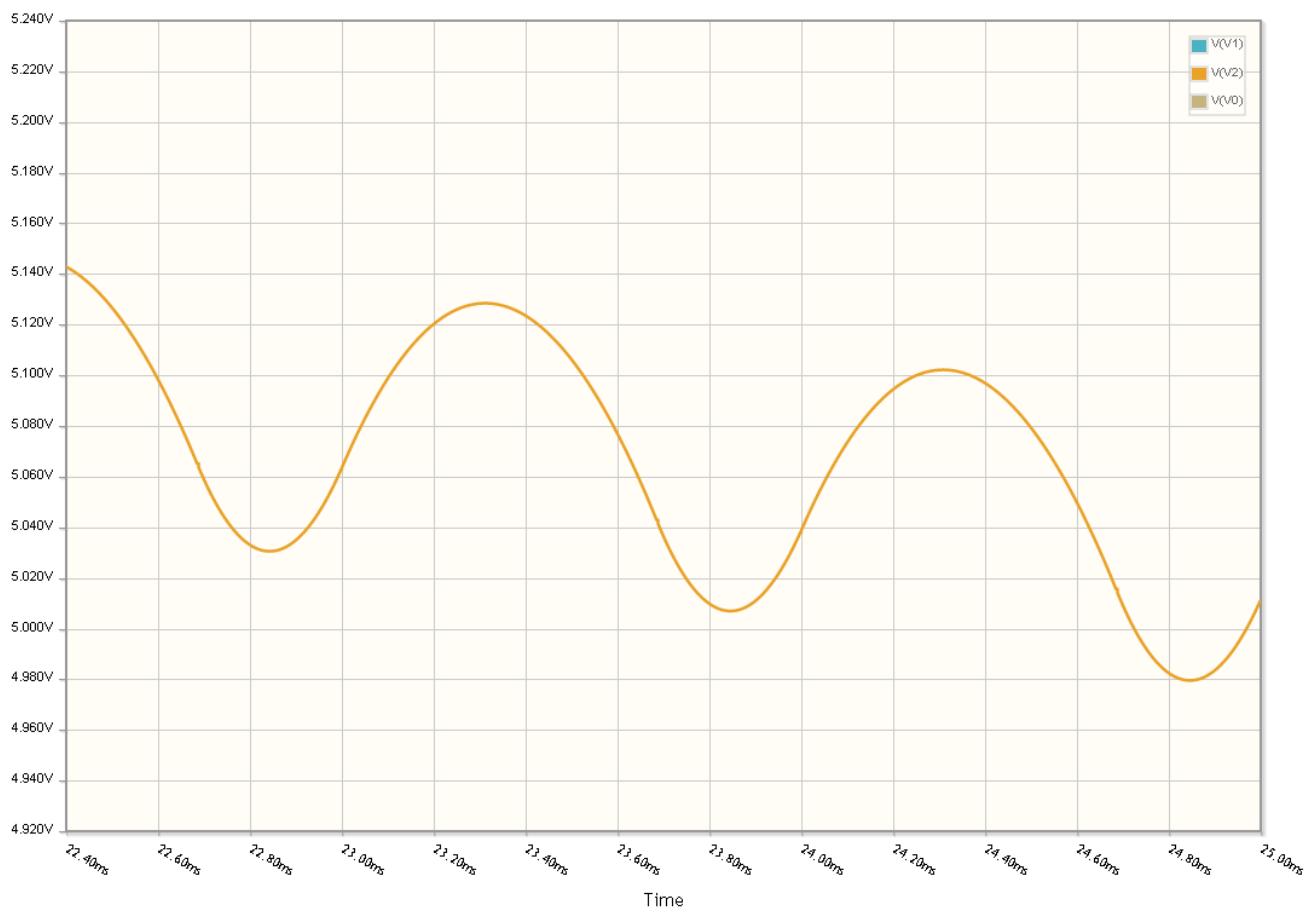6) Simulate the circuit for problem #5 in CircuitLab and determine V2 (DC and AC)

- DC = 5.083V (vs. 5.00V computed)
- AC = 153mVpp (vs. 300mVpp computed)



Fourier Transforms

The voltage V1 in problem #4 is a 35% duty cycle square wave

$$V_1(t) = V_1(t + 1\text{ms}) \quad V_1 \text{ is periodic in } 1\text{ms} - \text{i.e. it's a } 1\text{kHz square wave}$$

$$V_1(t) = \begin{cases} +20V & 0 < t < 350\mu\text{s} \\ -0.7V & 350\mu\text{s} < t < 1000\mu\text{s} \end{cases}$$

7) Determine the first five terms for the Fourier transform for V1(t)

$$V_1(t) = a_0 + a_1 \cos(\omega_0 t) + b_1 \sin(\omega_0 t) + a_2 \cos(2\omega_0 t) + b_2 \sin(2\omega_0 t)$$

```
>> t = [0:0.001:1]';
>> V1 = 20*(t<0.35) - 0.7*(t>=0.35);
>> t = t * 2 * pi;
>> a0 = mean(V1)
```

a0 = 6.5378

```
>> a1 = 2*mean(V1 .* cos(t))
```

a1 = 5.3567

```
>> b1 = 2*mean(V1 .* sin(t))
```

b1 = 10.4347


```
>> a2 = 2*mean(V1 .* cos(2*t))
```

a2 = -3.1044

```
>> b2 = 2*mean(V1 .* sin(2*t))
```

b2 = 4.3279
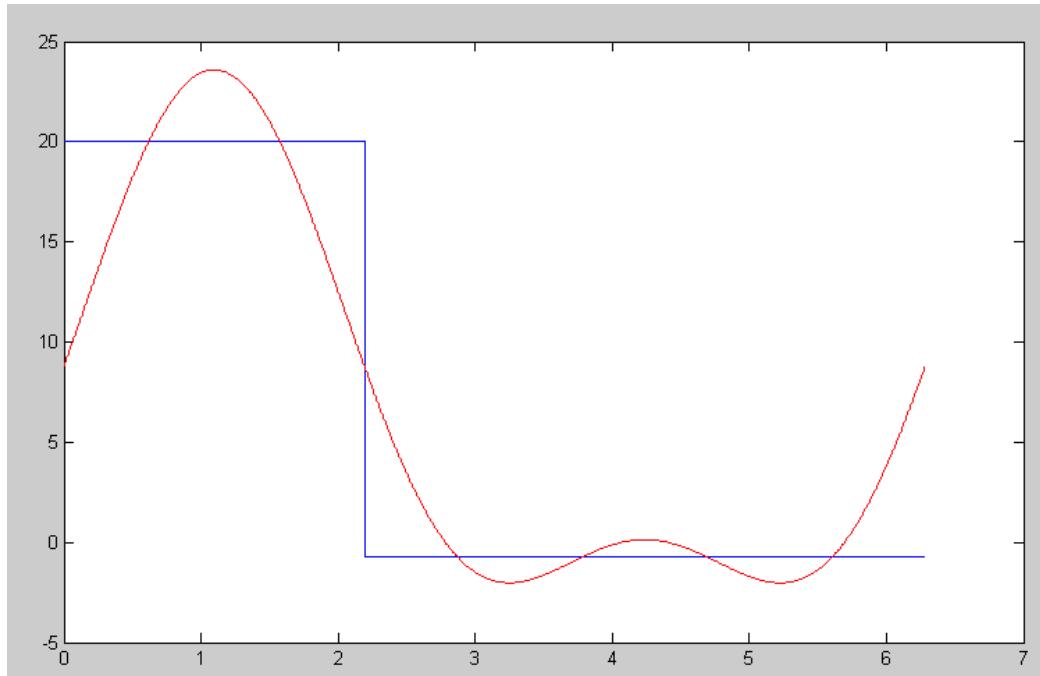
```
>> plot(t,V1,'b',t,a0+a1*cos(t)+b1*sin(t)+a2*cos(2*t)+b2*sin(2*t),'r')
```



8) Determine $V_2(t)$ at each frequency

$$V_1 = 6.5378 + 5.3567 \cos(\omega t) + 10.4347 \sin(\omega t) - 3.1044 \cos(2\omega t) + 4.3279 \sin(2\omega t)$$


DC

$$V_1 = 6.5378$$

By voltage division

$$V_2 = \left(\frac{100}{100+15} \right) V_1$$

$$V_2 = 5.6850 \text{ V}$$

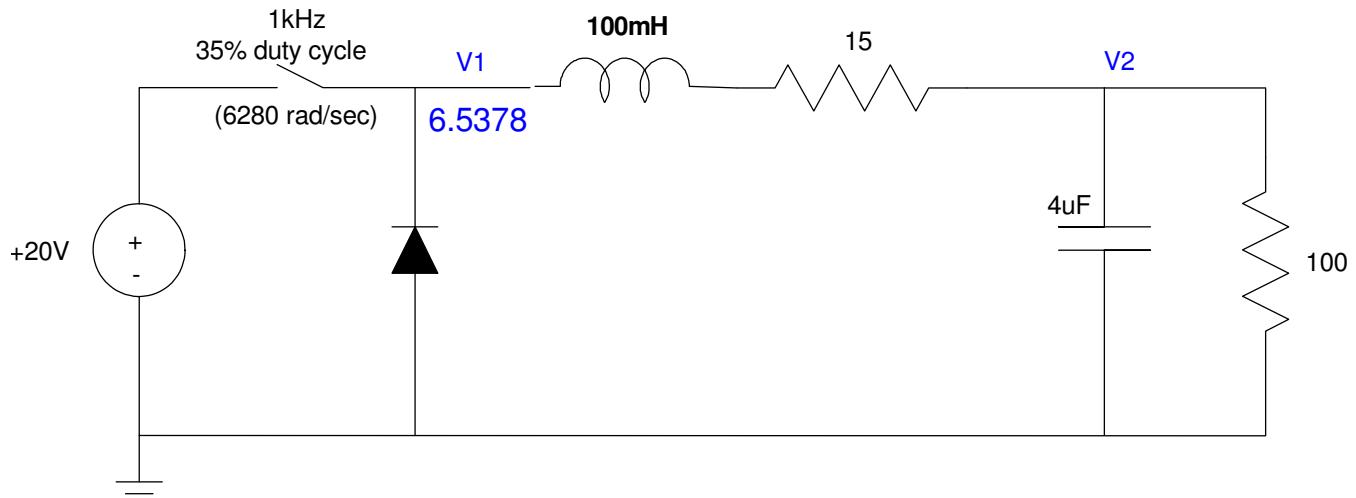

1kHz: w = 6280

$$V1 = 6.5378 + 5.3567 \cos(\omega t) + 10.4347 \sin(\omega t) - 3.1044 \cos(2\omega t) + 4.3279 \sin(2\omega t)$$

At 1kHz

$$V_1 = 5.3567 \cos(6280t) + 10.4347 \sin(6280t)$$

Converting to phasors

$$\omega = 6280 \frac{\text{rad}}{\text{sec}}$$

$$V_1 = 5.3567 - j10.4347$$

$$L \rightarrow j\omega L = j628$$

$$C \rightarrow \frac{1}{j\omega C} = -j39.81$$

By voltage division


$$V_2 = \left(\frac{(13.68-j34.36)}{(13.68-j34.36)+(15+j628)} \right) V_1$$

$$V_2 = \left(\frac{(13.68-j34.36)}{(13.68-j34.36)+(15+j628)} \right) (5.3567 - j10.4347)$$

$$V_2 = -0.5724 + j0.4529$$

meaning
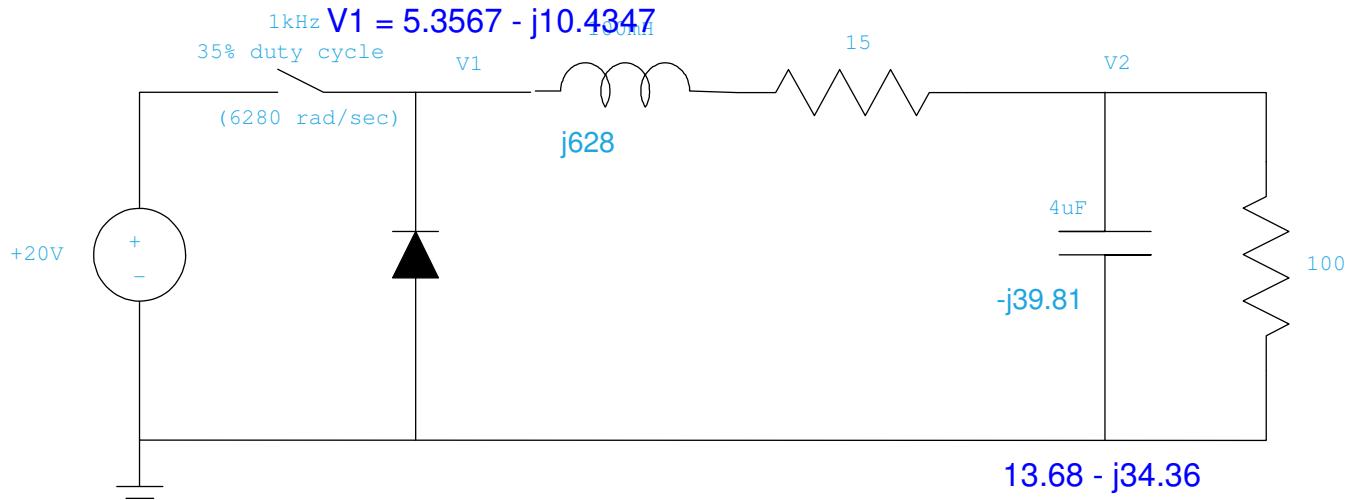
$$v_2(t) = -0.5724 \cos(6280t) - 0.4529 \sin(6280t)$$



$$V_1 = 6.5378 + 5.3567 \cos(\omega t) + 10.4347 \sin(\omega t) - 3.1044 \cos(2\omega t) + 4.3279 \sin(2\omega t)$$

2kHz: $\omega = 12,560$

$$v_1(t) = -3.1044 \cos(12560t) + 4.3279 \sin(12560t)$$

Convert to phasors

$$V_1 = -3.1044 - j4.3279$$

$$\omega = 12,560$$

$$L \rightarrow j\omega L = j1256\Omega$$

$$C \rightarrow \frac{1}{j\omega C} = -j19.90\Omega$$

By voltage division


$$V_2 = \left(\frac{3.811-j19.146}{(3.811-j19.146)+(15+j1256)} \right) V_1$$

$$V_2 = \left(\frac{3.811-j19.146}{(3.811-j19.146)+(15+j1256)} \right) (-3.1044 - j4.3279)$$

$$V_2 = 0.0335 + j0.0771$$

meaning
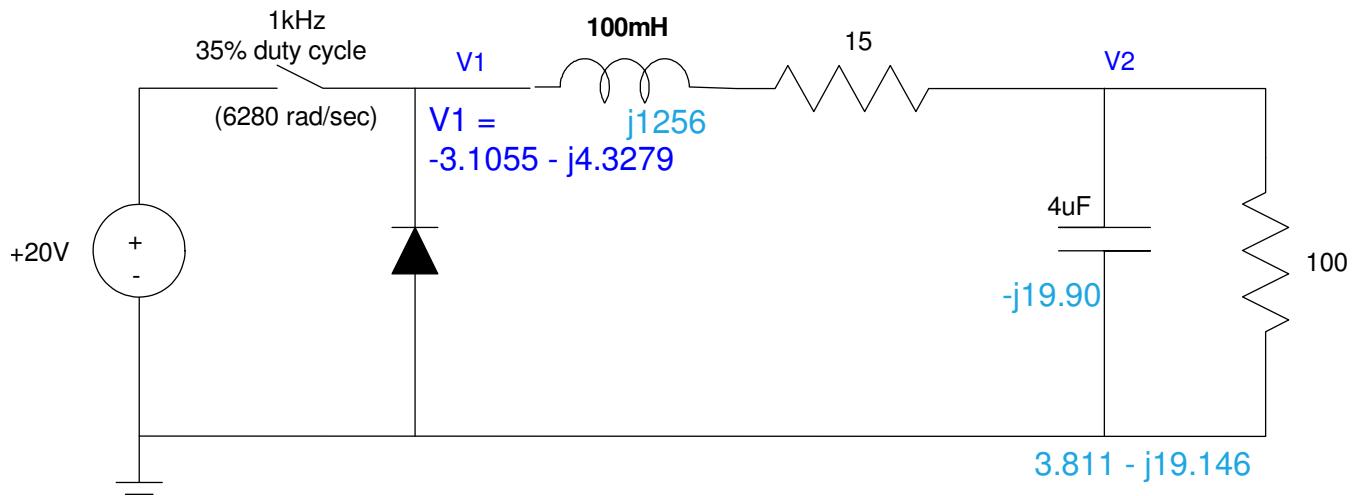
$$v_2(t) = 0.0335 \cos(12560t) - 0.0771 \sin(12560t)$$



Put it all together

$$V_2 = DC + 1\text{kHz} + 2\text{kHz terms}$$

$$V_2 = 5.6850 - 0.5724 \cos(6280t) - 0.4529 \sin(6280t) + 0.03350 \cos(12560t) - 0.0771 \sin(12560t)$$

9) How do your answers for problem #1 and problem #8 compare?

	Problem #4	Problem #8
V ₂ (DC)	5.6913	5.6850
V ₂ 1kHz term	1.2882 V _{pp}	- 0.5724 + j0.4529 1.4598 V _{pp}
V ₂ 2kHz term	0 V _{pp}	0.03350 + j0.0771 0.1681 V _{pp}