

ECE 320 - Homework #7



DC to AC, SCR, Boolean Logic. Due Monday, October 12th

DC to AC

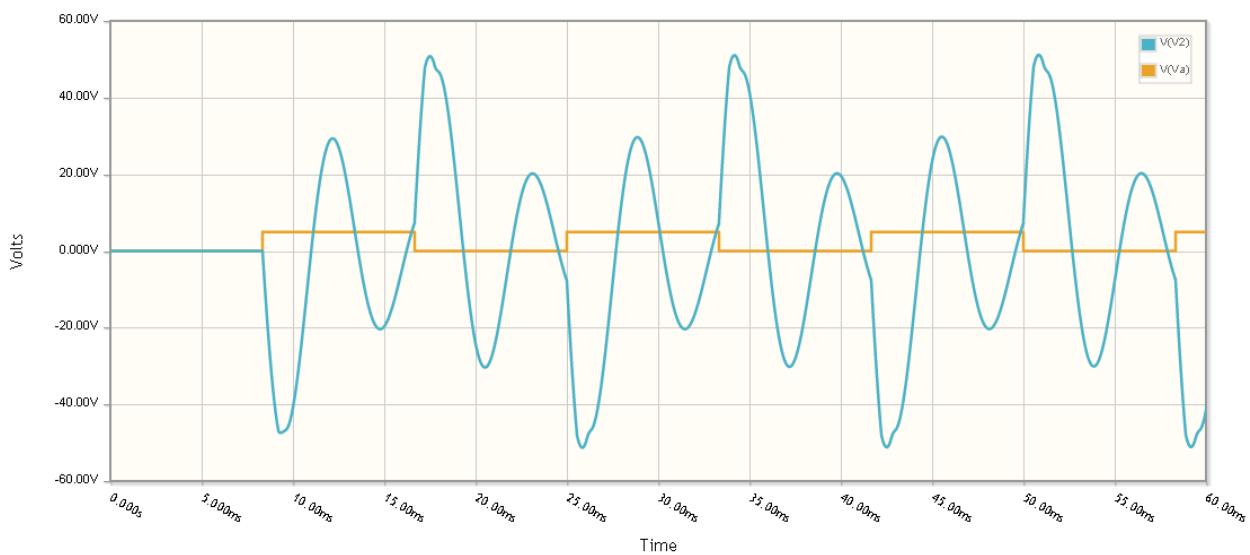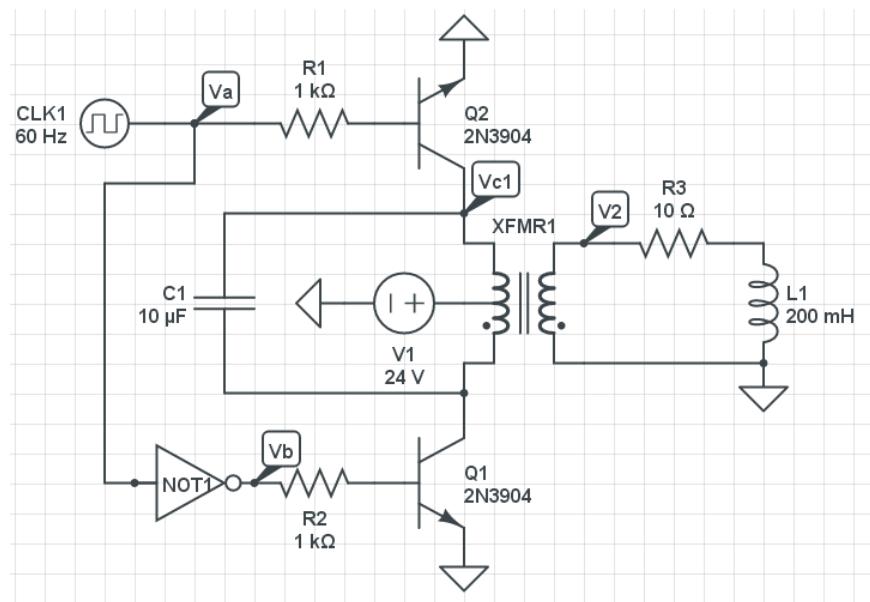1) Let

- A = 0V / 5V square wave, 60Hz, 0 degree time delay
- B = 0V / 5V square wave, 60Hz, 180 degree time delay
- C = 10uF

Determine using CircuitLab the voltage V2 (i.e. the voltage across a DC motor, modeled as a 10 Ohm & 200mH load) (note: The LC oscillator is tuned to 180Hz. Increase C to bring this down to 60Hz.)





2) Adjust C so that the voltage across the motor is as close to a sine wave as possible (trial and error)

The resonance of an LC oscillator is


$$\left(\frac{1}{LC}\right) = \omega^2$$

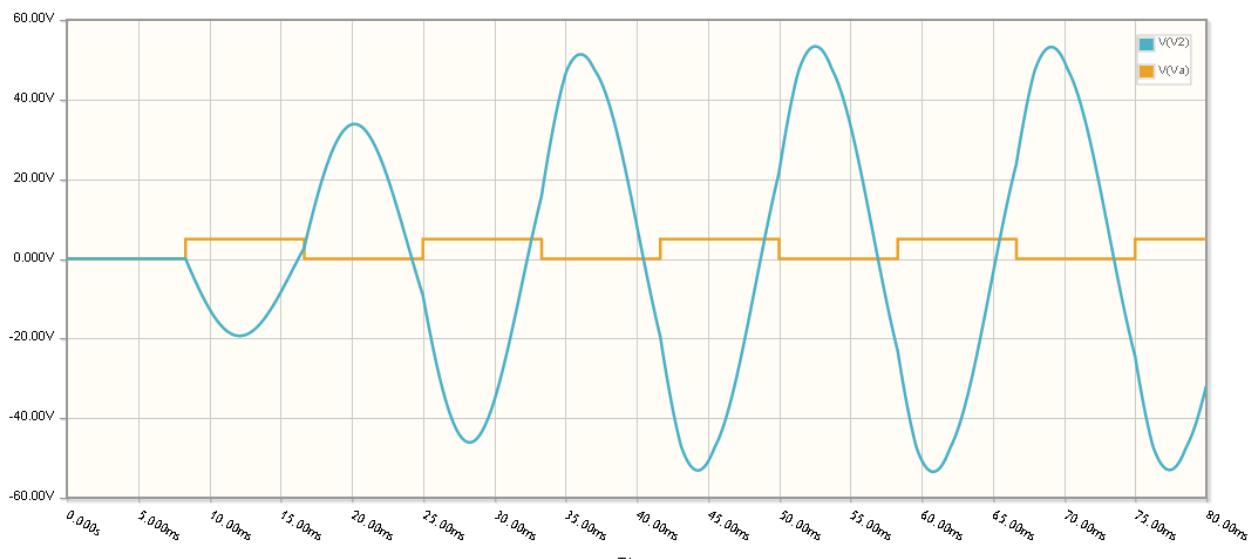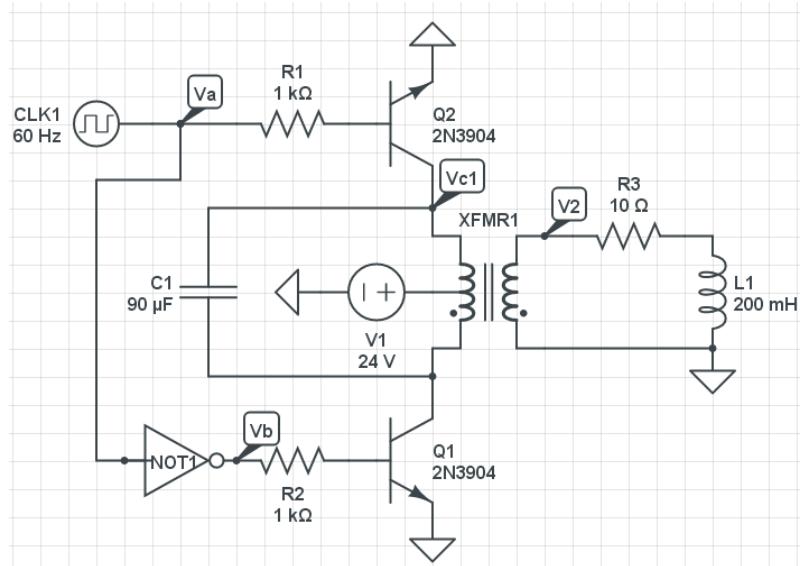To drop the resonance by 3x, make C 3x larger



SCR

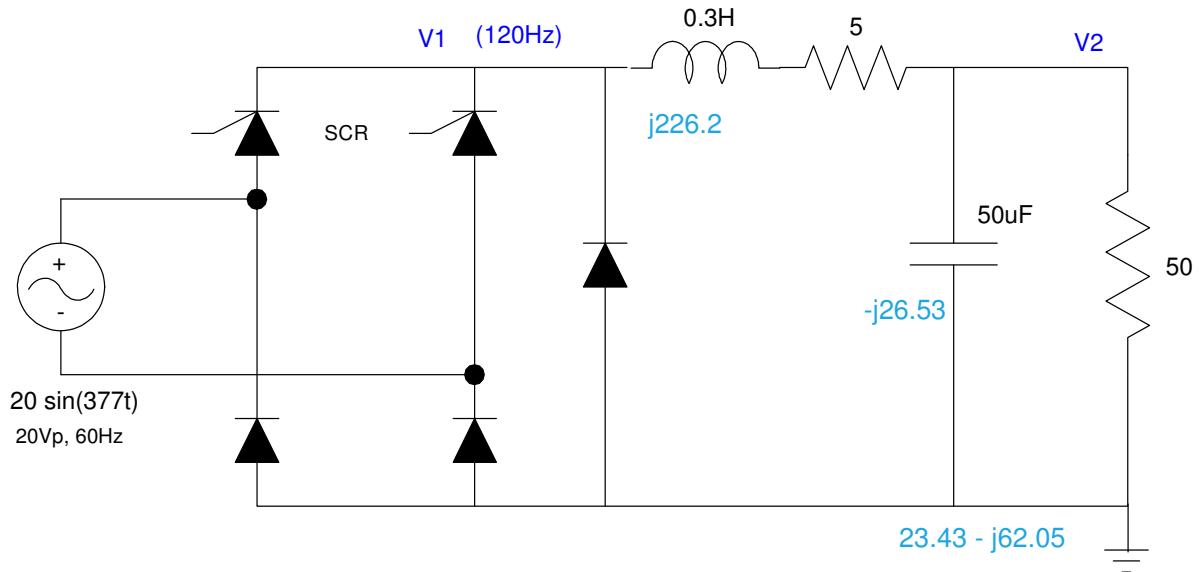3) Assume a firing angle of 25 degrees. Determine the voltage at V1 and V2 (both DC and AC).



$V_1(DC)$

$$V_1 = \left(\frac{V_p + 0.7}{\pi} \right) (1 + \cos \theta) - 0.7$$

$$V_1(DC) = \left(\frac{18.6 + 0.7}{\pi} \right) (1 + \cos (25^\circ)) - 0.7$$

$$V_1(DC) = 11.011$$

$$V_2(DC) = \left(\frac{50}{50+5} \right) 11.011$$

$$V_2(DC) = 10.01V$$

$$V_1(AC) = 18.6V - (-0.7V) = 19.3V_{pp}$$

$$V_2(AC) = \left(\frac{(23.43 - j62.05)}{(23.43 - j62.05) + (5 + j226.2)} \right) 19.3V_{pp}$$

$$V_2(AC) = 2.194V_{pp}$$

4) Change this circuit so that

- The voltage at V2 is 5.00V (DC)
- With a ripple of 500mVpp

$$V_1 = \left(\frac{50+5}{50} \right) V_2 = 5.50V$$

$$V_1 = 5.50V = \left(\frac{V_p + 0.7}{\pi} \right) (1 + \cos \theta) - 0.7$$

$$\theta = 89.47^\circ$$

C2:

50uF resulted in 2.194Vpp ripple


To reduce the ripple to 500mVpp

$$C_2 = \left(\frac{2.194V_{pp}}{500mV_{pp}} \right) 50\mu F$$

$$C_2 = 219.4\mu F$$

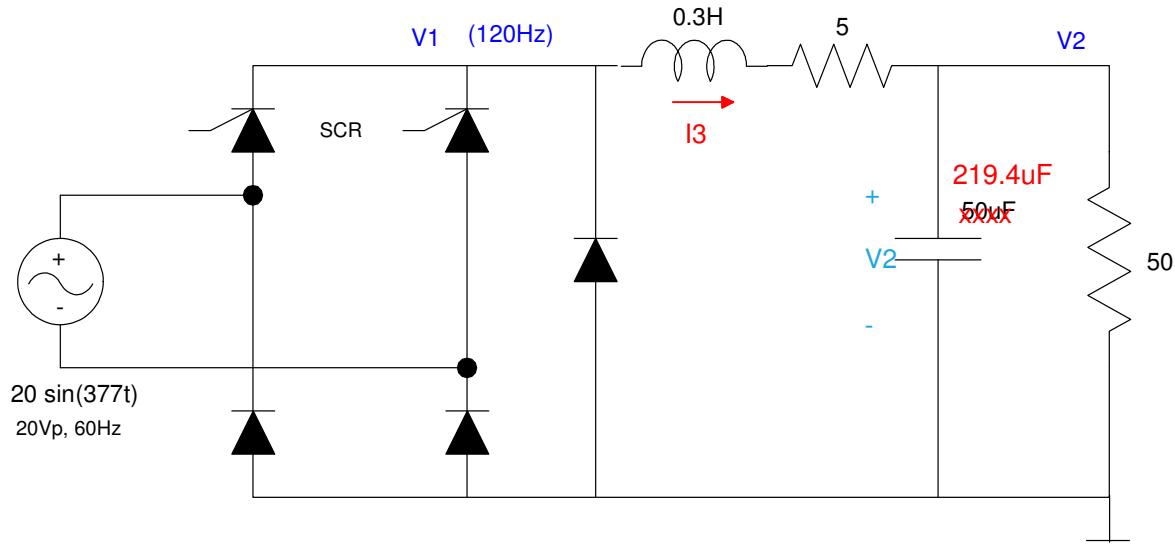5) Simulate this circuit in Matlab by

- Writing the differential equations which describe this circuit (state variables: IL and Vc)
- Specify $V1(t)$ as a full-wave rectified sine wave, clipped at X degrees (from problem #4)
- Use numerical integration to find $V2(t)$



$$\dot{V}_1 = L \dot{I}_3 = V_1 - 5I_3 - V_2$$

$$I_c = C \dot{V}_2 = I_3 - \frac{V_2}{50}$$


$$\dot{I}_3 = 3.333V_1 - 16.667I_3 - 3.333V_2$$

$$\dot{V}_2 = 4557.9I_3 - 91.158V_2$$


matlab code

```
t = [0:0.001:1]'/120/2;
dt = ( t(2) - t(1) );
phi = ( 89.47/360 ) * (1/120);
V1 = 18.6*sin(754*t) .* (t > phi) - 0.7*(t < phi);
V2 = 0*t;
I3 = 0*t;
npt = length(t);

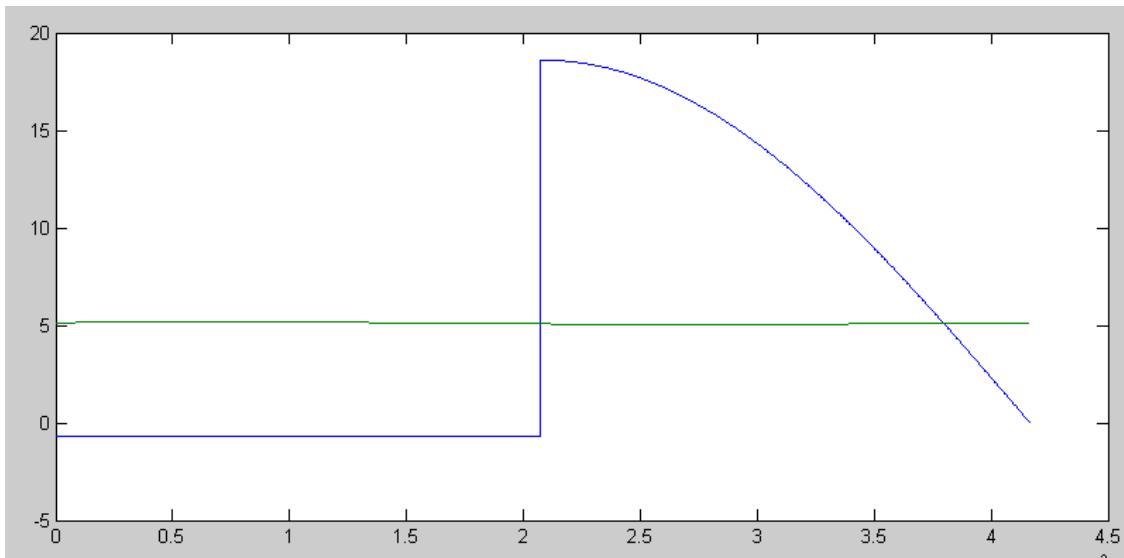for n=1:40
    V2(1) = V2(npt);
    I3(1) = I3(npt);
    for i=1:npt-1
        dI3 = 3.3333*V1(i) - 16.667*I3(i) - 3.333*V2(i);
        dV2 = 4557.9*I3(i) - 91.158*V2(i);
        V2(i+1) = V2(i) + dV2 * dt;
        I3(i+1) = I3(i) + dI3 * dt;
    end
    plot(t,V1,t,V2);
    pause(0.1);
end
plot(t,V2);
```



V1 (blue) and V2 (green)

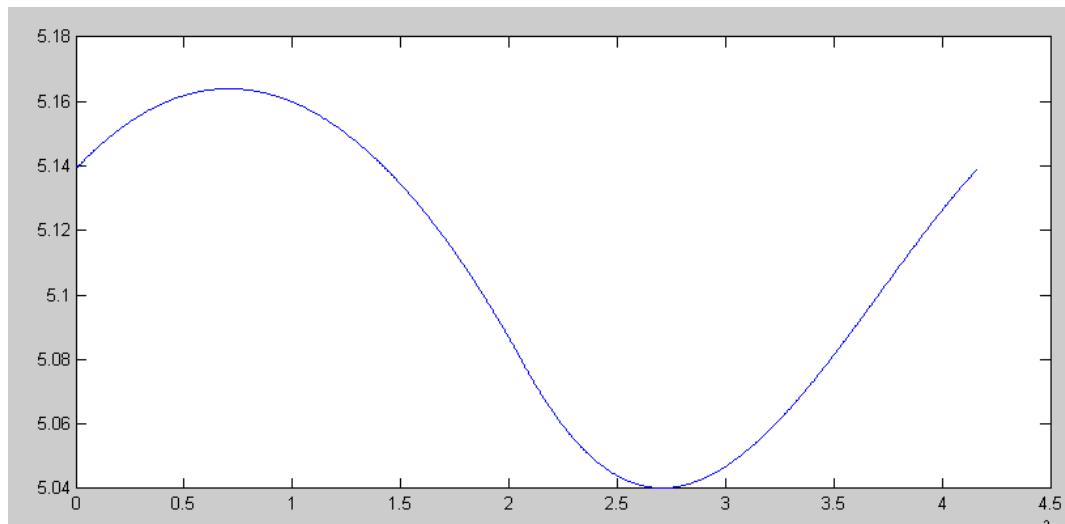


V2(t)


```
>> mean(V2)  
ans = 5.1070  
>> max(V2)-min(V2)  
ans = 0.1238
```

Boolean Logic:

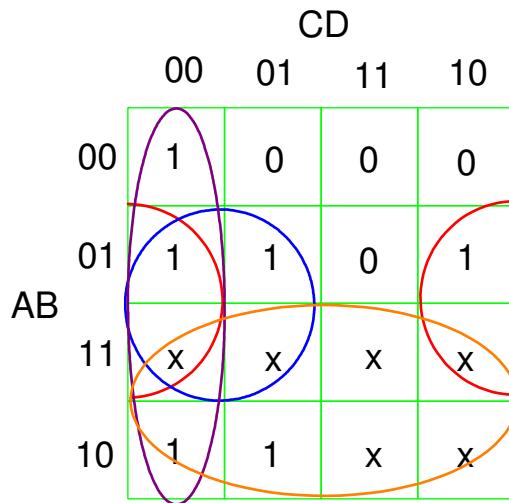
- 5) Implement the following function using NAND gates (i.e. circle the ones)



$$Y = C'D' + BC' + CD' + A$$

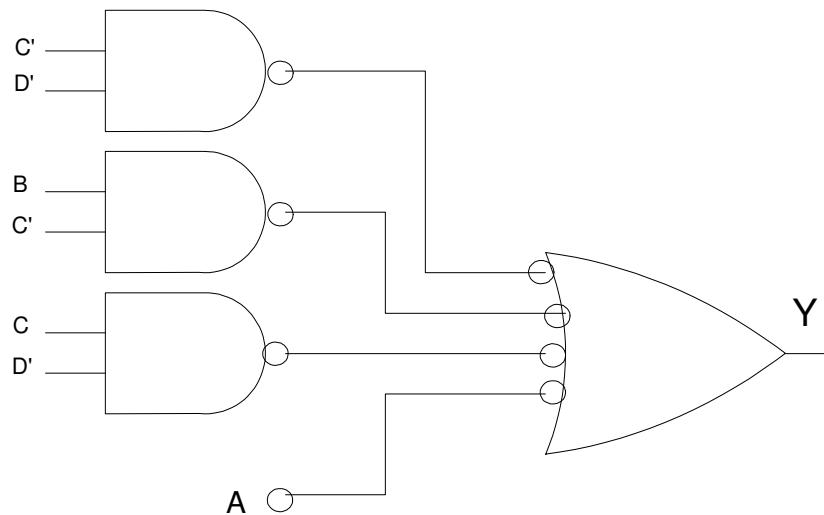

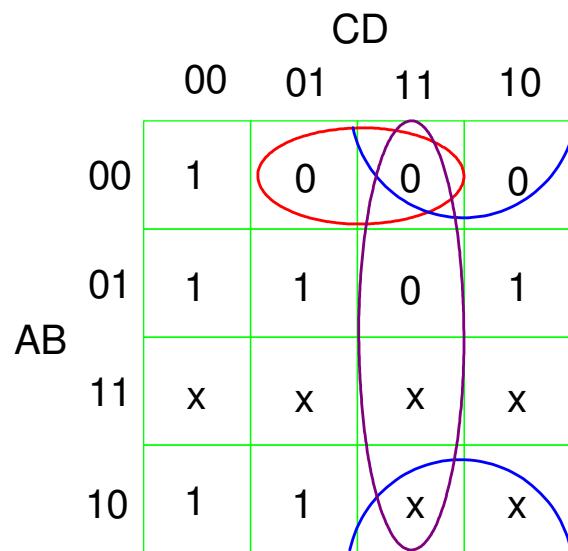6) Implement the following function using NOR gates (i.e. circle the zeros)



$$Y' = A'B'D + B'C + CD$$

$$Y = (A + B + D')(B + C')(C' + D')$$

