# ECE 320 - Homework #8

DTL, TTL Logic, MOSFET theory. Due Monday, October 19th

#### **DTL NOR Gate**

1) Determine the voltages and currents for the following DTL OR gate



2) Simulate this circuit in CircuitLab to verify your answers for problem #1

![](_page_0_Figure_6.jpeg)

## **DTL NAND Gate: Open Collector Logic**

The following circuit uses a DTL NAND gate to turn on a speaker when

- The output of a 555 timer is high (V1 = 5V), and
- The output of a comparitor is high (V2 = 5V)

The output is conencted directly to the collector of the transistor

- 3) Determine the voltage V3 and current I3 when
  - V1 = 0V
  - V2 = any

![](_page_1_Figure_8.jpeg)

![](_page_1_Figure_9.jpeg)

• V1 = V2 = 5V

![](_page_1_Figure_11.jpeg)

- 4) Simulate this circuit for 1/30ms in CircuitLab with
  - V1 = 600Hz clock signal (0V / 5V square wave)
  - V2 = 60Hz clock signal (0V / 5V)

![](_page_2_Figure_3.jpeg)

![](_page_2_Figure_4.jpeg)

Current through the Speaker: I(R2)

# Lab (include a photo to receive credit)

5) Build this circuit and measure the voltage you see at V3 for each case

![](_page_3_Picture_2.jpeg)

![](_page_3_Figure_3.jpeg)

Case 1: 0V applied to diode #2

- The transistor is always off
- Vc = 5V (transistor is off)

	STOP	CH1 DC 1X 1V/div	CH2 DC 1X 5V/div	200uS∕div	move fast	T Auto CH1 f	(	CTRL
							R	RUN7 Stop
								AUTO SET
								f CU Rsor
								/ CU RSOR
							N	MEAS JRES
1								SAVE PIC
1 VPP :	607mV	1 Freq : 374	Iz 1 Vavg:	+2.94V			S	SAVE NAVE

Case 2: 5V applied to diode #2

- Vc = 5V when the 555 timer outputs 0V (transistor off)
- Vc = 1.2V when the 555 timer outputs 5V (transistor is active mode)

Apparently, the current gain is less than 100 and I need more base current

$$I_c = \left(\frac{5V-1.2V}{28\Omega}\right) = 136mA$$
$$I_b = \left(\frac{5V-0.7V}{1k}\right) = 4.3mA$$
$$\beta = \frac{I_c}{I_b} = \frac{136mA}{4.3mA} = 31.6$$

![](_page_5_Figure_5.jpeg)

#### 6) Build this circuit using

- The 555 timer from homework set #5 for V1, and
- Connecting the The comparitor from homework set #5 for V2

#### Verify that

- The speaker turns on when T > Ton and
- The speaker turns off when T < Ton

Setting the comparitor to turn on at 1.80V

- Speaker turns on when Vr < 1.80V
- Speaker turns off when Vr > 1.83V

![](_page_6_Picture_9.jpeg)

Measuring the voltage where the speaker turns on and off

# TTL Logic

7) Determine the voltages for the following TTL inverter. Assume

- 3904 transistors.
- Current gain = 0.1 when used backwards

![](_page_7_Figure_4.jpeg)

8) Simulate these circuits in CircuitLab and determine the voltage and currents

![](_page_8_Figure_1.jpeg)

Case 1: 0V in produces 5V out (actually 4.545V due to loading)

![](_page_8_Figure_3.jpeg)

Case 2: 5V in produces 0V out (22.58mV actually) note: Ic = 4 Ib. Q1 has a gain of 4.00 when used backwards

## MOSFET

9) The VI characteristics for an n-channel MOSFET is shown on the following page. Assume Vth = 1.0V

- Determine the transconductance gain, kn
- Label the off / saturated / ohmic regions in the curve below.

kn: Point A (Ohmic region)

$$I_{ds} = k_n \left( V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$
$$4mA = k_n \left( 5V - 1V - \frac{2V}{2} \right) 2V$$
$$k_n = 666.7 \frac{\mu A}{V^2}$$

Point B (Saturated Region)

$$I_{ds} = \frac{k_n}{2} (V_{gs} - V_{th})^2$$
  
8.1mA =  $\frac{k_n}{2} (6V - 1V)^2$   
 $k_n = 648 \frac{\mu A}{V^2}$ 

The two answers should be the same (errors in reading the graph result in the slight difference)

![](_page_9_Figure_9.jpeg)

10) Draw the load line and mark the operating points for  $Vg = \{0V, 4V, 7V\}$  (change R to 1000 Ohms. Otherwise it's off the chart)

0V:

- Vds = 10V
- Ids = 0V
- Off region

4V:

- Vds = 7V
- Ids = 3mA
- Saturated Region

7V:

- Vds = 2.3V
- Ids = 7.5mA
- Ohmic Region

![](_page_10_Figure_13.jpeg)