

# ECE 320 - Homework #9

MOSFET switch, CMOS logic. Due Monday, October 26th

## MOSFET Switch

One of the MOSFET's that CircuitLab has is an IRF1047. It's specifications are

- $\text{max}(I_c) = 100\text{A}$  continuous
- $V_{gs(\text{th})} = 4\text{V}$  (max)
- $R_{ds} = 7.8\text{m}\Omega$  @  $I_{ds} = 78\text{A}$  @  $V_{gs} = 10\text{V}$
- \$0.53 each

1) Determine the transconductance gain,  $k_n$ , for this MOSFET. Assume  $V_{tn} = 4.00\text{V}$


In the Ohmic region:

$$V_{ds} = (7.8\text{m}\Omega)(78\text{A}) = 0.608\text{V}$$

$$I_{ds} = k_n \left( V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$

$$78\text{A} = k_n \left( 10 - 4 - \frac{0.608}{2} \right) 0.608$$
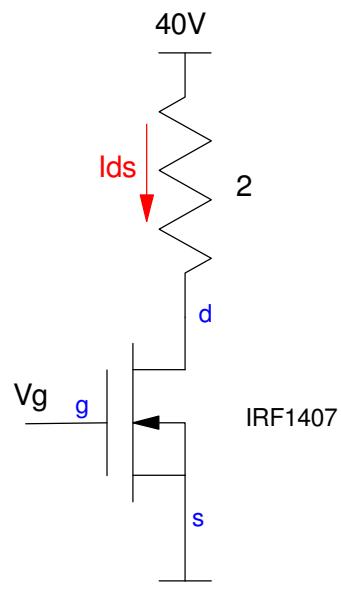
$$k_n = 22.509 \frac{\text{A}}{\text{V}^2}$$



2) Determine the voltages and currents for the following circuit when  $V_g = 5V$

Assume Ohmic:

$$I_{ds} = k_n \left( V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$

$$I_{ds} = 22.509 \left( 5 - 4 - \frac{V_{ds}}{2} \right) V_{ds}$$

$$V_{ds} + 2I_{ds} = 40$$

no solution.

Assume saturated

$$I_{ds} = \frac{k_n}{2} (V_{gs} - V_{th})^2$$

$$I_{ds} = \frac{22.509}{2} (5 - 4)^2$$


$$I_{ds} = 11.255A$$

$$V_{ds} = 40 - 2I_{ds}$$

$$V_{ds} = 17.491V$$

Check

$$V_{ds} > V_{gs} - V_{th}$$

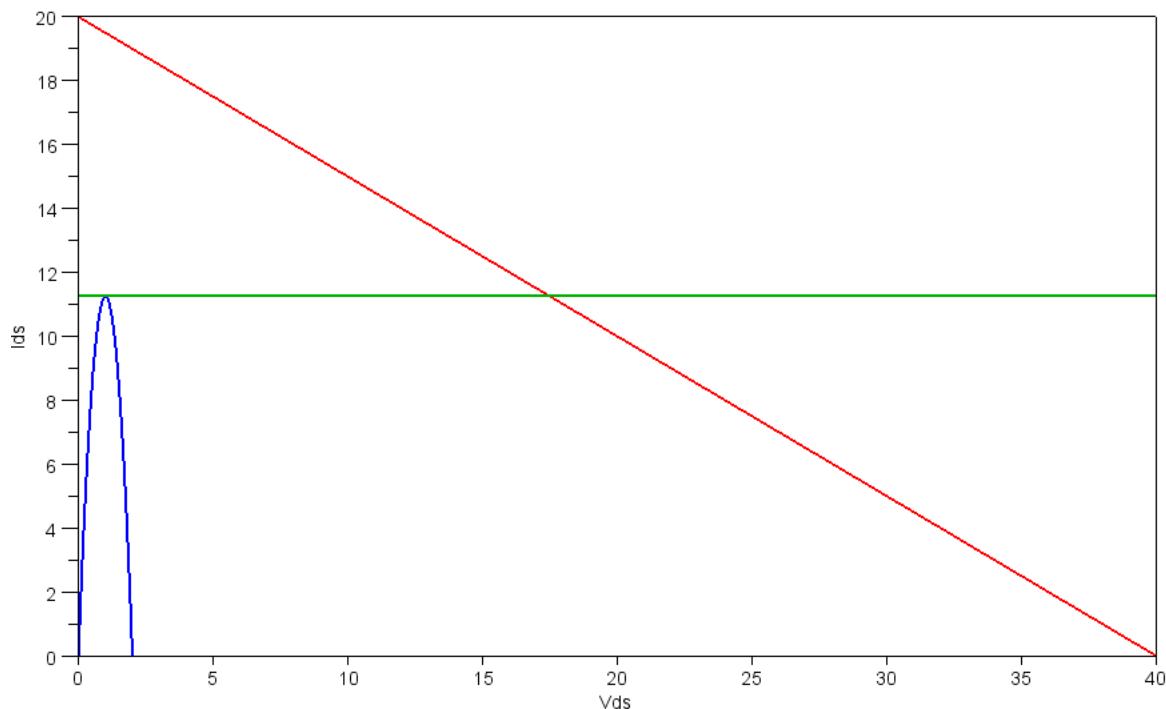


Load Line (red), Ohmic Model (blue), and Saturated Model (green)

matlab code:

```
Vds = [0:0.01:40]';  
I1 = 22.509*(5-4-Vds/2).*Vds;  
I2 = (40 - Vds)/2;  
I3 = 0*Vds + max(I1);  
  
plot(Vds,I1,'b',Vds,I2,'r',Vds,I3,'g');  
xlabel('Vds');  
ylabel('Ids');
```

Check your result in CircuitLab

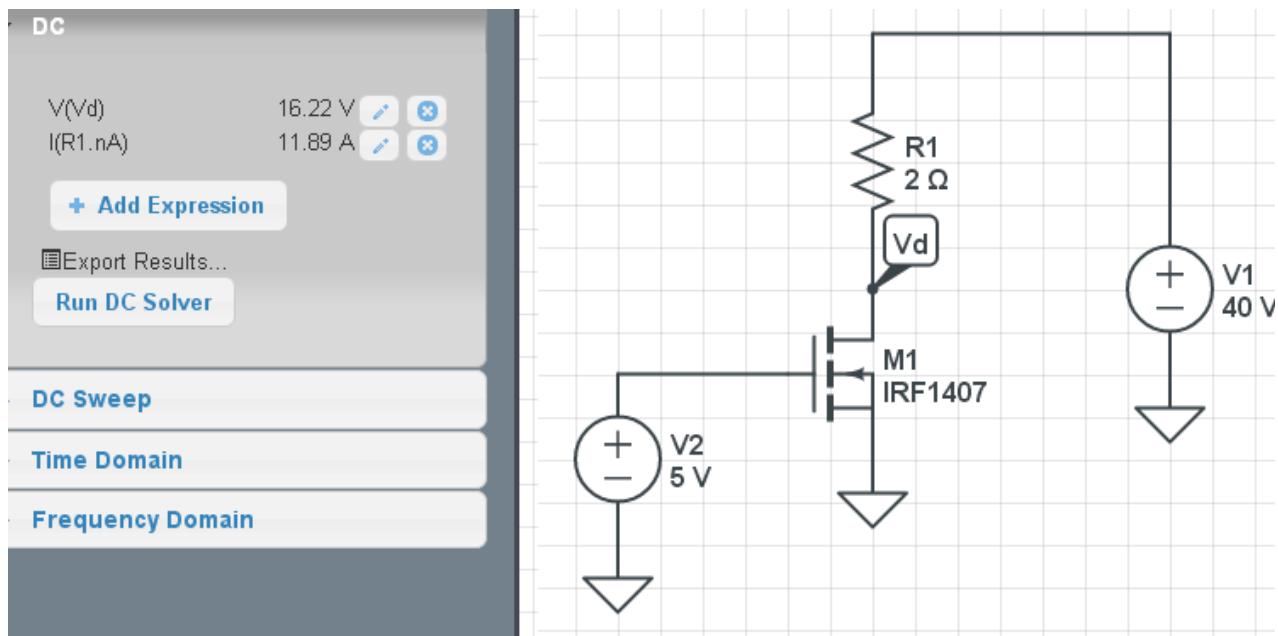

	Vds	Ids
Calculated	17.49V	11.26A
Simulated	16.22V	11.89A

3) Determine the voltages and currents for the following circuit when  $V_g = 10V$

- Check your result in CircuitLab

Assume Ohmic

$$I_{ds} = k_n \left( V_{gs} - 4 - \frac{V_{ds}}{2} \right) V_{ds}$$

$$I_{ds} = 22.509 \left( 10 - 4 - \frac{V_{ds}}{2} \right) V_{ds}$$

$$V_{ds} + 2I_{ds} = 40$$

Solving


$$V_{ds} = 149.4mV$$

$$I_{ds} = 19.925A$$

$$R_{ds} = \frac{V_{ds}}{I_{ds}} = 77.6m\Omega$$


Matlab Code
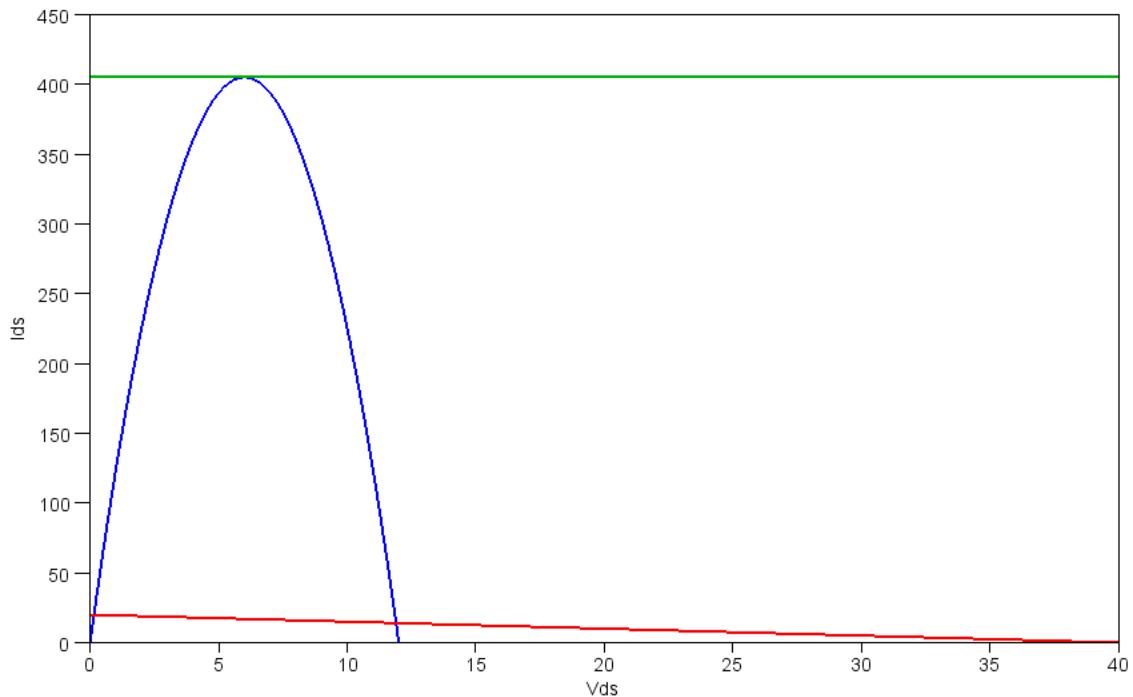
```
Vds = [0:0.01:40]';
I1 = 22.509*(10-4-Vds/2).*Vds;
I2 = (40 - Vds)/2;
I3 = 0*Vds + max(I1);
plot(Vds,I1,'b',Vds,I2,'r',Vds,I3,'g');
xlabel('Vds');
ylabel('Ids');
```



Load Line (red), Ohmic Model (blue), Saturated Model (green)

In CircuitLab

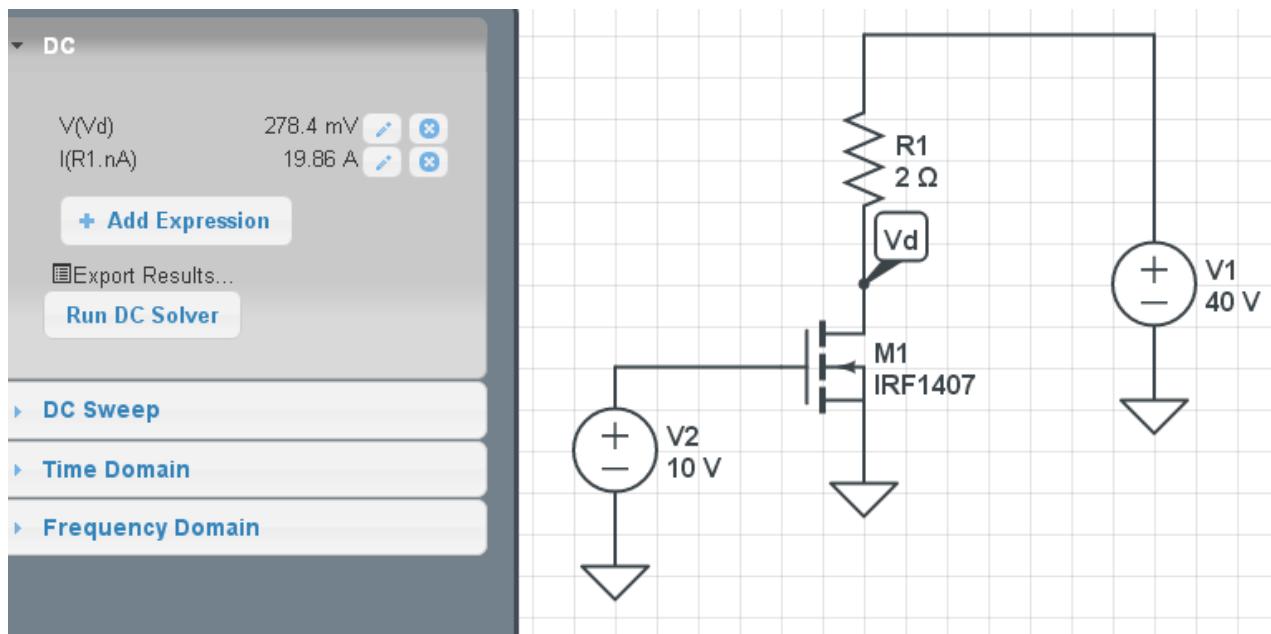


	$V_{ds}$	$I_{ds}$
Calculated	149mV	19.93A
Simulated	278mV	19.86A

## CMOS Logic

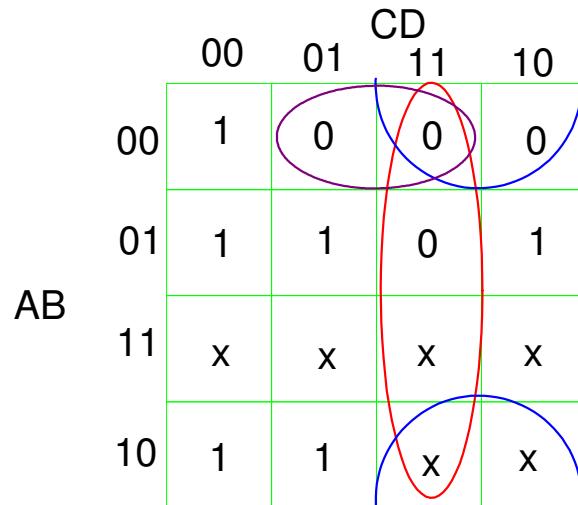4) Design a CMOS gate to implement the function:  $f(A, B, C, D)$

Circle the zeros (also works if you circle the ones)



$$\bar{Y} = CD + \bar{B}C + \bar{A}\bar{B}C$$

$$Y = (\bar{C} + \bar{D})(B + \bar{C})(A + B + \bar{C})$$

