


# ECE 320 - Quiz #1 - Name \_\_\_\_\_

EE 206 Review. September 2, 2021

1) Determine the resistance  $R_{ab}$ .

- Let  $R_0$  be  $1000 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$ .
- For example, May 14th would give  $R = 1514$  Ohms.


$R_0$ $1000 + 100 \cdot \text{mo} + \text{day}$	$R_{ab}$

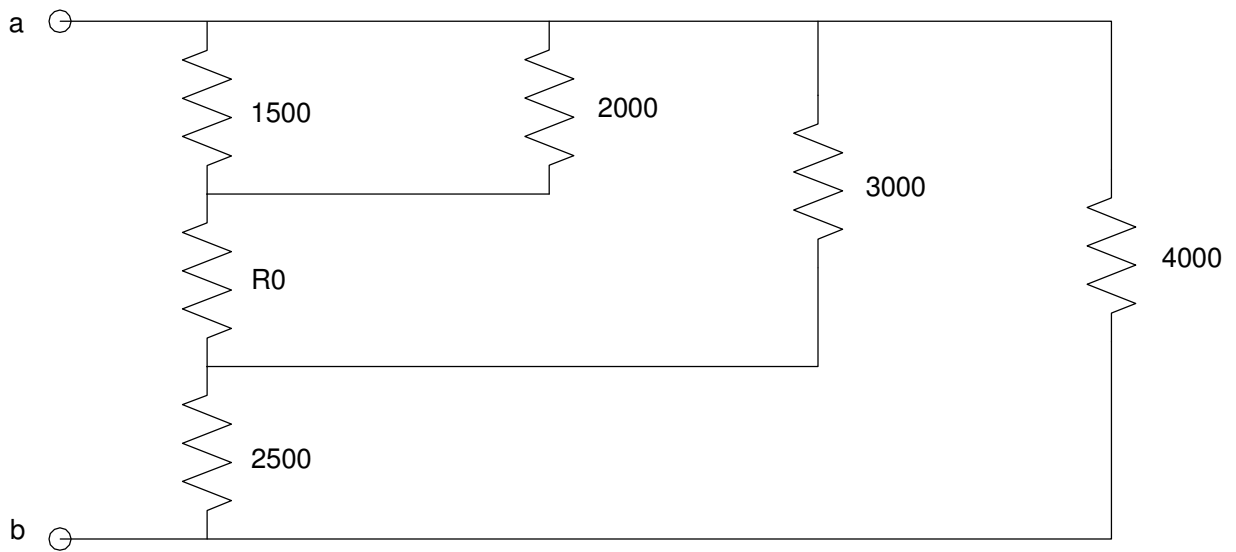

2) Determine the resistance  $R_{ab}$  (note: it will be a complex number)


- Let  $R$  be  $1000 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$ .
- For example, May 14th would give  $R = 1514$  Ohms.

$R_0$ $1000 + 100 \cdot \text{mo} + \text{day}$	$R_{ab}$

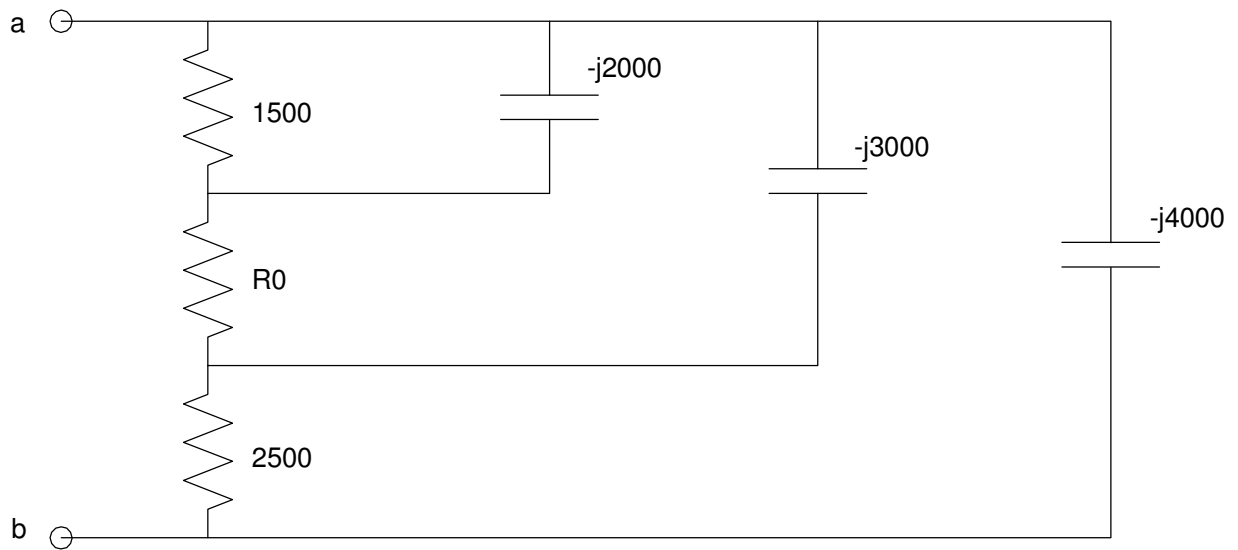

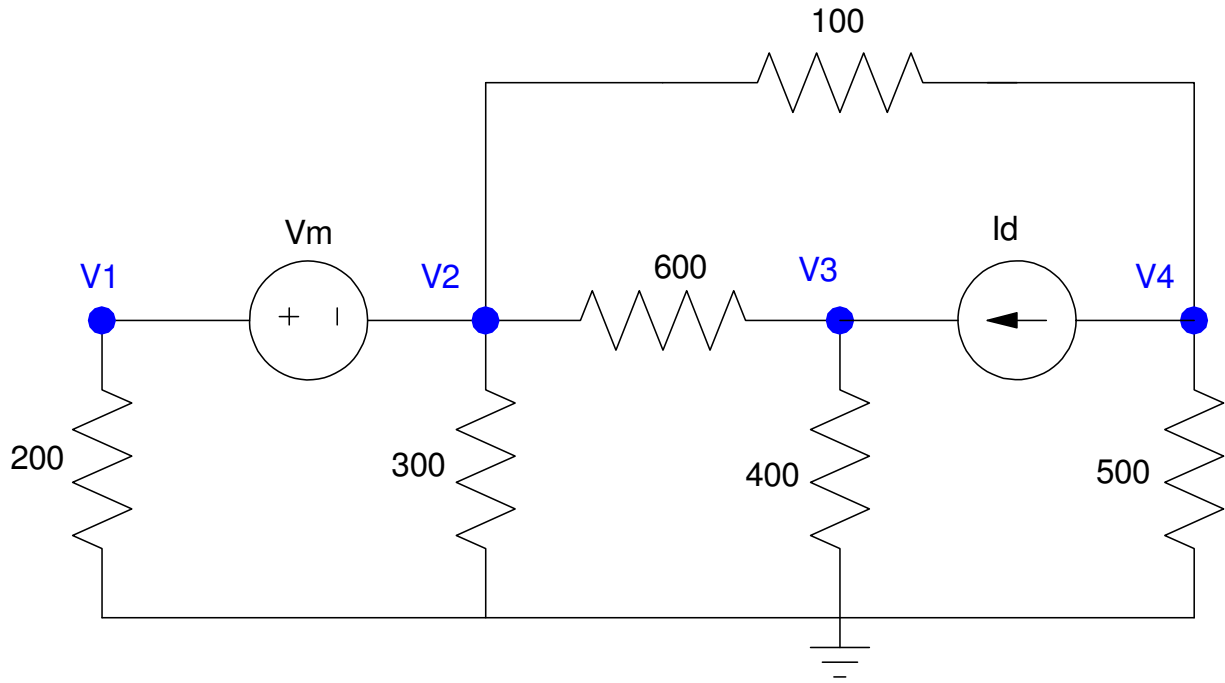3) Voltage Nodes: Write the voltage node equations for the following circuit. Assume


- $V_m$  is your birth month (1..12)
- $I_d$  is your birth date (1..31 mA)



$V_m$ (birth month: 1..12)	$I_d$ (birth date: 1..31) mA

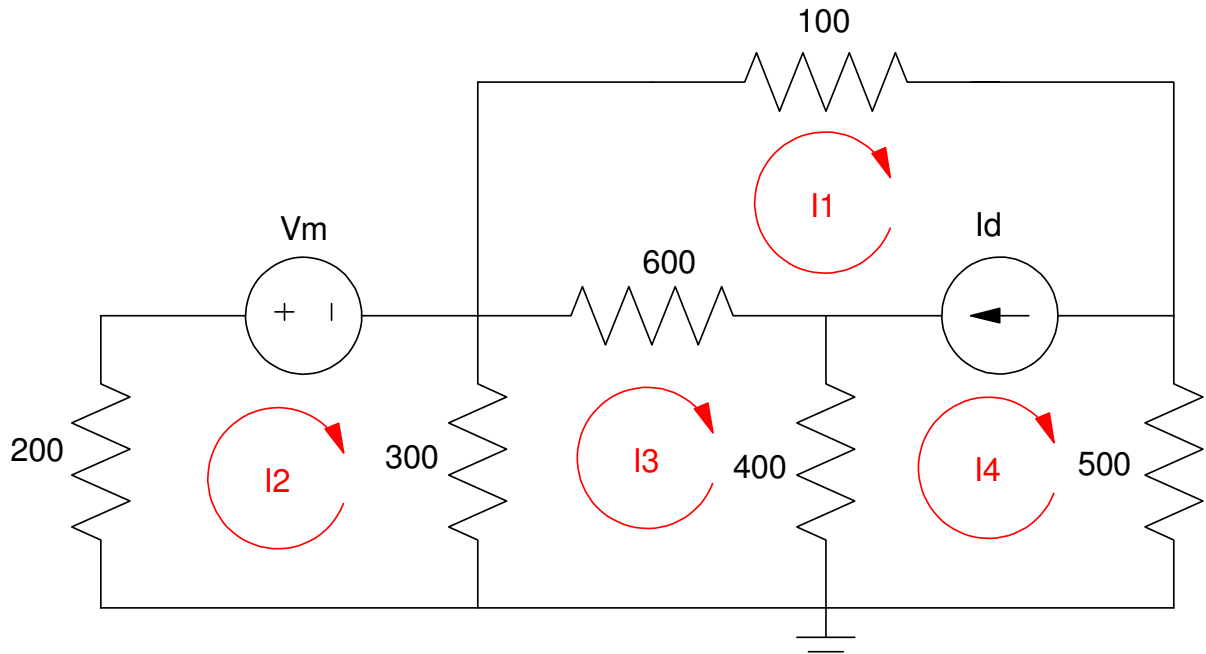4) Current Loops: Write the current loop equations for the following circuit. Assume


- $V_m$  is your birth month (1..12)
- $I_d$  is your birth date (1..31 mA)



$V_m$ (birth month: 1..12)	$I_d$ (birth date: 1..31) mA

5) Signals X and Y are displayed on an oscilloscope. Give the phasor representation for these two voltages

Frequency (Hz)	X		Y	
	Amplitude	Phase	Amplitude	Phase

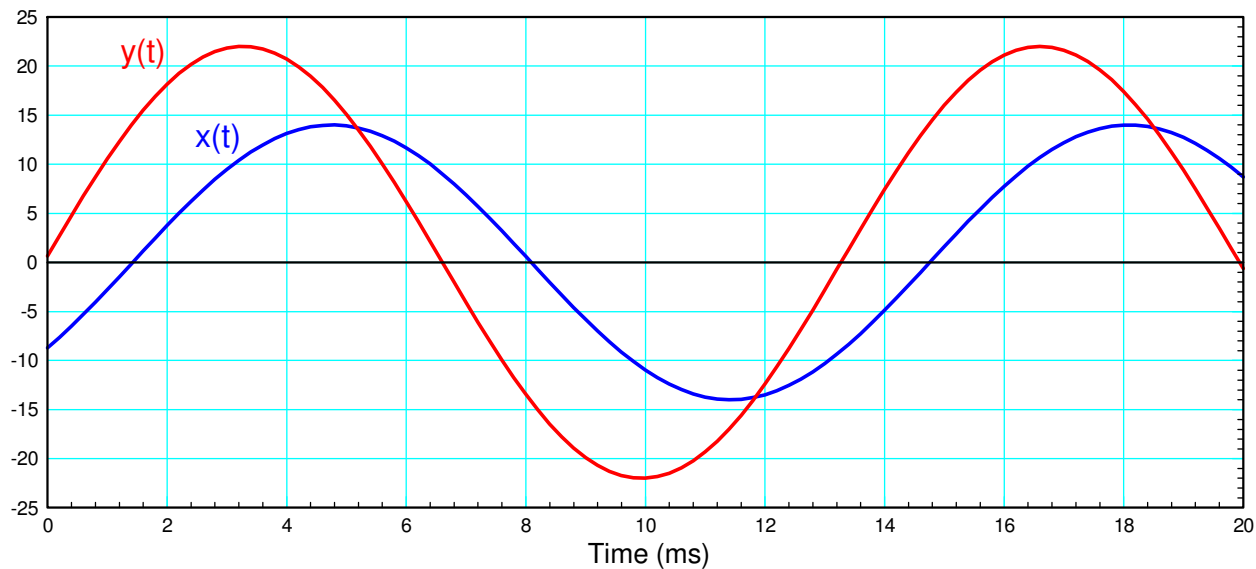

6) Assume  $R_0$  is  $1000 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$ .

- For example, May 14th would give  $R_0 = 1514$  Ohms

Determine  $V_2(t)$  assuming

$$V_1(t) = 10 + 8 \sin(250t)$$

R0 $1000 + 100 \cdot (\text{mo}) + (\text{day})$	V2(t)

