

ECE 320 - Quiz #1c - Name _____

EE 206 Review.


1) Let R be your birthday

$$R = 1000 + (\text{month}) * 100 + (\text{day})$$

For example, May 14th would give $R = 1514$ Ohms

Determine the resistance R_{ab}

R $1000 + 100 * \text{month} + \text{day}$	R_{ab}
1514	2701.161

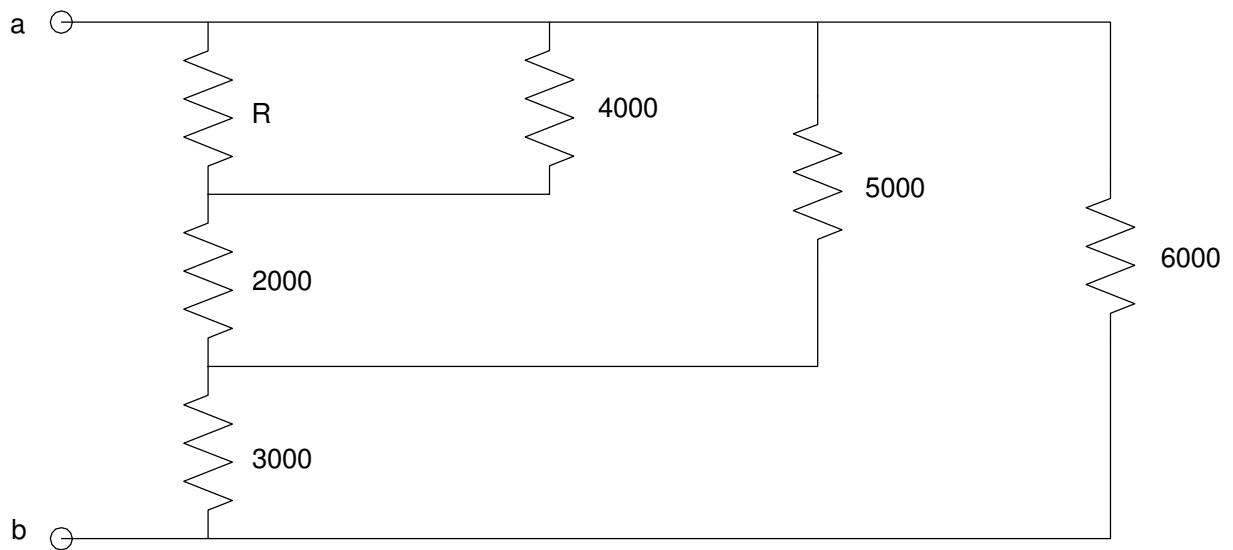

$$1514 \parallel 4000 = 1098.295$$

$$1098.295 + 2000 = 3098.295$$

$$3098.295 \parallel 5000 = 1912.931$$

$$1912.931 + 3000 = 4912.931$$

$$4912.931 \parallel 6000 = 2701.161$$


2) Let R be your birthday

$$R = 1000 + (\text{month}) * 100 + (\text{day})$$

For example, May 14th would give R = 1514 Ohms

Determine the resistance Rab (it will be a complex number)

R 1000 + 100*month + day	Rab
1514	2148.79 - j2710.89

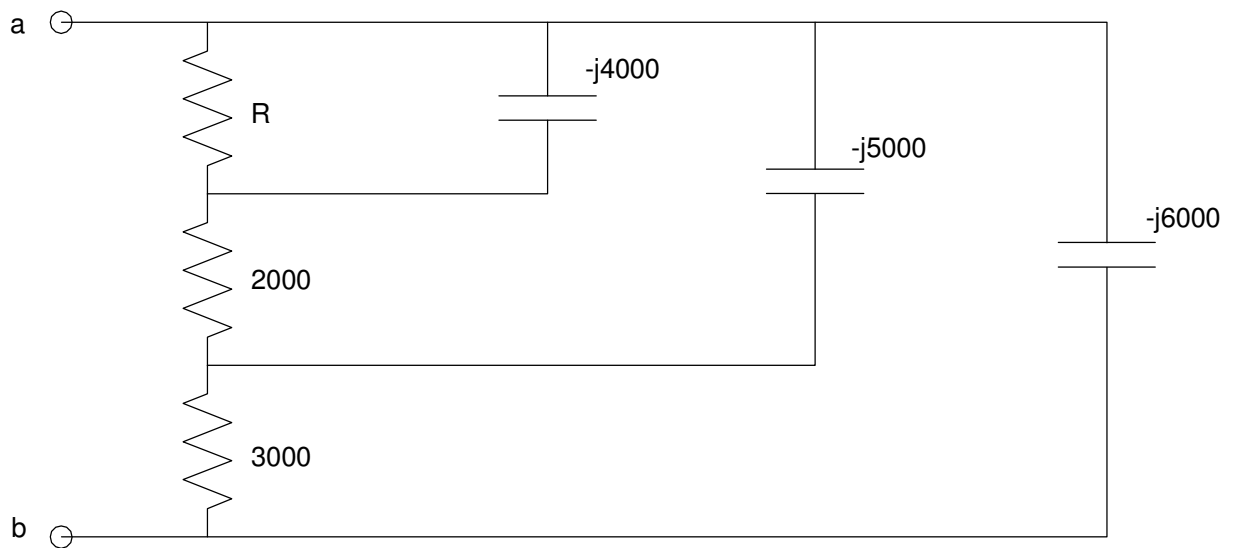

$$1514 \parallel -j4000 = 1324.28 - j501.24$$

$$1324.28 - j501.24 + 2000 = 3324.28 - j501.24$$

$$(3324.28 - j501.24) \parallel (-j5000) = 2011.57 - j1671.12$$

$$(2011.57 - j1671.12) + 3000 = 5011.57 - j1671.12$$


$$(5011.57 - j1671.12) \parallel (-j6000) = 2148.79 - j2710.89$$

3) Voltage Nodes. Let R be your birthday

$$R = 1000 + (\text{month}) * 100 + (\text{day})$$

For example, May 14th would give $R = 1514$ Ohms

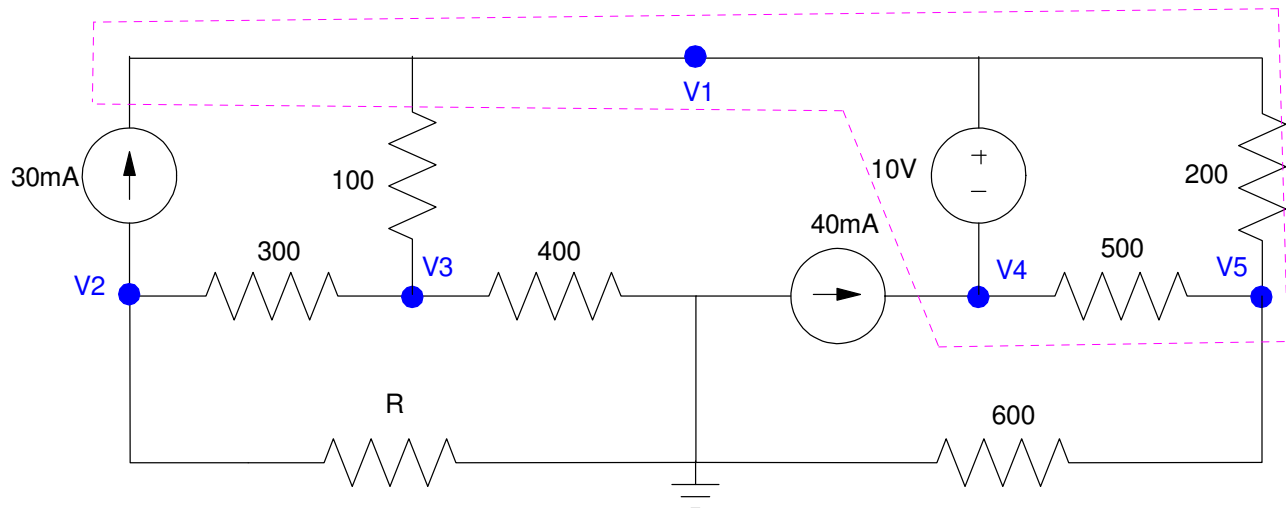Give 5 equations to solve for the 5 unknown voltages. (you don't need to solve)



$$V_1 - V_4 = 0$$

$$30mA + \left(\frac{V_2 - V_3}{300}\right) + \left(\frac{V_2}{1514}\right) = 0$$

$$\left(\frac{V_3 - V_2}{300}\right) + \left(\frac{V_3 - V_1}{100}\right) + \left(\frac{V_3}{400}\right) = 0$$

$$\left(\frac{V_5 - V_4}{500}\right) + \left(\frac{V_5}{600}\right) + \left(\frac{V_5 - V_1}{200}\right) = 0$$


$$-30mA + \left(\frac{V_1 - V_3}{100}\right) - 40mA + \left(\frac{V_5}{600}\right) = 0$$

4) Current Loops. Let R be your birthday

$$R = 1000 + (\text{month}) * 100 + (\text{day})$$

For example, May 14th would give $R = 1514$ Ohms

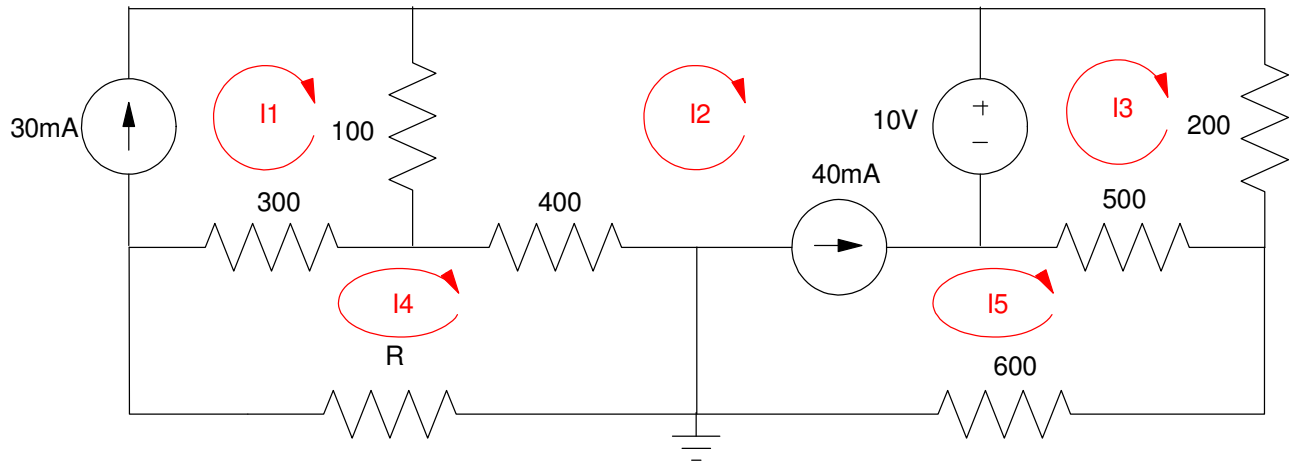Give 5 equations to solve for the 5 unknown currents



$$I_1 = 30mA$$

$$I_5 - I_2 = 40mA$$


$$-10 + 200I_3 + 500(I_3 - I_5) = 0$$

$$300(I_4 - I_1) + 400(I_4 - I_2) + 1514I_4 = 0$$

$$100(I_2 - I_1) + 200I_3 + 600I_5 + 400(I_2 - I_4) = 0$$

5) Signals X and Y are displayed on an oscilloscope. Give the phasor representation for these two voltages

Frequency (Hz)	X		Y	
	Amplitude	Phase	Amplitude	Phase

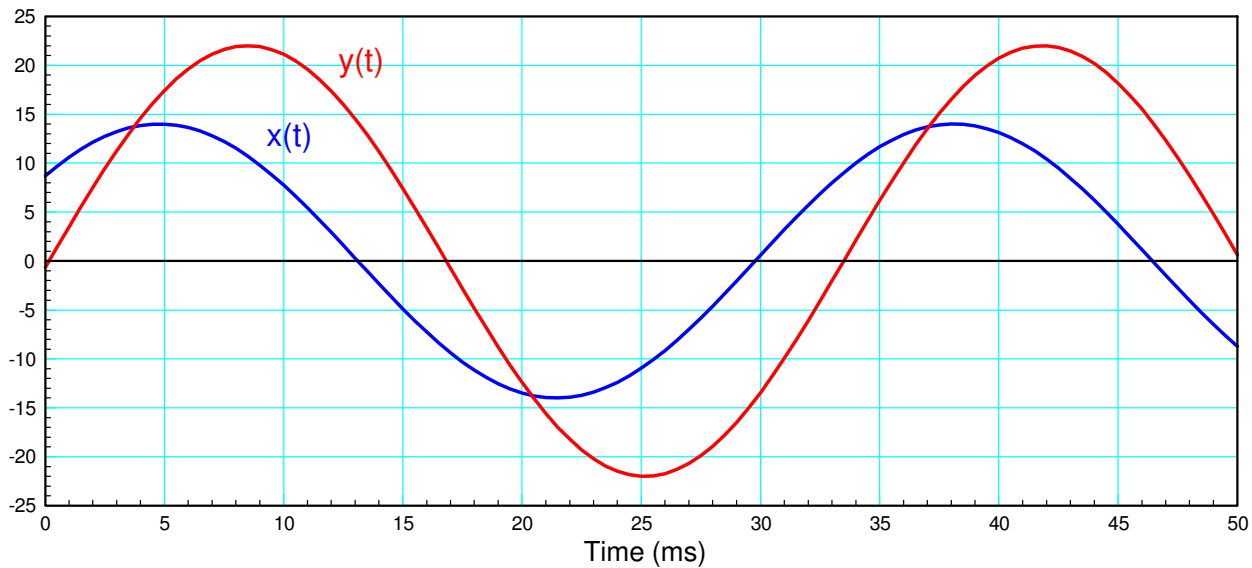

6) Let R be your birthday

$$R = 1000 + (\text{month}) * 100 + (\text{day})$$

For example, May 14th would give $R = 1514$ Ohms

Determine $V_2(t)$ assuming

$$V_1(t) = 14 + 13 \cos(800t) + 12 \sin(800t)$$

R =	
$V_2(t) =$	

