

ECE 320 - Quiz #1c - Name _____

EE 206 Review. Fall 2021


1) Let R be your birthday

$$R = 1000 + (\text{month}) * 100 + (\text{day})$$

For example, May 14th would give $R = 1514$ Ohms

Determine the resistance R_{ab}

R $1000 + 100 * \text{month} + \text{day}$	R_{ab}

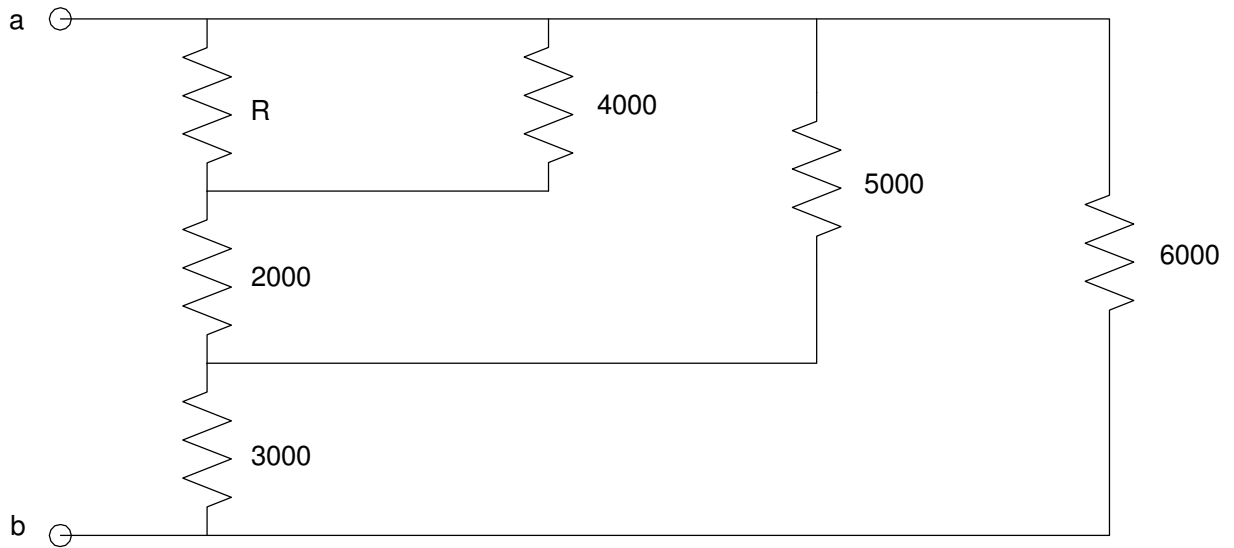


2) Let R be your birthday

$$R = 1000 + (\text{month}) * 100 + (\text{day})$$

For example, May 14th would give $R = 1514$ Ohms

Determine the resistace Rab (it will be a complex number)

R $1000 + 100 * \text{month} + \text{day}$	Rab

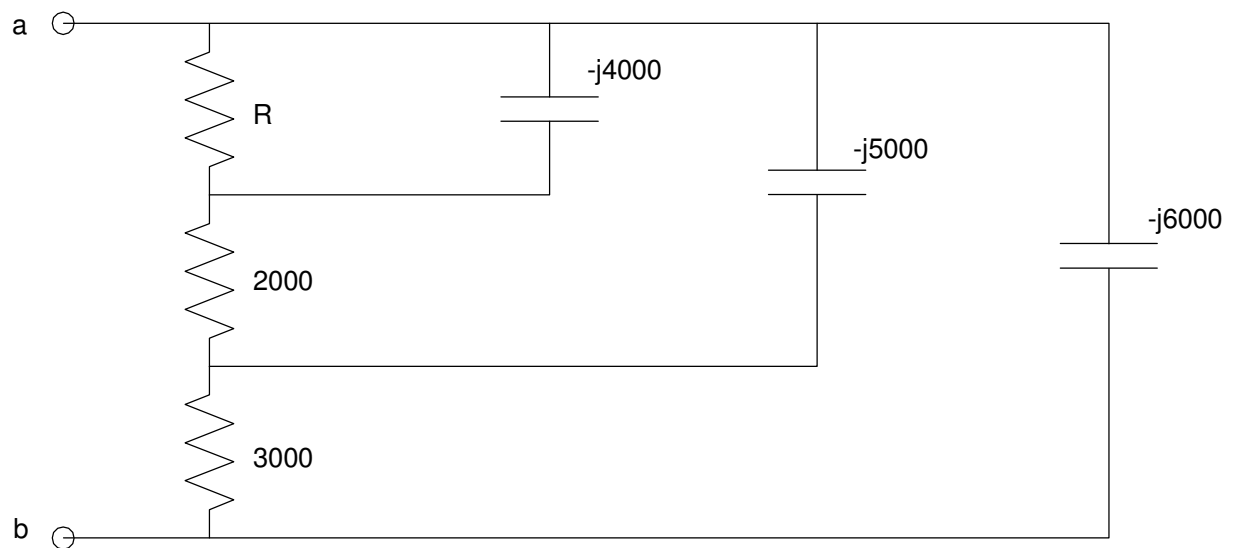


3) Voltage Nodes. Let R be your birthday

$$R = 1000 + (\text{month}) * 100 + (\text{day})$$

For example, May 14th would give $R = 1514$ Ohms

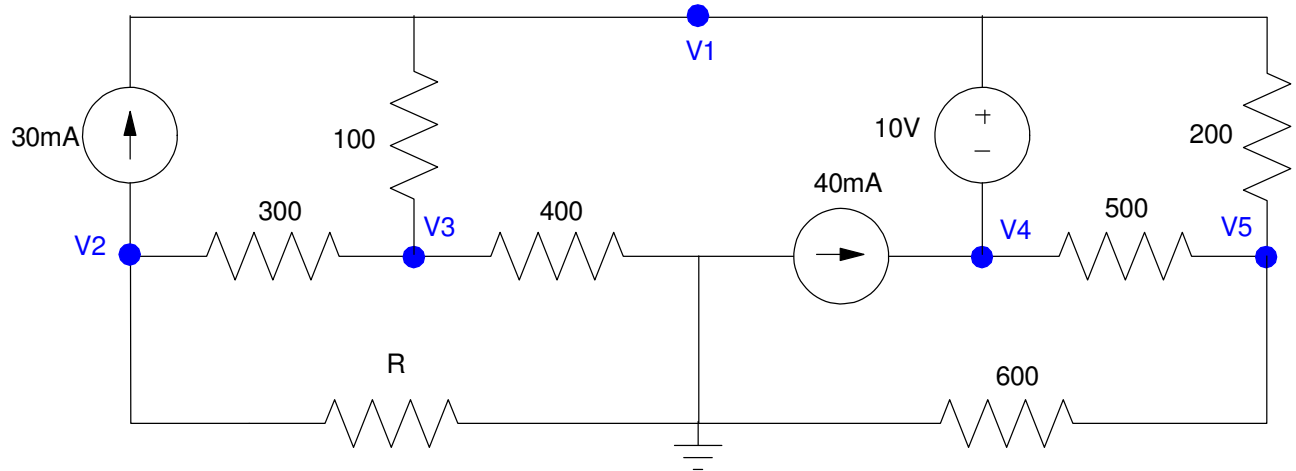Give 5 equations to solve for the 5 unknown voltages. (you don't need to solve)




4) Current Loops. Let R be your birthday

$$R = 1000 + (\text{month}) * 100 + (\text{day})$$


For example, May 14th would give $R = 1514$ Ohms

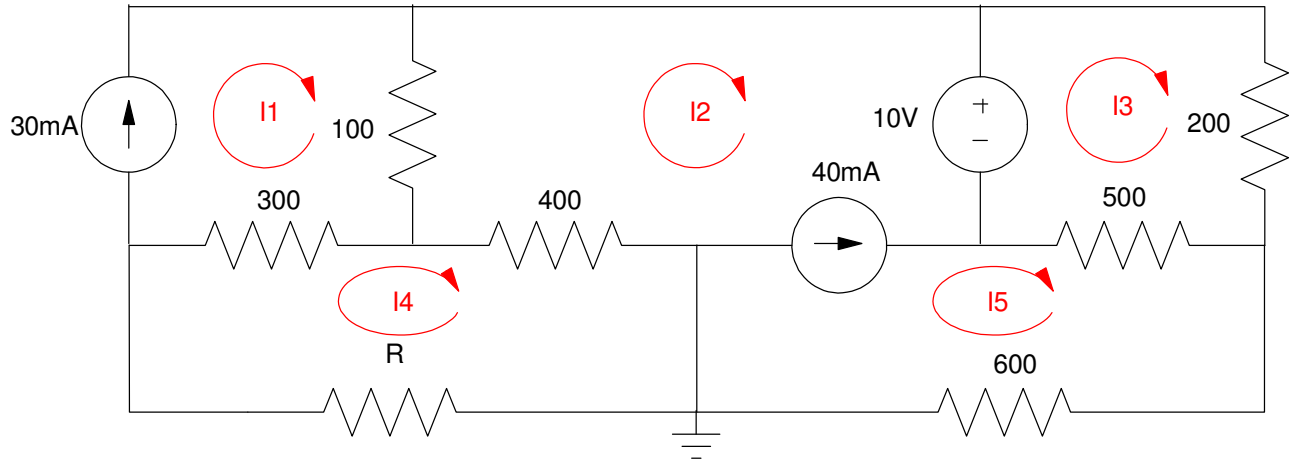Give 5 equations to solve for the 5 unknown currents



5) Signals X and Y are displayed on an oscilloscope. Give the phasor representation for these two voltages

Frequency (Hz)	X		Y	
	Amplitude	Phase	Amplitude	Phase

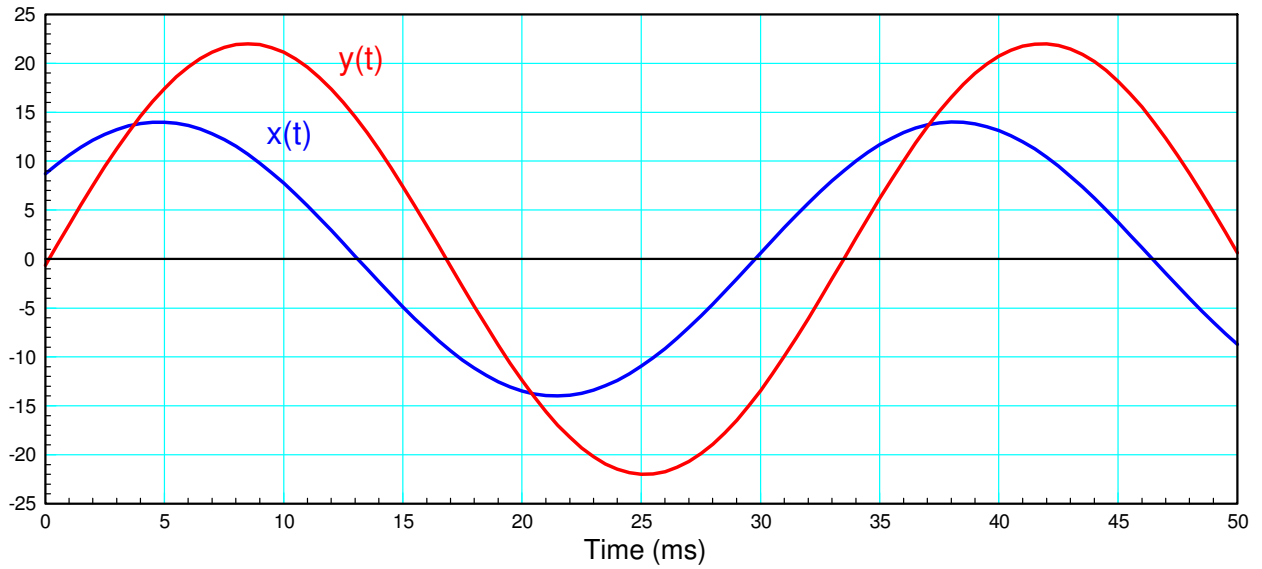

6) Let R be your birthday

$$R = 1000 + (\text{month}) * 100 + (\text{day})$$

For example, May 14th would give $R = 1514$ Ohms

Determine $V_2(t)$ assuming

$$V_1(t) = 14 + 13 \cos(800t) + 12 \sin(800t)$$

R =	
$V_2(t) =$	

