

ECE 320 - Quiz #2 - Name _____

Semiconductors, pn Junction, ideal diodes - Fall 2021

1a) When a silicon diode conducts current p to n, there is about a 0.7V drop across the diode. What causes this voltage drop?

At the pn junction

- *holes on the p-side diffuse to the n-side*
- *electrons on the n-side diffuse to the p-side*

This creates a depletion zone and a potential energy barrier (about 0.7V for silicon diodes). Any electron that crosses the pn junction has to expend 0.7V to overcome this.

1b) What are holes and electrons?

Electrons: We're not really certain. Current thought is that electrons are fundamental particles that can't be broken down into smaller parts (quarks).

Electrons are negative charged particles that surround the nucleus of an atom and are responsible for forming covalent bonds and for conducting charge (carrying current) in the conduction bands of a material (metals, n-type silicon).

Holes are a missing electron in a covalent bond. This can be caused by doping with Boron or from a thermal electron escaping its covalent bond, leaving a hole.


2) Thermistors: Assume the VI characteristics of a thermistor are

$$R_T = 1000 \exp\left(\frac{4200}{T+273} - \frac{4200}{298}\right) \Omega$$

where T is the temperature in degrees C. Determine R_T and the temperature if $V_1 = 2.2V$

Let R be $1000 + (\text{your birth month}) * 100 + \text{your birthday}$. For example, March 14th would give $R = 1514$ Ohms.

R 1000 + 100*Month + Day	R_T (Ohms) Thermistor	Temperature (C)
1514	427 Ohms varies with R	44.15 C varies with R_T

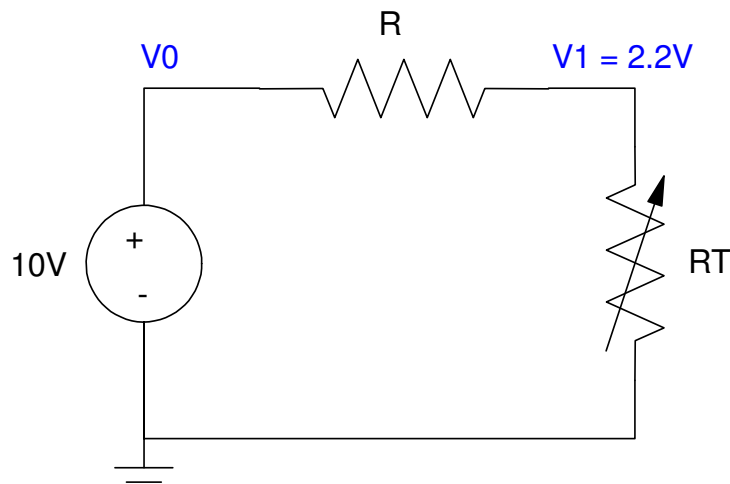

$$V_1 = \left(\frac{R_T}{R_T + 1514}\right) 10V$$

$$R_T = \left(\frac{V_1}{10 - V_1}\right) 1514 = 427.026\Omega$$

From



$$R_T = 1000 \exp\left(\frac{4200}{T+273} - \frac{4200}{298}\right) \Omega = 427.026\Omega$$

$$T = 44.148^\circ C$$

3) Load Lines: The VI characteristic for a diode is show on the graph below. Draw the load line for the following circuit and from the graph, determine Vd and Id

- Let R be 1000 + 100*(Birth Month) + (Birthday)

R 1000 + 100*Month + Day	Load Line	Vd	Id
1514	x intercept = 10V y intercept = 6.196mA	5.2V	3.0mA

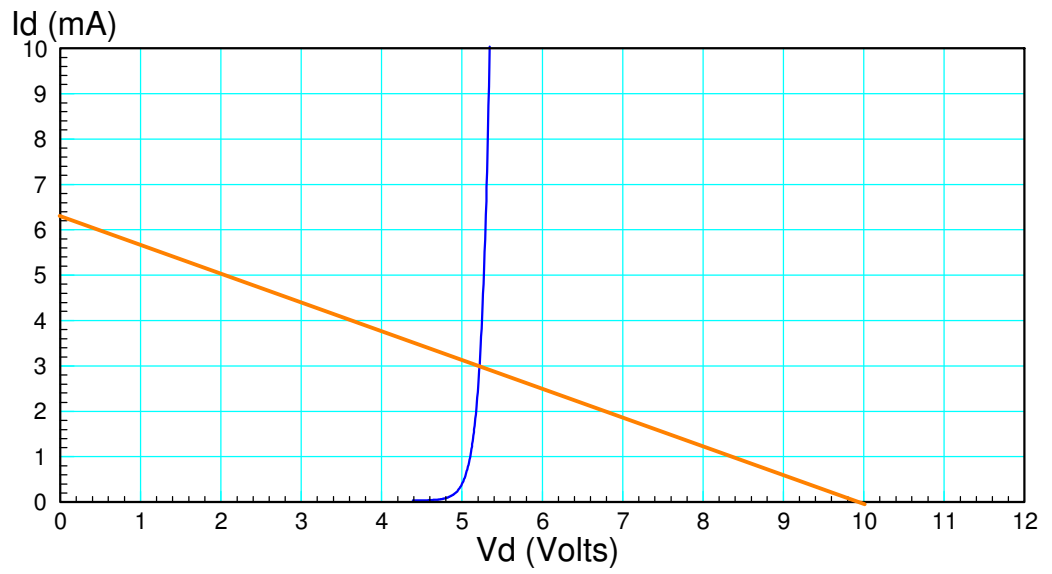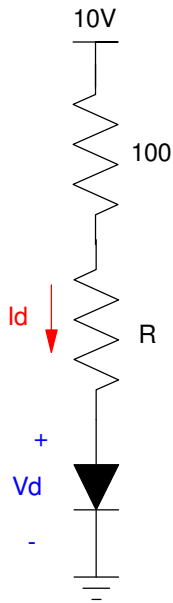

X-intercept = 10V

Y intercept:

$$I_d = \left(\frac{10V}{100\Omega + 1514\Omega} \right) = 6.196mA$$

4) Diodes (nonlinear equations): Assume


- The VI characteristics of a diode are

$$I_d = 10^{-8} \cdot \left(\exp\left(\frac{V_d}{0.052}\right) - 1 \right)$$

- $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$. For example, May 14th gives $R = 1514$ Ohms.

Write 6 equations so solve for $\{V_1, V_2, V_3, I_{d1}, I_{d2}, I_{d3}\}$

- note: don't solve.

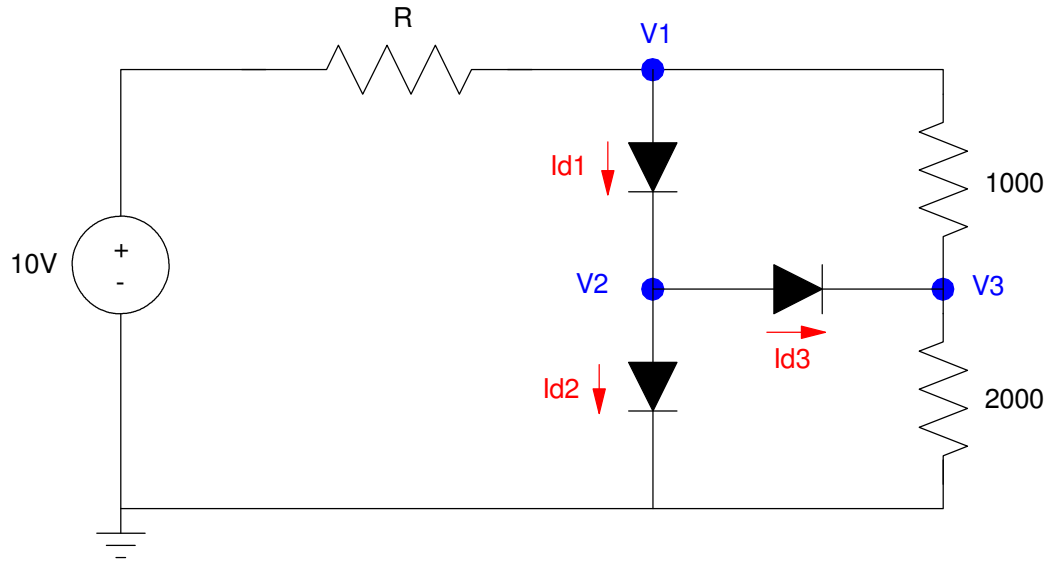

$$I_{d1} = 10^{-8} \cdot \left(\exp\left(\frac{V_1 - V_2}{0.052}\right) - 1 \right)$$

$$I_{d2} = 10^{-8} \cdot \left(\exp\left(\frac{V_2}{0.052}\right) - 1 \right)$$

$$I_{d3} = 10^{-8} \cdot \left(\exp\left(\frac{V_2 - V_3}{0.052}\right) - 1 \right)$$

Voltage node equations

$$\left(\frac{V_1 - 10}{1514}\right) + I_{d1} + \left(\frac{V_1 - V_3}{1000}\right) = 0$$

$$-I_{d1} + I_{d2} + I_{d3} = 0$$


$$\left(\frac{V_3 - V_1}{1000}\right) - I_{d3} + \left(\frac{V_3}{2000}\right) = 0$$

5) Assume

- $R = 1000 + 100 * (\text{your birth month}) + (\text{your birth date})$. For example, May 14th gives $R = 1514$ Ohms.
- Ideal silicon diodes ($V_f = 0.7V$).

Determine $\{V_1, V_2, V_3, I_{d1}, I_{d2}, I_{d3}\}$

V_1	V_2	V_3	I_{d1}	I_{d2}	I_{d3}
1.4V	0.7V	0.933V	5.214mA	5.214mA	0

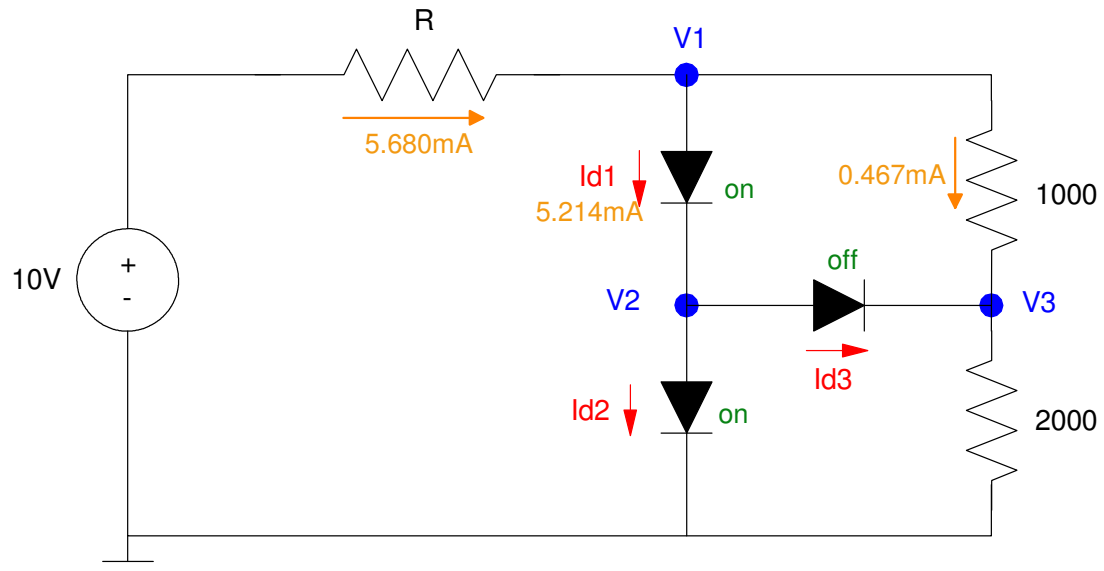

Diode #3 must be off. Otherwise, $V_3 = 0V$

Assume diodes #1 and #2 are on

$$V_2 = 0.7V$$

$$V_1 = 1.4V$$

by voltage division

$$V_3 = \left(\frac{2000}{2000+1000} \right) V_1 = 0.933V$$

Solve for I_{d1}

$$\left(\frac{V_1 - 10}{1514} \right) + I_{d1} + \left(\frac{V_1}{3000} \right) = 0$$

$$I_{d1} = 5.214mA$$


$$I_{d2} = I_{d1}$$

6) Assume

- $R = 1000 + 100 * (\text{your birth month}) + (\text{your birth date})$. For example, May 14th gives $R = 1514$ Ohms.
- Ideal silicon diodes ($V_f = 0.7V$).

Determine $\{V_1, V_2, V_3, I_{d1}, I_{d2}, I_{d3}\}$

V_1	V_2	V_3	I_{d1}	I_{d2}	I_{d3}
2.378V	1.4V	0.7V	0	0.978mA	2.656mA

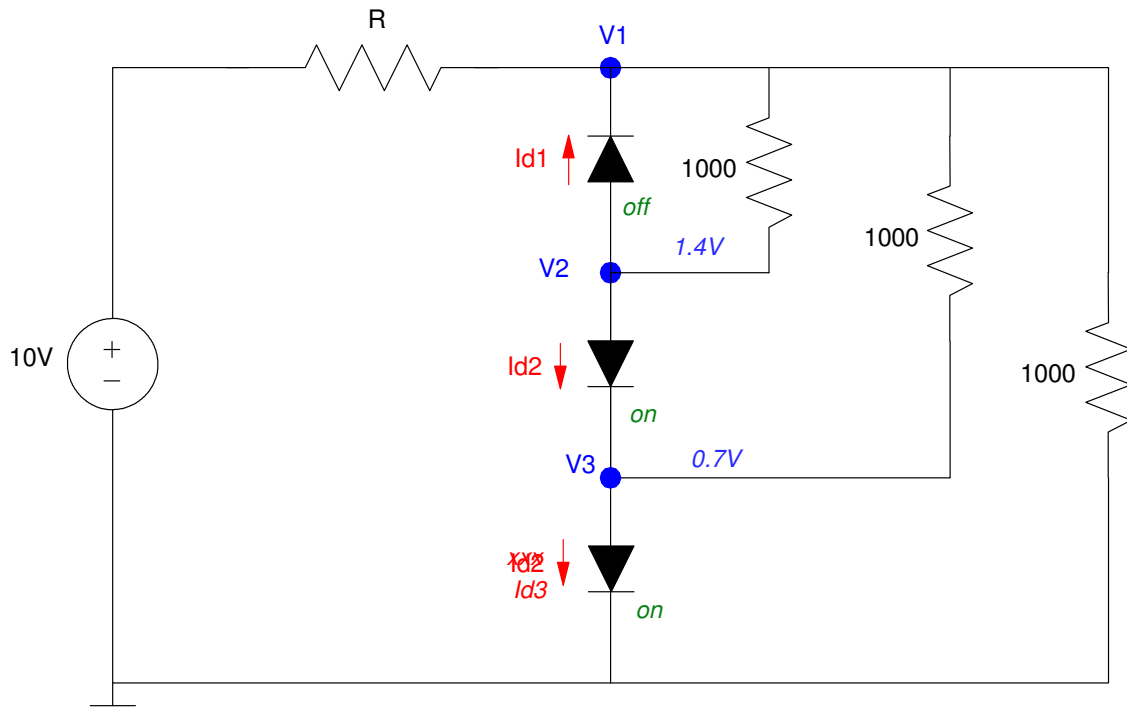

To find V_1 , write the voltage node equation

$$\left(\frac{V_1 - 10}{1514}\right) + \left(\frac{V_1 - 1.4}{1000}\right) + \left(\frac{V_1 - 0.7}{1000}\right) + \left(\frac{V_1}{1000}\right) = 0$$

$$V_1 = 2.378V$$

$$I_{d1} = 0$$

$$I_{d2} = \left(\frac{V_1 - 1.4}{1000}\right) = 0.978mA$$

$$I_{d3} = I_{d2} + \left(\frac{V_1 - 0.7}{1000}\right) = 2.656mA$$