

# ECE 320 - Quiz #2 - Name \_\_\_\_\_

Semiconductors, pn Junction, ideal diodes - Fall 2021

1a) When a silicon diode conducts current p to n, there is about a 0.7V drop across the diode. What causes this voltage drop?

1b) What are holes and electrons?


2) Thermistors: Assume the VI characteristics of a thermistor are

$$R_T = 1000 \exp\left(\frac{4200}{T+273} - \frac{4200}{298}\right) \Omega$$

where T is the temperature in degrees C. Determine  $R_T$  and the temperature if  $V_1 = 2.2V$

Let R be  $1000 + (\text{your birth month}) * 100 + \text{your birthday}$ . For example, March 14th would give  $R = 1514$  Ohms.



R 1000 + 100*Month + Day	RT (Ohms) Thermistor	Temperature (C)

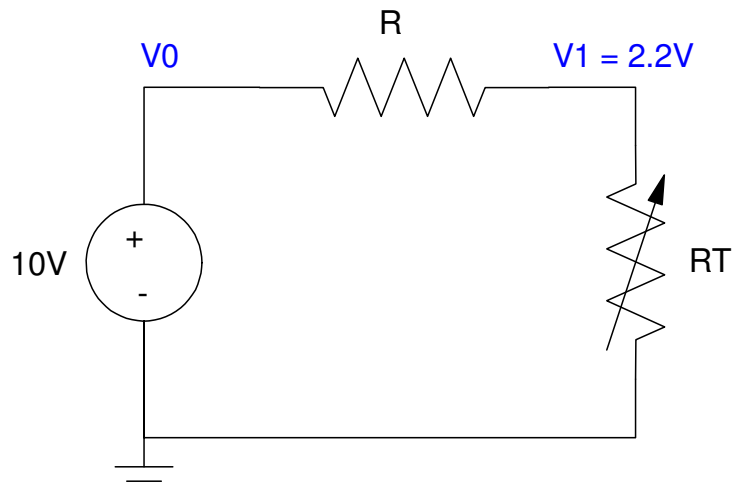

3) Load Lines: The VI characteristic for a diode is show on the graph below. Draw the load line for the following circuit and from the graph, determine  $V_d$  and  $I_d$

- Let  $R$  be  $1000 + 100 * (\text{Birth Month}) + (\text{Birthday})$

R $1000 + 100 * \text{Month} + \text{Day}$	Load Line	$V_d$	$I_d$
	show on graph		

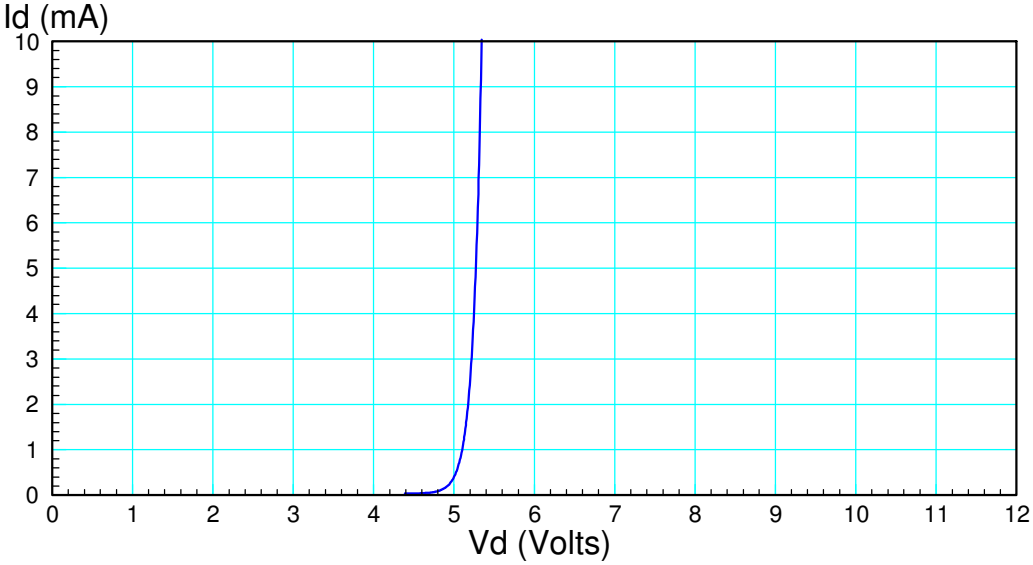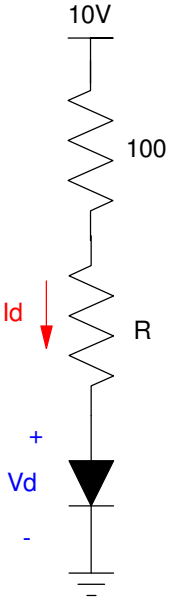

4) Diodes (nonlinear equations): Assume


- The VI characteristics of a diode are

$$I_d = 10^{-8} \cdot \left( \exp\left(\frac{V_d}{0.052}\right) - 1 \right)$$

- $R = 1000 + 100 * (\text{your birth month}) + (\text{your birth date})$ . For example, May 14th gives  $R = 1514$  Ohms.

Write 6 equations so solve for  $\{V_1, V_2, V_3, I_{d1}, I_{d2}, I_{d3}\}$

- note: don't solve.

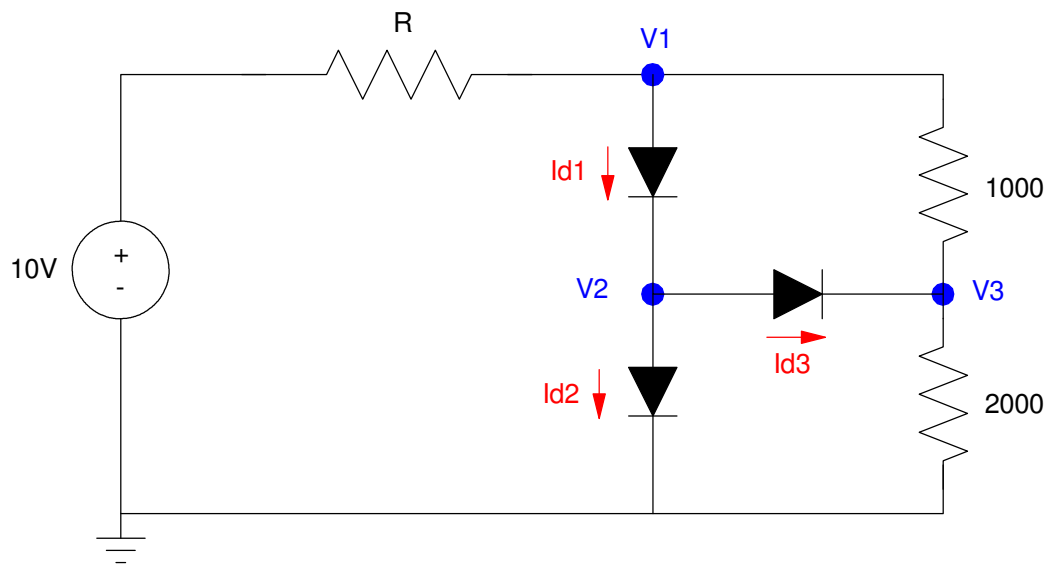


5) Assume

- $R = 1000 + 100 * (\text{your birth month}) + (\text{your birth date})$ . For example, May 14th gives  $R = 1514$  Ohms.
- Ideal silicon diodes ( $V_f = 0.7V$ ).

Determine  $\{V_1, V_2, V_3, I_{d1}, I_{d2}, I_{d3}\}$

V1	V2	V3	I <sub>d1</sub>	I <sub>d2</sub>	I <sub>d3</sub>

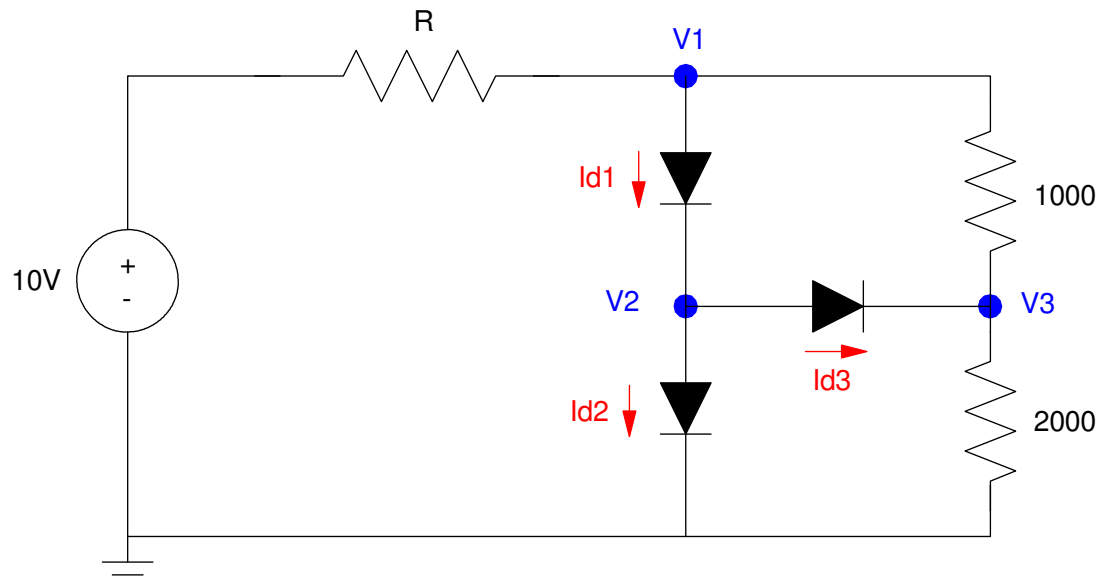

6) Assume

- $R = 1000 + 100 * (\text{your birth month}) + (\text{your birth date})$ . For example, May 14th gives  $R = 1514$  Ohms.
- Ideal silicon diodes ( $V_f = 0.7V$ ).

Determine  $\{V_1, V_2, V_3, I_{d1}, I_{d2}, I_{d3}\}$

V1	V2	V3	I <sub>d1</sub>	I <sub>d2</sub>	I <sub>d3</sub>

