


ECE 320 - Quiz #3 - Name _____

Ideal Diodes, LEDs, AC to DC Converters - Fall 2021

1) Determine the voltages and currents for the following circuit. Assume

- R is $1000 + 100 \cdot (\text{your birth month}) + (\text{your birthday})$. For example, May 14 = 1514 Ohms
- Red LED: $V_f = 1.9V @ 20mA$ 8000 mcd @ 20mA
- Green LED: $V_f = 3.0V @ 20mA$ 8000 mcd @ 20mA
- White LED: $V_f = 5.2V @ 20mA$ 8000 mcd @ 20mA


R 1000 + 100*mo + day	V1	I1 (red LED)	I2 (green LED)	I3 (white LED)

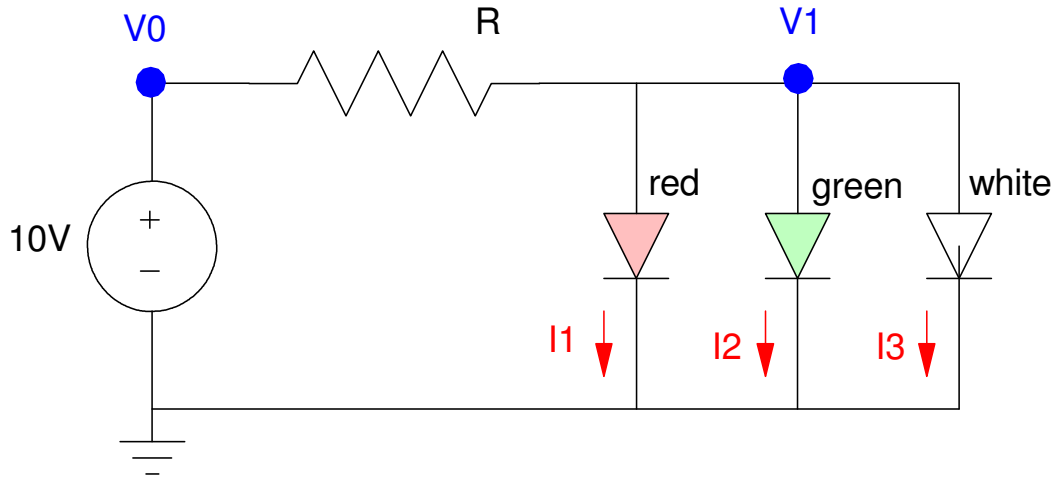

2) Determine the voltages and currents for the following circuit. Assume

- Ideal green LEDs ($V_f = 3.0V$).
- R is $1000 + 100 * (\text{your birth month}) + (\text{your birthday})$. For example, May 14 = 1514 Ohms

V1	V2	V3	Id1	Id2	Id3

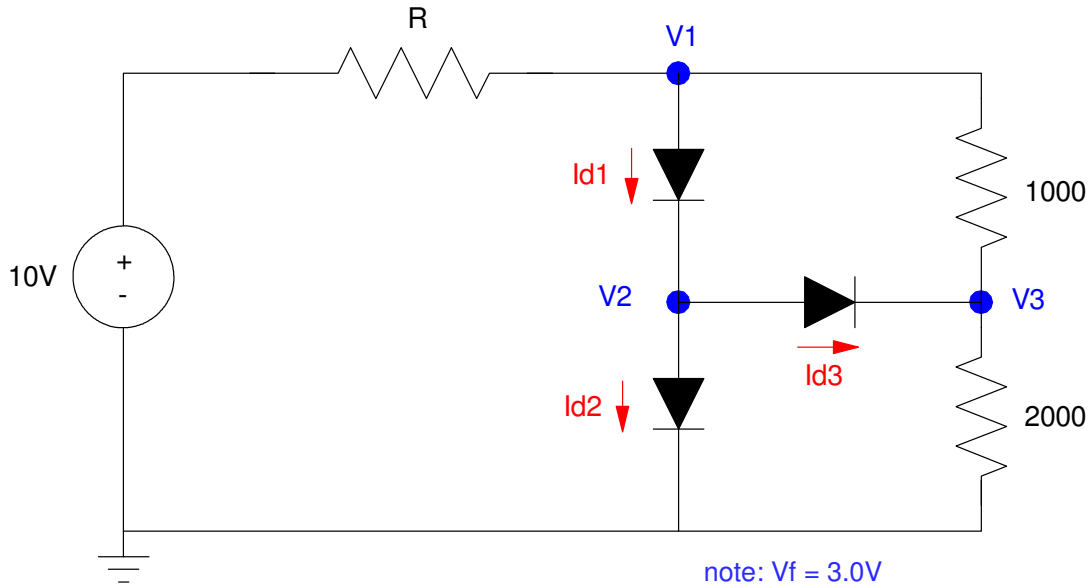


3) A red and green LED are connected to a 10V source. Determine the current and brightness of each LED.

Assume


- R is $1000 + 100 \cdot (\text{your birth month}) + (\text{your birthday})$. For example, May 14 = 1514 Ohms
- Green LED: $V_f = 3.0\text{V}$ @ 20mA , 8000mcd @ 20mA
- White LED: $V_f = 5.2\text{V}$ @ 20mA , 8000mcd @ 20mA

R	Green LED		White LED	
	I_g	mcd(green)	I_w	mcd(white)

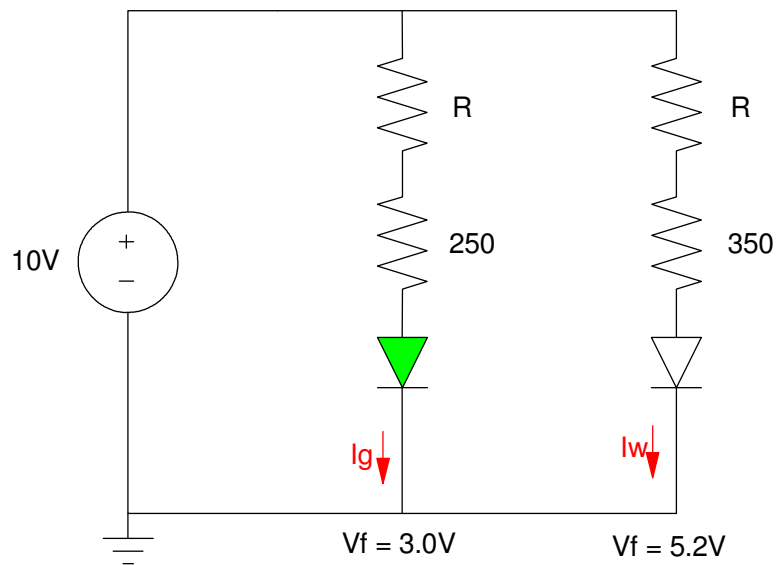

4) The following waveforms are found using CircuitLab for V2 for an AC to DC converter. Determine the following


Frequency (Hz)	V2 (blue waveform)	
	DC (average)	AC (V _{pp})

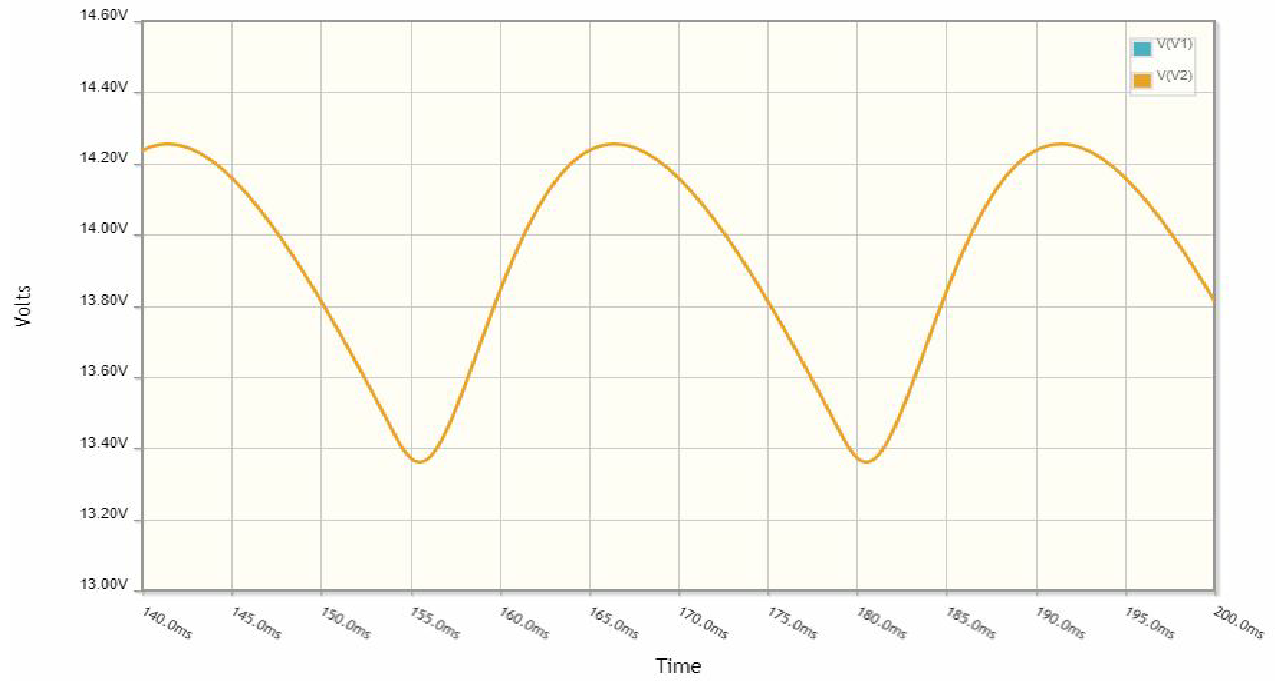

5) Determine the voltages V1 and V2 (both DC and AC). Assume

- Ideal silicon diodes ($V_f = 0.7V$)
- R is $1000 + 100 * (\text{your birth month}) + (\text{your birthday})$. For example, May 14 = 1514 Ohms

V1		V2	
DC (mean(V1))	AC (V1pp)	DC (mean(V2))	AC (V2pp)

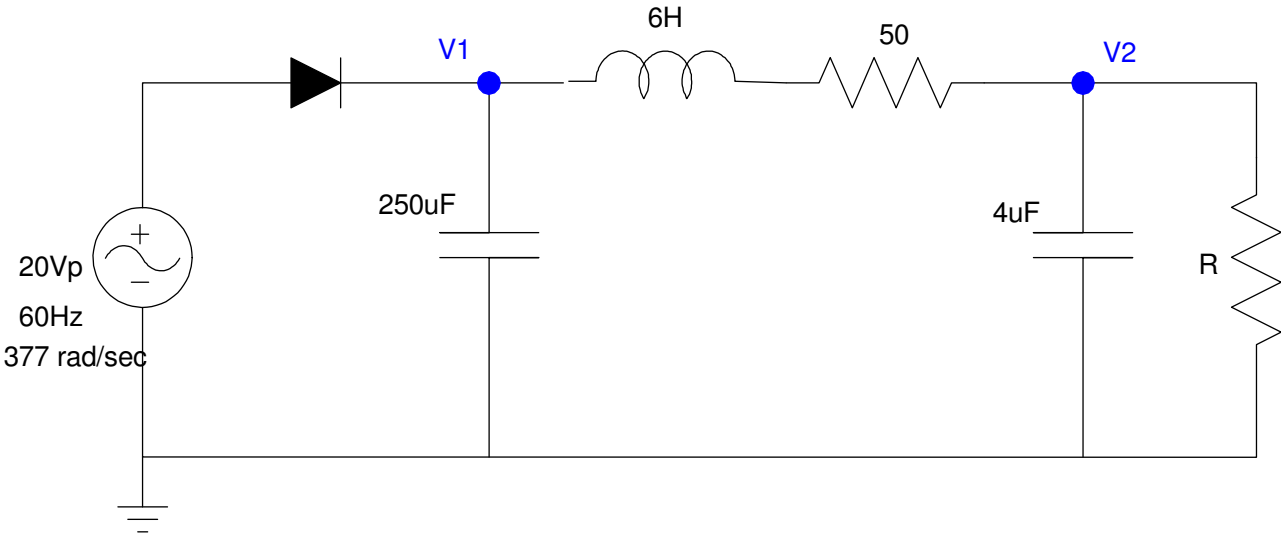

6) Determine C1, and C2 so that

- The ripple at V1 is 3Vpp and
- The ripple at V2 = 500mVpp

Let R be $1000 + 100 \cdot (\text{your birth month}) + (\text{your birthday})$. For example, May 14 = 1514 Ohms)

R	C1	C2

