


ECE 320 - Quiz #4 - Name _____

Max/Min, Clipper, Transistors. Fall 2021

1) Max/Min: Determine the voltages and currents for the following min/max circuit.

- Assume ideal silicon diodes ($V_f = 0.7V$)
- $R = 1000 + 100 * \text{Birth Month} + \text{Birth Day}$. May 14th for example gives $R = 1514$ Ohms


R <small>1000 + 100*Mo + Day</small>	V1	V2	V3	I4	I5
1514	6.30V	7.00V	7.30V	3.30mA	0

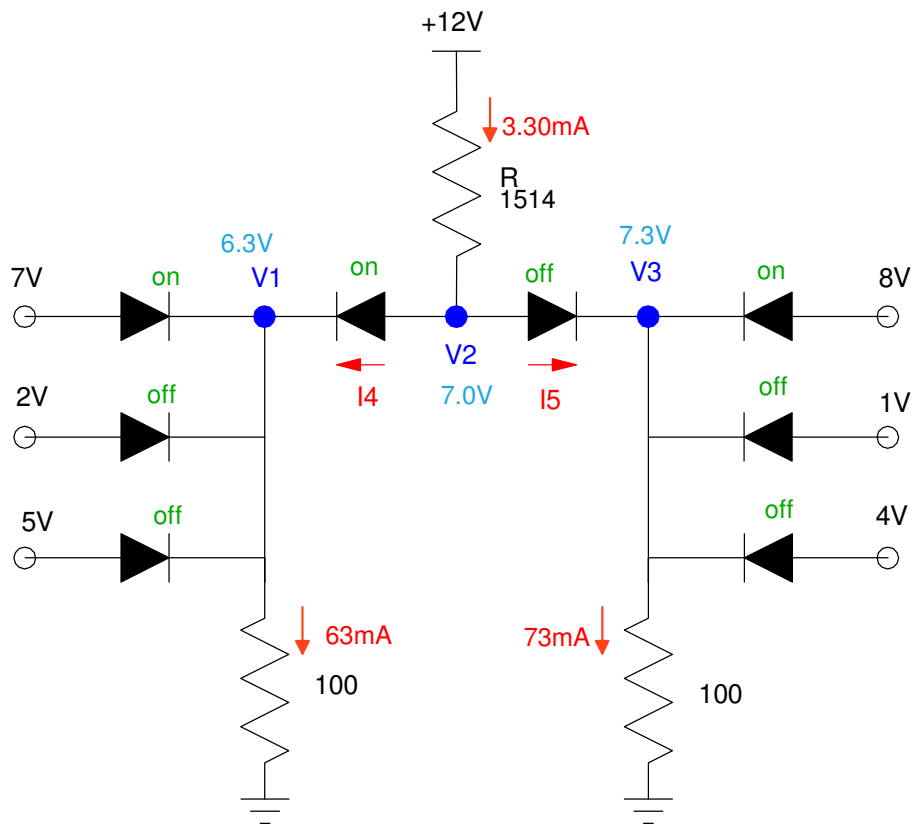

2) Max/Min: Determine the voltages and currents for the following min/max circuit.

- Assume ideal silicon diodes ($V_f = 0.7V$)
- $R = 1000 + 100 * \text{Birth Month} + \text{Birth Day}$. May 14th for example gives $R = 1514$ Ohms



R 1000 + 100*Mo + Day	V1	V2	V3	I4	I5
1514	2.7V	2.0V	1.7V	1.32mA	0

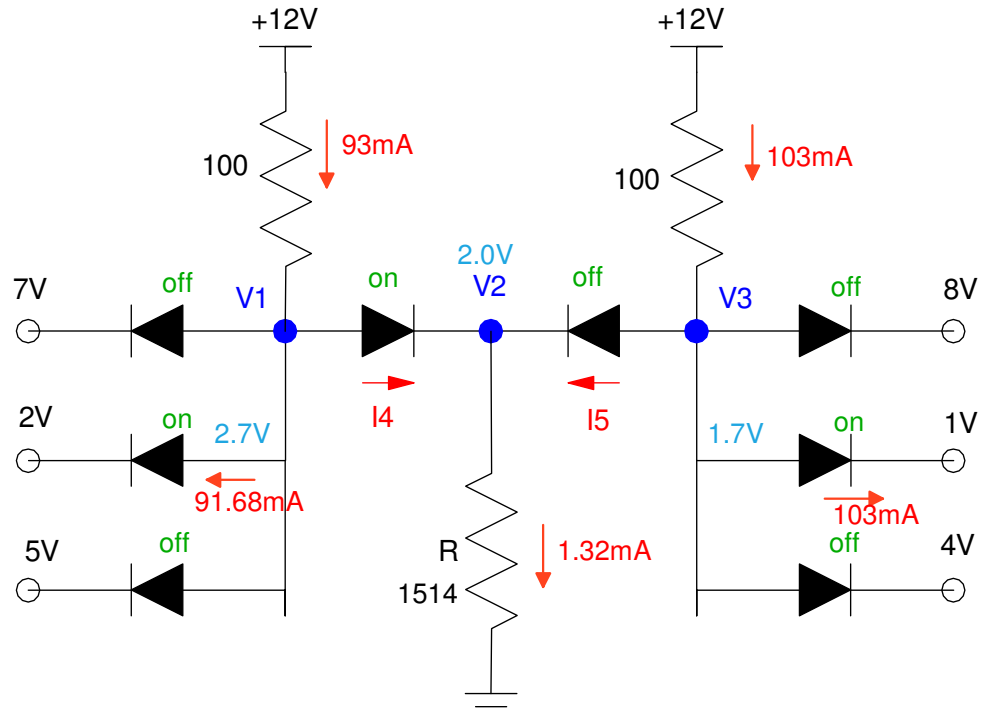

3) Clipper: Determine {R0, R1, R2, Vz1, Vz2} to implement the following function.

- Let R3 be 1000 + 100 * your birth month + your birth day. May 14th would give R = 1514 Ohms.

R3 1000 + 100*Mo + Day	R0	Vz1	R1	Vz2	R2
1514	1500	5V	648.8	8V	363.4

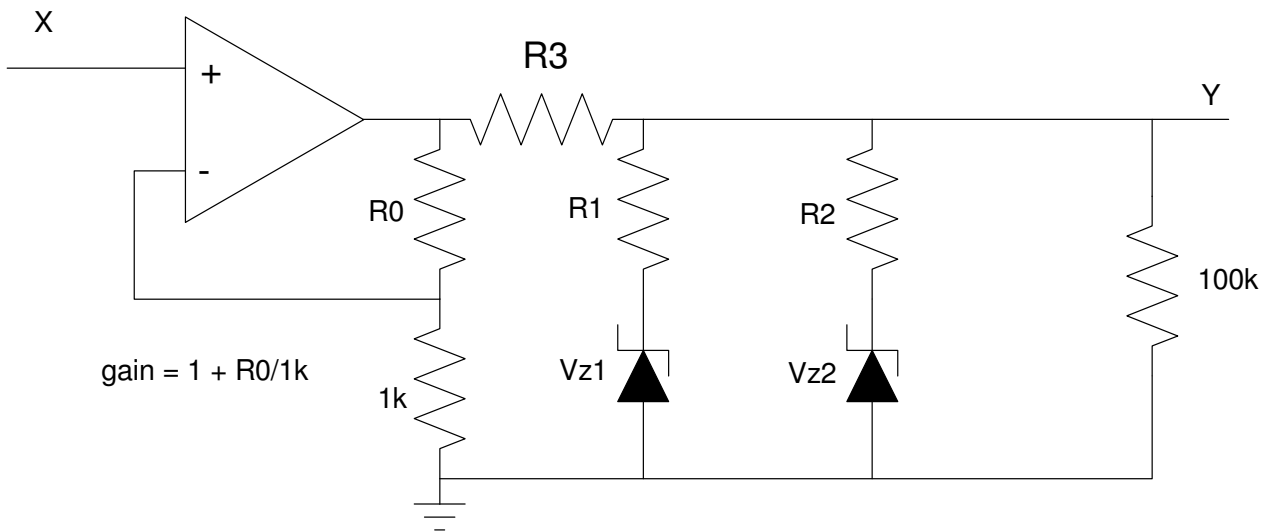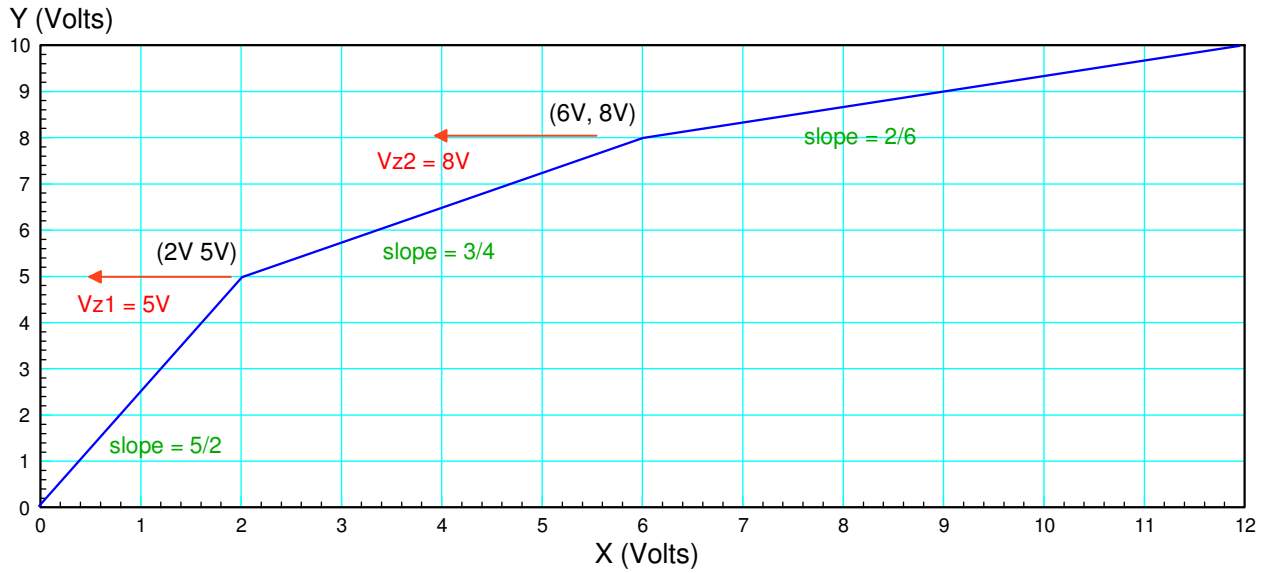


$$\left(\frac{R_1}{R_1+1514}\right)\left(\frac{5}{2}\right) = \frac{3}{4} \quad R_1 = 648.8\Omega$$

$$\left(\frac{R_2}{R_2+1514}\right)\left(\frac{5}{2}\right) = \frac{2}{6} \quad R_2 = 363.4\Omega$$

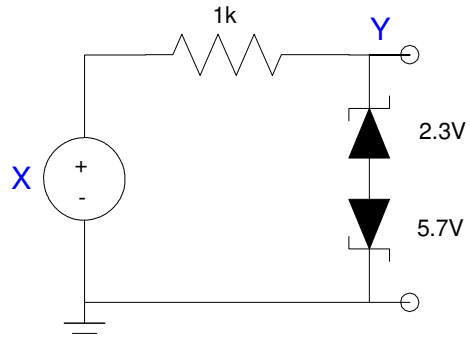4) Clipper: Design a circuit to clip the voltage at +7V and -3V

$$y = \begin{cases} +3V & x > 3 \\ x & -6 < x < 3 \\ -6V & x < -6 \end{cases}$$




5) The VI characteristics for an NPN transistor are shown below

- Draw the load line for the following circuit
- Show on the load line the operating point (V_{ce} , I_c) when $V_{in} = 4V$ & $8V$.

Assume

- $V_{be} = 0.7V$
- $V_{ce} = 0.2V$ when saturated

R 1000 + 100*Mo + Day	Load Line	$V_{in} = 4.0V$	$V_{in} = 8.0V$
1514	x and y intercept or show on graph	V_{ce} and I_c or show on graph	V_{ce} and I_c or show on graph

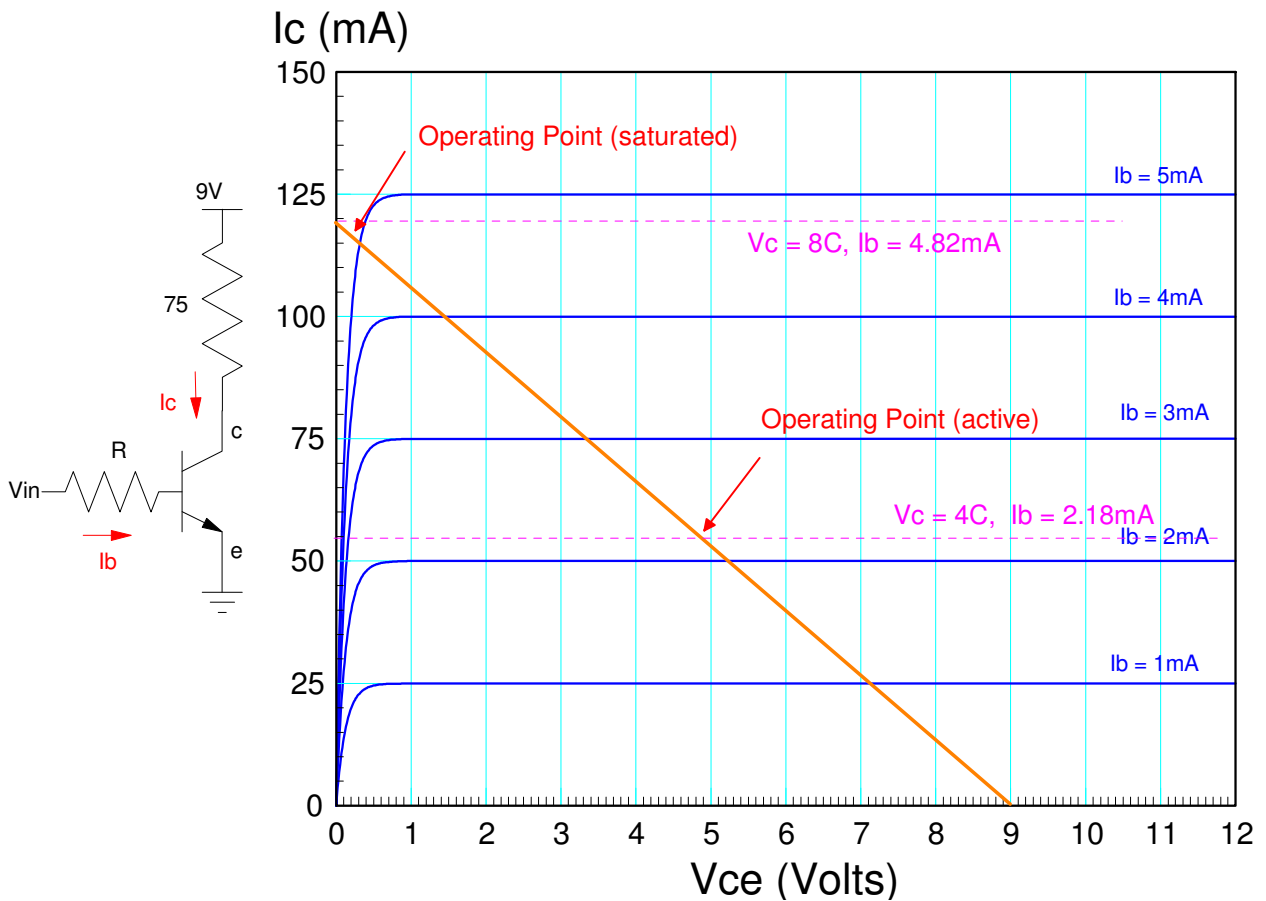

6) The voltages for the following circuit are measured (shown below). From these measurements, determine the following:

R 1000 + 100*Mo + Day	I _b (mA)	I _c (mA)	Current Gain (beta)	Operating Region off / active / saturated
1514	2.8303mA	46.40mA	16.39	active

