

ECE 320 - Quiz 1: Name Solution

January 29, 2015 - Semiconductors, PN Junction, Diode Equation

1) Semiconductors can be p-type, n-type, or intrinsic.

1a) What is meant by the term 'p-type semiconductor'? (4 points)

The majority of charge carriers are holes

Current travels by electrons hopping hole-to-hole (missing electrons in the covalent bonds)

Silicon doped with Boron is how you make p-type silicon (-2 points)

1b) What is meant by the term 'n-type semiconductor'? (4 points)

The majority of charge carriers are electrons

(more accurate): The majority of charge carriers are electrons traveling in the conduction bands

Current travels by electrons flowing in the conduction bands (i.e. not in covalent bonds)

Silicon doped with Phosphorous is how you make n-type silicon (-2 points)

1c) What is meant by the term 'intrinsic semiconductor'? (2 points)


Silicon which is neither p-type nor n-type

The number of holes and electrons are approximately the same

2) Determine the resistance and temperature of the thermistor if the output voltage is 3.14V. Assume the temperature-voltage relationship is as follows where T is the temperature in degrees C

$$R = 1000 \cdot e^{-0.04(T-25)} \Omega$$

R (Ohms)	T (degrees C)
183 Ohms	67.44 C

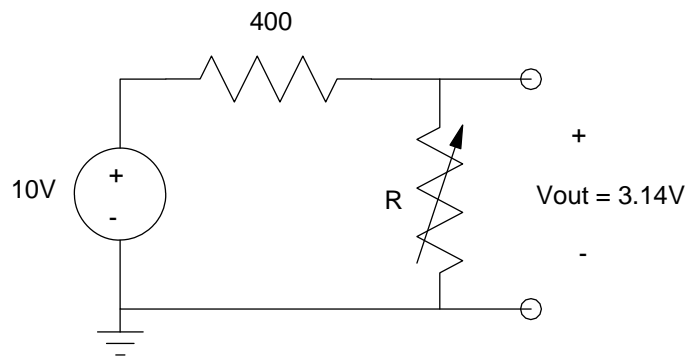

$$V_{out} = \left(\frac{R}{R+400} \right) 10V$$

$$R = \left(\frac{V}{10-V} \right) 400\Omega$$

$$R = 183\Omega$$

$$R = 1000 \cdot e^{-0.04(T-25)} \Omega$$

$$T = 25 - 25 \ln \left(\frac{R}{1000} \right)$$


$$T = 67.44$$

3) Write the voltage node equations at nodes V1 and V2. Assume silicon diodes with

$$I_d = I_{dss}(e^{20V_d} - 1)A$$

$$V_d = 0.05 \ln \left(\frac{I_d}{I_{dss}} + 1 \right) V$$


Node V1 (orange)	$\left(\frac{V_1 - 10}{50} \right) + \left(\frac{V_1}{70} \right) + I_{dss}(e^{20(V_1 - V_2)} - 1) = 0$
Node V2 (blue)	$\left(\frac{V_2 - 10}{60} \right) + \left(\frac{V_2}{40} \right) - I_{dss}(e^{20(V_1 - V_2)} - 1) = 0$

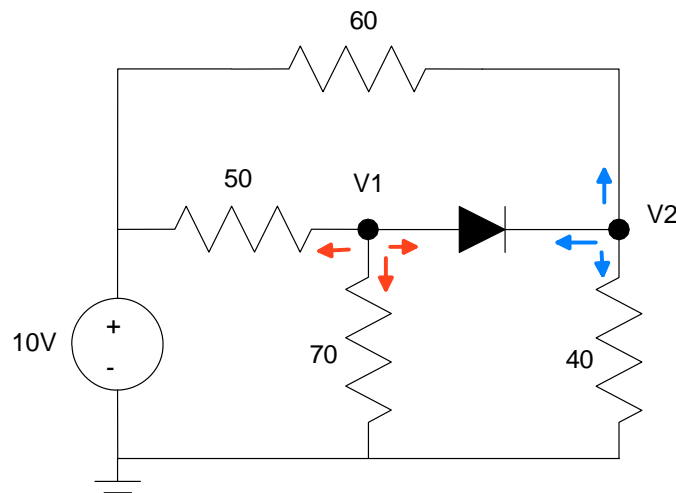


4) Write the current-loop equations for I1, I2, and I3. Assume silicon diodes with

$$I_d = I_{dss}(e^{20V_d} - 1)A \quad V_d = 0.05 \ln\left(\frac{I_d}{I_{dss}} + 1\right) V$$

Loop I1	$50(I_1 - I_2) + 60I_1 - 0.05 \ln\left(\frac{I_3 - I_1}{I_{dss}} + 1\right) = 0$
Loop I2	$-10 + 50(I_2 - I_1) + 70(I_2 - I_3) = 0$
Loop I3	$70(I_3 - I_1) + 0.05 \ln\left(\frac{I_3 - I_1}{I_{dss}} + 1\right) + 40I_3 = 0$

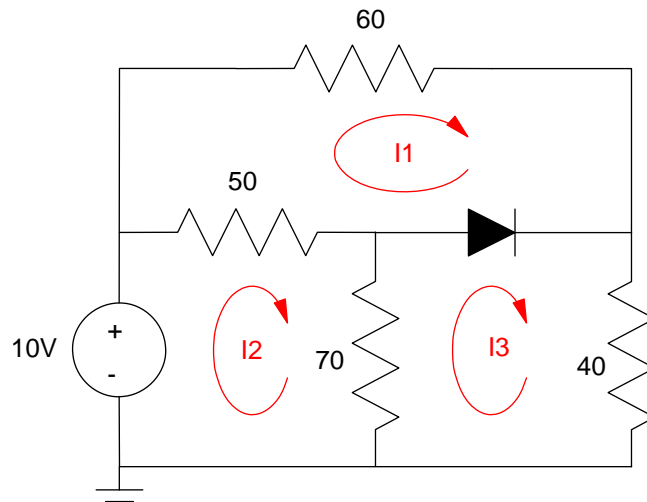

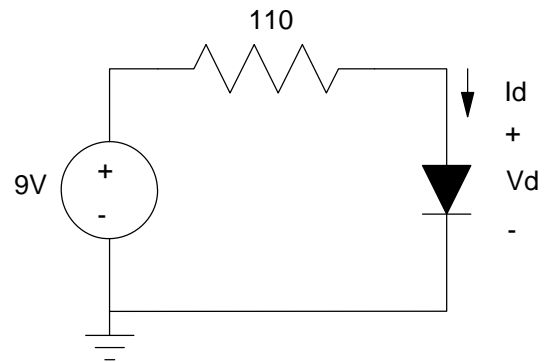5) The following circuit is used to power a white LED where the VI characteristics are shown on the following graph.



a) Draw the load-line for the following circuit

b) Determine V_d and I_d

V_d (Volts)	I_d (mA)
1.8 V	66 mA

