

ECE 320 - Homework #8

TTL Logic - MOSFETs Due Monday, March 23rd

MOSFET Switch:


1) Design a circuit using a MOSFET to turn on and off a 90V DC servo motor:

- MotionTek SM341100 (<http://www.motiontek.ca/dcservomotor.html>)
- 90V DC, 40A
- 0.408 Ohm resistance

If you ignore the 40A max current, you need a circuit which can turn on and off 0.408 Ohms at 90V (220A)

Select an Infineon Technologies IPT004N03LATMA1

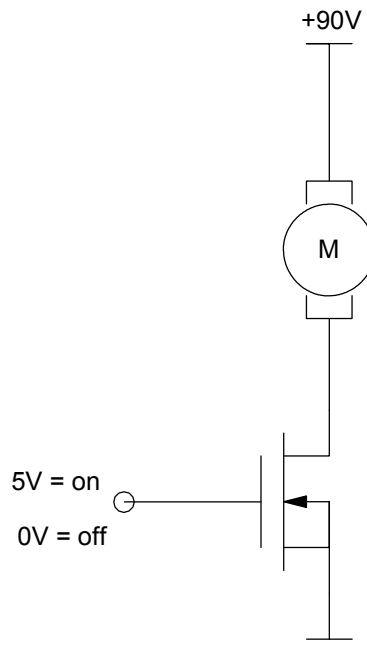- $V_{th} = 2.2V$
- $R_{ds} = 0.0004 \text{ Ohms @ } 120A \text{ @ } V_{gs} = 4.5V$
- $I_c \text{ max} = 300A$




Note: If you did this, you would burn out the motor. The start-up current is 220A.

2) For problem 1, note that 90V @ 0.408 Ohms is more than the rated current. This causes problems at start-up. Design a circuit using MOSFETs which allows you to add or remove a 3 Ohm resistor in series with the motor.

- On start-up, you add in this resistor
- Once up to speed, you remove it.

Add in a 2.25 Ohm resistor so that the start-up current is 40A.

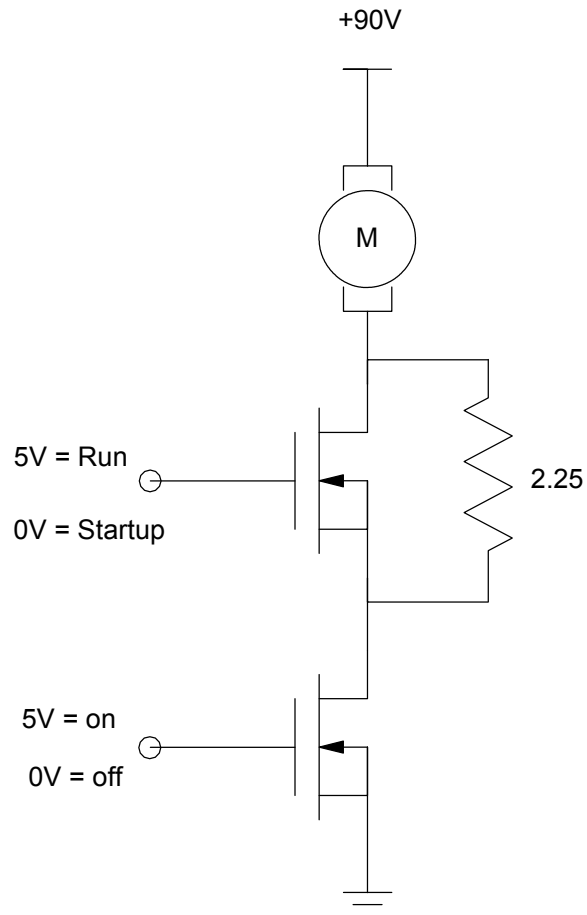Use a second MOSFET to short out this resistor with 0.0004 Ohms when the motor gets up to speed



3 - 4) Assume a thermistor with the following temperature - resistance relationship

$$R \approx 1000 \cdot e^{-0.04(T-25)} \Omega$$

where T is the temperature in degrees C.


3) Comparitor: Design a circuit which outputs

- 0V for $T < 30^\circ\text{C}$
- 5V for $T > 30^\circ\text{C}$

At 30°C , $R = 818 \text{ Ohms}$

Using a voltage divider with 5V and 1k, at 30°C

$$V_a = 2.25\text{V}$$

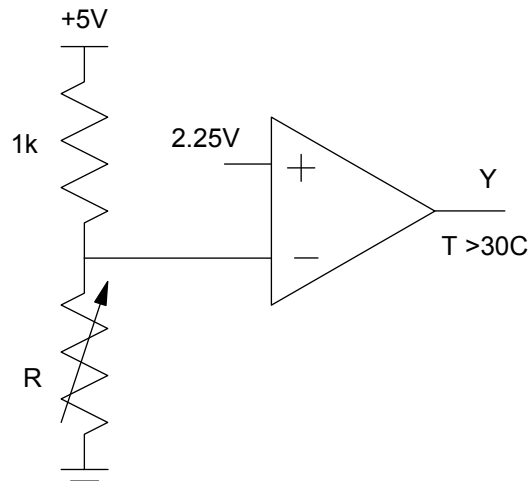

4) Schmitt Trigger: Design a circuit which outputs

- 0V when $T < 25^{\circ}\text{C}$
- 5V when $T > 30^{\circ}\text{C}$

Assuming the same 1k voltage divider

At 30°C

$$R = 818 \text{ Ohms}$$

$$V_a = 2.25\text{V}$$

At 25°C

$$R = 1000 \text{ Ohms}$$

$$V_a = 2.5\text{V}$$

Gain:

$$\text{gain} = \frac{5\text{V} - 0\text{V}}{2.5\text{V} - 2.25\text{V}} = 20$$



+ / - Input:

When the voltage becomes large (really cold), the output becomes small (0V). Connect to the - input.

Offset:

When the output is 0V (cold) and you're on the edge of switching, $V_{in} = 2.25\text{V}$.

$$\text{Offset} = 2.25\text{V}$$

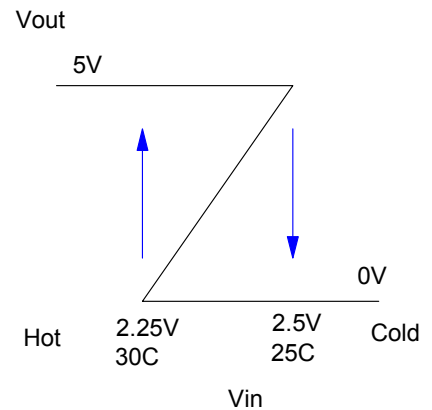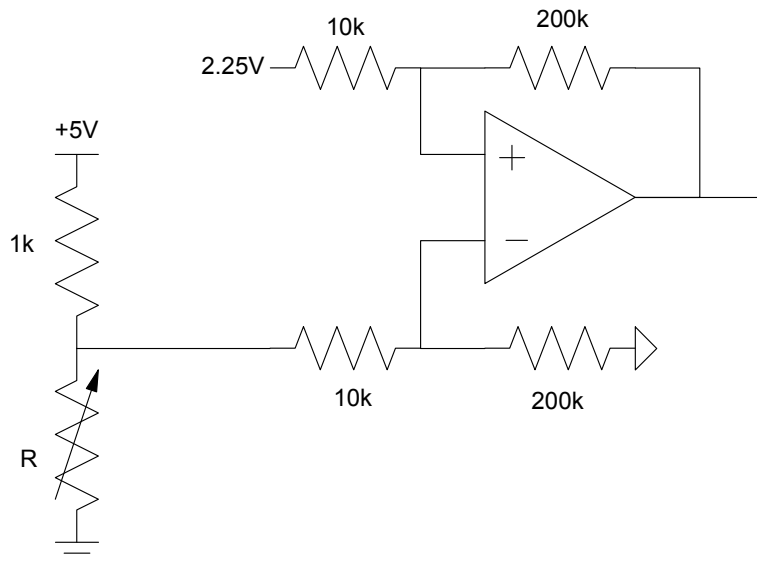

Term Project

Take one section for your term project. For that section

- 5) Requirements: Specify the inputs / outputs / and how they relate
- 6) Analysis: Design a circuit to meet these requirements. Include calculations for resistors and capacitors (if any).
- 7) Simulation: Check your analysis in simulation.
- 8) Testing: Build your circuit and collect data to check your analysis.