

ECE 320 - Homework #3

Ideal Diode, LED, Clipper Circuits. Due Monday, February 1st

Assume ideal diodes with

Silicon Diode

$V_f = 0.7V$

Red LED

$V_f = 1.9V$

Green LED


$V_f = 3.0V$

Blue LED


$V_f = 3.0V$

8000 mcd @ 20mA

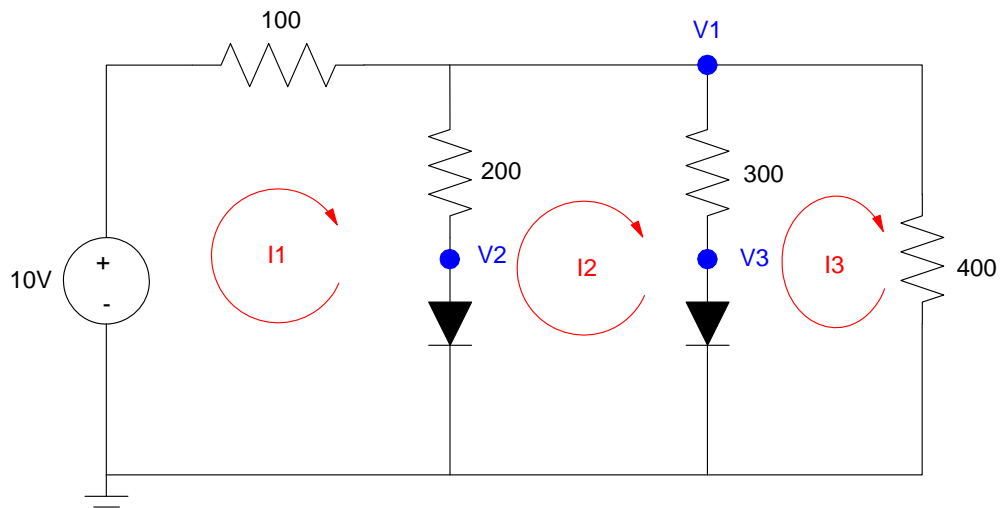1) Assume ideal silicon diodes. Determine V_1 , V_2 , and V_3



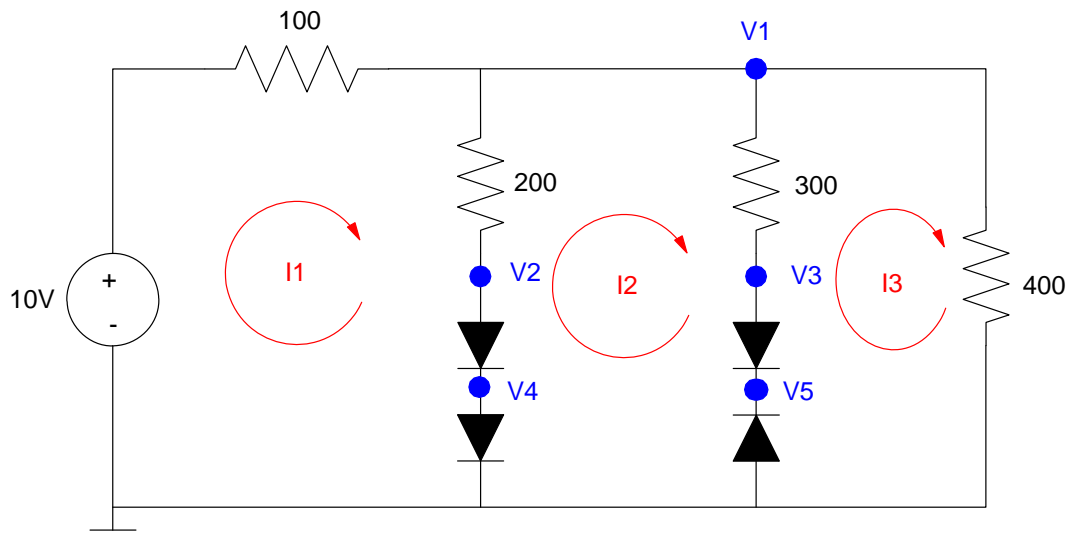2) Assume ideal silicon diodes. Determine V_1 .. V_5



A Piranah RGB LED has the following characteristics:

- Red: $V_f = 1.9V$, 8000 mcd @ 20mA
- Green: $V_f = 3.0V$, 8000 mcd @ 20mA
- Blue: $V_f = 3.0V$, 8000 mcd @ 20mA

Color wheel: go to

<http://www.rapidtables.com/web/color/color-wheel.htm>

3) Design a circuit which output purple light

- Red = 2000mcd,
- Green = 0mcd,
- Blue = 8000 mcd

4) Design a circuit which outputs gold light

- Red = 8000mcd
- Green = 6300 mcd
- Blue = 2800 mcd

Lab: Build a clipper circuit

Requirements:

- Input: 0 to 10V DC, capable of 100mA
- Output: 0 to 10V DC, capable of driving a 1M resistance (10uA)
- Relationship: Approximate $Y = \sqrt{X} \pm 1V$

5) Analysis: Design a circuit to meet the above requirements.

6) Test: Test your circuit in simulation (PartSim or similar program. Note you may need to check several points).

7) Validation: Build your circuit and test it in lab. Note: It makes the write-up easier if you measure the input / output voltages at the same points you simulated.

Note: Plan ahead for problem #7. Designing a circuit where the diodes turn on at 0.7V, 1.4V, 2.1V is easy (cascade 1, 2, or 3 diodes). Other voltages are more difficult to implement.)

