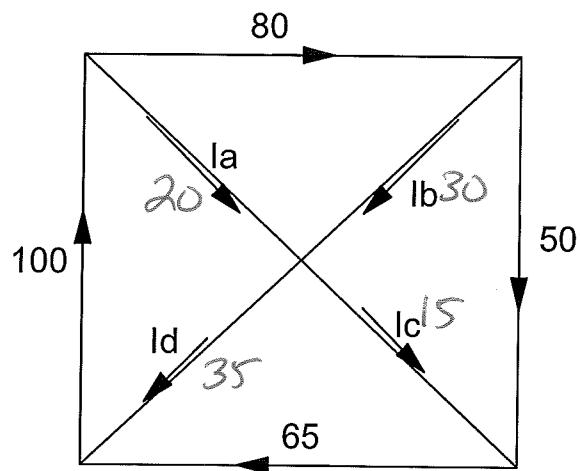


ECE 320: Quiz #1: Name _____

EE 206 Review


- 1) Conservation of Current: Determine the currents I_a , I_b , I_c , and I_d

I_a	I_b	I_c	I_d
20	30	15	35




2) Conservation of Voltage: Determine the voltages V1, V2, V3, and V4

V1	V2	V3
45	27	67

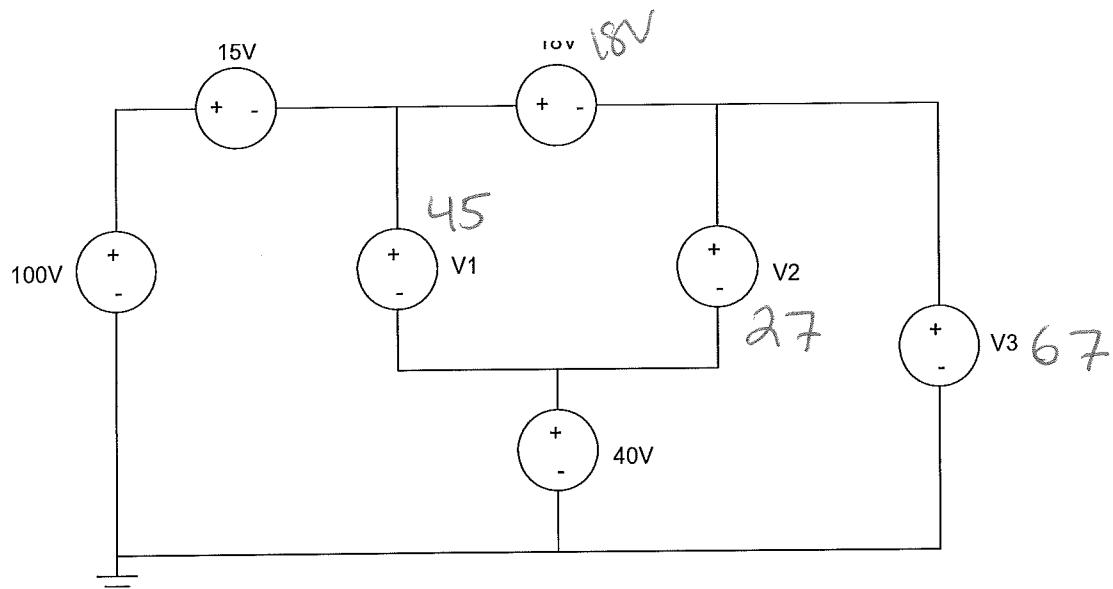

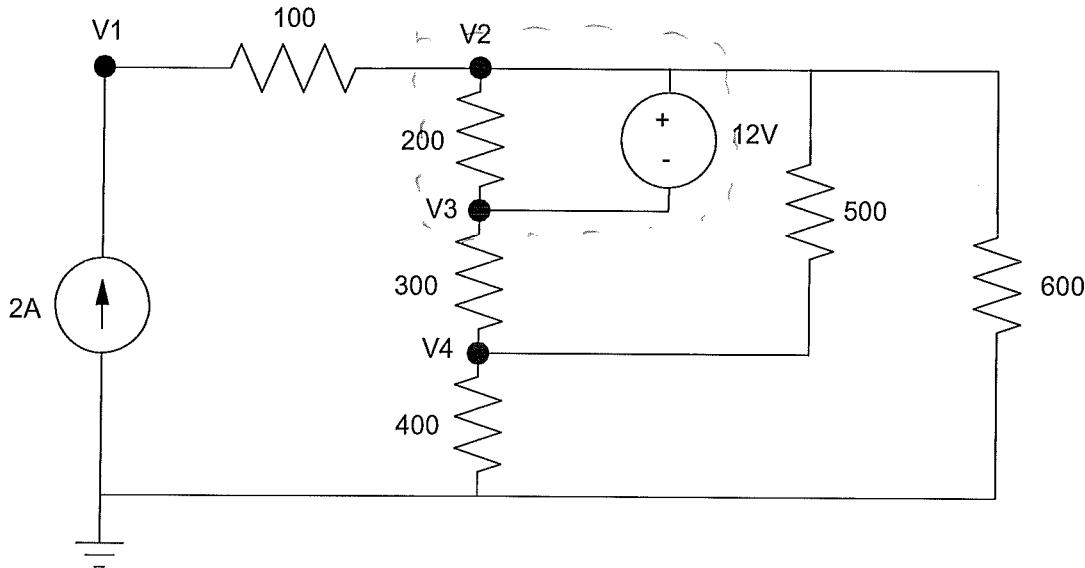3) KVN: Write the voltage node equations for V1..V4 (sum of currents = zero).




$$2 = \frac{V_1 - V_2}{100}$$

$$V_2 - V_3 = 12$$

$$\frac{V_2 - V_1}{100} + \frac{V_2 - V_4}{500} + \frac{V_2}{600} + \frac{V_3 - V_4}{300} = 0$$

$$\frac{V_4 - V_3}{300} + \frac{V_4}{400} \cancel{+ \frac{V_4 - V_2}{500}} = 0$$

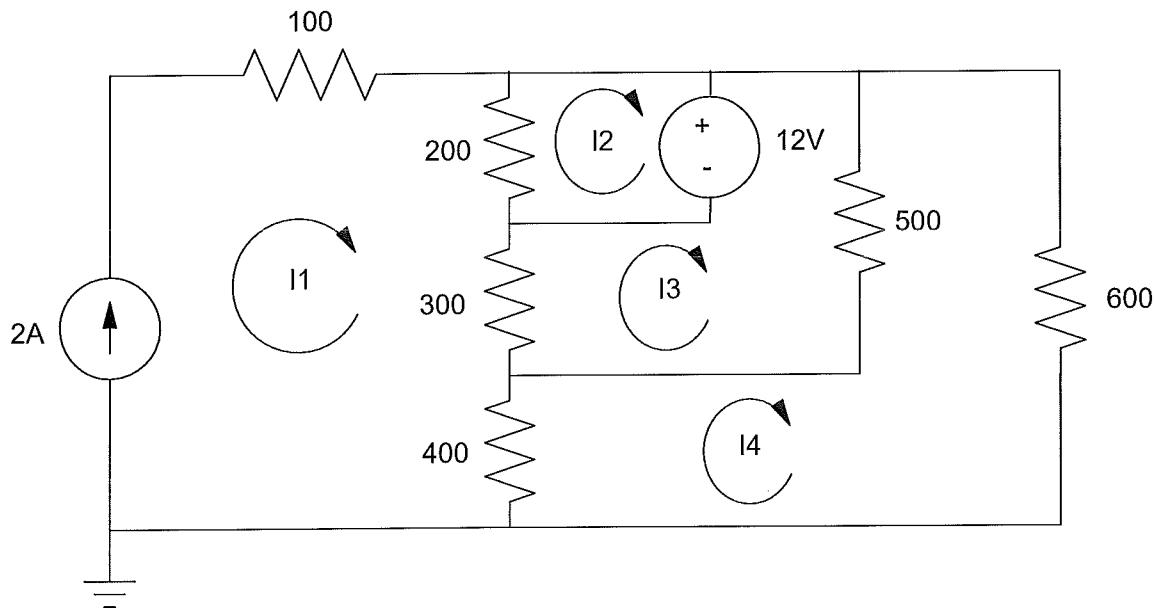4) KCL: Write the current loop equations for I₁..I₄ (sum of voltages equals zero)



$$I_1 = 2$$



$$12 + 200(I_2 - I_1) = 0$$

$$300(I_3 - I_1) - 12 + 500(I_3 - I_4) = 0$$

$$400(I_4 - I_1) + 500(I_4 - I_3) + 600I_4 = 0$$

5) Thevenin Equivalents: Find the Thevenin equivalent for the following circuit:

V _{th}	R _{th}
$\frac{90}{69} \cancel{+30V}$ $8.26V$	$400 \parallel 366.67$ 191.52

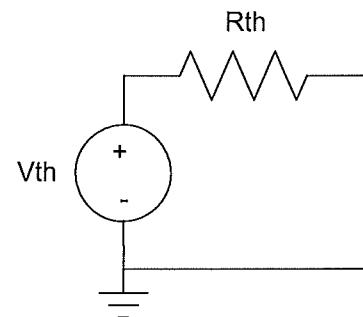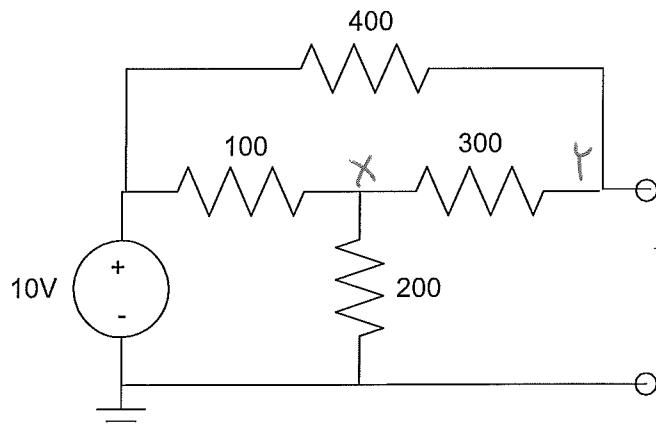

$$R_{th} = 100 \parallel 200 = 66.67 \Omega$$

$$+30V = 366.67$$

$$R_{th} = 400 \parallel 366.67$$

=

$$(100) \quad \frac{x-10}{100} + \frac{x}{200} + \frac{x-y}{300} = 0$$

$$6(x-10) + 3x + 2(x-y) = 0$$

$$12 \quad \frac{y-10}{400} + \frac{y-x}{300} = 0$$

$$3(y-10) + 4(y-x) = 0$$

$$\begin{aligned} x &= 4 \\ -4x + 7y &= 30 \end{aligned}$$

Bonus! In Fargo, 1kWh of electricity costs about \$0.10. How many pounds of coal does it take to produce 1kWh?


1 lb

$$\frac{77}{69}$$

$$69y = 570$$

$$y = \frac{570}{69}$$

$$= 8.26V$$

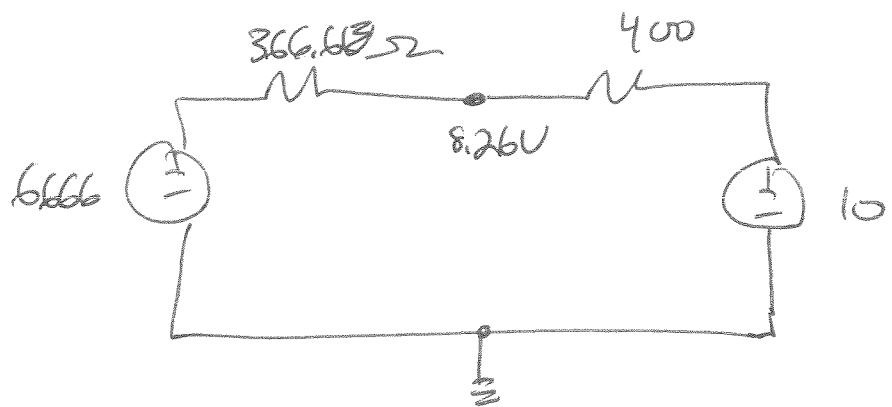

19(2)