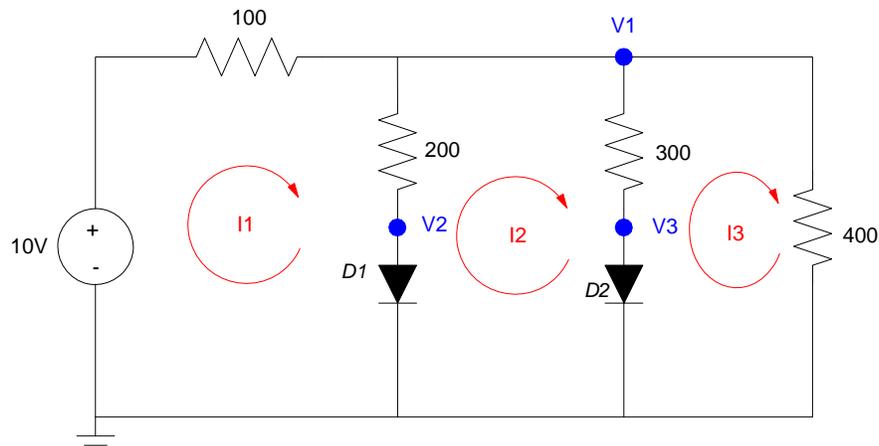


# ECE 320 - Solution to Homework #3

Ideal Diode, LED, Clipper Circuits. Due Monday, February 1st

1) Assume ideal silicon diodes. Determine V1, V2, and V3



Assume D1 and D2 are on


- $V_2 = 0.7V$
- $V_3 = 0.7V$

Solve for V1:


$$\left(\frac{V_1-10}{100}\right) + \left(\frac{V_1-0.7}{200}\right) + \left(\frac{V_1-0.7}{300}\right) + \left(\frac{V_1}{400}\right) = 0$$

- $V_1 = 5.08V$

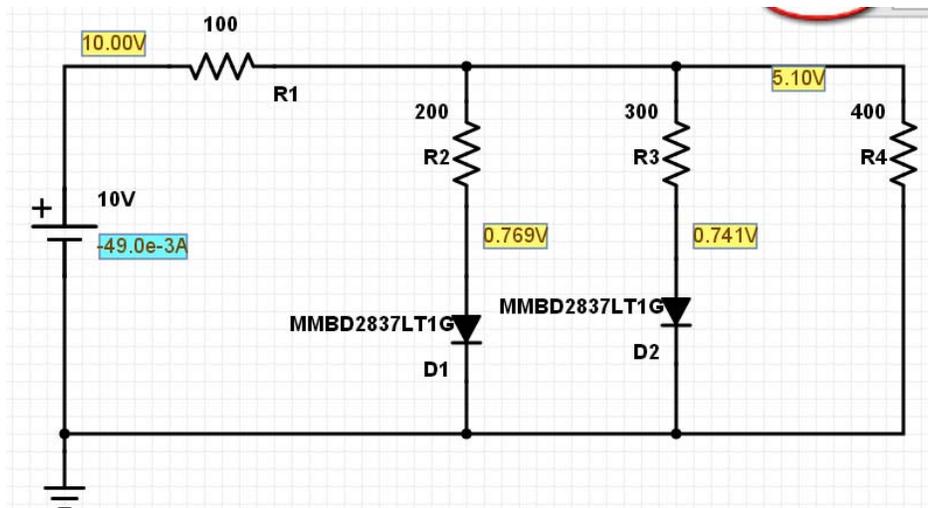From PartSim, the voltages are about the same



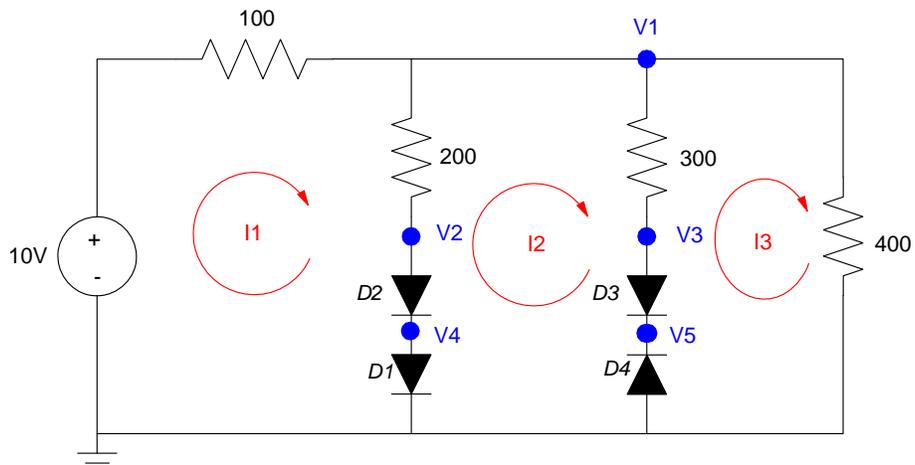2) Assume ideal silicon diodes. Determine V1 .. V5




Assume D1, D2 are on, D4 is off

- V4 = 0.7V
- V2 = 1.4V

$$\left(\frac{V_1-10}{100}\right) + \left(\frac{V_1-1.4}{200}\right) + \left(\frac{V_1}{400}\right) = 0$$

- V1 = 6.1143V
- V3 = 6.1143V
- V5 = 6.1143V

From PartSim, the voltages are close

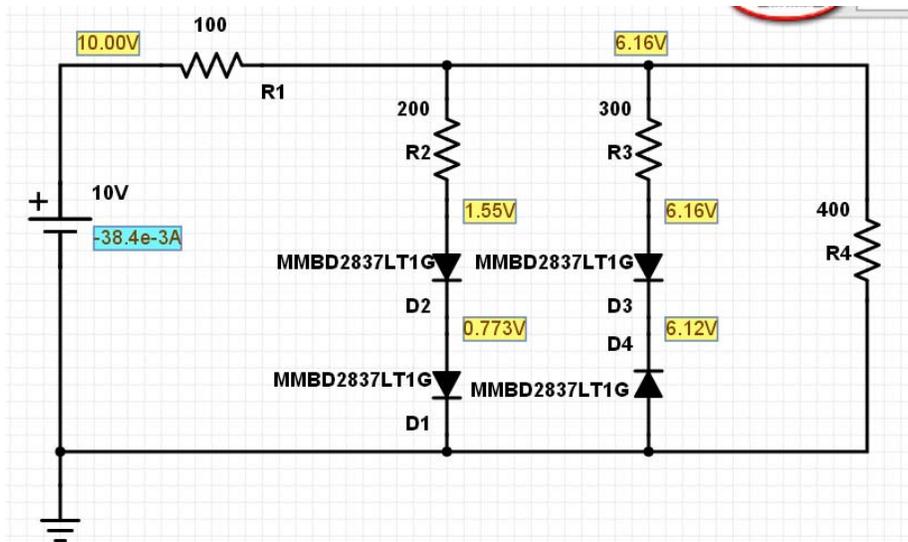


A Piranah RGB LED has the following characteristics:

- Red:  $V_f = 1.9V$ , 8000 mcd @ 20mA
- Green:  $V_f = 3.0V$ , 8000 mcd @ 20mA
- Blue:  $V_f = 3.0V$ , 8000 mcd @ 20mA

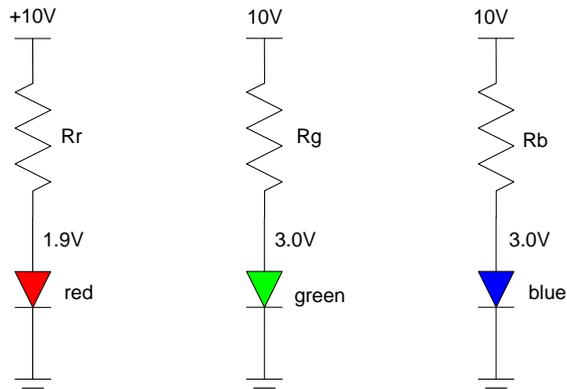3) Design a circuit which output purple light

- Red = 2000mcd,
- Green = 0mcd,
- Blue = 8000 mcd



	Red	Green	Blue
mcd	2,000	0	8,000
$V_f$	1.9	3	3
I (mA)	5	0	20
R (Ohms)	1,620	infinite	350

4) Design a circuit which outputs gold light

- Red = 8000mcd
- Green = 6300 mcd
- Blue = 2800 mcd

	Red	Green	Blue
mcd	8,000	6,300	2,800
$V_f$	1.9	3	3
I (mA)	20	15.75	7
R (Ohms)	405	444.44	1,000


# Lab: Build a clipper circuit

Requirements:

- Input: 0 to 10V DC, capable of 100mA
- Output: 0 to 10V DC, capable of driving a 1M resistance (10uA)
- Relationship: Approximate  $Y = \sqrt{X} \pm 1V$

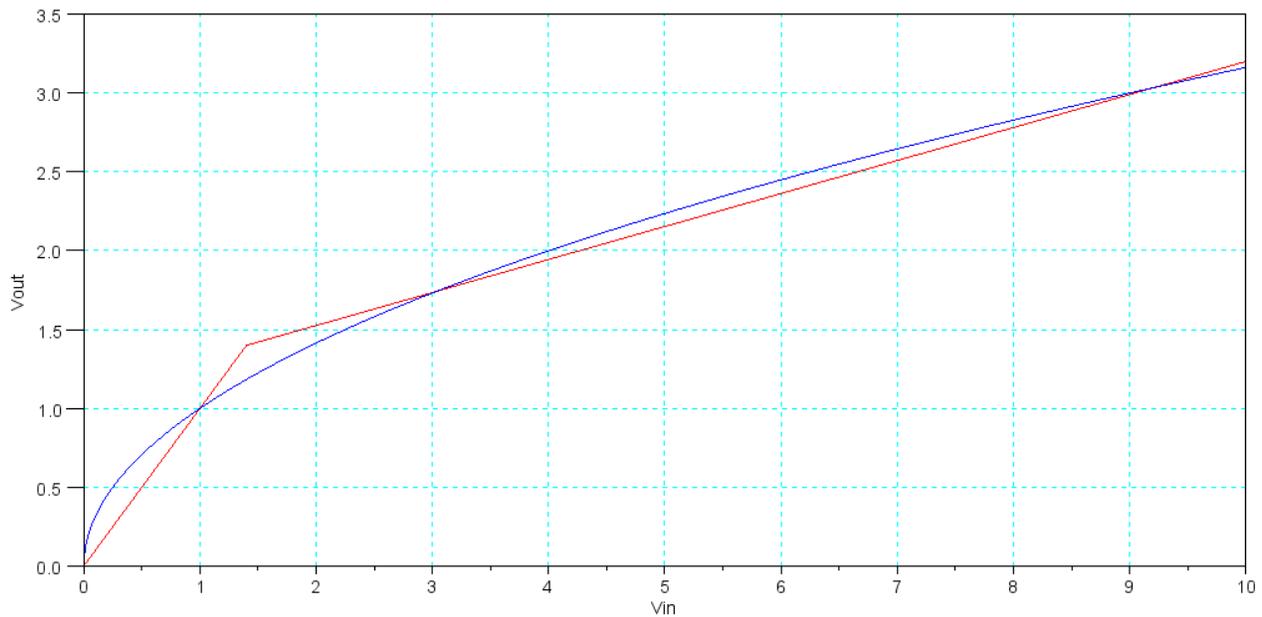5) Analysis: Design a circuit to meet the above requirements.

First, draw a straight-line approximation to the curve (shown in red)



Generate the slope using voltage division

$V_{out} < 1.4V$ :

Slope = 1

$$\left(\frac{R}{R+1000}\right) = 1$$

$R = \text{infinity}$



$V_{out} > 1.4V$

Slope = 0.2093

$$\left(\frac{R}{R+1000}\right) = 0.2093$$

$$R = \left(\frac{0.2093}{1-0.2093}\right) 1000\Omega = 264\Omega$$

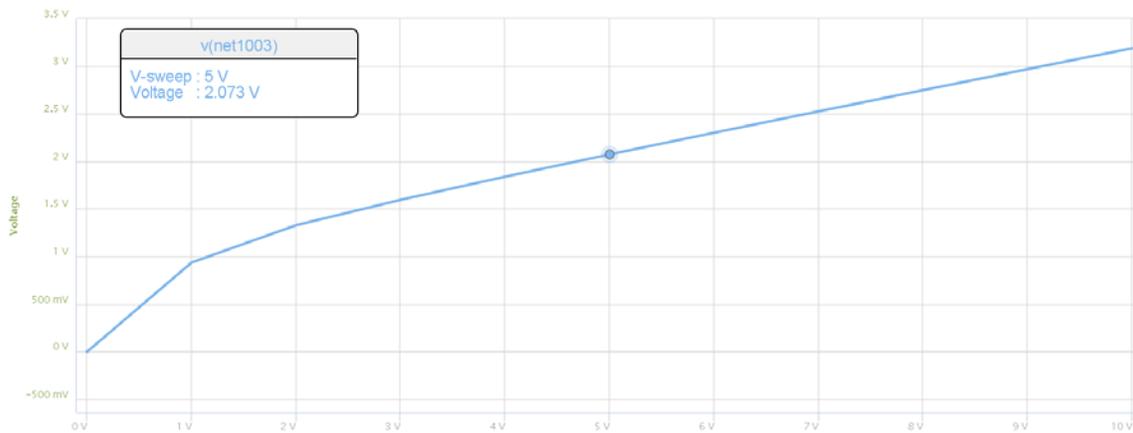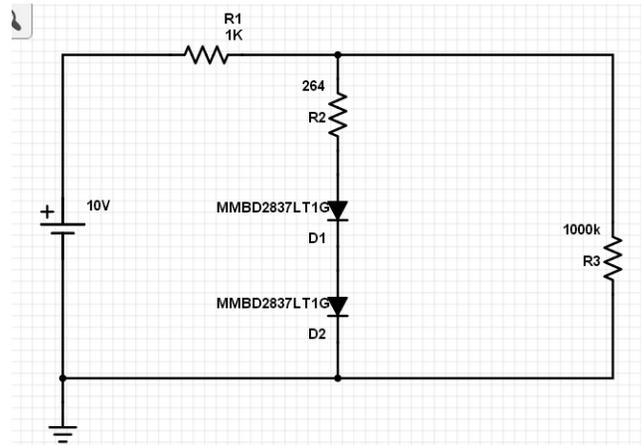6) Test: Test your circuit in simulation (PartSim or similar program. Note you may need to check several points).



Vin	0V	1V	3V	5V	7V
Vout (theory)	0	1	1.73	2.15	2.57
Vout (PartSim)	0	0.94	1.6	2.07	2.53
Vout (Lab)	-	-	-	-	-

7) Validation: Build your circuit and test it in lab. Note: It makes the write-up easier if you measure the input / output voltages at the same points you simulated.