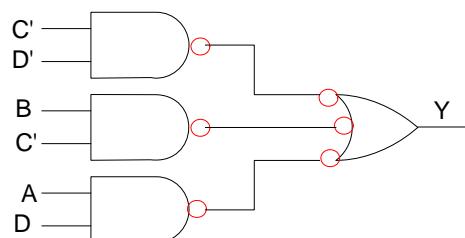


# ECE 320 - Homework #7

Boolean Logic, DTL Logic, TTL Logic. Due Monday, February 29th


- 1) Determine a circuit to implement  $Y(A,B,C,D)$  using NAND gates (circle the ones)

		CD	
		00	01
AB		00	01
	00	x	0
01	00	1	1
01	01	1	0
11	00	1	1
11	01	1	0
10	00	1	1
10	01	1	x




- 2) Determine a circuit to implement  $Y(A,B,C,D)$  using NOR gates (circle the zeros)

		CD	
		00	01
AB		00	01
	00	x	0
01	00	1	1
01	01	0	0
11	00	1	1
11	01	1	0
10	00	1	1
10	01	1	x

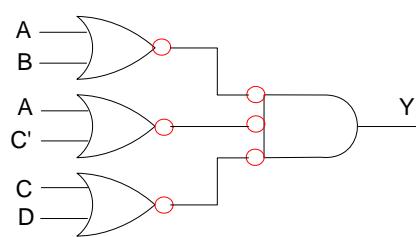


3) Determine the voltages and the currents through each diode for the following DTL circuit when

3a)  $A = B = 5V$ .

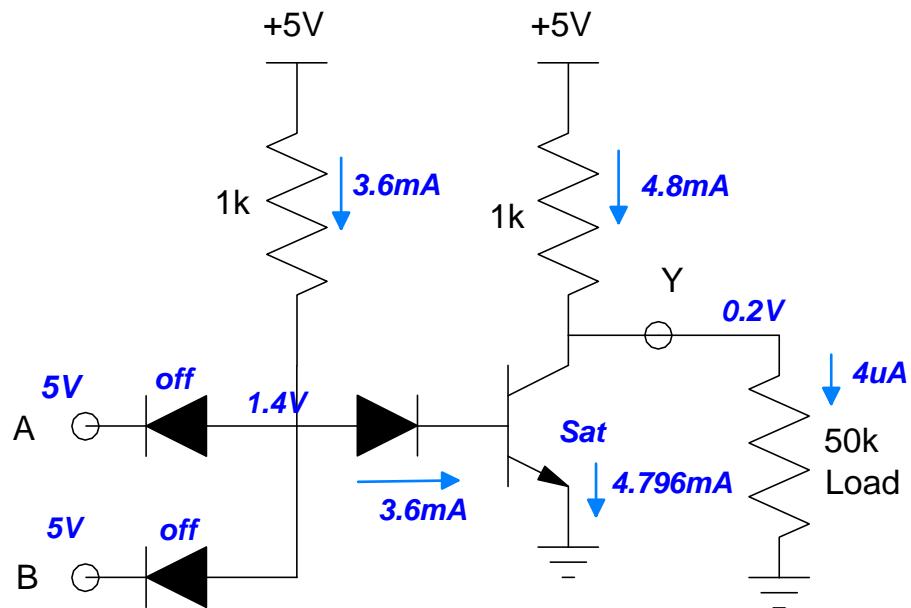


3b)  $A = 5V, B = 0V$

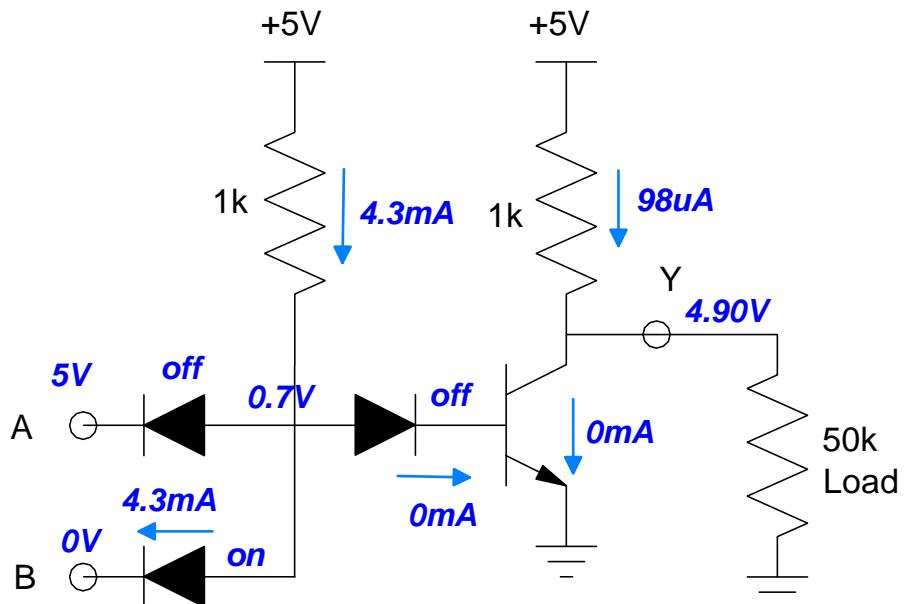


4) Determine the voltages and the currents through each diode for the following DTL circuit when

4a)  $A = 5V$ .

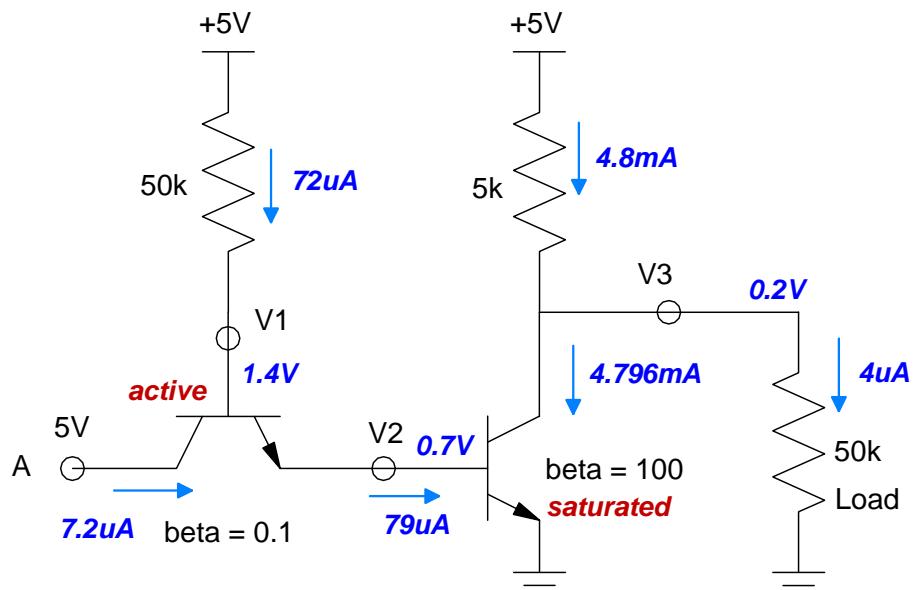

4b)  $A = 0V$

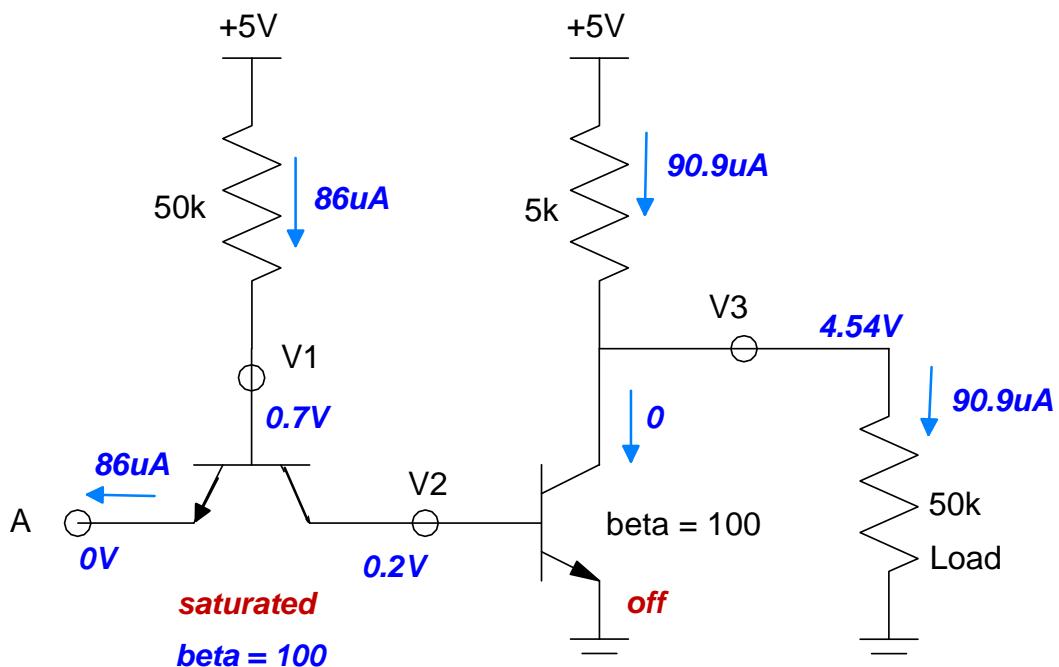

Lab: For one of these circuits (DTL, TTL)

- 5) Simulate in PartSim to test your analysis
- 6) Build in lab to validate your design