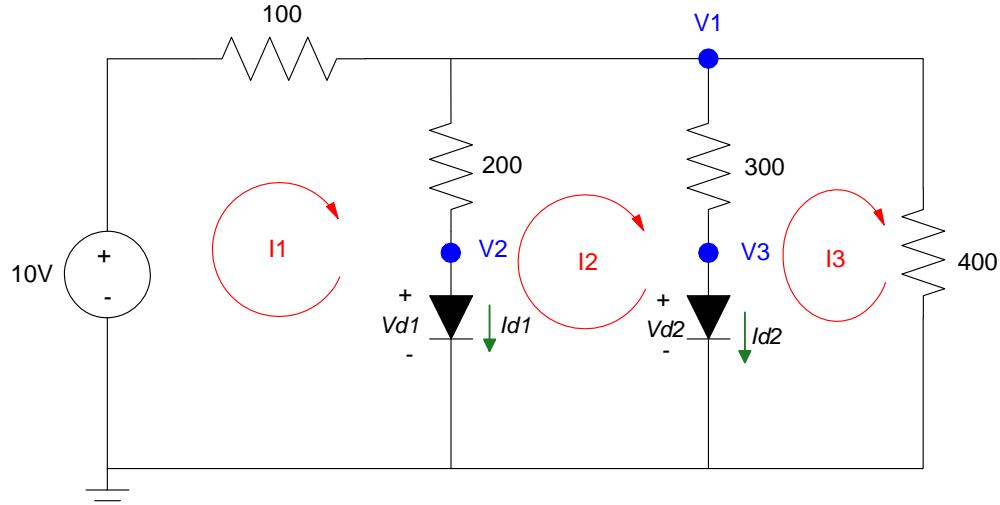


# ECE 320 - Homework #2

PN Junction, Diode VI Characteristics. Due Monday, Jan 25th

$$V_d = 0.052 \cdot \ln(10^8 I_d + 1) \quad I_d = 10^{-8} \left( \exp\left(\frac{V_d}{0.025}\right) - 1 \right)$$



- 1) Write the current loop equations

$$V_{d1} = 0.052 \cdot \ln(10^8(I_1 - I_2) + 1)$$

$$V_{d2} = 0.052 \cdot \ln(10^8(I_2 - I_3) + 1)$$

Loop I1:

$$-10 + 100I_1 + 200(I_1 - I_2) + V_{d1} = 0$$


Loop I2

$$-V_{d1} + 200(I_2 - I_1) + 300(I_2 - I_3) + V_{d2} = 0$$

Loop I3

$$-V_{d2} + 300(I_3 - I_2) + 400I_3 = 0$$

2) Write the voltage node equations

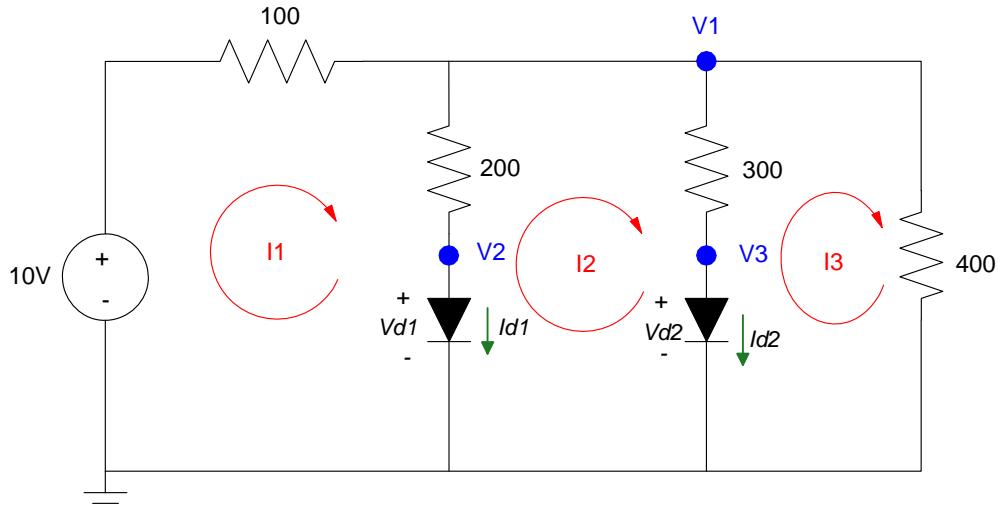

$$I_{d1} = 10^{-8} \left( \exp \left( \frac{V_2}{0.025} \right) - 1 \right)$$

$$I_{d2} = 10^{-8} \left( \exp \left( \frac{V_3}{0.025} \right) - 1 \right)$$

Node V1:

$$\left( \frac{V_1 - 10}{100} \right) + \left( \frac{V_1 - V_2}{200} \right) + \left( \frac{V_1 - V_3}{300} \right) + \left( \frac{V_1}{400} \right) = 0$$


Node V2:

$$\left( \frac{V_2 - V_1}{200} \right) + I_{d1} = 0$$

Node V3:

$$\left( \frac{V_3 - V_1}{300} \right) + I_{d2} = 0$$

3) Write the current loop equations

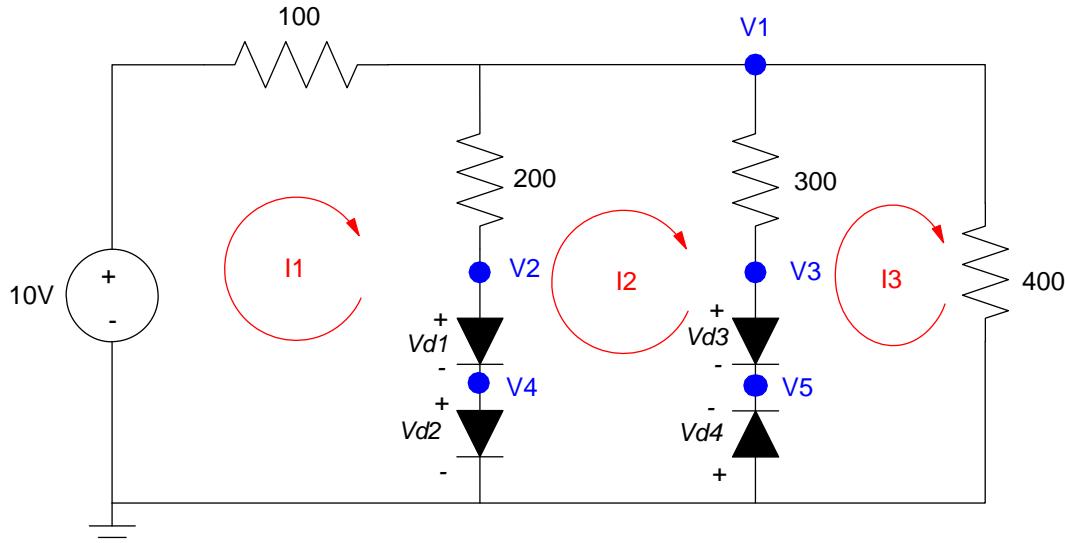

$$V_{d1} = 0.052 \cdot \ln(10^8(I_1 - I_2) + 1)$$

$$V_{d2} = 0.052 \cdot \ln(10^8(I_1 - I_2) + 1)$$

$$V_{d3} = 0.052 \cdot \ln(10^8(I_2 - I_3) + 1)$$

$$V_{d4} = 0.052 \cdot \ln(10^8(I_3 - I_2) + 1)$$

Loop I1:

$$-10 + 100I_1 + 200(I_1 - I_2) + V_{d1} + V_{d2} = 0$$


Loop I2:

$$-V_{d1} - V_{d2} + 200(I_2 - I_1) + 300(I_2 - I_3) + V_{d3} - V_{d4} = 0$$

Loop I3:

$$V_{d4} - V_{d3} + 300(I_3 - I_2) + 400I_3 = 0$$

4) Write the voltage node equations

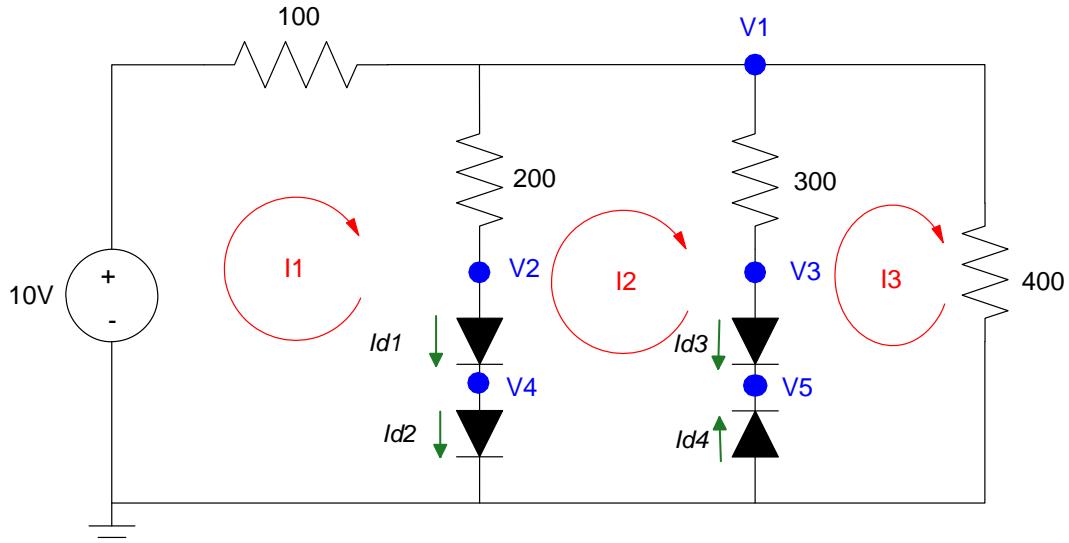

Diode Equations

$$I_{d1} = 10^{-8} \left( \exp \left( \frac{V_2 - V_4}{0.025} \right) - 1 \right)$$

$$I_{d2} = 10^{-8} \left( \exp \left( \frac{V_4}{0.025} \right) - 1 \right)$$

$$I_{d3} = 10^{-8} \left( \exp \left( \frac{V_3 - V_5}{0.025} \right) - 1 \right)$$

$$I_{d4} = 10^{-8} \left( \exp \left( \frac{-V_5}{0.025} \right) - 1 \right)$$

Voltage Node Equations:

$$\left( \frac{V_1 - 10}{100} \right) + \left( \frac{V_1 - V_2}{200} \right) + \left( \frac{V_1 - V_3}{300} \right) + \left( \frac{V_1}{400} \right) = 0$$

$$\left( \frac{V_2 - V_1}{200} \right) + I_{d1} = 0$$

$$I_{d1} = I_{d2}$$

$$\left( \frac{V_3 - V_1}{300} \right) + I_{d3} = 0$$

$$I_{d3} + I_{d4} = 0$$