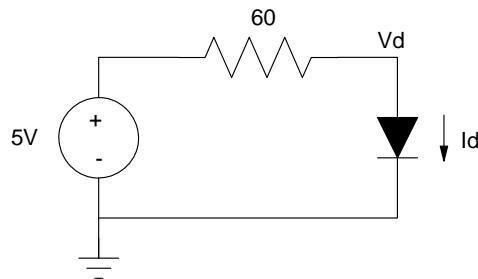



# ECE 320: Final Name \_\_\_\_\_

Part 1: Semiconductors and Diodes - March 23, 2017

- 1) The VI characteristics for a red LED are given below. Draw the load-line and determine the current and voltage for the following circuit.




Load Line	$V_d$	$I_d$
show on graph	<b>1.75V</b>	<b>53mA</b>

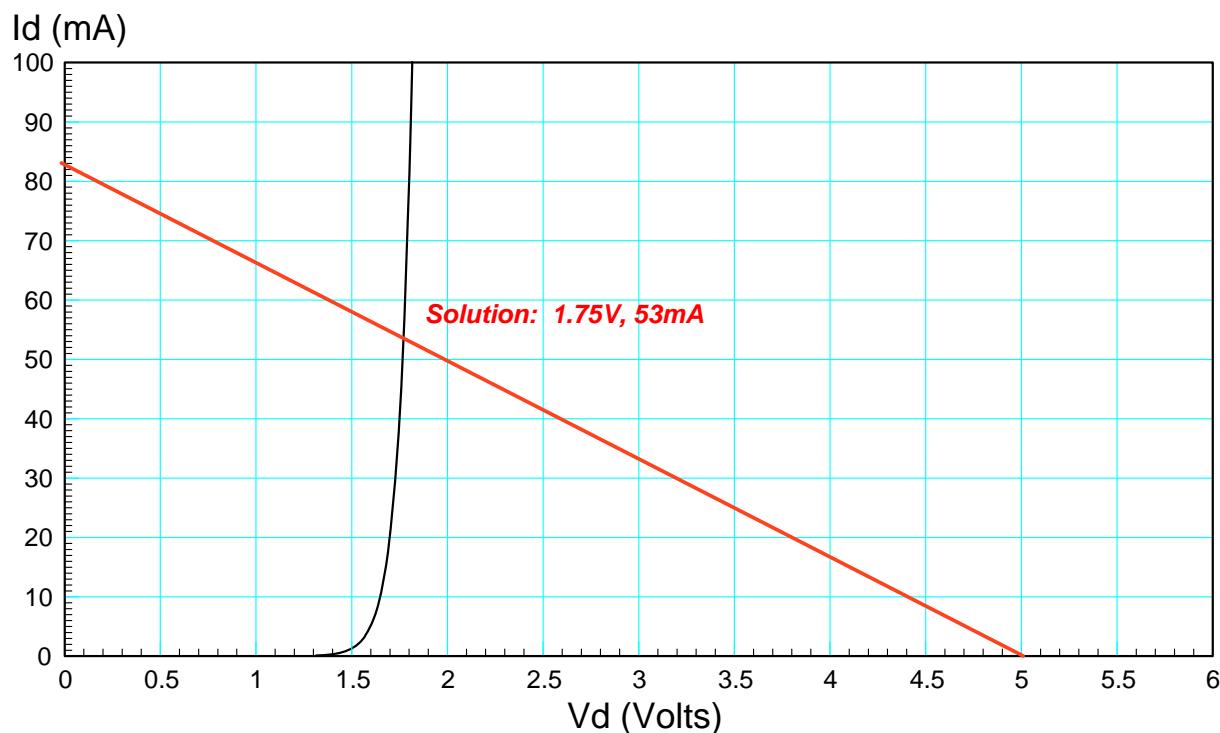


2) Assume ideal diodes with  $V_f = 0.7V$ . Determining the currents  $I_1 \dots I_4$

$I_1$	$I_2$	$I_3$	$I_4$
<b>58mA</b> $= 79mA - I_2 - I_3 - I_4$	<b>3.5mA</b>	<b>7.0mA</b>	<b>10.5mA</b>

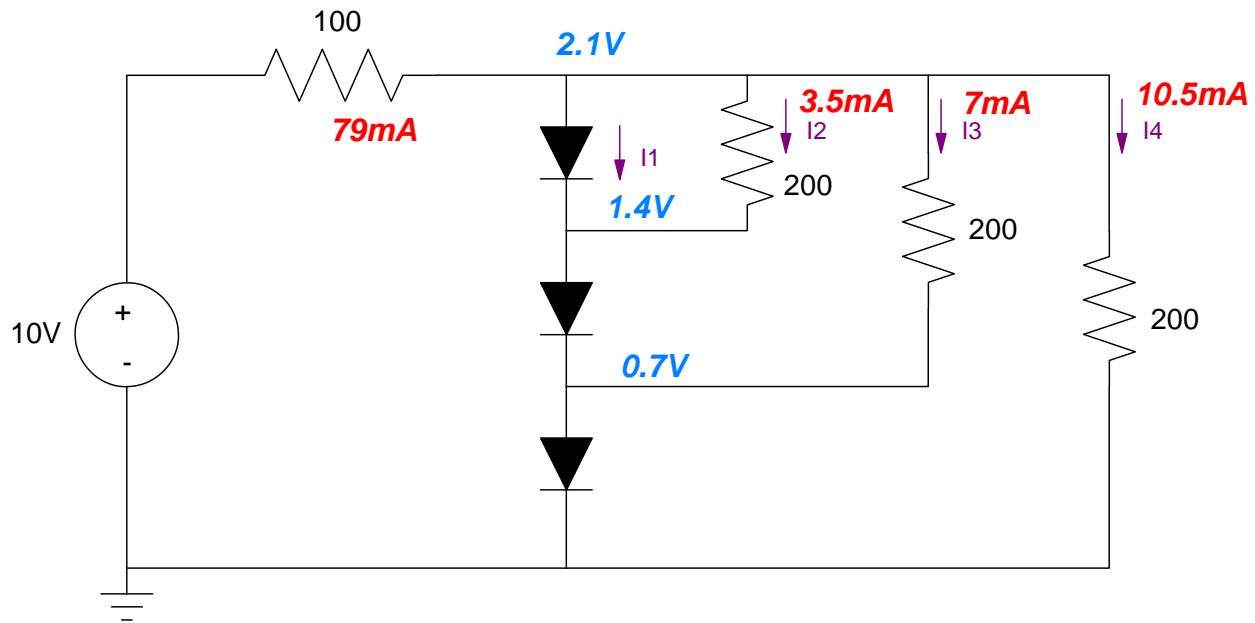

3) Max/Min: Determine the currents, I<sub>1</sub>, I<sub>2</sub>, I<sub>3</sub>, I<sub>4</sub> for the following max/min circuit. Assume ideal silicon diodes ( $V_f = 0.7V$ )


I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>	I <sub>4</sub>
<b>0 mA</b>	<b>2.42mA</b> 3.3mA - 0.88mA	<b>0.88mA</b>	<b>0 mA</b>

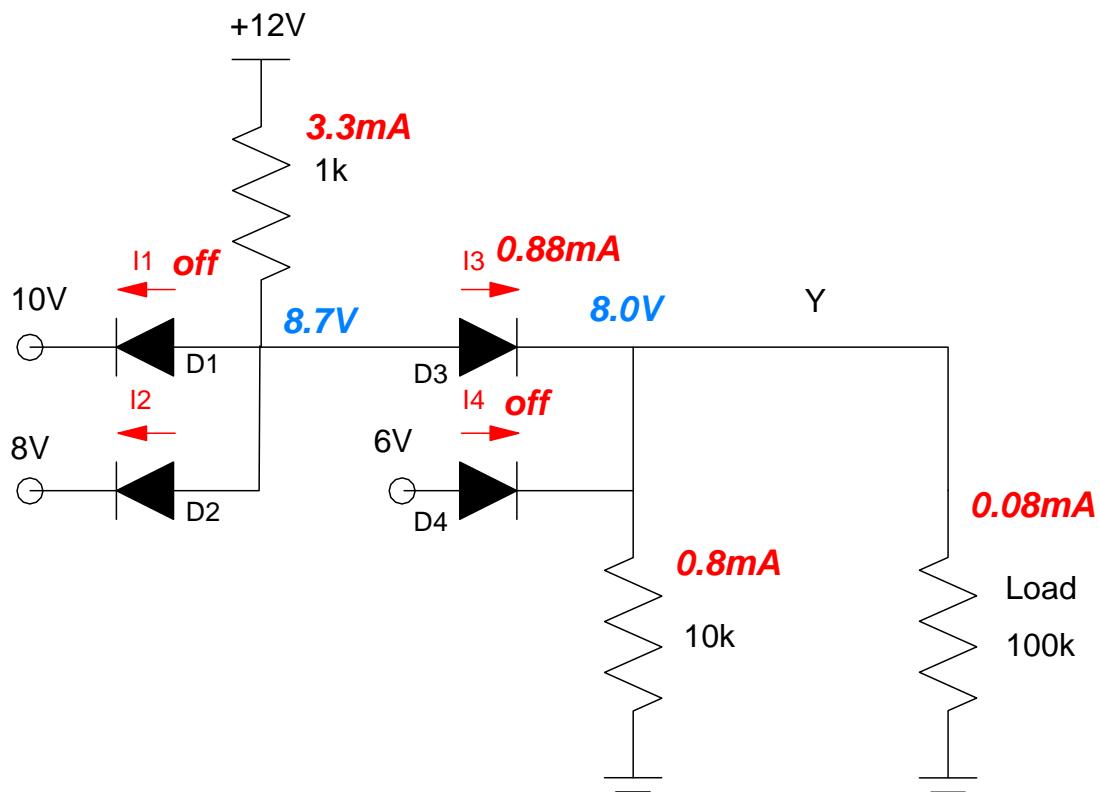

4) AC to DC Converter. Assume ideal silicon diodes with  $V_f = 0.7V$ . Find R, L, and C for the following 1/2 wave AC to DC converter which results in

- 100mA to the load
- 2Vpp ripple at V1
- 1Vpp ripple at V2

$V_2$ (DC)	R 100mA to load	C 2Vpp @ $V_1$	L 1Vpp @ $V_2$
<b>4.3V</b> <small>max = 5.3V min = 3.3V (2V ripple) avg = 4.3V</small>	<b>43 Ohms</b>	<b>833uA</b> <small><math>100mA = C (2V) / (1/60s)</math></small>	<b>228mH</b> <small><math>j w L = j86 \text{ Ohms}</math> 2x R reduces the ripple 2x</small>

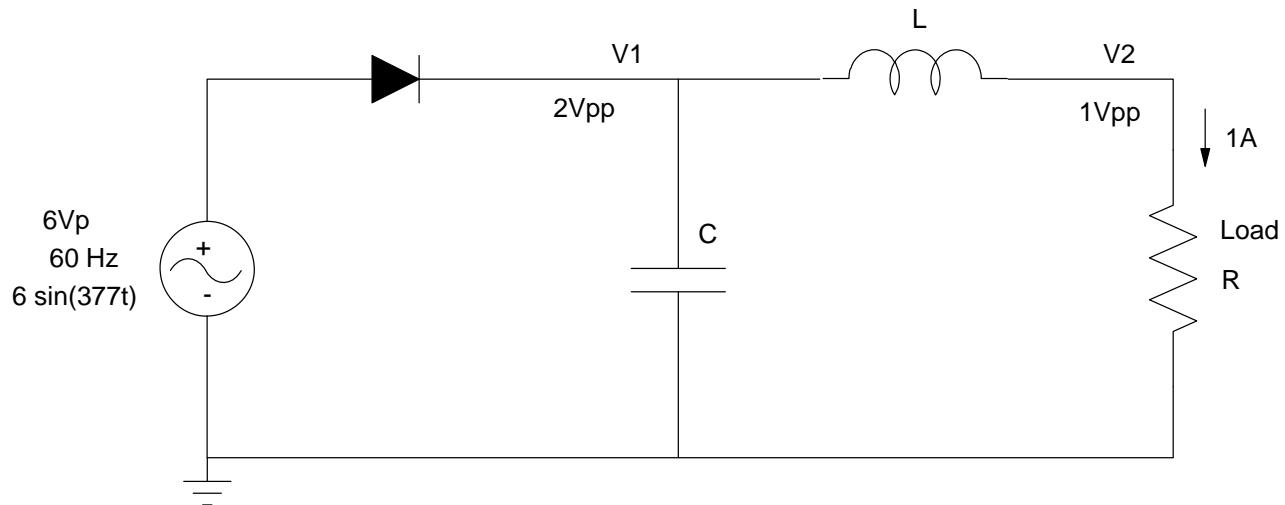


5) A 10V peak, 60Hz sine wave drives an AC to DC converter with a firing angle of 90 degrees, resulting in

$$V_1(t) = \begin{cases} 8.6 \sin(377t) & 90^\circ < 377t < 180^\circ \\ -0.7V & otherwise \end{cases}$$

Determine the following:

DC Voltage @ V1	AC Voltage at V1 V1pp	AC Voltage at V2 if C = 0 (V2pp)	AC Voltage at V2 C = 25uV (V2pp)
<b>5.921V</b>	<b>9.3Vpp</b> $(10V - 1.4V) + 0.7V$	<b>246.6mVpp</b> $20 / (20+j754) * 9.3V$	<b>232.8mVpp</b> $-j53 \parallel 20 = 18.7 \text{ Ohms}$ Then use voltage division

$$\frac{1}{\pi} \int_{\pi/2}^{\pi} (18.6 \sin(t)) dt = \frac{18.6}{\pi} (-\cos(t)) \Big|_{\pi/2}^{\pi} = \frac{18.6}{\pi} =$$

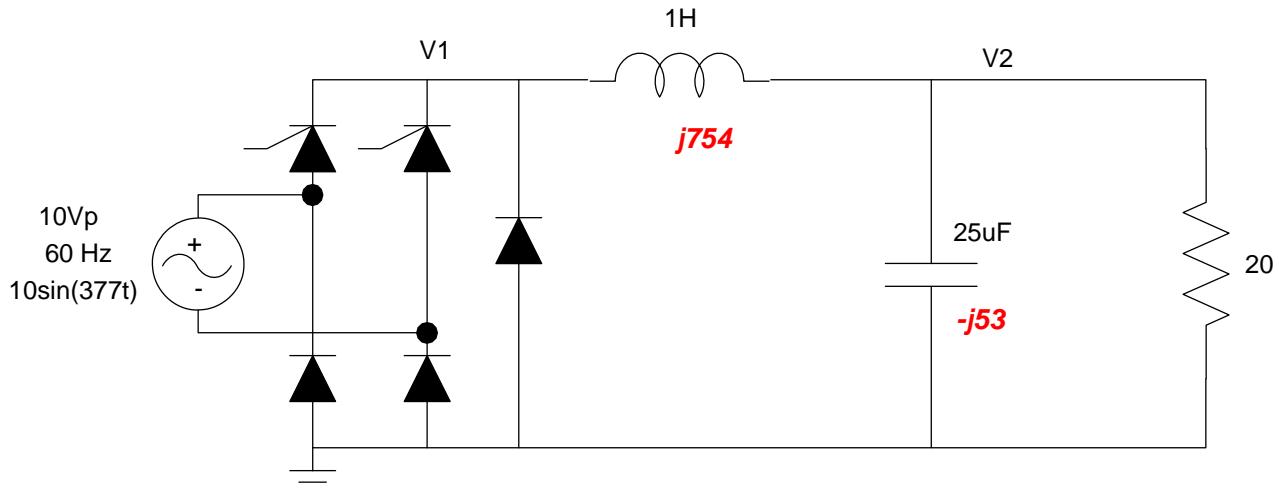

Bonus! According to NREL, there is enough wind energy in North Dakota to produce 1.1 trillion kWh of electricity every year, which is worth \$110 billion at 10 cents / kWh. To put this in perspective, what is the entire gross domestic product of North Dakota?

**\$51 billion / year (2015)**