
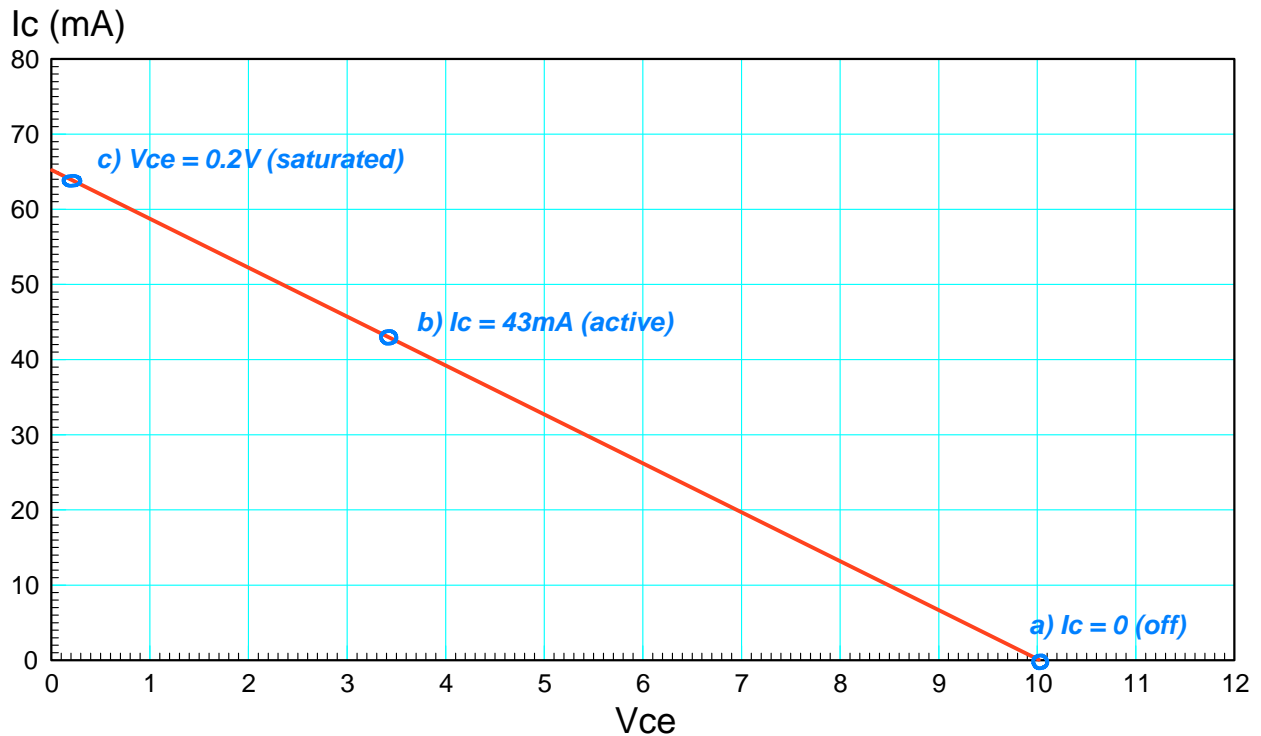


ECE 320: Final Name _____

Part 2: Digital Circuits with Transistors and Op-Amps - March 24, 2017

1) Assume an ideal silicon transistor with $V_{be} = 0.7V$ and $\beta = 100$. Draw the load-line for the following circuit and show the operating point for $V_{in} = \{ 0.5V, 5V, 10V \}$

Load Line	Q-Point for $V_{in} = 0.5V$	Q-Point for $V_{in} = 5V$	Q-Point for $V_{in} = 10V$
Show on graph	Mark on load line	Mark on load line	Mark on load line

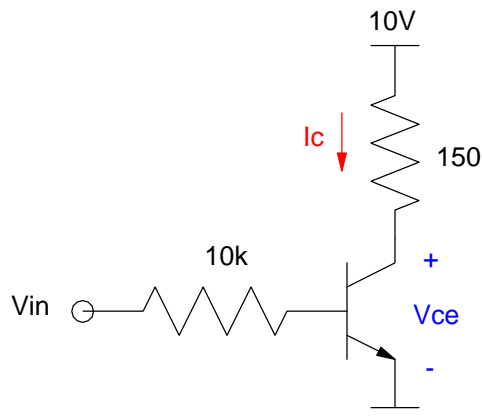

2) Design a circuit so that the output of an op-amp can turn on and off a 1W LED at 300mA.

Input: 0V / 10V binary signal capable of 20mA

Output: 1W LED, $V_f = 3.3V$ @ 100mA


Relationship:

- When the input is 0V, the LED is off (0mA)
- When the input is 10V, the LED is on (100mA)

Assume a transistor with


- $V_{be} = 0.7V$
- $V_{ce(sat)} = 0.2V$
- $\beta = 100$

R_b	R_c	For your design, how low V_{in} can go and still saturate the transistor
1000 $465 < R_b < 3100$	21.67 $(10 - 0.2 - 3.3V) / 300mA$	3.7V (varies) $3mA * 1000\text{ Ohms} + 0.7V$

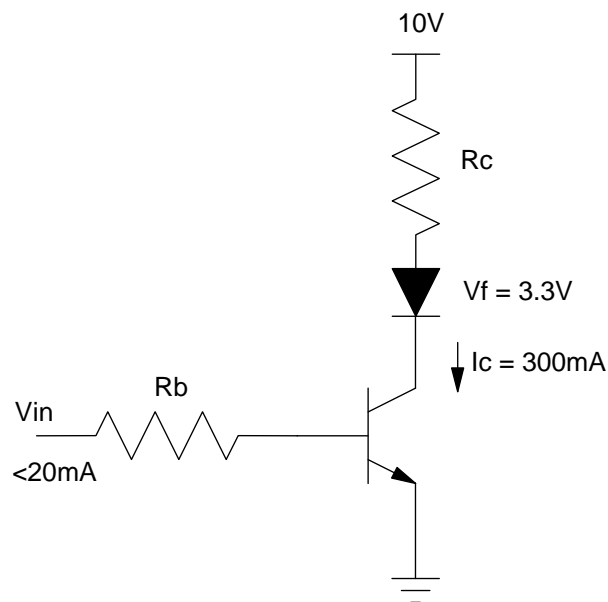

3) Assume ideal transistors with $|V_{be}| = 0.7V$ and $\beta = 100$. Determine the voltages and currents.


I1	V2	I3	V4	I5
1.86mA	9.8V	93mA	5.15V	0.93mA
9.3V / 5k	saturated	min(186mA, 192mA, 93mA)	9.8V - 93mA * 50 Ohms	9.3V / 10k

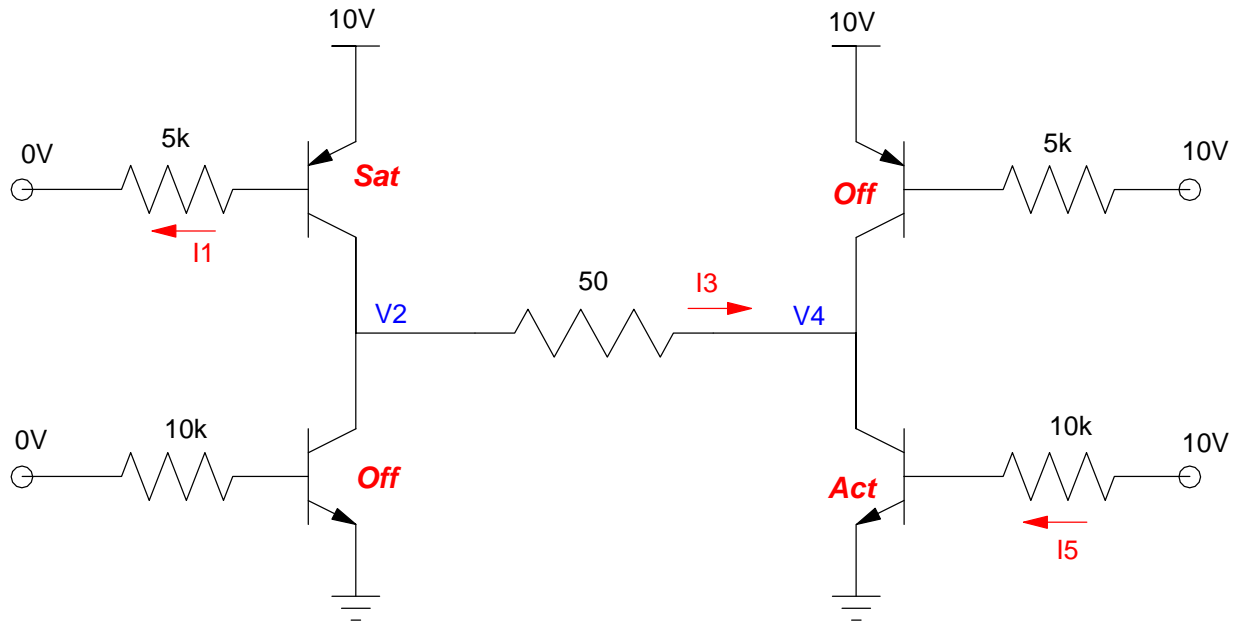

4) The following is a DTL NOR gate. Determine the currents and voltages. Assume ideal silicon transistors and diodes with

- $V_f = 0.7V$
- $V_{ce(sat)} = 0.2V$, and
- $\beta = 100$

I1	I2	V3	V4
0mA	390uA (6V - 2.1V) / 10k	5.4V	0.2V Beta Ib = 39mA max(Ic) = 10mA Beta * Ib > Ic (saturated)

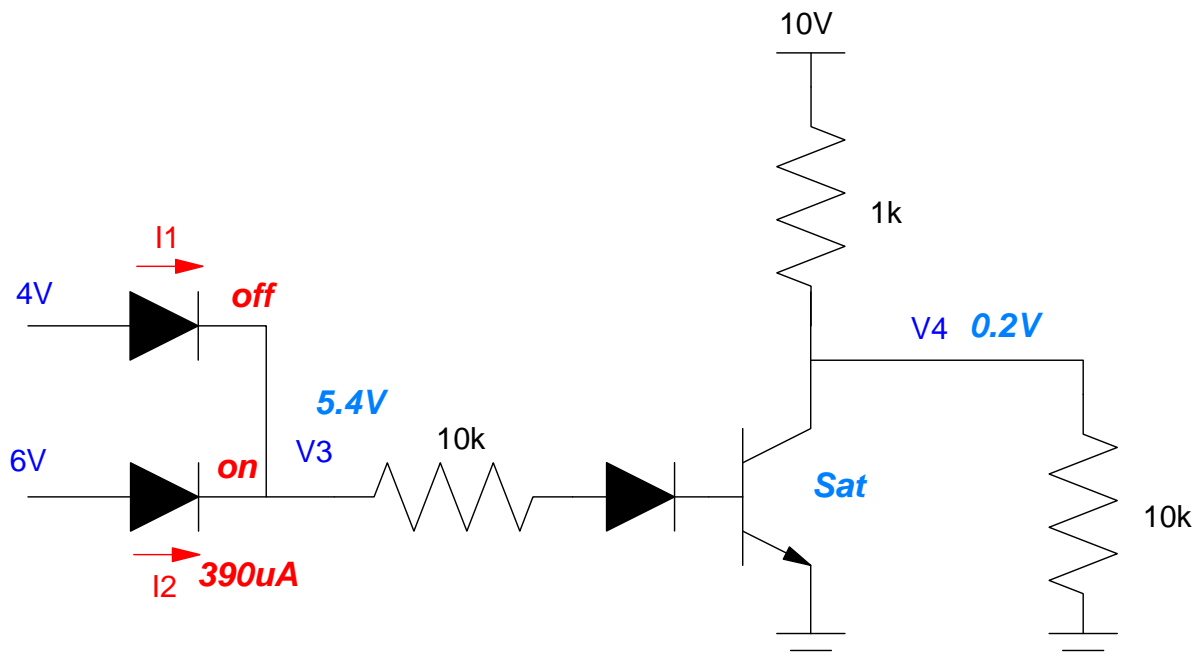


5) Design a Schmitt Trigger to turn a 1W LED on and off:

- Off ($I_c = 0\text{mA}$) when $V_{in} < 3\text{V}$
- On ($I_c = 300\text{mA}$) when $V_{in} > 4\text{V}$
- No change (on or off) for $3\text{V} < V_{in} < 4\text{V}$

Assume an ideal silicon diode, capable of 300mA , with $\beta = 100$

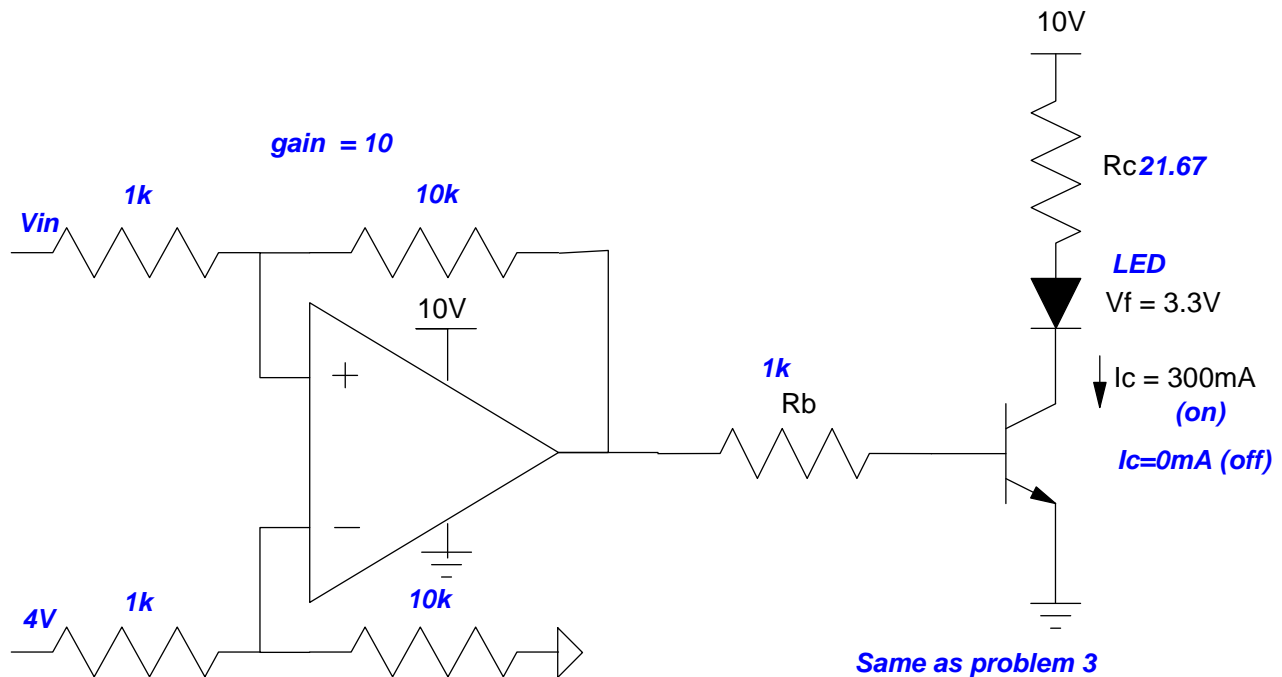Assume the op-amp outputs $0\text{V} / 10\text{V}$, capable of up to 20mA



Bonus! The wall between the U.S. and Mexico is estimated to cost \$2 trillion to build. For comparison, how much would it cost to build enough wind turbines to completely power the U.S. with wind energy?

400,000 1MW wind turbines would provide 4 trillion kWh assuming 100% utilization. This would cost \$400 billion.

You'll need more since the wind doesn't always blow and demand isn't constant. Maybe make that \$1 trillion (1/2 of the cost of a wall)