

# ECE 320 - Homework #2


Phasors Review. Due Monday January 23rd, 2017

1a) Convert the following circuit to phasor notation

- At DC ( $V_{in} = 15V$ )
- At 60Hz ( $V_{in} = 2 \sin(377t)$ )

1b) Solve for  $y(t)$  using phasors.

2) Check your answer in PartSim.

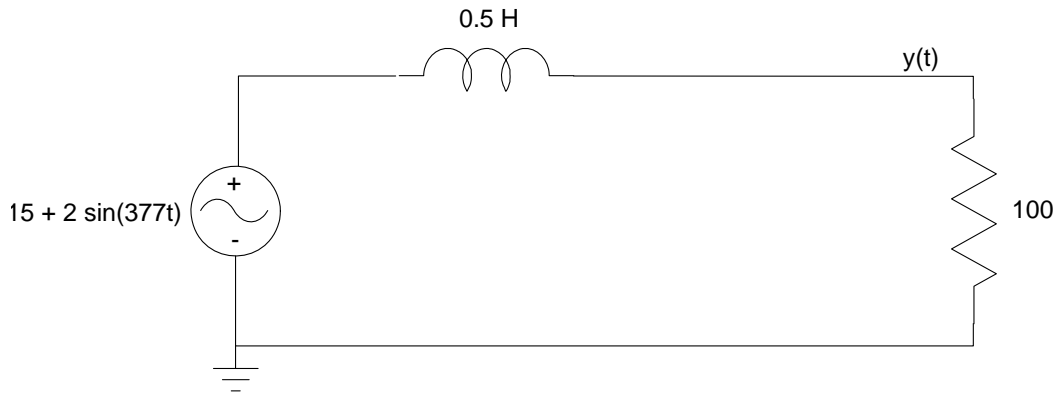


problem 1 & 2

3a) Convert the following circuit to phasor notation

3b) Solve for  $y(t)$  using phasors.

4) Check your answer in PartSim.

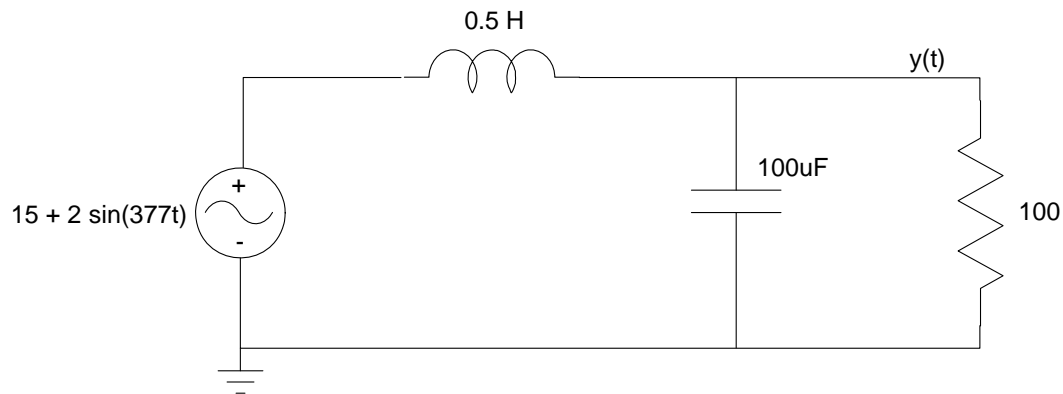

Problem 3 & 4

5) Determine the differential equation which satisfies the following transfer function

$$Y = \left( \frac{100}{(s+3)(s+10)} \right) X$$

6) Determine  $y(t)$  assuming  $x(t)$  is

$$x(t) = 3 + 4 \cos(5t)$$