

# ECE 320: Quiz #1 Name \_\_\_\_\_


9:00 / 11:00

Circuits I Review - January 19, 2016


1) Find the resistance between A and B

R =

262.5

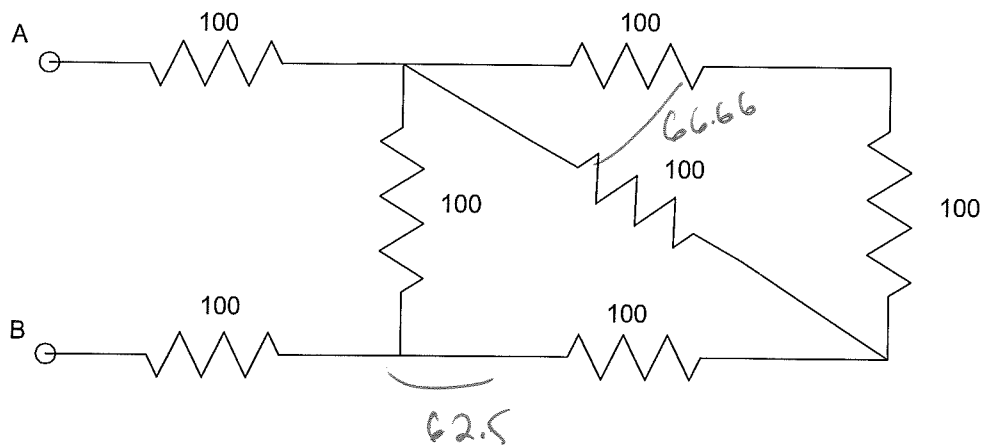

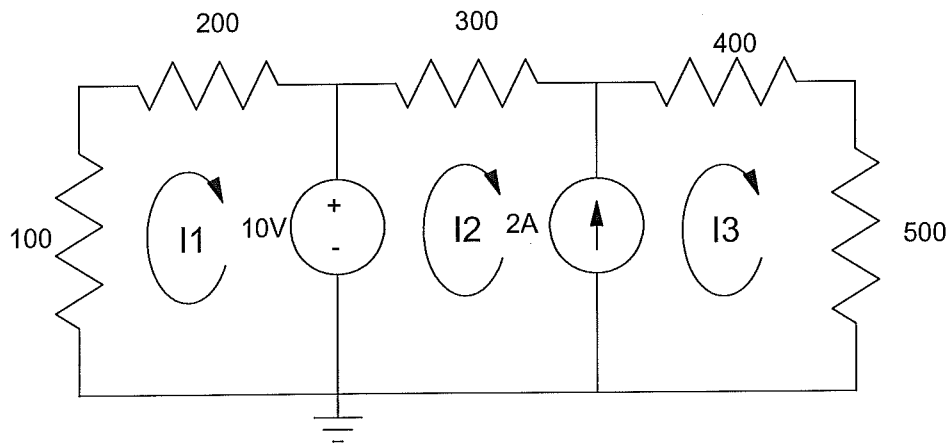2) Write 3 current loop equations that allow you to solve for  $I_1$ ,  $I_2$ , and  $I_3$ . You don't need to solve - just give the 3 equations.




$$100 I_1 + 200 I_1 + 10 = 0$$

$$I_3 - I_2 = 2$$

$$100 I_1 + 200 I_1 + 300 I_2 + 400 I_3 + 500 I_3 = 0$$

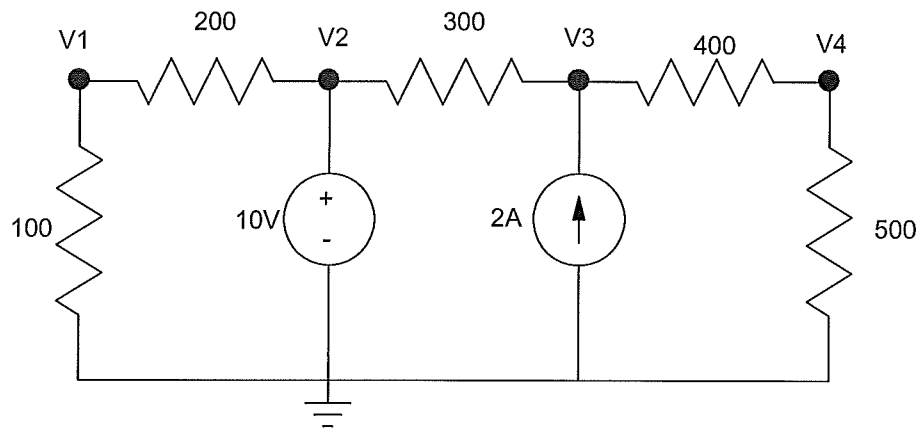3) Write 4 current loop equations that allow you to solve for  $V_1$ ,  $V_2$ ,  $V_3$ , and  $V_4$ . You don't need to solve - just give the 4 equations.



$$\frac{V_1}{100} + \frac{V_1 - V_2}{200} = 0$$



$$V_2 = 10$$

$$\frac{V_3 - V_2}{300} + \frac{V_3 - V_4}{400} - 2 = 0$$

$$\frac{V_4 - V_3}{400} + \frac{V_4}{500} = 0$$

4) Find the Thevenin equivalent for the following circuit:

Vth	Rth
6.25V	587.5

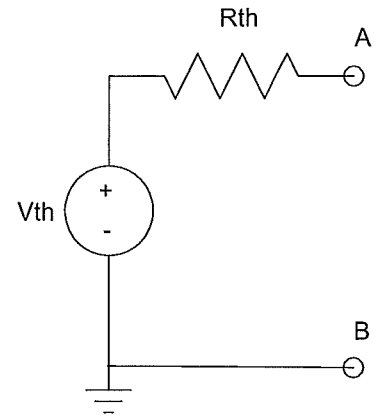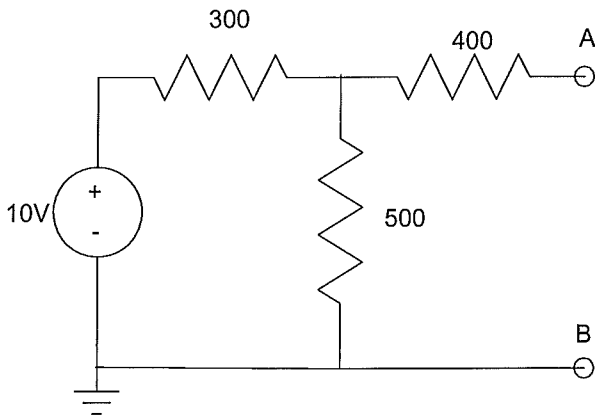


$$V_{th} = \left(\frac{5}{8}\right) 10 = 6.25V$$

$$R_{th} = 400 + 500 \parallel 300 = 587.5$$

5) Determine  $I_b$ ,  $I_c$ ,  $V_1$ , and  $V_2$

$I_b$	$I_c$	$V_1$	$V_2$
$24.6\mu A$	$2.46mA$	$4.975V$	$-2.315V$

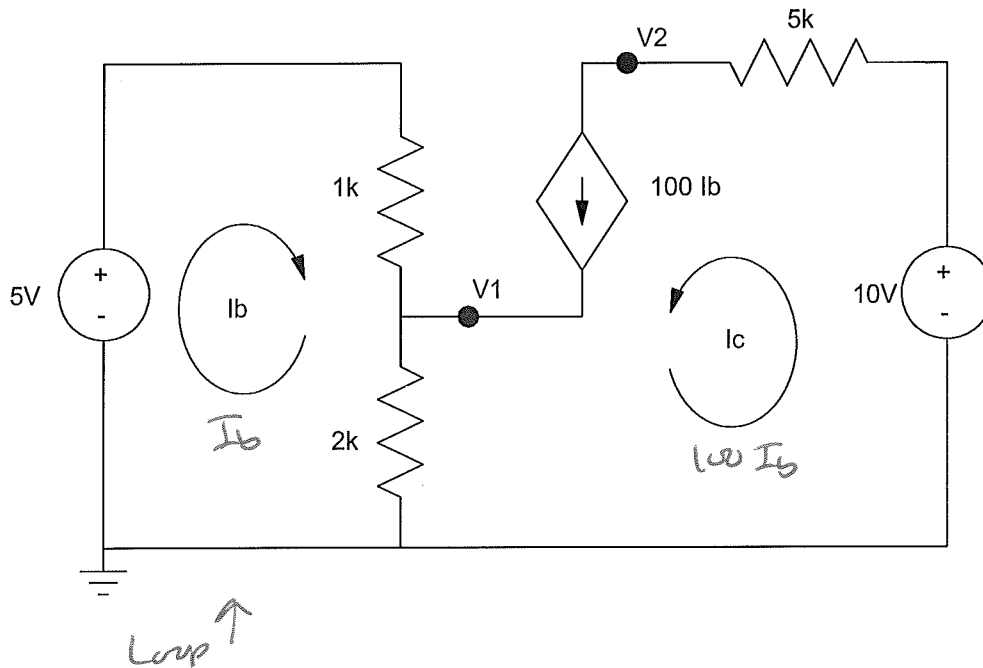

$$-5 + 1k \cdot I_b + 2k(I_b + 100I_b) = 0$$

$$I_b = \frac{5}{1k + 2k(101)} = 24.6\mu A$$

$$V_1 = (I_b + I_c) \cdot 2k$$

$$V_2 = 10 - 5k \cdot I_c = -2.315V$$

Bonus! Assume

- A typical cell phone uses 1 Watt-hour of energy per day (it has a 3V 1000mAh battery and it needs recharging every 3 days).
- There are 300 million people in the U.S., and
- It takes one pound of coal to produce 1kWh of electricity.

How many pounds of coal does it take to power the cell phones in the U.S. assuming every person has one?

$$\frac{1kWh}{1000Wh} \cdot 1.365 \frac{d}{y} \cdot 300 \text{ million} = 109 \cdot 10^6 \text{ lb coal/year}$$

$$= \frac{109 \cdot 10^6 \text{ lb coal/year}}{365 \text{ days/year}} = 298,630 \text{ lb coal/day}$$