


# ECE 320: Quiz #3: Name \_\_\_\_\_

9:00 - 11:00

Diodes, Ideal Diodes. February 2, 2017


- 1) Assume the VI characteristics for a diode are given in the following graph. Draw the load line for the following circuit and determine the voltage and current for the diode.

Load Line	$V_d$	$I_d$
show on graph	0.7V	72mA

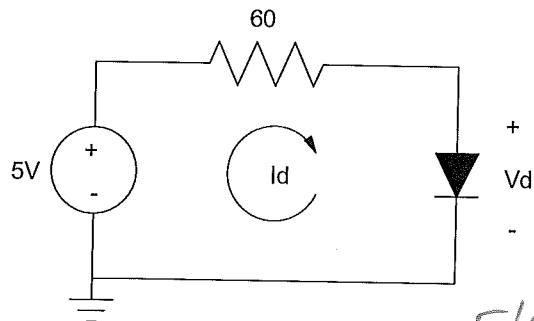


$$5/60 = 83.3 \text{ mA}$$

$I_d$  (mA)

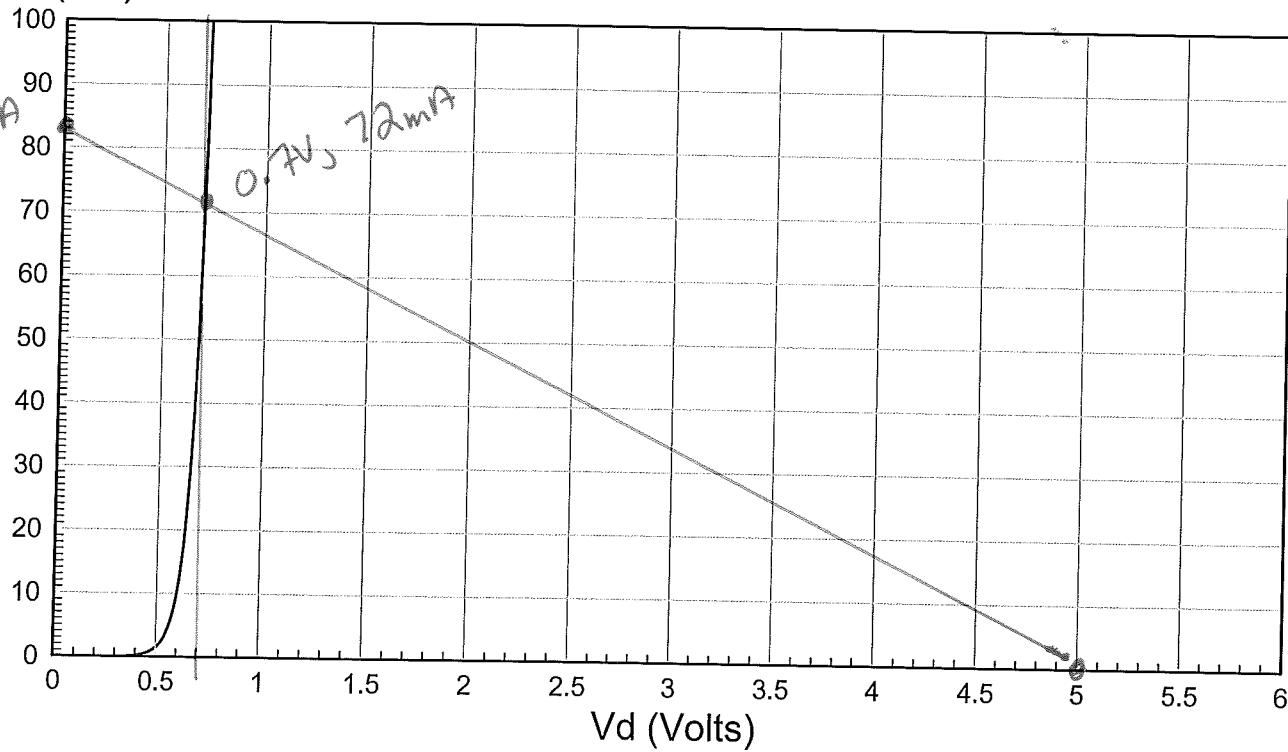

- 2) Assume an ideal diode with  $V_f = 0.7V$ . Determine the voltage and current for the following circuit.


$V_d$	$I_d$
0.7V	71.7 mA

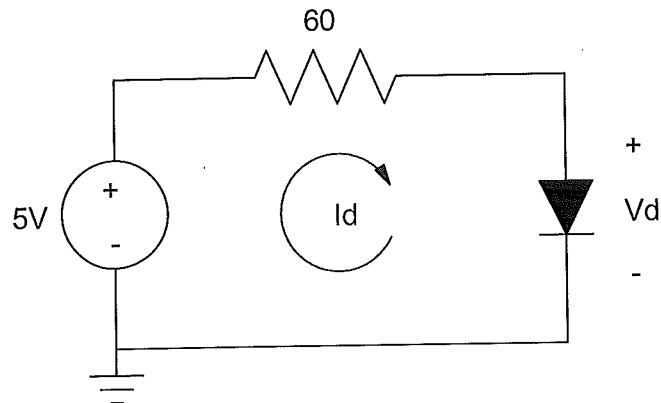

$$I_d = \frac{5 - 0.7}{60} = 71.7 \text{ mA}$$

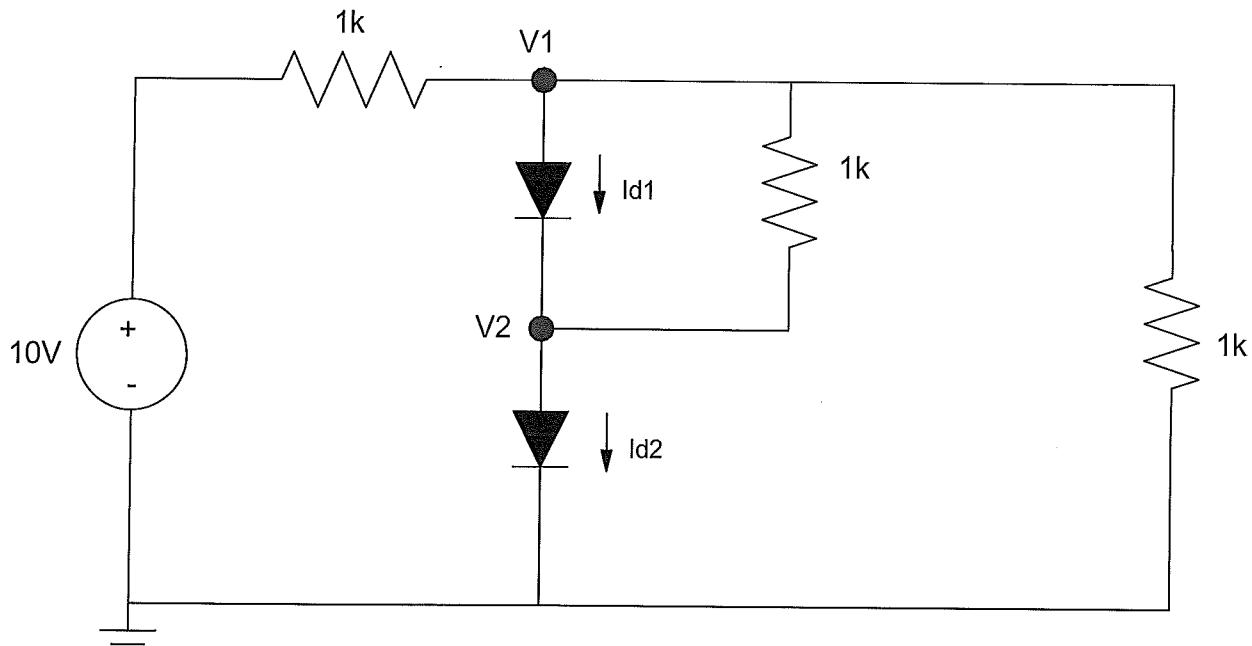3) Write N equations to solve for N unknowns for the following circuit. Assume the VI characteristics for the diodes are:

$$V_d = 0.052 \ln(10^7 I_d + 1) \quad I_d = 10^{-7} \left( \exp\left(\frac{V_d}{0.052}\right) - 1 \right)$$



$$I_{d1} = 10^{-7} \left( \exp\left(\frac{V_1 - V_2}{0.052}\right) - 1 \right)$$

$$I_{d2} = 10^{-7} \left( \exp\left(\frac{V_2 - V_1}{0.052}\right) - 1 \right)$$

$$\frac{V_1 - 10}{1000} + I_{d1} + \frac{V_1 - V_2}{1000} + \frac{V_1}{1000} = 0$$

$$-I_{d1} + I_{d2} + \frac{V_2 - V_1}{1000} = 0$$


- 4) Assume ideal diodes with  $V_f = 0.7V$ . Determine the currents  $I_1$ ,  $I_2$ ,  $I_3$ , and  $I_4$

$I_1$	$I_2$	$I_3$	$I_4$
$8.6\text{mA}$	$6.5\text{mA}$	$0.7\text{mA}$	$1.4\text{mA}$

$$\frac{(10 - 1.4)}{1000}$$

remainder


$$\frac{1.4 - 0.7}{1000}$$

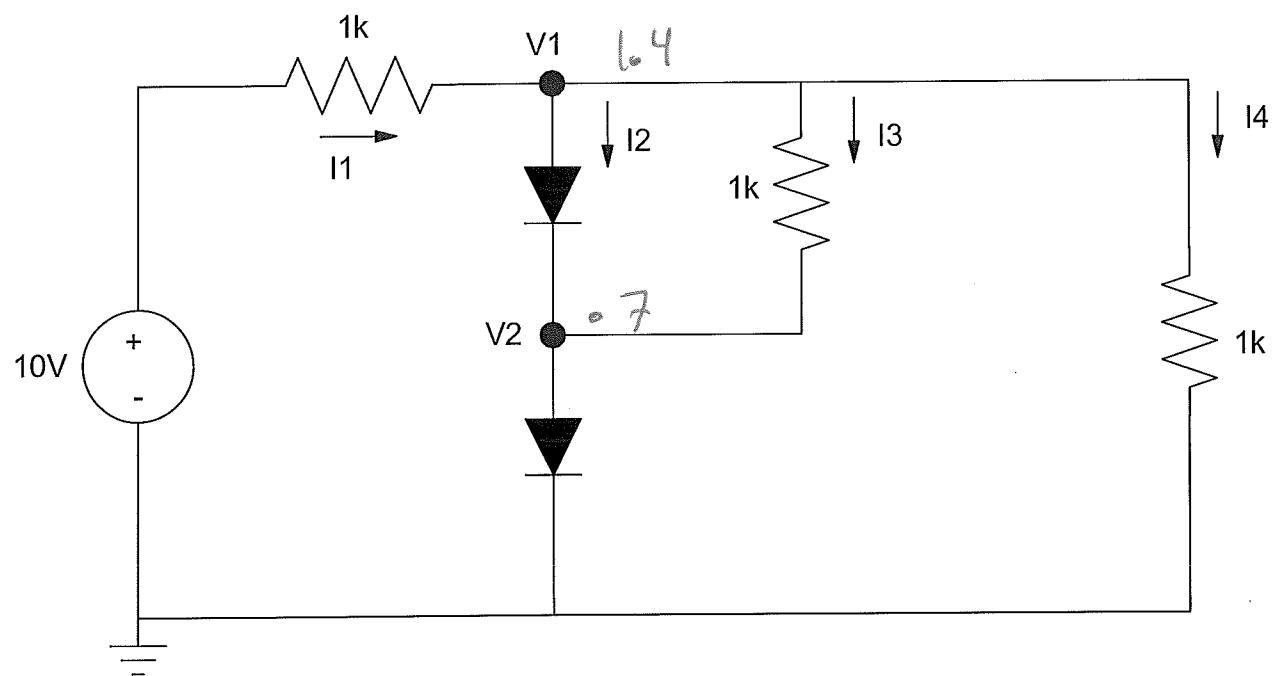

5) Assume ideal diodes with  $V_f = 0.7V$ . Determine the currents  $I_1$ ,  $I_2$ ,  $I_3$ , and  $I_4$

$I_1$	$I_2$	$I_3$	$I_4$
$1.1mA$	$0$	$0.2mA$	$0.9mA$

$$\frac{2 - .9}{1000} \text{ off}$$

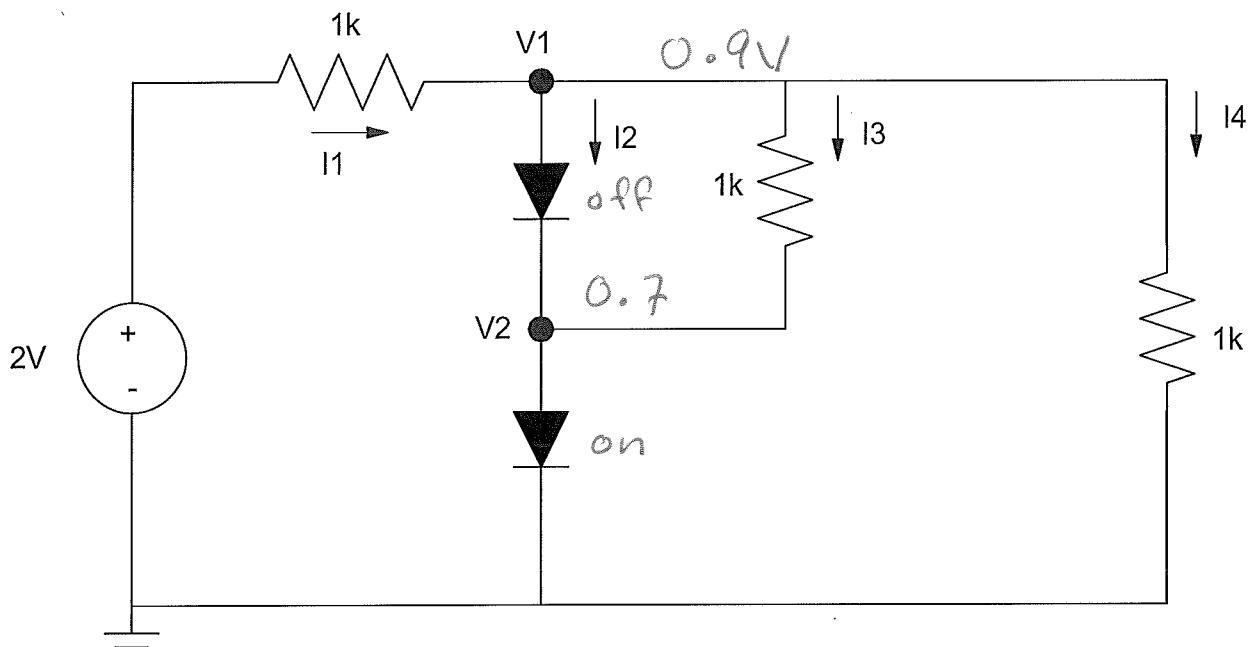

$$\frac{V_1 - 2}{1000} + \frac{V_1 - .7}{1000} + \frac{V_1}{1000} = 0$$

$$3V_1 = 2.7$$

$$V_1 = 0.9V$$

Assume a 600kW wind turbine, which costs \$600,000 to build, outputs on average 300kW of electricity.

- How many kWh of energy will that wind turbine produce over 10 years (the expected life of a typical wind turbine)?
- How many pounds of coal will that offset (1 pound of coal produces 1kWh of electricity)
- What is the gross revenue for this wind turbine assuming 10 cents a kWh for electricity?

(source: Danish Wind Energy Association)

$$(300\text{kw})(24\text{hr})(365\text{d})(10\text{y}) = 26.28 \text{ million kWh}$$

$$= 26.28 \text{ million lb coal}$$

$$= \$2.628 \text{ million}$$