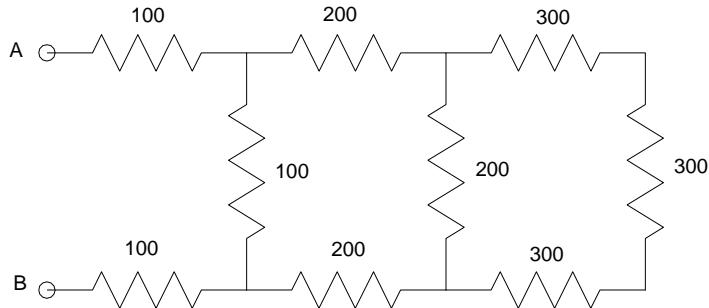


ECE 320 - Homework #1

EE 206 Review. Due Wednesday, January 18th, 2017

- 1) Determine the resistance between nodes A and B



Problem 1

Starting on the right:

$$300 + 300 + 300 = 900 \text{ Ohms}$$

$$900 \parallel 200 = 163.63 \text{ Ohms}$$

$$200 + 163.63 + 200 = 563.63 \text{ Ohms}$$


$$563.63 \parallel 100 = 84.93 \text{ Ohms}$$

$$100 + 94.93 + 100 = 284.93 \text{ Ohms}$$

ans: 284.93 Ohms

Current Loops:

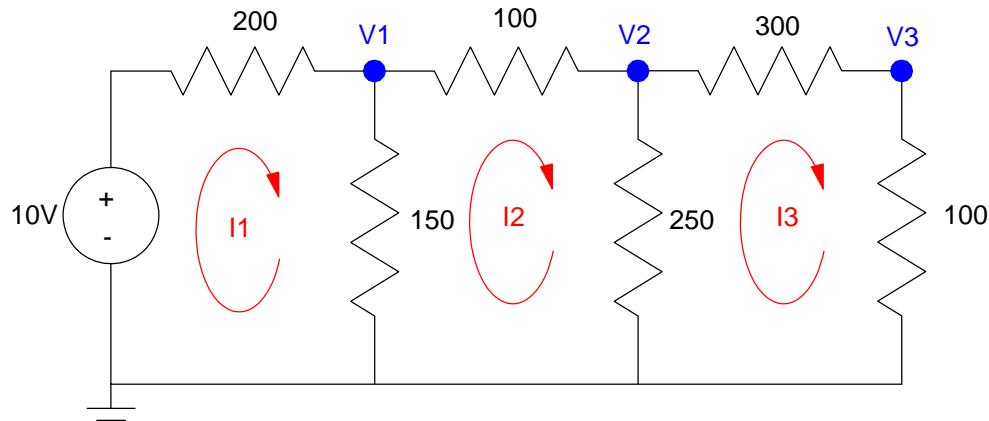2) Write the current loop equations for the following circuit



Loop I1:

$$-10 + 200I_1 + 150(I_1 - I_2) = 0$$

Loop I2:

$$150(I_2 - I_1) + 100(I_2) + 250(I_2 - I_3) = 0$$

Loop I3:

$$250(I_3 - I_2) + 300(I_3) + 100(I_3) = 0$$

3) Solve using Matlab (or similar program)

Grouping Terms:

$$350I_1 - 150I_2 = 10$$

$$-150I_1 + 500I_2 - 250I_3 = 0$$

$$-250I_2 + 650I_3 = 0$$

Put in Matrix Form:

$$\begin{bmatrix} 350 & -150 & 0 \\ -150 & 500 & -250 \\ 0 & -250 & 650 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$

```
->A = [ 350, -150, 0 ; -150, 500, -250 ; 0, -250, 650 ]
A =
```

$$\begin{array}{ccc} 350. & -150. & 0. \\ -150. & 500. & -250. \\ 0. & -250. & 650. \end{array}$$

```
-->B = [ 10; 0; 0 ]
```


B =

10.
0.
0.

-->I = inv(A)*B
I =

0.0339806
0.0126214
0.0048544


4) Check your answers in PartSim (or similar circuit simulator)

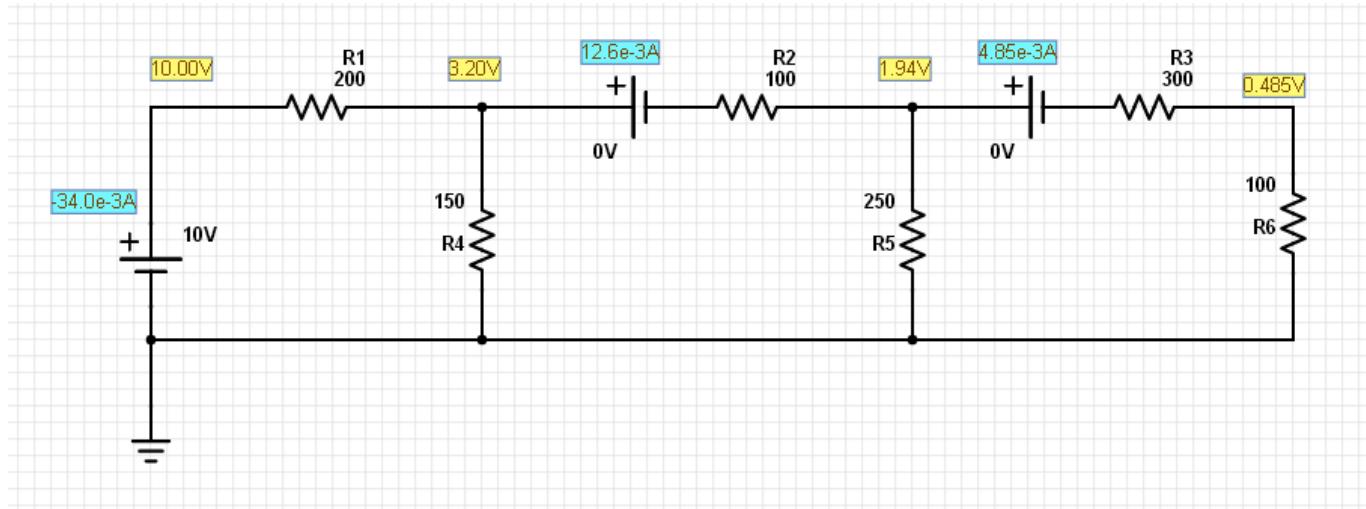

Problem 2-7

Voltage Nodes:

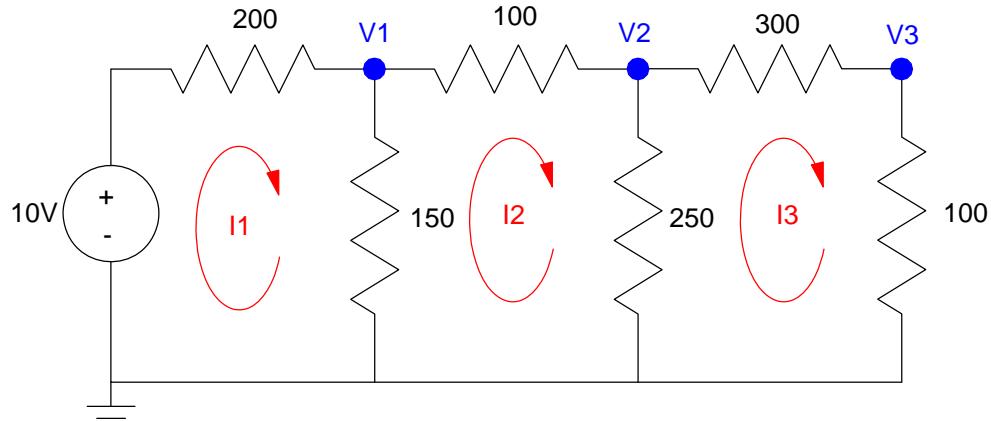5) Write the voltage node equations for the following circuit



Node V1:

$$\left(\frac{V_1 - 10}{200}\right) + \left(\frac{V_1}{150}\right) + \left(\frac{V_1 - V_2}{100}\right) = 0$$

Node V2:

$$\left(\frac{V_2 - V_1}{100}\right) + \left(\frac{V_2}{250}\right) + \left(\frac{V_2 - V_3}{300}\right) = 0$$

Node V3:

$$\left(\frac{V_3 - V_2}{300}\right) + \left(\frac{V_3}{100}\right) = 0$$

6) Solve using Matlab (or similar program)

Group terms

$$\left(\frac{1}{200} + \frac{1}{150} + \frac{1}{100}\right)V_1 + \left(\frac{-1}{100}\right)V_2 = \left(\frac{10}{200}\right)$$

$$\left(\frac{-1}{100}\right)V_1 + \left(\frac{1}{100} + \frac{1}{250} + \frac{1}{300}\right)V_2 + \left(\frac{-1}{300}\right)V_3 = 0$$

$$\left(\frac{-1}{300}\right)V_2 + \left(\frac{1}{100} + \frac{1}{300}\right)V_3 = 0$$

Put in matrix form

$$\begin{bmatrix} \left(\frac{1}{200} + \frac{1}{150} + \frac{1}{100}\right) & \left(\frac{-1}{100}\right) & 0 \\ \left(\frac{-1}{100}\right) & \left(\frac{1}{100} + \frac{1}{250} + \frac{1}{300}\right) & \left(\frac{-1}{300}\right) \\ 0 & \left(\frac{-1}{300}\right) & \left(\frac{1}{100} + \frac{1}{300}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} \left(\frac{10}{200}\right) \\ 0 \\ 0 \end{bmatrix}$$

Solve in Matlab

```
-->A = [1/200+1/150+1/100,-1/100,0];  
-->A = [A; -1/100,1/100+1/250+1/300,-1/300];  
-->A = [A; 0, -1/300,1/100+1/300]  
A =  
  
0.0216667  - 0.01      0.  
- 0.01       0.0173333  - 0.0033333  
0.          - 0.0033333  0.0133333  
  
-->B = [10/200;0;0]  
B =  
  
0.05  
0.  
0.  
  
-->V = inv(A)*B  
V =  
  
3.2038835  
1.9417476  
0.4854369
```

7) Check your answers in PartSim (or similar circuit simulator)

