ECE 320 - Homework #2

Phasors Review. Due Monday January 23rd, 2017

1a) Convert the following circuit to phasor notation





1b) Solve for y(t) using phasors.

Vin = 15:

w = 0

$$L \rightarrow j\omega L = j0$$

By voltage division:

$$y = \left(\frac{100}{100+j0}\right) \cdot 15 = 15$$

 $Vin = 2 \sin(377t)$

w = 377 $L \rightarrow j\omega L = j188.5$ $V_{in} = 2\sin(377t) \rightarrow 0 - j2$ by voltage division

$$Y = \left(\frac{100}{100+j188.5}\right) \cdot (0-j2)$$

$$Y = 0.9373 \angle -152^{0}$$

$$y(t) = 0.9373 \cos(377t - 152^{0})$$

To get the total input, add the two inputs together.

To get the total output, add the two outputs together

 $y(t) = 15 + 0.9373\cos(377t - 152^{\circ})$

2) Check your answer in PartSim.



PartSim Circuit



PartSim Transient Response. Vin (blue) and Y (black)

As expected

- The DC level of Vout = 15V
- The peam if 0.973V above the DC level (0.9373 computed)
- The output is a cosine delayed by about 135 degrees (-152 degrees computed)

- 3a) Convert the following circuit to phasor notation
- 3b) Solve for y(t) using phasors.



Phasor Representation at w = 0 (blue) and w = 377 (red)

$$Vin = 15$$

w = 0

$$L \rightarrow j\omega L = j0$$

 $C \rightarrow \frac{1}{j\omega C} = -j\infty$

By voltage division

$$Y = \left(\frac{100}{100+j0}\right)15 = 15$$

Vin = 2sin(377t)

w = 377

$$V_{in} = 2\sin(377t) \rightarrow 0 - j2$$

 $L \rightarrow j\omega L = j188.5$
 $C \rightarrow \frac{1}{j\omega C} = -j26.5$

By voltage division

$$-j26.5||100 = 25.63 \angle -75^{\circ}$$
$$Y = \left(\frac{25.63 \angle -75^{\circ}}{25.63 \angle -75^{\circ} + j188.5}\right) \cdot (0 - j2) = 0.313 \angle 107^{\circ}$$
$$y(t) = 0.313 \cos \left(377t + 107^{\circ}\right)$$

To get the total input, add the two inputs together.

To get the total output, add the two outputs together

$$y(t) = 15 + 0.313\cos(377t + 107^{\circ})$$

4) Check your answer in PartSim.



PartSim Circuit



PartSim Transient Response showing Vin (blue) and Y (black)

As expected

- The DC level of Vout = 15V
- The peam if 0.297V above the DC level (0.313 computed)
- The output is a cosine delayed by about 260 degres (-253 degrees = +107 degrees computed)

5) Determine the differential equation which satisfies the following transfer function

$$Y = \left(\frac{100}{(s+3)(s+10)}\right)X$$

Multiply out and cross multiply

,

$$(s^2 + 13s + 30)Y = 100X$$

meaning

$$\frac{d^2y}{dt^2} + 13\frac{dy}{dt} + 30y = 100x$$

.

or using prime notation

$$y'' + 13y' + 30y = 100x$$

6) Determine y(t) assuming x(t) is

$$x(t) = 3 + 4\cos(5t)$$

Use superposition

$$x(t) = 3$$

$$s = 0$$

$$\left(\frac{100}{(s+3)(s+10)}\right)_{s=0} = 3.333$$

Output = gain * input

$$Y = (3.333) \cdot 3 = 10$$

 $y(t) = 4\cos(5t)$

s = j5

$$\left(\frac{100}{(s+3)(s+10)}\right)_{s=j5} = 1.533 \angle -85.6^{\circ}$$

Output = gain * input
 $Y = (1.533 \angle -85.6^{\circ}) \cdot (4\cos(5t))$
 $y(t) = 6.13\cos(5t - 85.6^{\circ})$

Add the two inputs together to get the total input Add the two outputs together to get the total output

$$y(t) = 10 + 6.13\cos(5t - 85.6^{\circ})$$