

ECE 320 - Final pt2. Name _____


Transistors and Op-Amps. April 11, 2018

1) A silicon transistor has the following characteristics:

- $V_{be} = 0.7V$ when $I_{be} > 0$
- $V_{ce:sat} = 0.2V$
- $\beta = 100$

Draw the load-line for the following circuit and determine the operating point when $V_{in} = 1V$, $5V$, and $10V$.

Load Line	(V_{ce} , I_c) when $V_{in} = 1V$	(V_{ce} , I_c) when $V_{in} = 5V$	(V_{ce} , I_c) when $V_{in} = 10V$
show on graph	show on graph	show on graph	show on graph

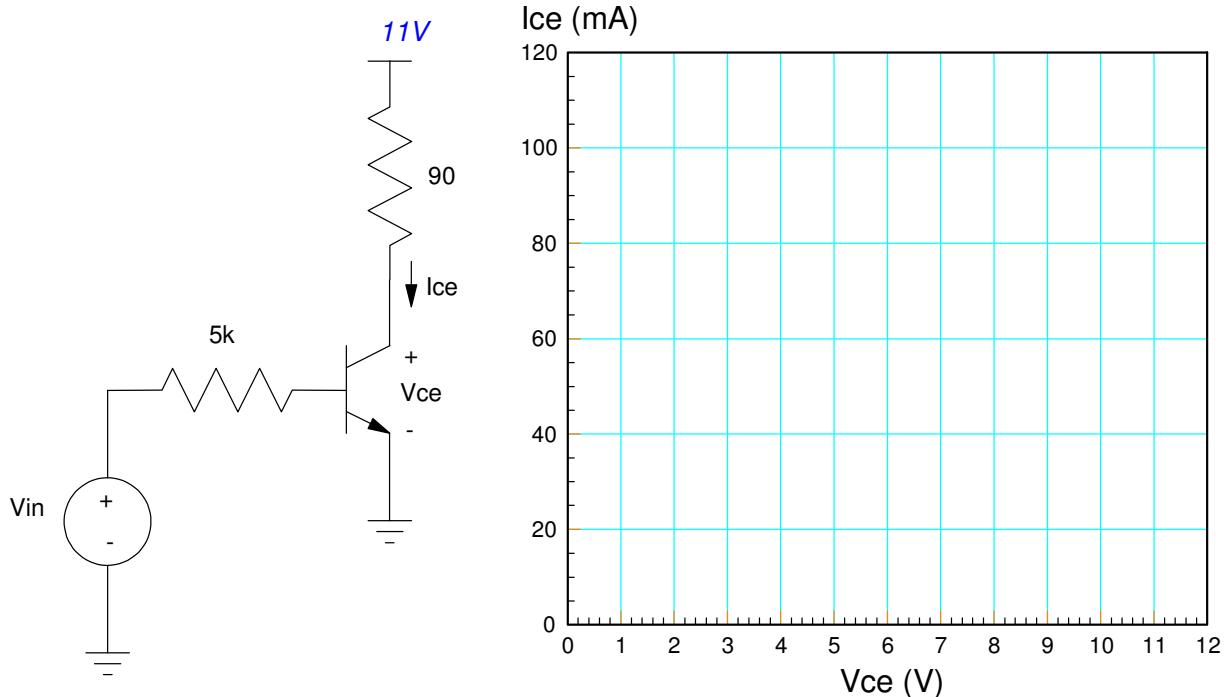

2) Determine R_c and the range of R_b so that the following transistor switch allows the input to turn on and off the current to an LED

- Off current = 0mA
- On Current = 250mA

Assume the LED has the following characteristics


- $V_f = 3V @ 200mA$

Assume the transistor has the following characteristics

- $V_{be(on)} = 0.7V$
- $V_{ce(sat)} = 0.2V$

The input can supply at most 20mA


$\min(R_b)$ Smallest R_b can be	$\max(R_b)$ Largest R_b can be	R_c Current = 250mA when $V_{in} = 5V$

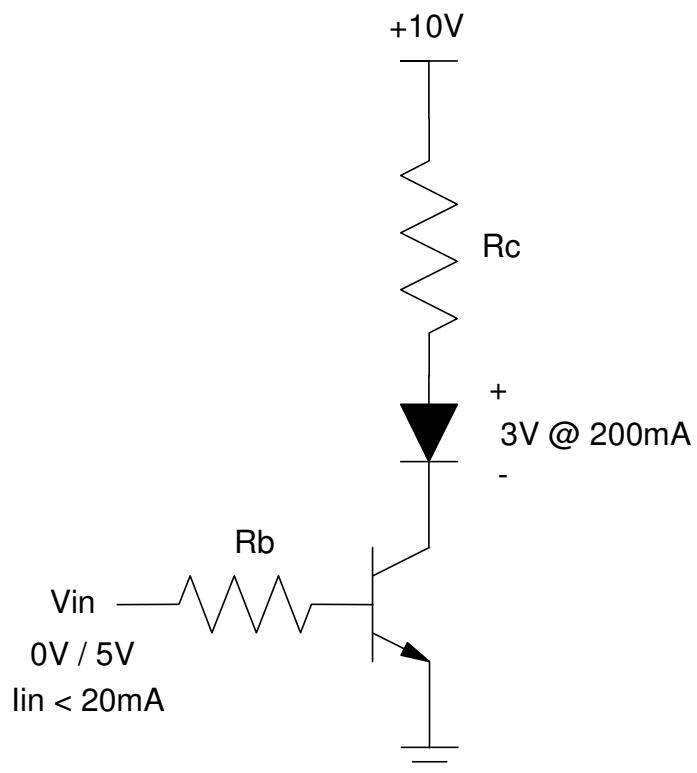

3) Determine the voltages and currents to the followign H-bridge. Assume


- $|V_{be(on)}| = 0.7V$
- $|V_{ce(sat)}| = 0.2V$
- $\beta = 100$

I1	Va	I3	Vb	I5

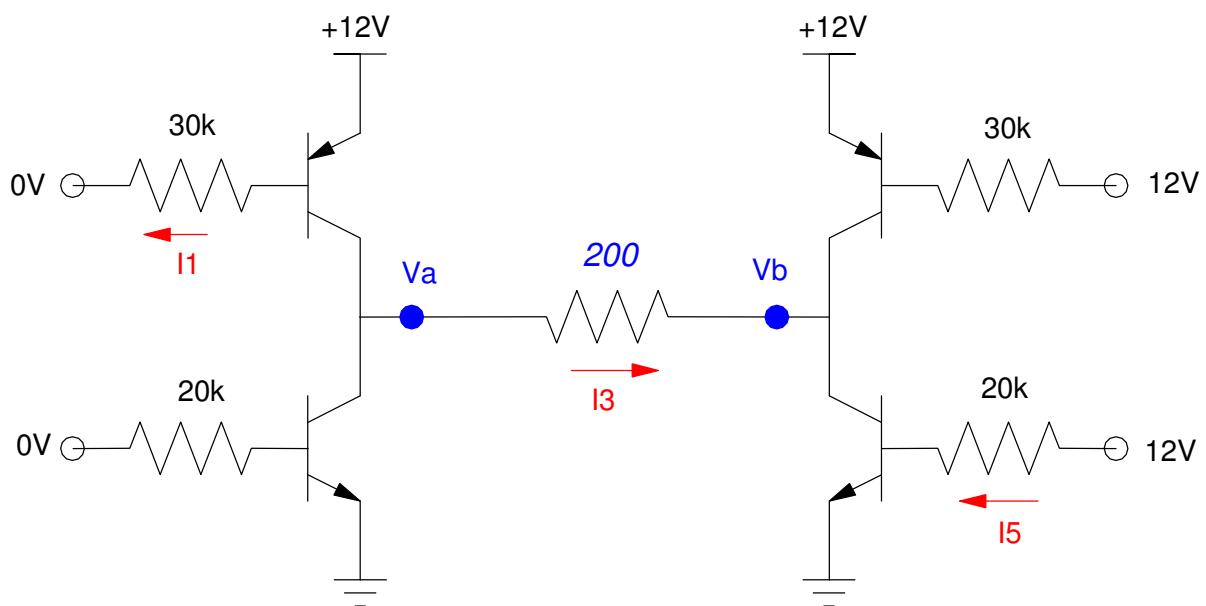

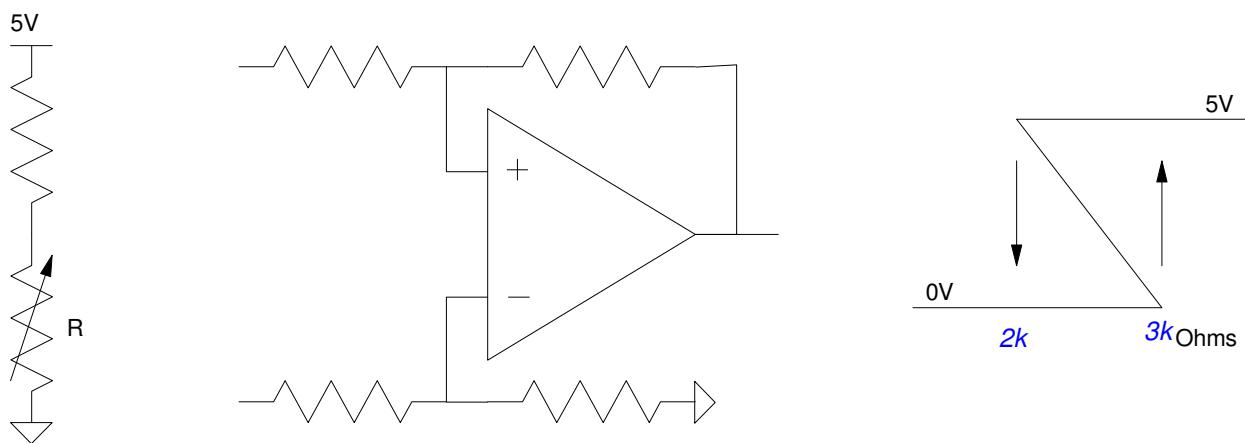4) Design a Schmitt Trigger so that the output is


- 5V when $R > 3k$
- 0V when $R < 2k$
- No change for $2k < R < 3k$



5) Determine the voltages and currents for the following DTL NAND gate. Assume

- Ideal silicon diodes ($V_f = 0.7V$)
- $\beta = 100$
- $V_{ce(sat)} = 0.2V$

I1	I2	Va	Vb

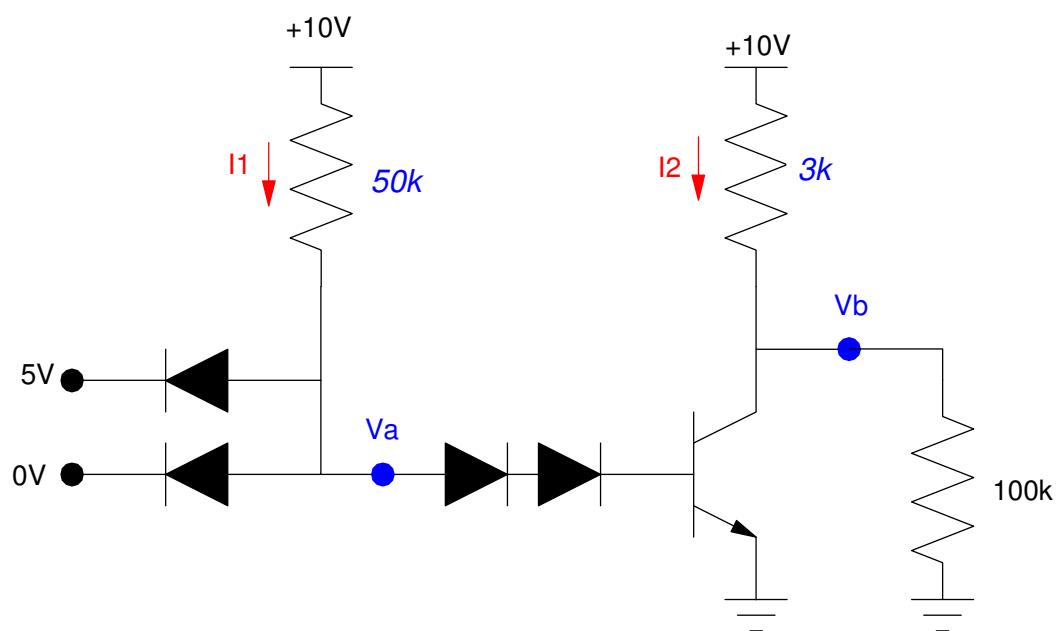

6) The following connects two transistors as a Darlington pair. Determine the voltages and currents. Assume

- Ideal silicon diodes ($V_f = 0.7V$)
- $\beta = 100$

V1	V2	V3	I4	I5

