ECE 320 - Homework #7

SCR, Op-Amp Amplifiers. Due Monday, February 26th, 2018

SCR

1) Assume a firing angle of 50 degrees. Determine the voltages (DC and AC) at V1 and V2.



DC:

$$V_{1} \approx \frac{1}{\pi} \left(\int_{0}^{0.8272} (-0.7) \cdot dt + \int_{0.8272}^{\pi} 169.7 \sin(t) \cdot dt \right)$$
$$V_{1} \approx \frac{1}{\pi} (-0.579 + 169.7 (-\cos(t))_{0.8272}^{\pi})$$
$$V_{1} \approx -0.1843 + 54.01 (1 + \cos(50^{\circ}))$$
$$V_{1} \approx 88.55V$$

note: The voltage is large enough that the 0.7V drop from the diode for 50 degrees doesn't have much effect on the output. You could also use

$$V_1 \approx \left(\frac{1+\cos\theta}{\pi}\right) V_p$$
$$V_1 \approx 88.74V$$

AC:

$$max (V_1) = 169.7 - 1.4 = 168.3V$$
$$min(V_1) = -0.7V$$
$$V_{1pp} = 169V_{pp}$$

AtV2:

$$\omega = 120Hz = 754 \frac{rad}{sec}$$
$$L \rightarrow j\omega L = j75.4\Omega$$
$$C \rightarrow \frac{1}{j\omega C} = -j0.66\Omega$$

R in parallel with C is

$$\left(\frac{1}{5} + \frac{1}{-j0.66}\right)^{-1} = 0.0864 - j0.6571\Omega$$

By voltage division

$$V_{2pp} = \left(\frac{(0.0864 - j0.6571)}{(0.0864 - j0.6571) + j75.4}\right) V_{1pp}$$
$$V_{2pp} = 1.486 \angle -172^{0}$$

All we care about is the amplitude

$$V_2 = 1.486 V_{pp}$$

- 2) (Not Assigned). Use a transistor as a switch to turn on and off a full-wave rectified sine wave.
 - NPN transistors act as switches to ground (+Vcc = on, 0V = off)
 - PNP transistors act as switches to power: (+Vcc = off, 0V = on)



For a resistive load, this results in ...



Looks good: Adding in C and L







V2(DC) = 83V (approx)V2(AC) = 1.22Vpp (approx)

3) Determine the firing angle, C, and L so that

The DC voltage at the load is 50V

$$V_1 \approx \left(\frac{1+\cos\theta}{\pi}\right) V_p$$

$$50 \approx \left(\frac{1+\cos\theta}{\pi}\right) 169$$

$$\theta = 94.04^0$$

The ripple at the load is 1Vpp

 $\max (V_1) = 169.7 \cdot \sin (94.04^0) - 1.4V$ $\max(V_1) = 167.9V$ $\min(V_1) = -0.7V$ $V_{1pp} = 168.6V_{pp}$

Pick L to make the ripple 20x smaller (somewhat arbitrary)

$$|j\omega L| = 20R$$
$$\omega L = 100$$
$$L = \frac{100}{754} = 132.6mH$$

This should result in a ripple at V2 that is 20x smaller

$$V_2 = \frac{168.6}{20} = 8.42 V_{pp}$$

To bring the ripple down to 1Vpp, add a capacitor which is 8.42 times smaller than R

$$\frac{1}{\omega C} = \frac{1}{8.42} \cdot 5\Omega$$
$$\frac{1}{\omega C} = 0.5932$$
$$C = 2235 \mu F$$

4) For the following op-amp circuit with a gain of 'only' 2000:



a) Write the voltage node equations

$$\begin{pmatrix} \frac{V_p - 2}{1k} \end{pmatrix} + \begin{pmatrix} \frac{V_p}{2M} \end{pmatrix} = 0$$
$$\begin{pmatrix} \frac{V_m}{2M} \end{pmatrix} + \begin{pmatrix} \frac{V_m}{1k} \end{pmatrix} + \begin{pmatrix} \frac{V_m - Y}{2k} \end{pmatrix} = 0$$
$$\begin{pmatrix} \frac{Y - V_3}{75} \end{pmatrix} + \begin{pmatrix} \frac{Y - V_m}{2k} \end{pmatrix} + \begin{pmatrix} \frac{Y}{1k} \end{pmatrix} = 0$$
$$V_3 = 2000(V_p - V_m)$$

b) Solve for the voltages at Vp, Vm, and Y

Multiply each equation by 1000 and separate terms

$$1.0005V_p = 2$$

$$1.5005V_m - 0.5Y = 0$$

$$14.8333Y - 13.333V_3 - 0.5V_m = 0$$

$$V_3 - 2000V_p + 2000V_m = 0$$

Place in matrix form

$$\begin{bmatrix} 1.005 & 0 & 0 & 0 \\ 0 & 1.5005 & 0 & -0.5 \\ 0 & -0.5 & -13.333 & 14.8333 \\ -2000 & 2000 & 1 & 0 \end{bmatrix} \begin{bmatrix} V_p \\ V_m \\ V_3 \\ Y \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve

```
--->A = [1.005,0,0,0 ; 0,1.5005,0,-0.5 ; 0,-0.5,-13.3333,14.83333 ; -2000,2000,1,0]
A =
1.005 0. 0. 0.
0. 1.5005 0. - 0.5
```

```
0. - 0.5 - 13.3333 14.83333

- 2000. 2000. 1. 0.

-->B = [2;0;0;0]

B =

2.

0.

0.

0.

-->V = inv(A)*B

V =

1.9900498 Vp

1.9867705 Vm

6.5585677 V3

5.9622982 Y
```

- 5) For the following op-amp circuit

 - a) Write the voltage node equationsb) Solve for the voltages at Vp, Vm, and Y

Assume an ideal op-amp.



$$V_p = 2V$$
$$V_p = V_m$$
$$\left(\frac{V_m}{1k}\right) + \left(\frac{V_m - Y}{2k}\right) = 0$$

Solving

$$Y = \left(1 + \frac{2k}{1k}\right) 2V$$
$$Y = 6V$$

The previous answer was 5.9622V. About the same

6) Assume ideal op-amps. Write the voltage node equations for the following circuit



The impedance of a capacitor is $\frac{1}{Cs}$

$$V_{3} = V_{2}$$

$$\left(\frac{V_{1}-V_{0}}{R}\right) + \left(\frac{V_{1}-V_{2}}{R}\right) + \left(\frac{V_{1}-V_{4}}{1/Cs}\right) = 0$$

$$\left(\frac{V_{2}-V_{1}}{R}\right) + \left(\frac{V_{2}}{1/Cs}\right) = 0$$

$$\left(\frac{V_{3}}{R_{b}}\right) + \left(\frac{V_{3}-V_{4}}{R_{a}}\right) = 0$$