

# **ECE 320: Final - Part 1. Name** \_\_\_\_\_

Semiconductors & Diodes - March 21, 2019

1a) Define the following terms:



p-type semiconductor

n-type semiconductor

Why does the resistance of silicon decrease as temperature increases?


- 2) The VI characteristics for an LED is shown below. Draw the load line for the following circuit and determine the operating point.

Load Line	$V_d$	$I_d$
show on graph		

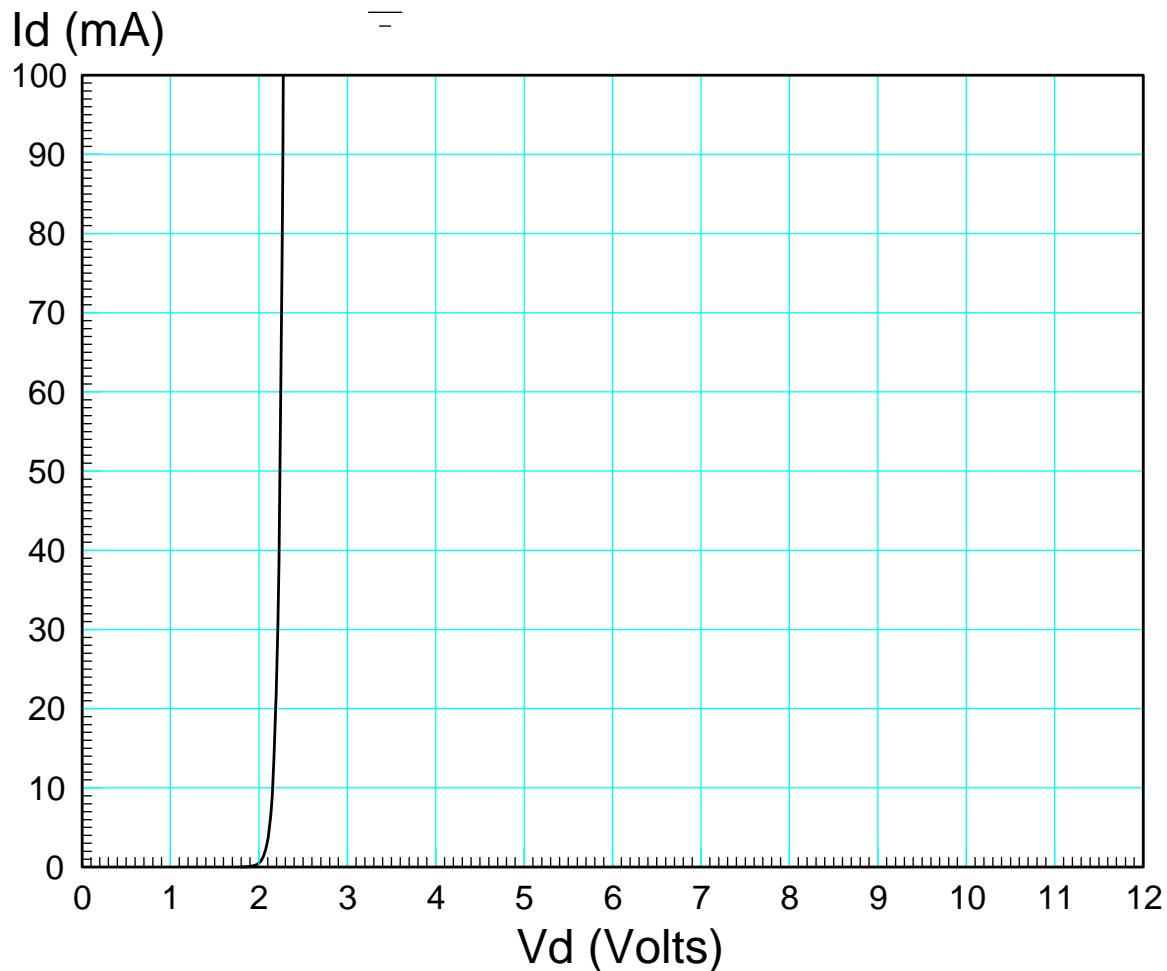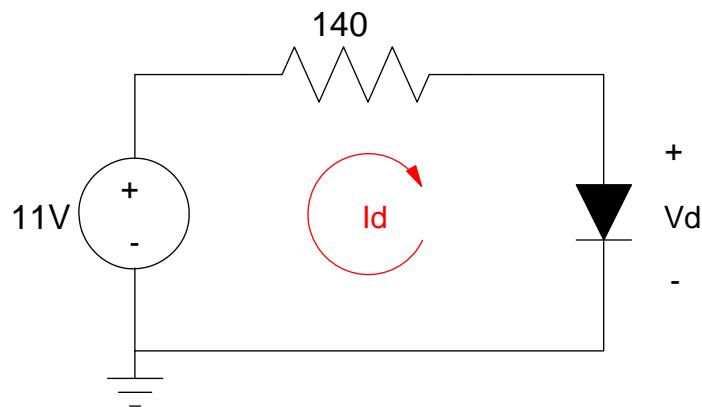


3) Assume ideal silicon diodes ( $V_f = 0.7V$ ). Determine the currents,  $I_1 - I_4$

$I_1$	$I_2$	$I_3$	$I_4$

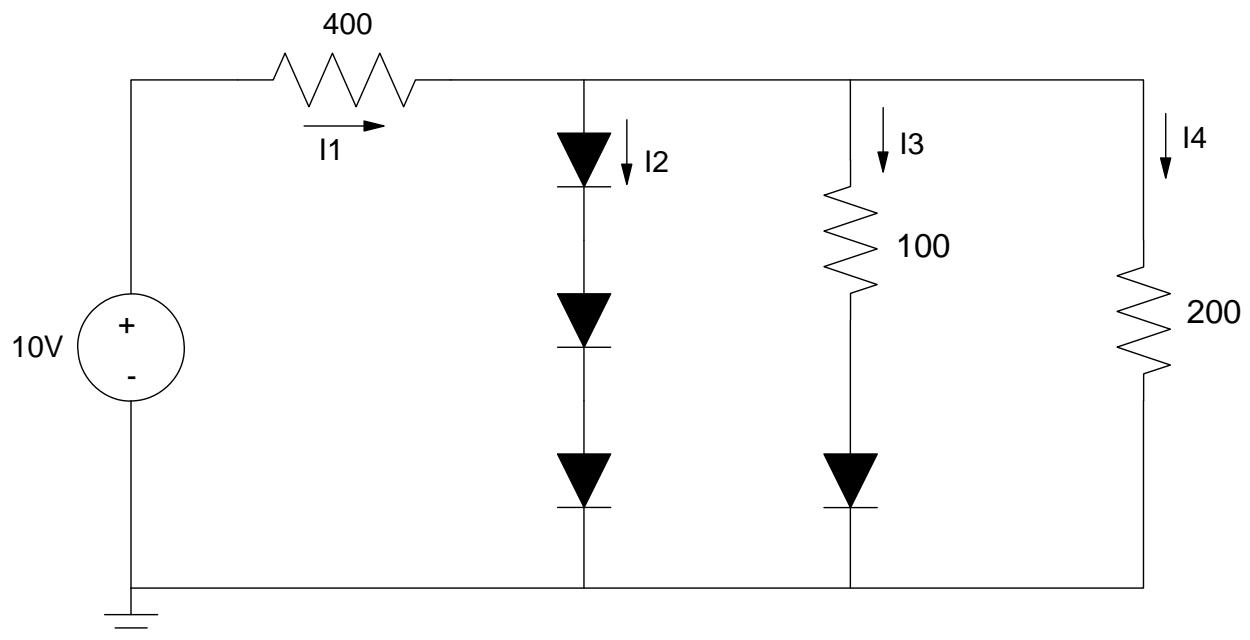


4) Assume ideal silicon diodes ( $V_f = 0.7V$ ). Determine the currents, I1 - I4

I1	I2	I3	I4

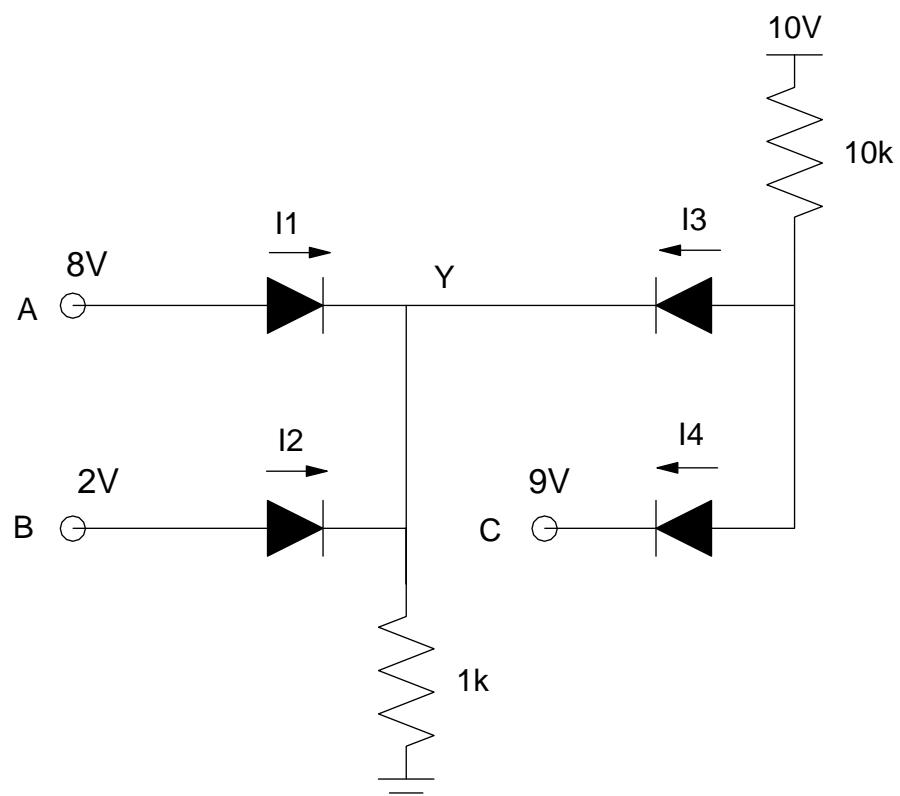

5) For the following AC to DC converter, determine the following

V1 (peak)	V1pp (AC)	V2 (DC)	V2pp (AC)

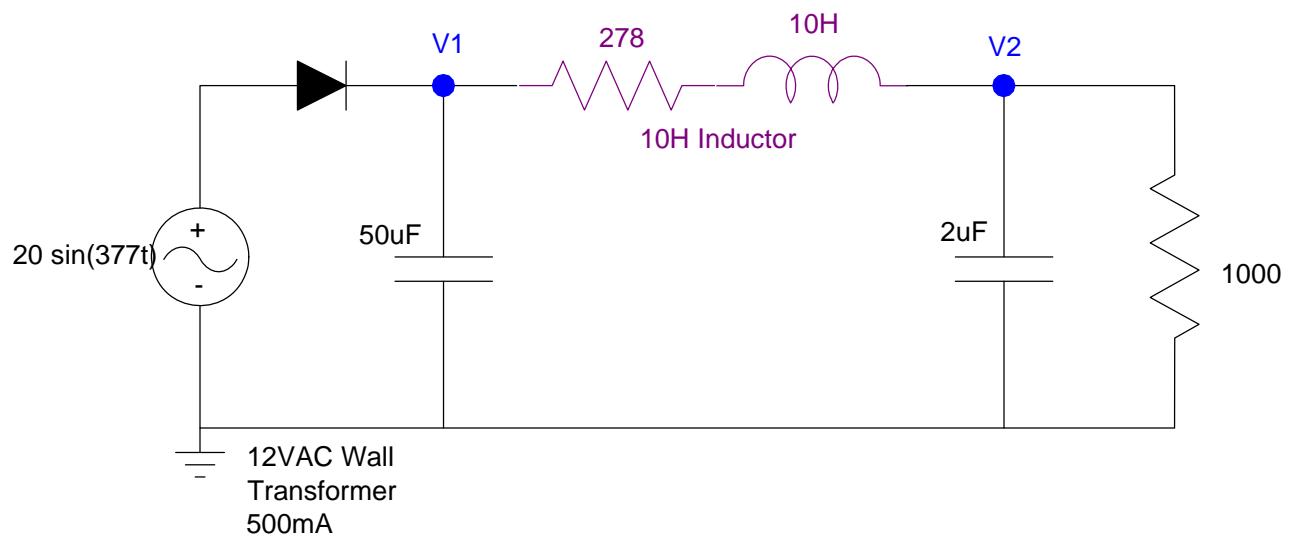


# ECE 320: Final - Part 2. Name \_\_\_\_\_

BJT Transistors & MOSFET Circuits - March 22, 2019

- 1) The VI characteristics for an NPN transistor are shown below. Draw the load-line and mark the operating point for  $V_{in} = \{0V, 5V, 10V\}$

Load Line	a) $V_{in} = 0V$	b) $V_{in} = 5V$	c) $V_{in} = 10V$
show on graph	show on graph	show on graph	show on graph

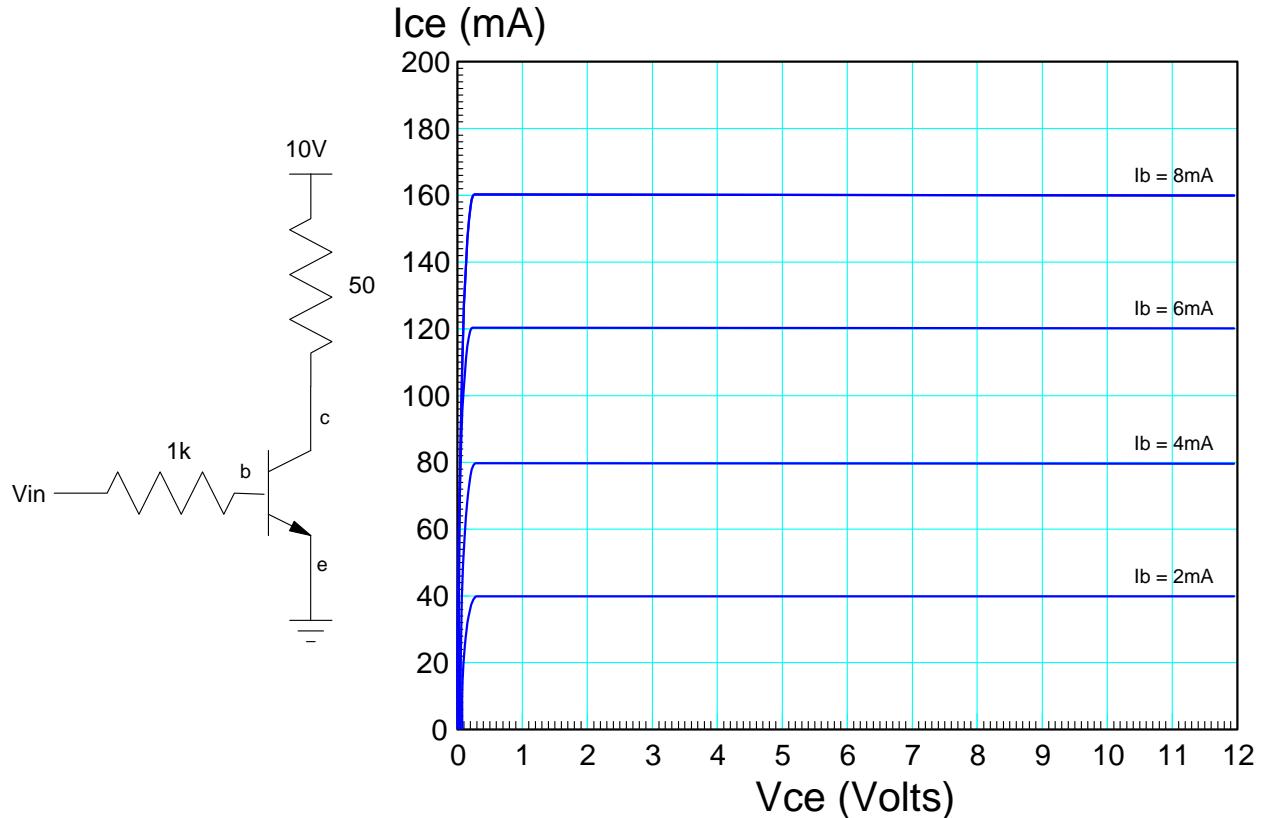


2) Transistor Switch: A circuit to allow a function generator to turn on and off an LED is shown below.

- $V_{in} = 5V$ : LED is on ( $I_c = 100mA$ )
- $V_{in} = 0V$ : LED is off ( $I_c = 0mA$ )

Find the range of  $R_b$  and  $R_c$  for this circuit to work as a switch. Assume


- $V_{in}$  can only supply 10mA (or less)
- An ideal silicon transistor ( $V_f = 0.7V$ ) with  $\beta=100$
- The LED has a 3.0V drop when  $I_d = 200mA$

Smallest Value of $R_b$	Largest Value of $R_b$	$R_c$

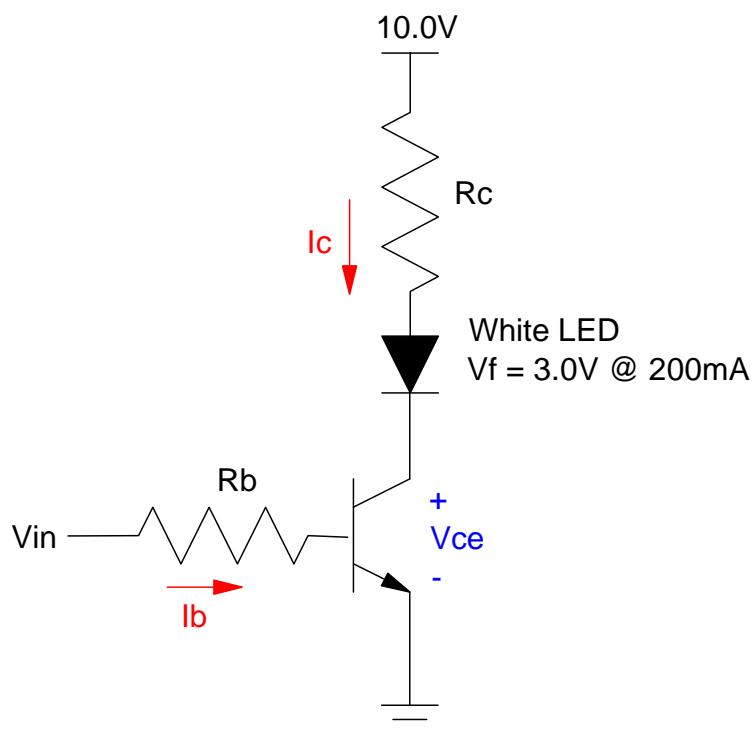


3) H-Bridge. Determine the currents and voltages for the following H-bridge. Assume ideal silicon transistors with  $\beta = 100$

I1	I2	I3	V1	V2

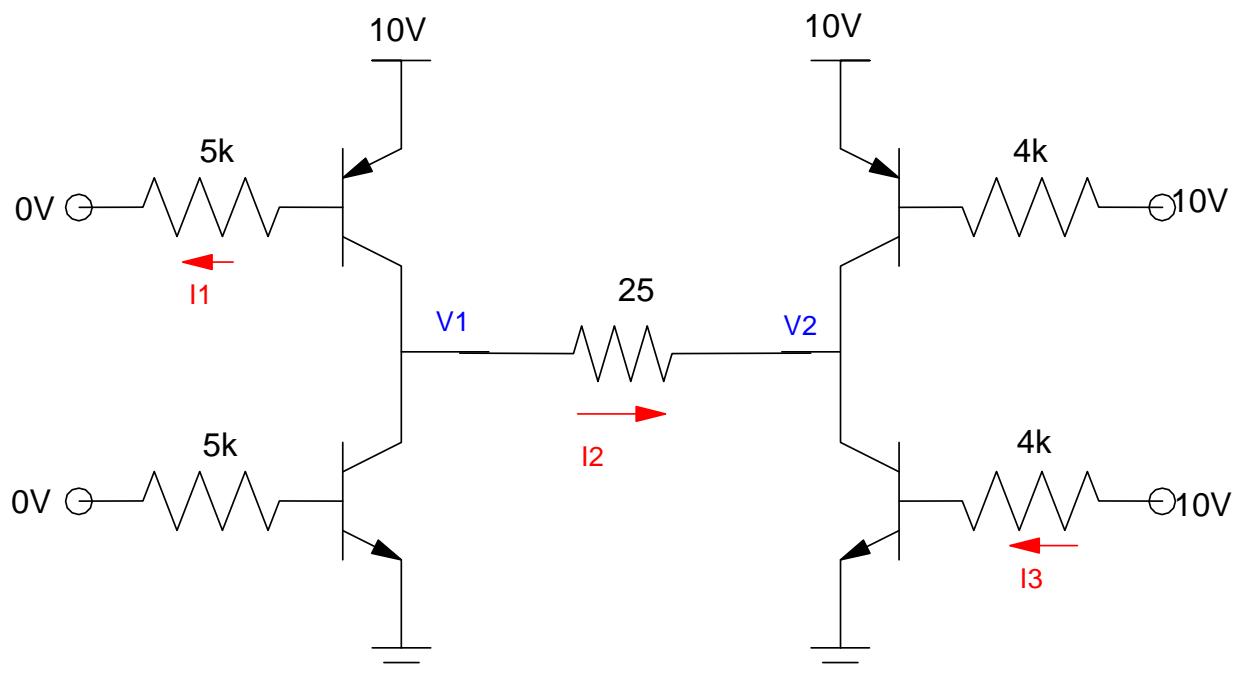

4) DTL Logic: Determine the voltages for the following DTL logic gate. Assume  $\beta = 100$

V1	V2	V3	V4

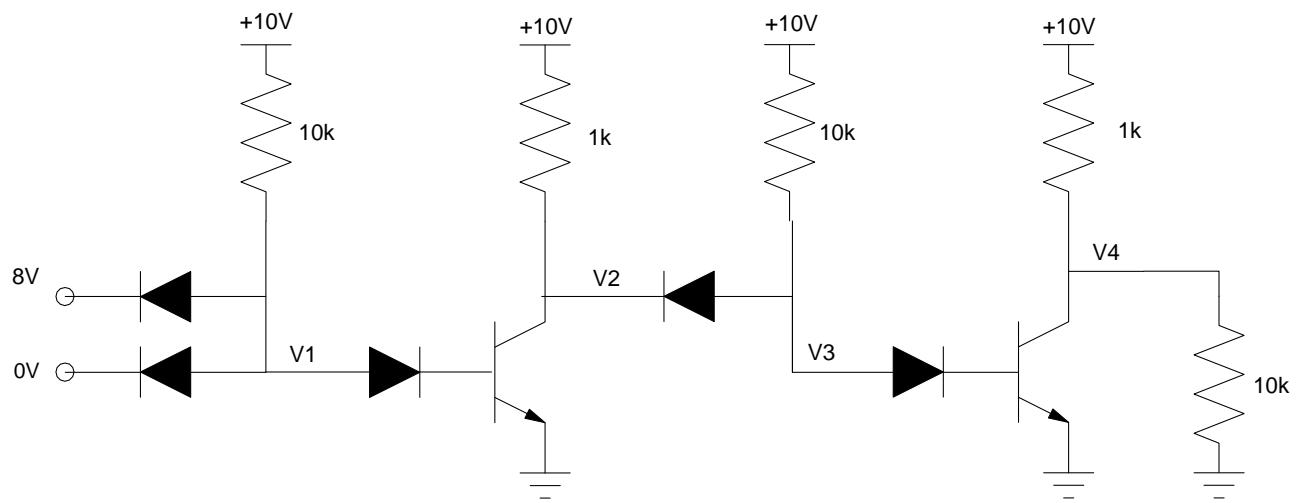

5) Design a Schmitt Trigger which outputs

- +10V when  $R > 7k$  Ohms
- 0V when  $R < 6k$  Ohms, and
- Is unchanged for  $6k < R < 7k$

