

# ECE 320 - Homework #9


DTL, TTL Logic, MOSFETs. Due Monday, March 18th, 2019

Assume 3904 transistors:


- $\beta = 100$
- $V_{be} = 0.7V$
- $\min(V_{ce}) = 0.2V$

## DTL Logic:

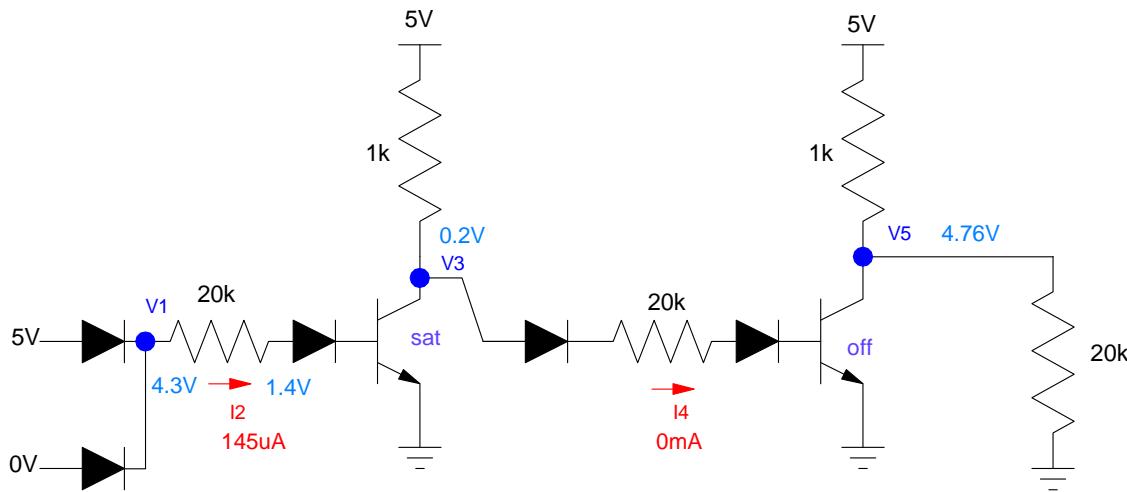1) Determine the voltages and currents for the following DTL OR gate.





2) Check your answers in PartSim

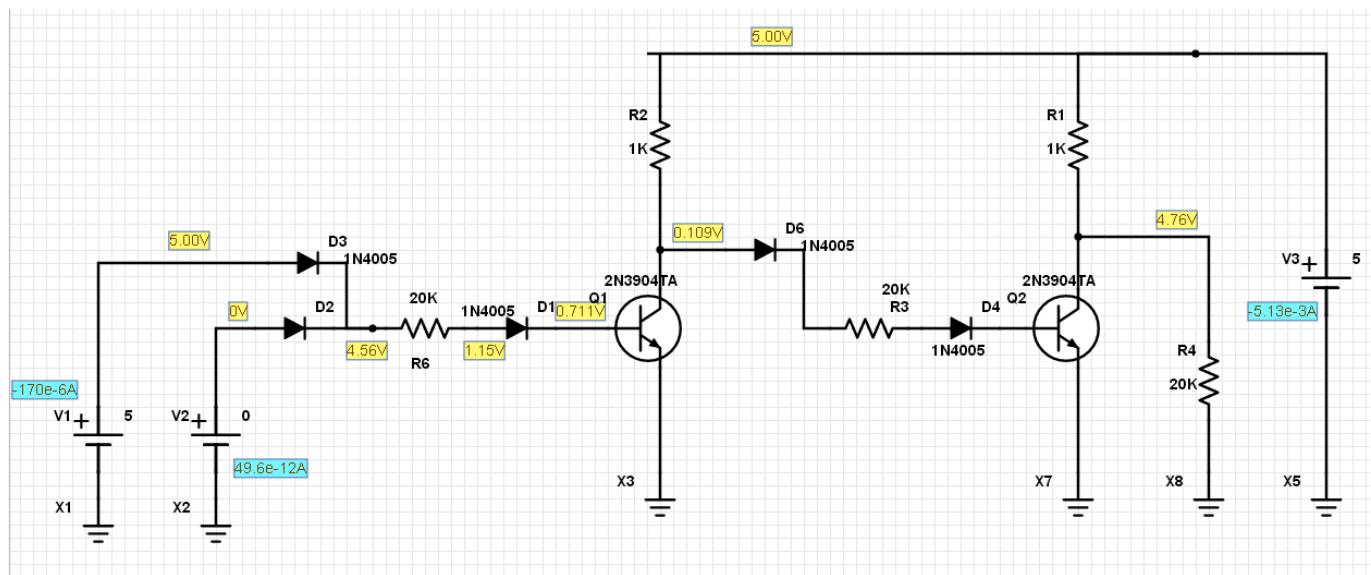



## TTL Logic:

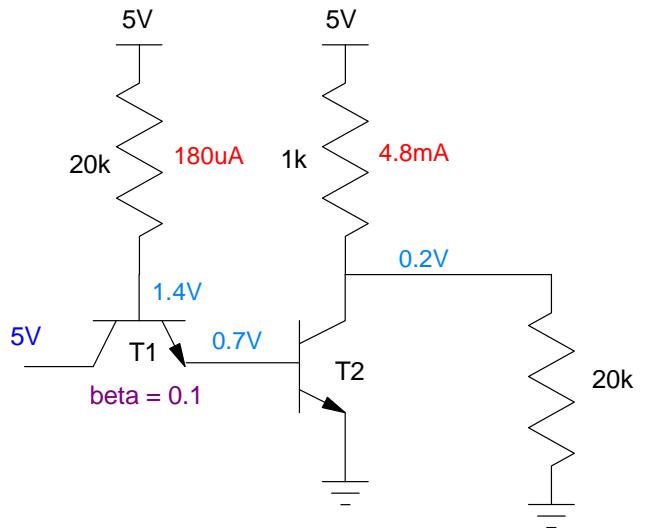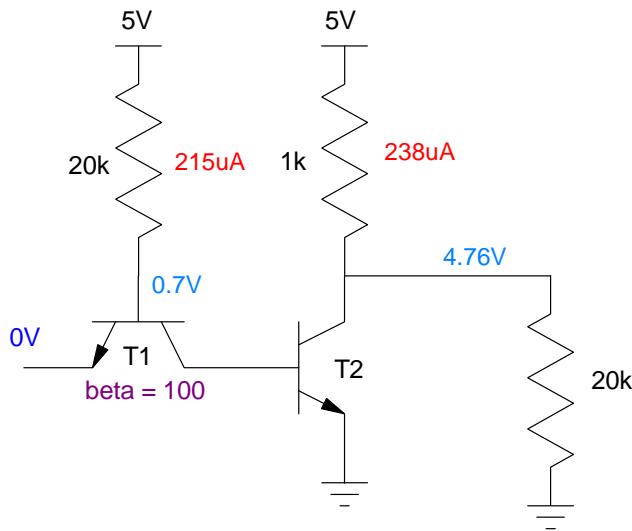3) Determine the voltages and currents for the following TTL inverter



4) Check your answers in PartSim

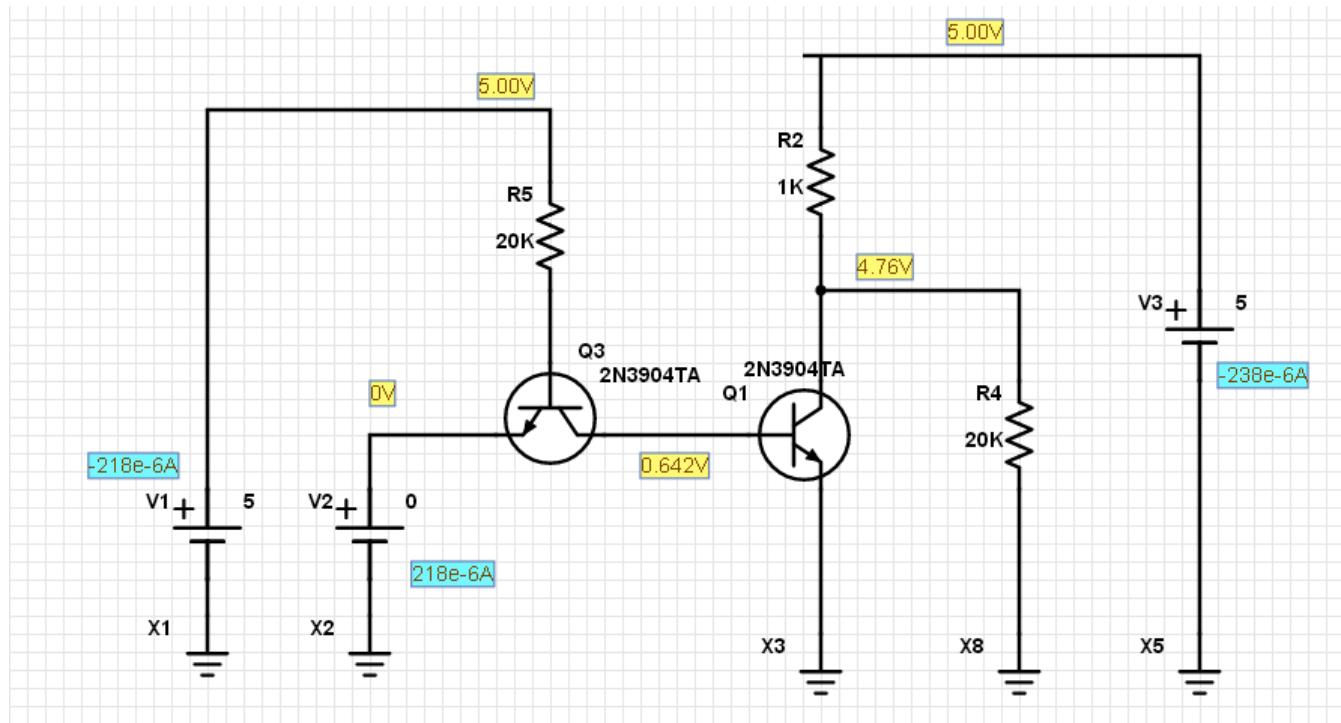

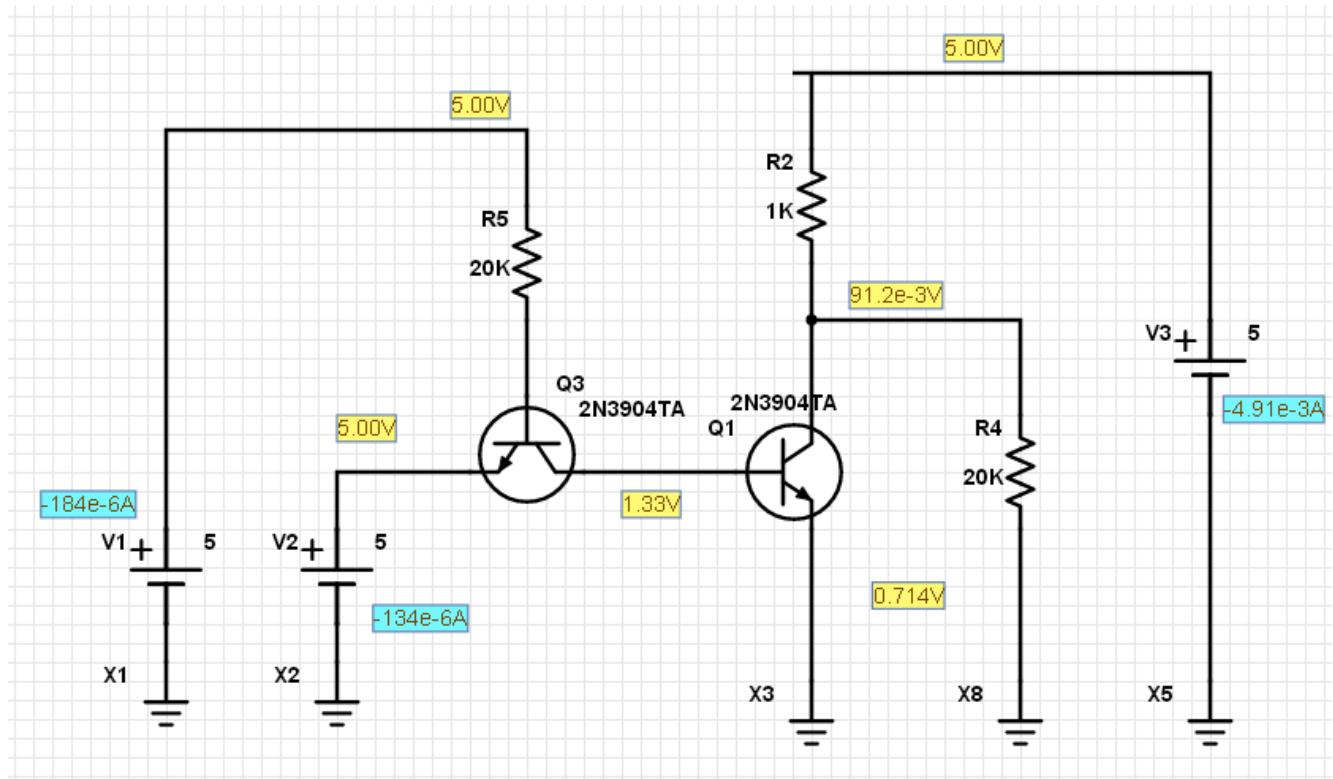

## MOSFETs

5) Label the off / saturated / ohmic regions for the following MOSFET and determine the transconductance gain,  $k_n$

6a) Draw the load line for the circuit below on this MOSFET

6b) Assume the threshold voltage is  $V_{gs} = 2.0V$ . Determine the operating point when

- $V_g = 0V \quad V_{ds} = 10V \quad I_{ds} = 0mA \quad \text{Off}$
- $V_g = 4V \quad V_{ds} = 8.5V \quad I_{ds} = 20mA \quad \text{Saturated}$
- $V_g = 7V \quad V_{ds} = 2.1V \quad I_{ds} = 92mA \quad \text{Ohmic}$

